

ECE 342

Electronic Circuits

Lecture 35

CMOS Logic

Jose E. Schutt-Aine
Electrical & Computer Engineering
University of Illinois
jesa@Illinois.edu

Digital Logic - Generalization

De Morgan's Law

$$\overline{A + B + C + \dots} = \bar{A} \cdot \bar{B} \cdot \bar{C} \cdot \dots$$

$$\overline{A \cdot B \cdot C \cdot \dots} = \bar{A} + \bar{B} + \bar{C} + \dots$$


Distributive Law

$$AB + AC + BC + BD = A(B + C) + B(C + D)$$

- **General Procedure**
 1. Design PDN to satisfy logic function
 2. Construct PUN to be complementary of PDN in every way
 3. Optimize using distributive rule

CMOS Logic Gate Circuits

 - **Two Networks**
 - Pull-down network (PDN) with NMOS
 - Pull-up network (PUN) with PMOS




PUN conducts when inputs are low and consists of PMOS transistors


PDN consists of NMOS transistors and is active when inputs are high

- **PDN and PUN utilize devices**
 - In parallel to form OR functions
 - In series to form AND functions

Pull-Down Networks

 


$$\bar{Y} = A + B$$

 


$$\bar{Y} = AB$$

Pull-Up Networks

 

$$Y = \bar{A} + \bar{B}$$

 

$$Y = \bar{A}\bar{B}$$

Basic Logic Function




Basic Function

INVERTER

NOR

NAND

Symbol

   

Devices
PUN

1
PMOS

2
PMOS-Series

2
PMOS-Parallel

Devices
PDN

1
NMOS

2
NMOS-Parallel

2
NMOS-Series

Truth Table

	A	Y
	0	1
	1	0

	A	B	Y
	0	0	1
	0	1	0
	1	0	0
	1	1	0

	A	B	Y
	0	0	1
	0	1	1
	1	0	1
	1	1	0


Pull-Down and Pull-Up Functions

Pull-up network (PUN)

Pull-down network (PDN)


- **Key features**

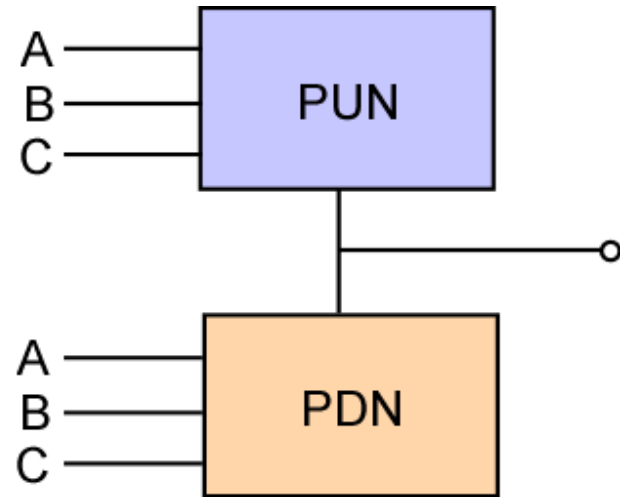- When PDN switch is on, PUN switch is off and vice versa
- Conditions for being on and off are complementary




Pull-Down and Pull-Up

PDN-parallel NMOS

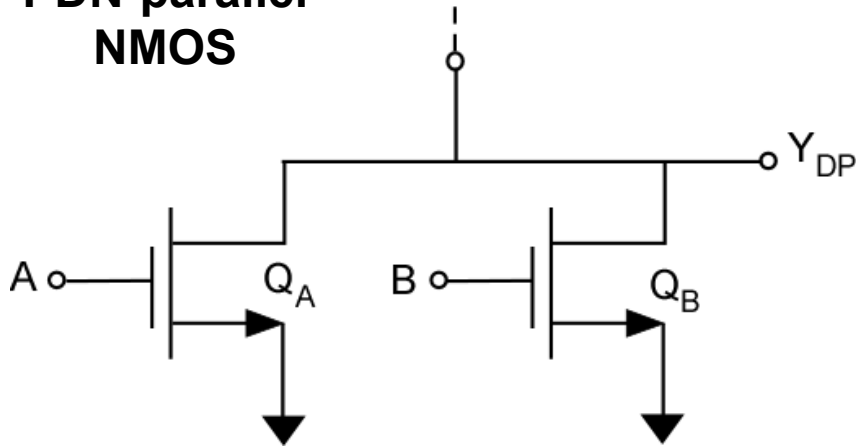

PUN-series PMOS

 

$$Y_{DP} = \overline{A + B}$$

Truth Tables

	A	B	Y_{DP}
	0	0	1
	0	1	0
	1	0	0
	1	1	0

$$Y_{US} = \overline{A} \overline{B}$$

	A	B	Y_{US}
	0	0	1
	0	1	0
	1	0	0
	1	1	0



Pull-Down and Pull-Up

When Y_{DP} in PDN-parallel is low, this means that either A or B (or both) is high. When either A or B (or both) is high, either transistor (or both) in PUN-series are off $\rightarrow Y_{US} = \text{low}$

When Y_{DP} in PDN-parallel is high, both A and B are low. Both transistors in PUN-Series are on creating a path to VDD. $Y_{US} = \text{high} \rightarrow Y_{US} = Y_{DP}$.

PDN-Parallel and PUN-series are complementary

Pull-Down and Pull-Up

  

$$Y_{DS} = \overline{AB}$$

Truth Tables

	A	B	Y_{DS}
	0	0	1
	0	1	1
	1	0	1
	1	1	0

$$Y_{UP} = \overline{A} + \overline{B}$$

	A	B	Y_{UP}
	0	0	1
	0	1	1
	1	0	1
	1	1	0


Pull-Down and Pull-Up

If Y_{DS} is low, both A and B must be high in which case both transistors in PUN-Parallel are off providing no path to $V_{DD} \rightarrow Y_{UP} = \text{low} \rightarrow Y_{UP} = Y_{DS}$.

If Y_{DS} is high, then either A or B (or both) are off (low) in which case either Q_{PA} or Q_{PB} in PUN-Parallel will be on and present a path to V_{DD} ; thus $Y_{UP} = \text{high} \rightarrow Y_{UP} = Y_{DS}$


PDN-Series and PUN-Parallel are complementary

Two-Input NOR Gate

 


$$Y = \overline{A + B} = \overline{A} \overline{B}$$

Two-Input NOR Gate

 


Actual

 

Ideal

Two-Input NAND Gate

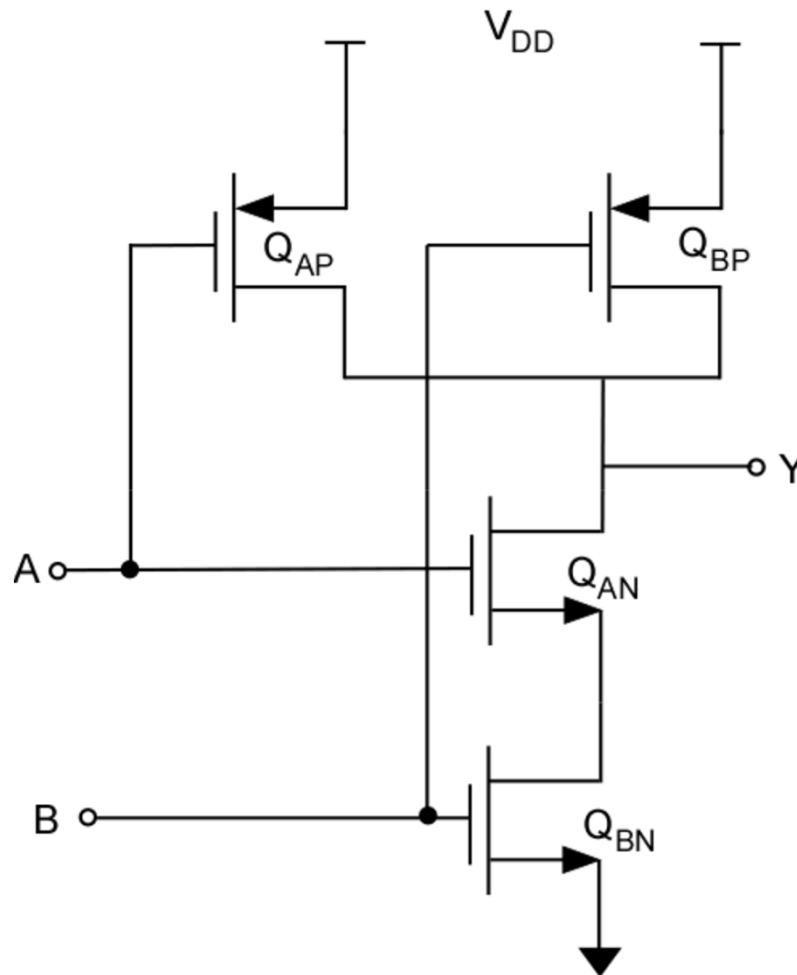

$$Y = \overline{AB} = \overline{A} + \overline{B}$$


Example

$$Y = \overline{\overline{AB} \cdot \overline{CD}}$$


Using De Morgan's Law

$$Y = \overline{\overline{AB} \cdot \overline{CD}} = AB + CD = (\overline{\overline{A} + \overline{B}}) \cdot (\overline{\overline{C} + \overline{D}})$$

Pull-down network

 


Pull-up network

 

Example 1

Evaluate Logic Function

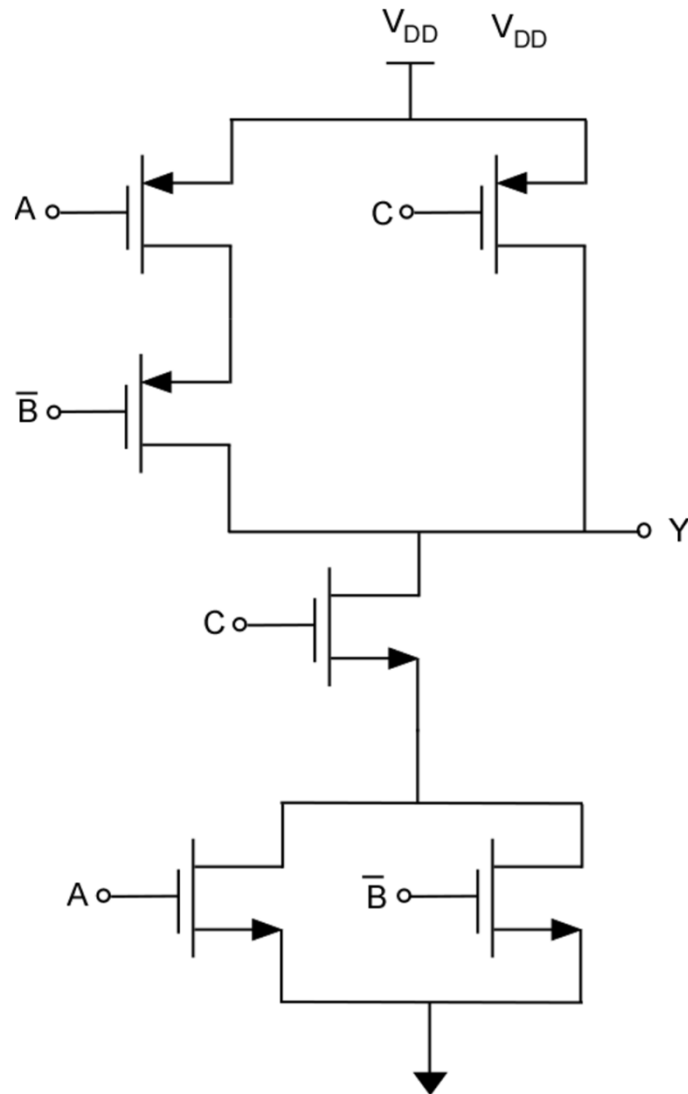

$$Y = \overline{(A + \bar{B})C} \text{ from pull down}$$


$$Y = \bar{A}B + \bar{C} \text{ from pull up}$$

$$\bar{A}B + \bar{C} = \overline{\overline{\bar{A}B} \cdot C} = \overline{(A + \bar{B})C}$$

Example 2

Implement the function


$$\bar{Y} = A\bar{B} + C$$

 


$$Y = \overline{A\bar{B} + C} = \overline{A\bar{B}} \cdot \bar{C} = (\bar{A} + B) \cdot \bar{C}$$

Exclusive-OR (XOR) Function
 
$$Y = A\bar{B} + \bar{A}B \quad \bar{Y} = (\bar{A} + B)(A + \bar{B})$$



pull down

 

pull up

XOR

	A	B	Y
	0	0	0
	0	1	1
	1	0	1
	1	1	0

Transistor Sizing

Objectives


- PDN provides discharge current of at least that of an NMOS
- PUN provides charging current of at least that of a PMOS
- Worst case gate delay equal to that of basic inverter
- Find combination that results in lowest output current
- For transistors in parallel aspect ratios add
- For transistors in series, inverses of aspect ratios add

$$\text{Series} : \frac{1}{(W/L)_{eq}} = \frac{1}{(W/L)_1} + \frac{1}{(W/L)_2} + \dots + \frac{1}{(W/L)_M}$$


$$\text{Parallel} : (W/L)_{eq} = (W/L)_1 + (W/L)_2 + \dots + (W/L)_M$$

$$p = (W/L)_p \quad n = (W/L)_n$$

Transistor Sizing

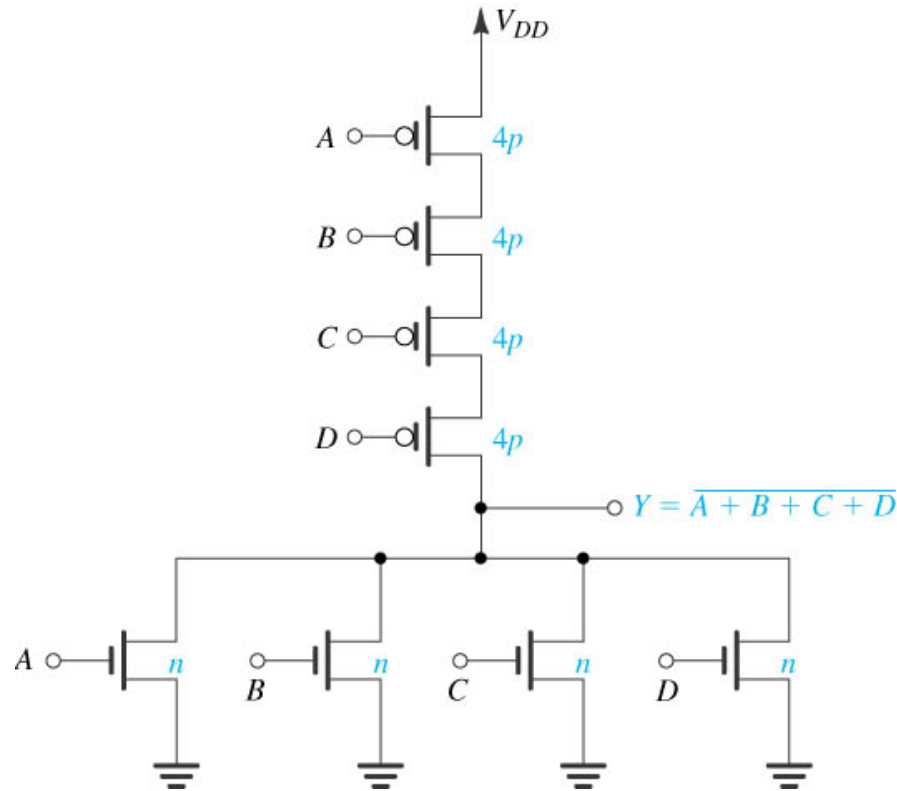



NOR

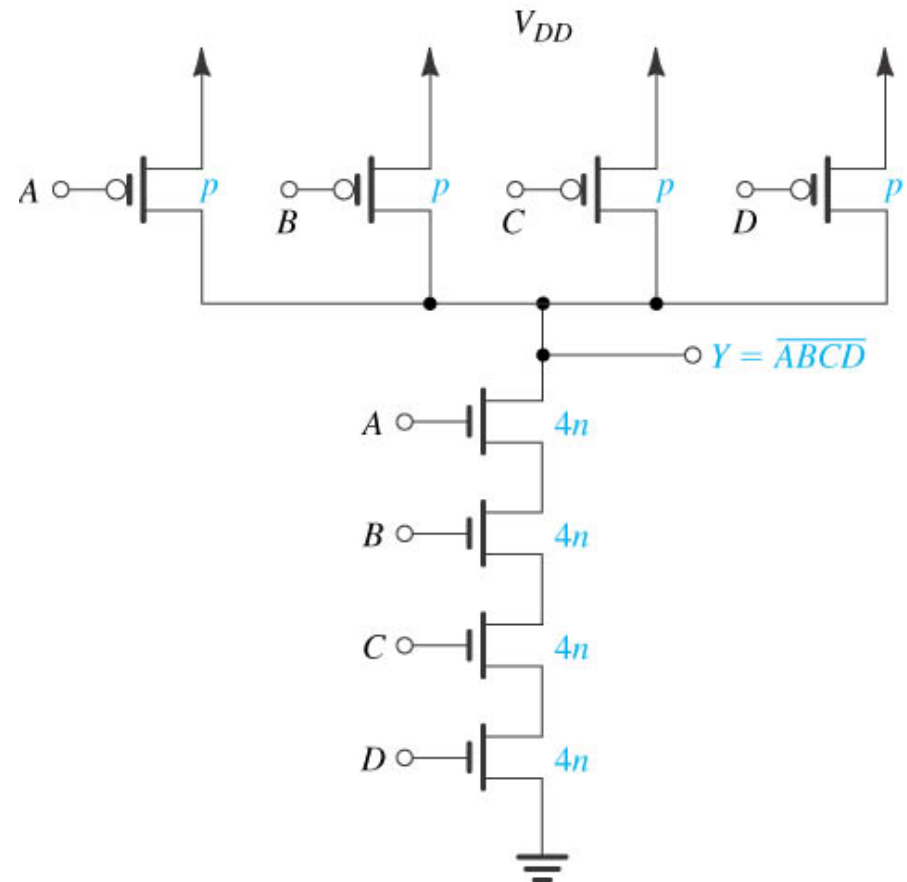

NAND

Transistor Sizing – Example 1

Two approaches to realizing the OR function of six input variables. Assuming that the transistors in both circuits are properly sized to provide each gate with a current-driving capability equal to that of the basic matched inverter, find the number of transistors and the total area of each circuit. Assume the basic inverter to have a $(W/L)_n$ ratio of $1.2 \mu\text{m}/0.8 \mu\text{m}$ and a $(W/L)_p$ ratio of $3.6 \mu\text{m}/0.8 \mu\text{m}$.

  

10.36

Transistor Sizing – Example 1

For design (a), there are $2(6)+2=14$ transistors:

All 7 NMOS use $(W/L)_n = n$

1 PMOS uses $(W/L)_p = p$

6 PMOS use $(W/L)_p = 6p$

Total Area = $7(1.2)0.8 + 1(3.6)0.8 + 6(6)(3.6)0.8 = 113.3 \mu\text{m}^2$

For design (b), there are $2(3)2 + 1(2)2=16$ transistors:

6 NMOS use $(W/L)_n = n$

6 PMOS use $(W/L)_p = 3p$


2 PMOS use $(W/L)_p = p$

2 NMOS use $(W/L)_n = 2n$

Total Area = $70(1.2)0.8 = 67.2 \mu\text{m}^2$, or 59% of (a)

Transistor Sizing – Example 2

Transistors in two-input NOR gate are properly sized so that the current-driving capability in each direction is equal to that of a matched inverter. For $|V_t| = 1\text{ V}$ and $V_{DD} = 5\text{ V}$, find the gate threshold in the cases for which (a) input terminal A is connected to ground and (b) the two input terminals are tied together. Neglect the body effect in Q_{PB} .

 

10.37

Transistor Sizing – Example 2

Corresponding to a matched inverter characterized by n and p where $k_p = k_n = k$, the two-input NOR uses transistors n and $2p$ where $k_p = 2k_n$

- a) For A grounded, V_{thB} occurs near $V_{DD}/2$, with Q_{PB} and Q_{NB} in saturation and Q_{PA} in triode. Let $V_{th} = v$, and the voltage across Q_{PA} be x

$$\text{Thus } i_D = k_p \left[(5-1)x - x^2 / 2 \right]$$

$$\text{and } i_D = \frac{1}{2} k_p (5 - x - v - 1)^2$$

$$\text{and } i_D = \frac{1}{2} k_n (v - 1)^2$$

Transistor Sizing – Example 2

$$\text{For } k_p = 2k_n, i_D = 2k_n \left(4x - x^2 / 2\right) = k_n \left(8x - x^2\right) \quad (1)$$

$$\text{and } i_D = k_n (4 - x - v) \quad (2)$$

$$\text{and } i_D = \frac{1}{2} k_n (v - 1)^2 \quad (3)$$

$$\text{From 2) 3): } \pm(v - 1)(0.07) = 4 - x - v$$

$$\text{Thus, } 1.707v = 4.707 - x \Rightarrow x = 4.707 - 1.707v$$

$$\text{or, } 0.293v = 3.293 - x \Rightarrow x = 3.293 - 0.293v$$

Transistor Sizing – Example 2

Now $x \approx 0$, in which case, $v = 4.707 / 1.707 \approx 2.38$ (ok)

or $v = 3.293 / 0.293 \approx 11.2$ (Clearly too large)

$$\text{Thus, } x = 4.707 - 1.707v \quad (4)$$

$$\text{Now from 1) 3) : } (v - 1)^2 = 2(8x - x^2)$$

$$\text{With 4), } v^2 - 2v + 1 = 16(4.707 - 1.707v) - 2(4.707 - 1.707v)^2$$

$$\text{or } v^2 - 2v + 1 = 75.32 - 27.3v - 44.31 + 32.13v - 5.83v^2$$

$$\text{or } 6.83v^2 + v(-2 + 27.32 - 32.13) + (1 - 75.32 + 44.31) = 0$$

$$\text{or } 6.83v^2 + 6.81v - 30.01 = 0$$

Transistor Sizing – Example 2

$$\begin{aligned} \text{whence } v &= \left(- - 6.81 \pm \left(6.81^2 - 4(6.83)30.01 \right)^{1/2} \right) / 2(6.83) \\ &= (6.81 \pm 29.43) / 13.66 = 2.65V \end{aligned}$$

Check: [> 2.5 V probably ok since one PMOS is full on]

$$\text{Thus } V_{th} = 2.65V$$

b) For A and B joined, the PMOS can be approximated as a single device with twice the length, for which the width is twice that in a matched inverter. Thus, for the equivalent PMOS device, $(W/L)_{peq} = p$ and $k_p = k$. For each of the two NMOS, $(W/L)_n = n$ and $k_n = k$.

Thus, at $V_{th} = v$ with all devices in saturation:

$$i_D = 2 \frac{k}{2} (v - 1)^2 = \frac{k}{2} (5 - v - 1)^2$$

Transistor Sizing – Example 2

$$2(v-1)^2 = (4-v)^2, \text{ and } \pm\sqrt{2}(v-1) = (4-v)$$

$$\text{Thus } 1.414v - 1.414 = 4 - v, \quad 2.414v = 5.414$$

$$\text{whence } V_{th} = v = 2.24V$$

See this is reduced from the single-input value (of 2.65V)!

Note that this fact can be used to control the relative threshold of multiple gates connected to a single fan-out node, in order to guarantee operation sequence for slowly changing signals