
 


 1. Consider the classical biasing scheme shown, using a 15 V supply. For the MOSFET, $V_t = 1.2\text{V}$, $\lambda = 0$, $k_n' = 80 \mu\text{A}/\text{V}^2$. $W = 240 \mu\text{m}$, and $L = 6 \mu\text{m}$. Arrange that the drain current is 2 mA, with about one-third of the supply voltage across each of R_S and R_D . Use $22 \text{ M}\Omega$ for the larger of R_{G1} and R_{G2} . What are the values of R_{G1} , R_{G2} , R_S , and R_D that you have chosen? Specify them to two significant digits. For your design, how far is the drain voltage from the edge of saturation?




2. Given $\mu_n C_{ox} = 0.1 \text{ mA}/\text{V}^2$ and $V_t = 1\text{V}$ Determine the current I_B in the circuits shown in figure below. Note that the fractions next to transistors represent W/L



 3. An enhancement NMOS transistor is connected in the bias circuit shown, with $V_G = 4\text{V}$ and $R_S = 1 \text{ k}\Omega$. The transistor has $V_t = 2\text{V}$ and $k_n'(W/L) = 2 \text{ mA}/\text{V}^2$. What bias current results? If a

transistor for which $k_n'(W/L)$ is 50% higher is used, what is the resulting percentage increase in I_D ?




4. Design the circuit shown below so that the transistor operates in saturation with V_D biased 1 V from the edge of the triode region, with $I_D = 1$ mA and $V_D = 3$ V for each of the following two devices (use a 10- μ A current in the voltage divider):

(a) $|V_t| = 1$ V and $k_p'W/L = 0.5$ mA/V²

(b) $|V_t| = 2$ V and $k_p'W/L = 1.25$ mA/V²

 For each case, specify the values of V_G , V_D , V_S , R_1 , R_2 , R_S and R_D .



5. In the circuit below, find the unknown node voltages V_1 and V_2 , given $V_{tp}=-1\text{V}$, $k_p'W/L=1\text{mA/V}^2$, and $\lambda=0$ for all transistors.

