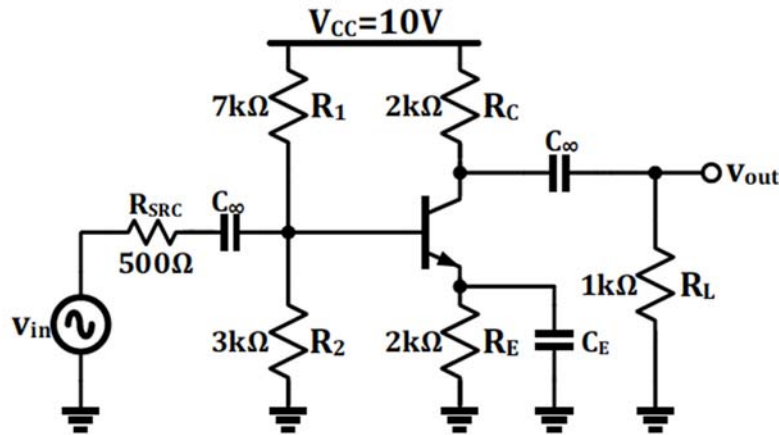



1. Given $V_{BE(on)} = 0.7V$, $\beta = 50$, $V_A = -20V$, determine the voltage gain $A_v = \frac{v_{out}}{v_{in}}$. Assume $V_T = 25mV$ and $C_E \rightarrow \infty$.




- Determine the DC bias point $Q = (V_B, V_C, V_E, I_C)$. Is the transistor in Forward-Active (FA) mode?
- Draw the small-signal model of this circuit, and derive expressions for G_m , input resistance R_i , the output resistance R_o , the small-signal voltage v_{be} (in terms of v_{in}), and the voltage gain $A_v = \frac{v_{out}}{v_{in}}$.
- Using the answers to part a) and b), assuming $v_{in} = 5mV$, determine numerical values for G_m , input resistance R_i , the output resistance R_o , the small-signal voltage v_{be} , and the voltage gain $A_v = \frac{v_{out}}{v_{in}}$.
- If $v_b = 5mV$, determine the value of the small-signal collector current i_c .

2. Repeat Problem 1 but this time assume $C_E = 0$. Compare the results of part b)-d) with that of Problem 1.

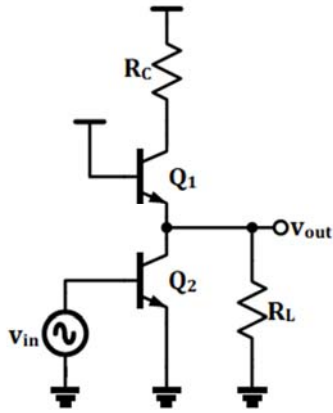
3. Determine expressions for G_m , R_i , and R_o for the following circuits by parsing the circuit appropriately and using the concept of BJT driving point (terminal) resistances. Assume $\beta \gg 1$ and FA-mode.



(a)

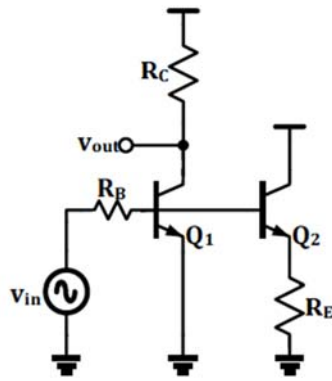

(b)

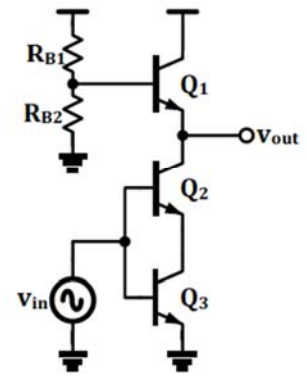

(c)