

ECE 342


Electronic Circuits

Lecture 4

Diode Models

Jose E. Schutt-Aine
Electrical & Computer Engineering
University of Illinois
jesa@illinois.edu





The Diode

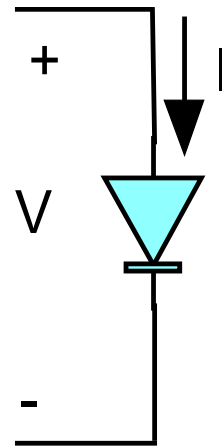


- **Diode Properties**

- Two-terminal device that conducts current freely in one direction but blocks current flow in the opposite direction.
- The two electrodes are the anode which must be connected to a positive voltage with respect to the other terminal, the cathode in order for current to flow.

Ideal Diode Characteristics

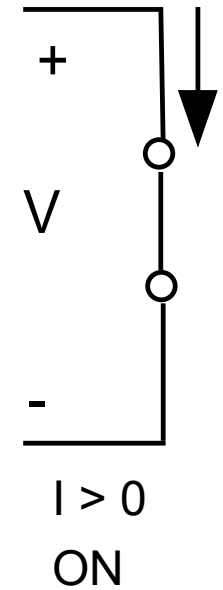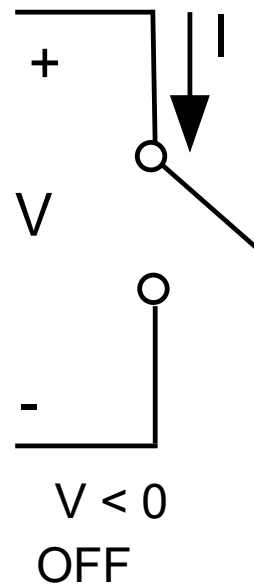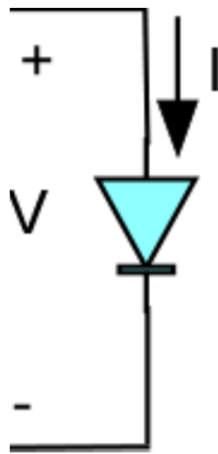
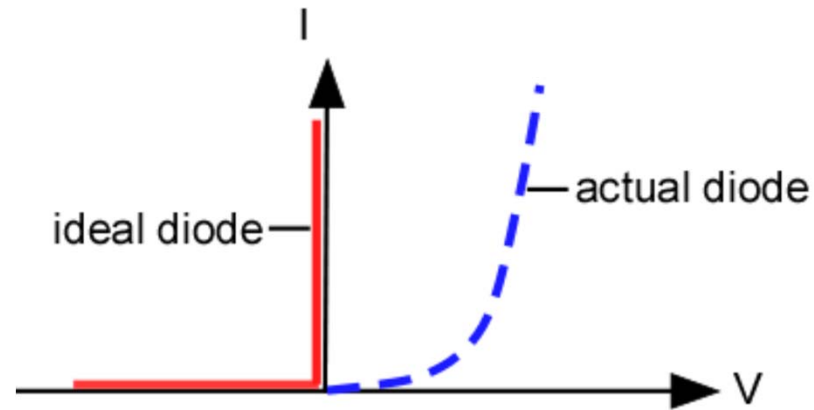


Ideal Diode Characteristics


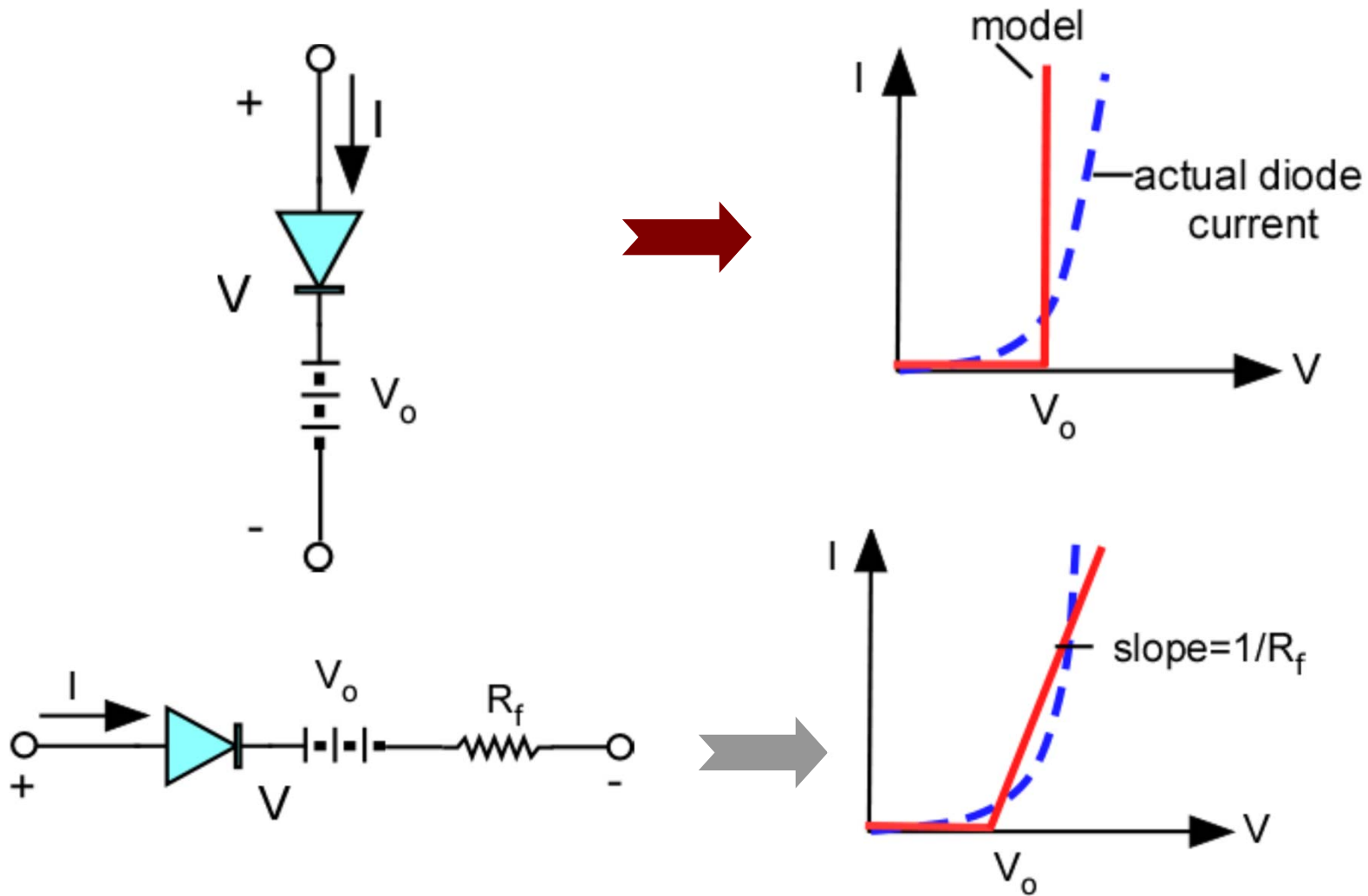


Diode Models



Exponential

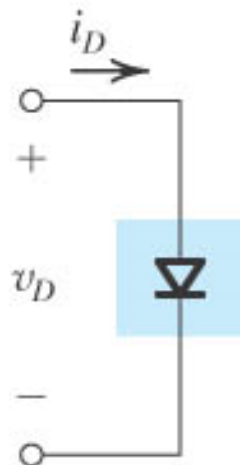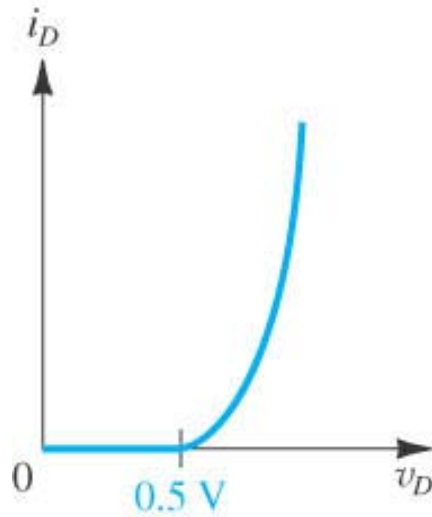





Piecewise Linear

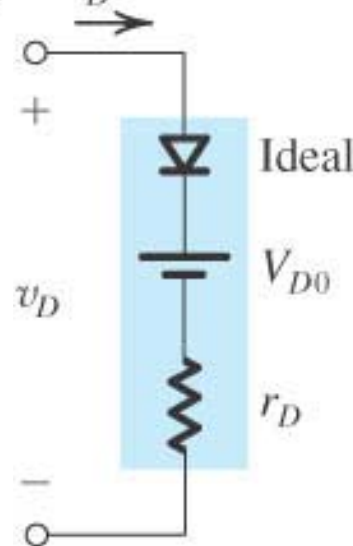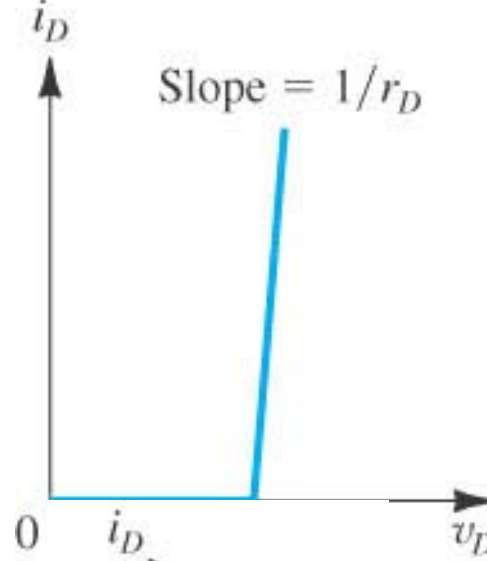

Constant-Voltage-Drop

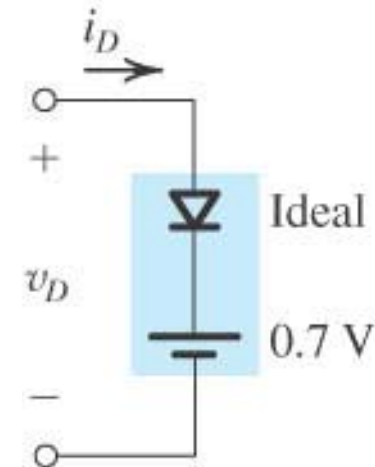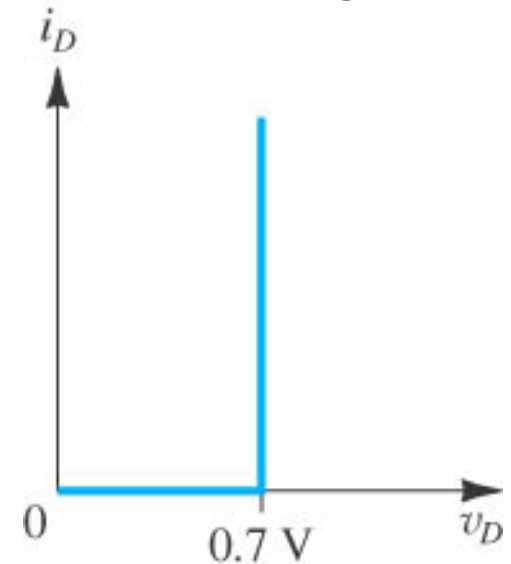


Diode Models

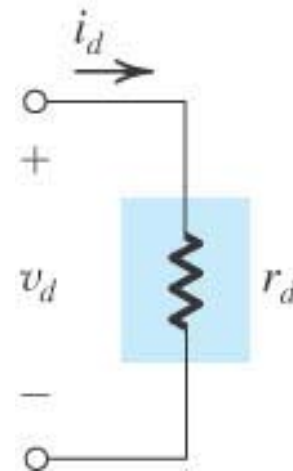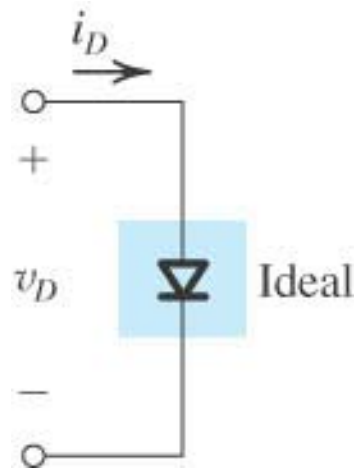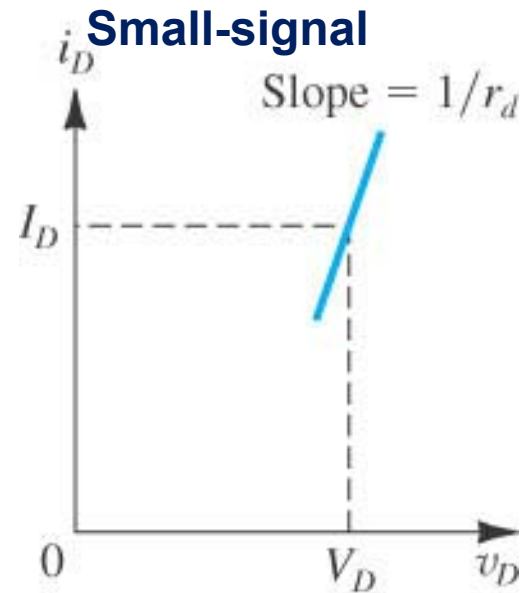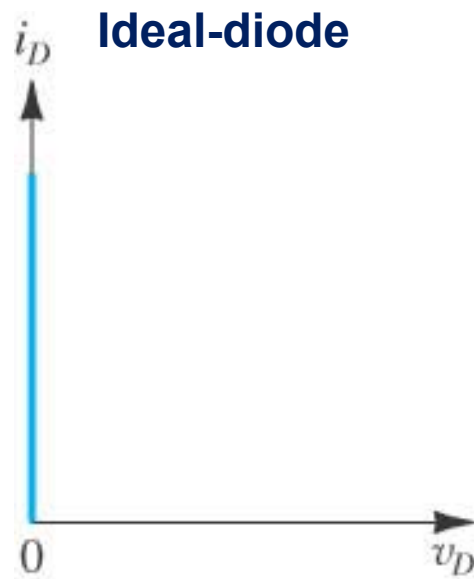


Piecewise-Linear Model

$$\text{for } v_D \leq V_{D0} : i_D = 0$$
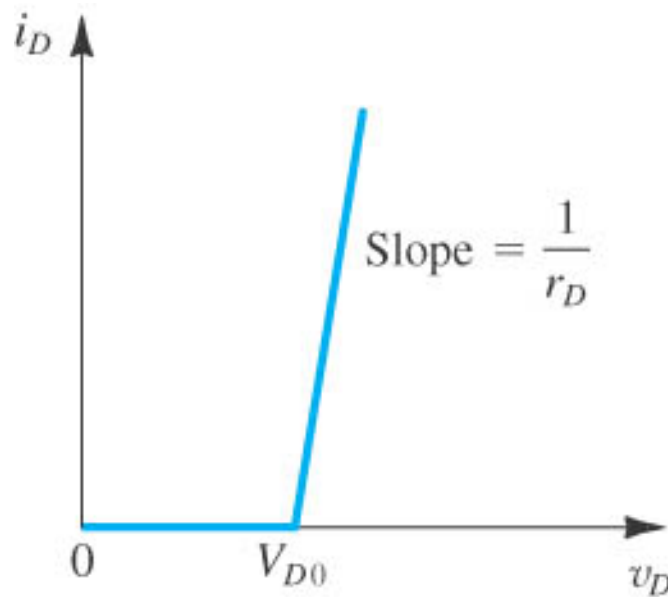
$$\text{for } v_D \geq V_{D0} : i_D = \frac{1}{r_D} (v_D - V_{D0})$$




(a)

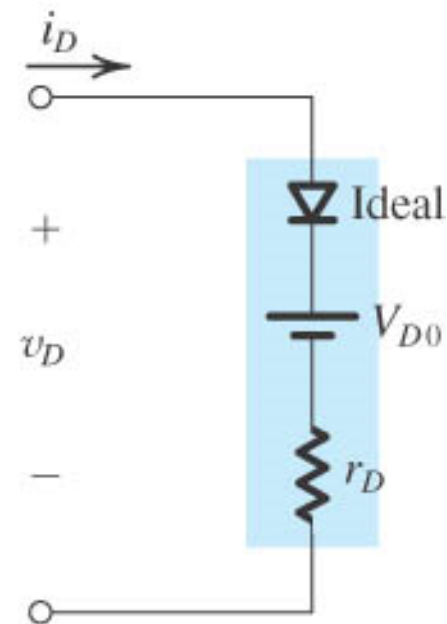



(b)

Piecewise-Linear Model

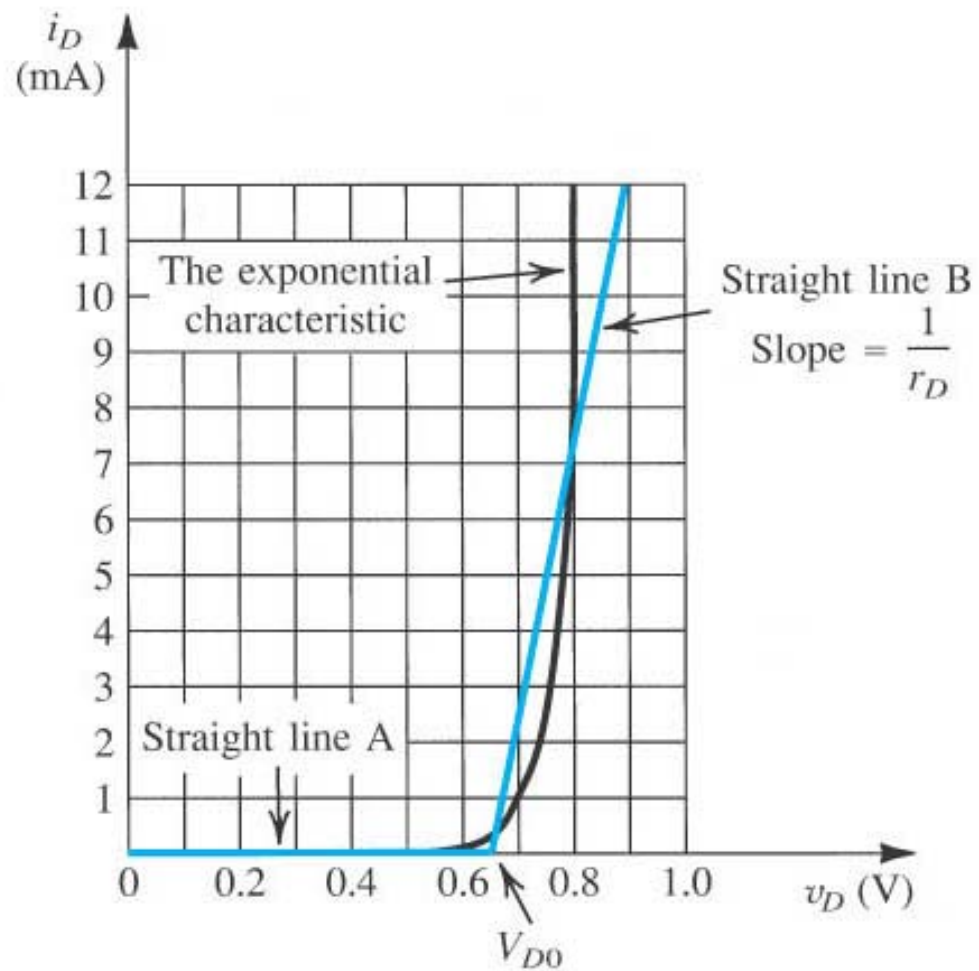


Constant-Voltage-Drop Model


for $i_D > 0$: $v_D = 0.7\text{ V}$

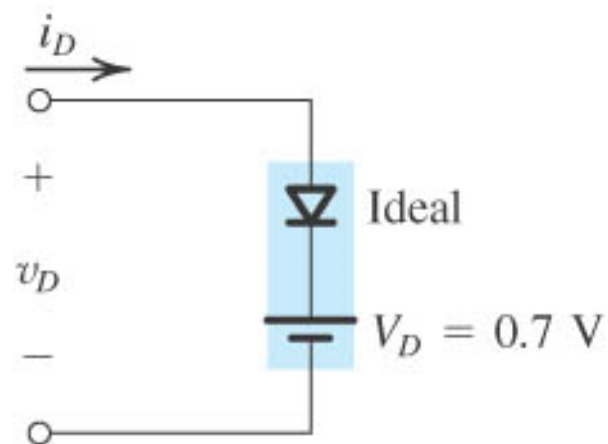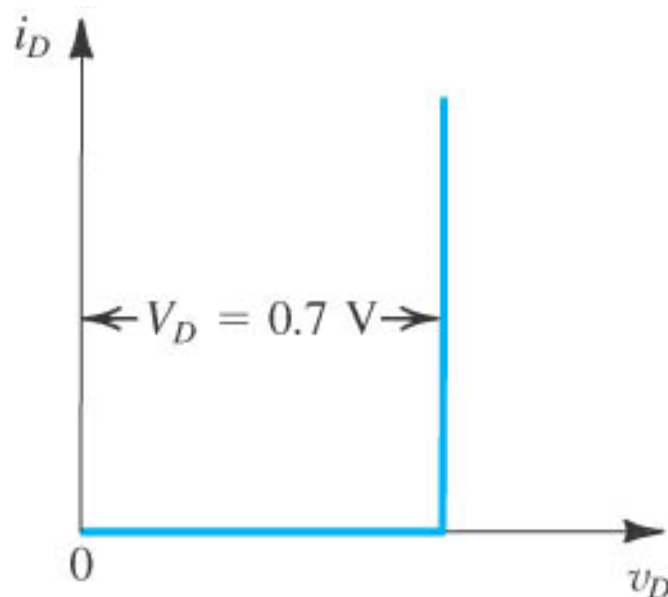

Constant-Voltage-Drop Model

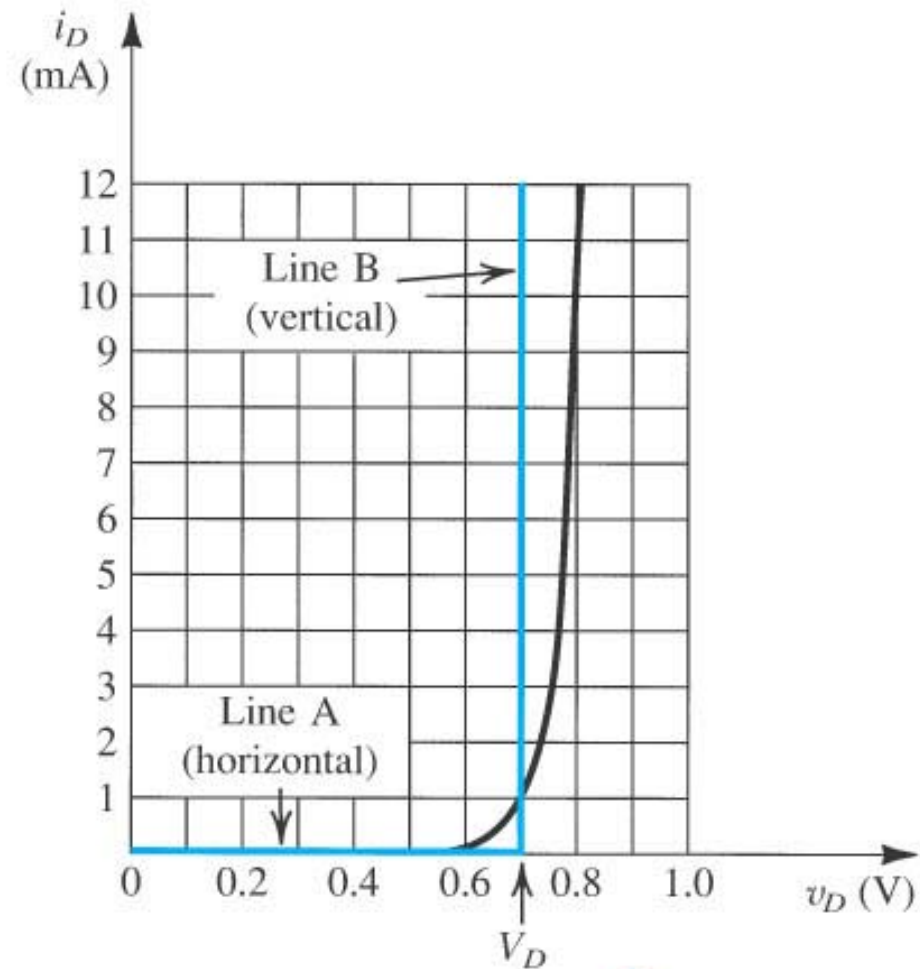


Diodes Logic Gates

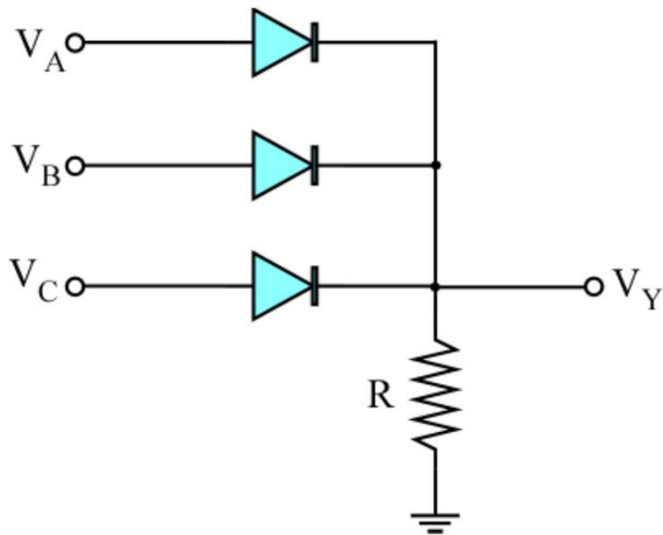

OR Function

$$Y = A + B + C$$

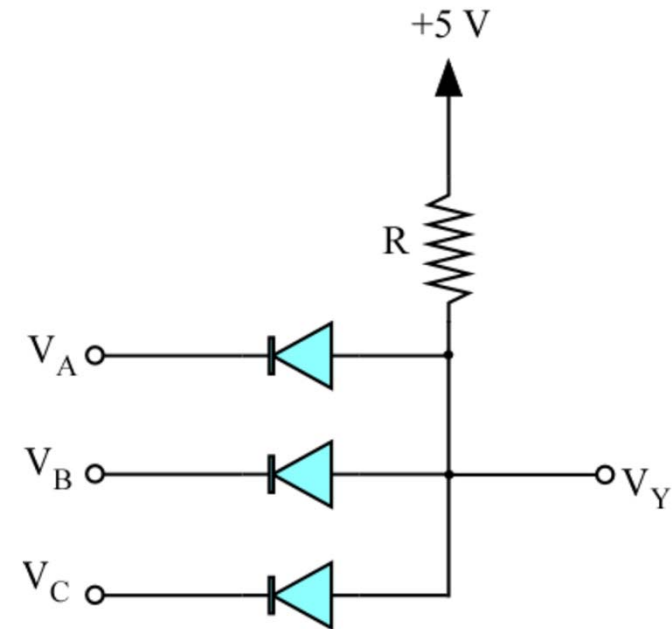

AND Function

$$Y = A \cdot B \cdot C$$

Diode Circuit Example 1

IDEAL Diodes

Assume both diodes are on; then


$$V_B = 0 \quad \text{and} \quad V = 0$$

$$I_{D2} = \frac{10 - 0}{10} = 1 \text{ mA}$$

At node B


$$I + 1 = \frac{0 - (-10)}{5} \Rightarrow I = 1 \text{ mA}, V = 0 \text{ V}$$

D₁ is conducting as originally assumed

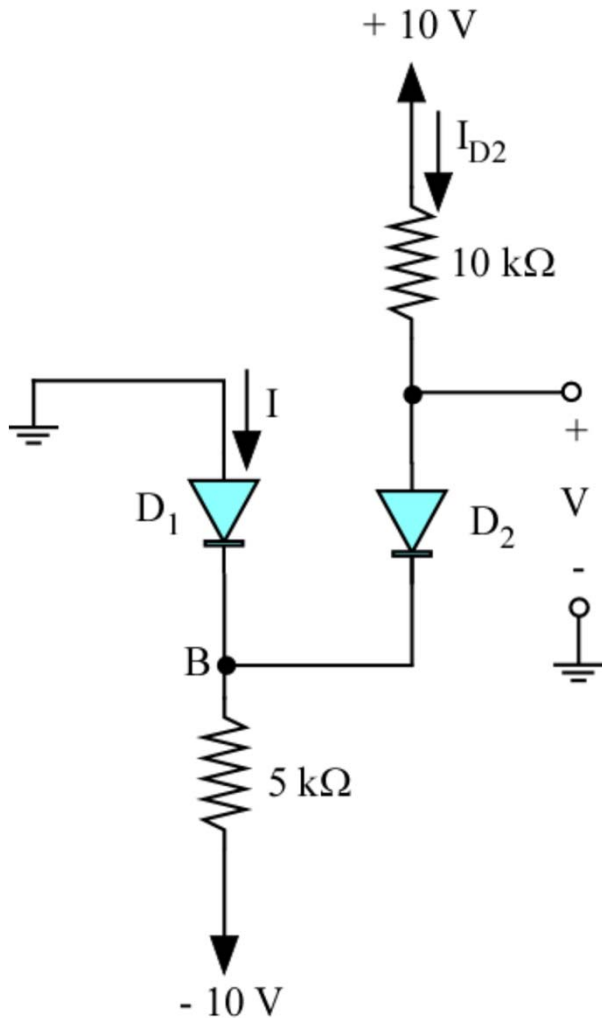

Diode Circuit Example 2

IDEAL Diodes

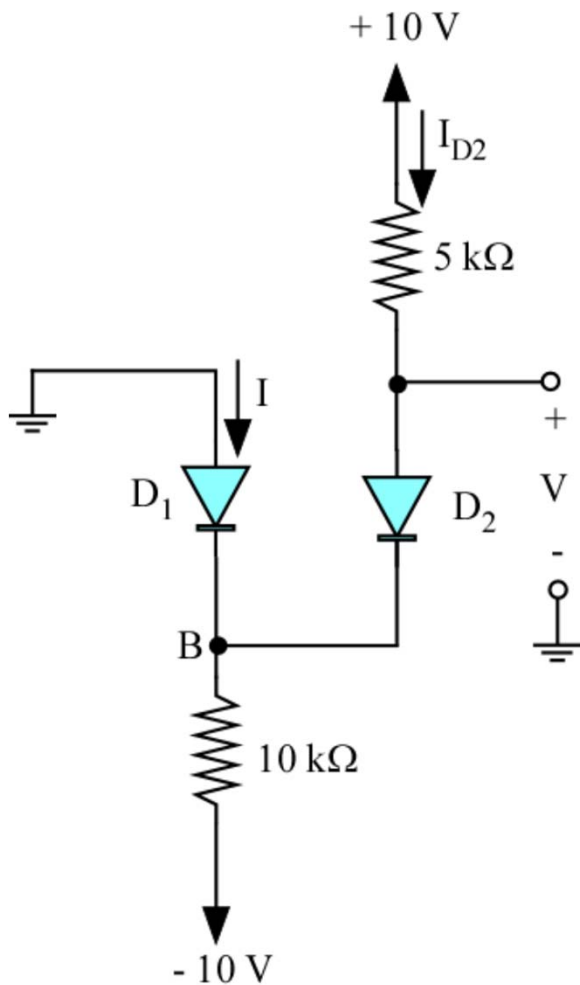

Assume both diodes are on; then

$$V_B = 0 \quad \text{and} \quad V = 0$$

$$I_{D2} = \frac{10 - 0}{5} = 2 \text{ mA}$$

At node B

$$I + 2 = \frac{0 - (-10)}{10} \Rightarrow I = -1 \text{ mA} \Rightarrow \text{wrong}$$

**original assumption is not correct ...
assume D_1 is off and D_2 is on**

$$I_{D2} = \frac{10 - (-10)}{15} = 1.33 \text{ mA}$$

$$V_B = -10 + 10 \times 1.33 = +3.3 \text{ V}$$

D_1 is reverse biased as assumed

Example

The diode has a value of $I_S = 10^{-12}$ mA at room temperature (300° K)

- (a) Approximate the current I assuming the voltage drop across the diode is 0.7V
- (b) Calculate the accurate value of I
- (c) If I_S doubles for every 6° C increase in temperature, repeat part (b) if the temperature increases by 40° C


(a) The resistor will have an approximate voltage of $6 - 0.7 = 5.3$ V. Ohm's law then gives a current of

$$I = \frac{5.3}{2} = 2.65 \text{ mA}$$

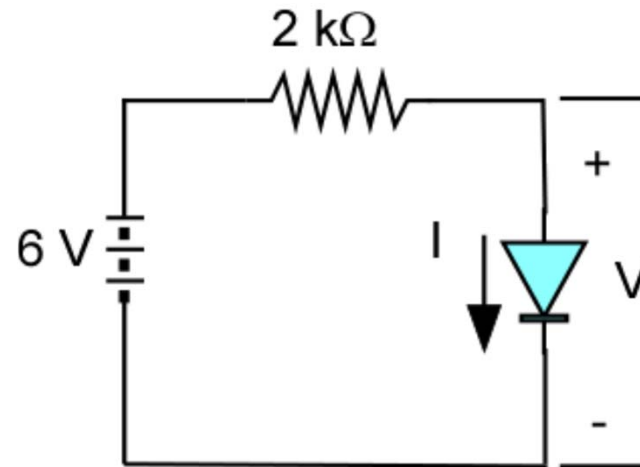(b) The current through the resistor must equal the diode current; so we have

$$I = \frac{6 - V}{2} \text{ (resistor current)}$$

$$I = I_S e^{V/V_T} \text{ (diode current)}$$



Example (cont'd)

$$\frac{6-V}{2} = 10^{-12} e^{V/0.026}$$

Nonlinear equation → must be solved iteratively

Solution: $V = 0.744 \text{ V}$

Using this value of the voltage, we can calculate the current

$$I = \frac{6-V}{2} = \frac{6-0.744}{2} = 2.63 \text{ mA}$$

When the temperature changes, both I_s and V_T will change. Since $V_T = kT/q$ varies directly with T , the new value is:

$$V_T(340) = V_T(300) \times \frac{340}{300} = 0.0295$$

Example (cont'd)

The value of I_s doubles for each 6° C increase, thus the new value of I_s is

$$I_s(340) = I_s(300) \times 2^{40/6} = 1.016 \times 10^{-10} \text{ mA}$$

The equation for I is then


$$I = \frac{6 - V}{2} = 1.016 \times 10^{-10} \times e^{V/0.0295}$$

Solving iteratively, we get

$$V = 0.640 \text{ V} \quad \text{and} \quad I = 2.68 \text{ mA}$$

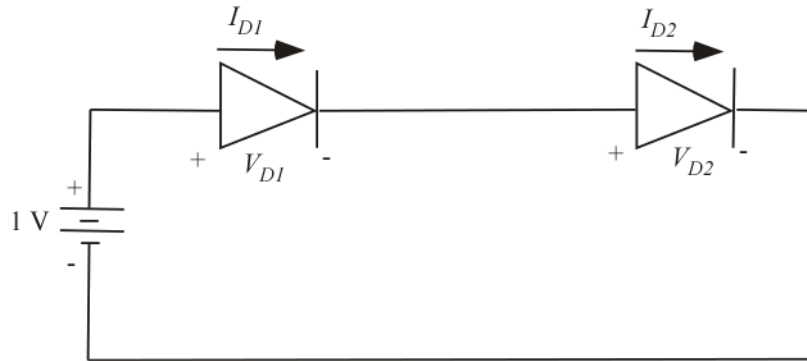Example

Two diodes are connected in series as shown in the figure with $I_{s1} = 10^{-16}$ A and $I_{s2} = 10^{-14}$ A. If the applied voltage is 1 V, calculate the currents I_{D1} and I_{D2} and the voltage across each diode V_{D1} and V_{D2} .



The diode equations can be written as:

$$I_{D1} = I_{S1} e^{V_{D1}/V_T} \quad I_{D2} = I_{S2} e^{V_{D2}/V_T} \quad \frac{I_{S1}}{I_{S2}} e^{\frac{V_{D1}-V_{D2}}{V_T}} = \frac{I_{D1}}{I_{D2}} = 1$$

$$\text{from which } V_{D1} - V_{D2} = -V_T \ln\left(\frac{I_{S1}}{I_{S2}}\right) = -0.12$$

$$\text{Using KVL, we get } V_{D1} + V_{D2} = 1 \quad \text{from which } V_{D2} = 0.44 \text{ V and } V_{D1} = 0.56 \text{ V}$$

$$I_{D1} = 10^{-16} e^{0.56/0.026} = 0.22 \mu\text{A} = I_{D2}$$

Small Signal Model

Approximation - valid for small fluctuations about bias point


$$i_D = I_D e^{v_d/nV_T}$$

$$r_d = \left[\frac{\partial i_D}{\partial v_D} \right]_{i_D=I_D} = \frac{nV_T}{I_D}$$


$$i_D = I_D + i_d$$

↑ Total ↑ DC ↑ applied (small)

$$v_D = V_D + v_d$$

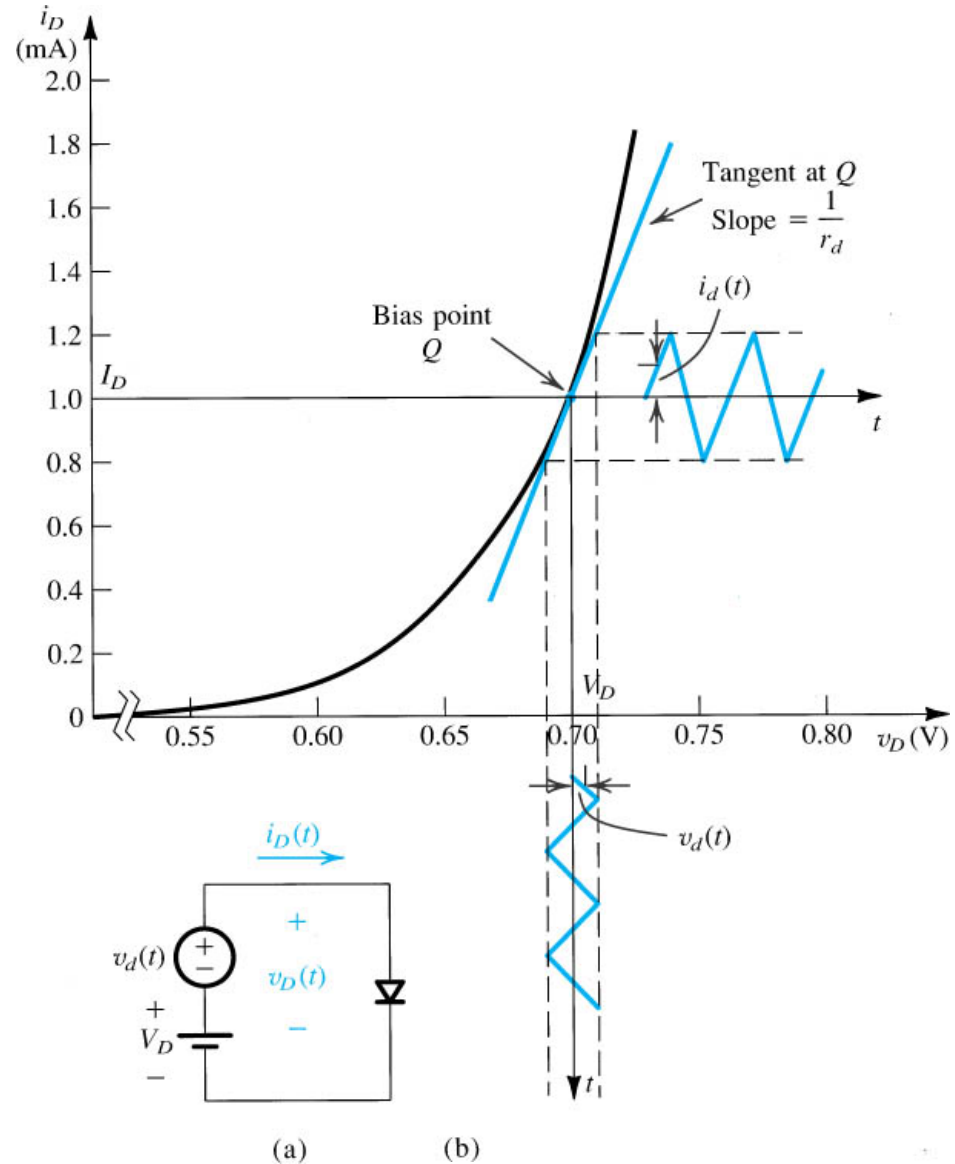

Diode Circuits

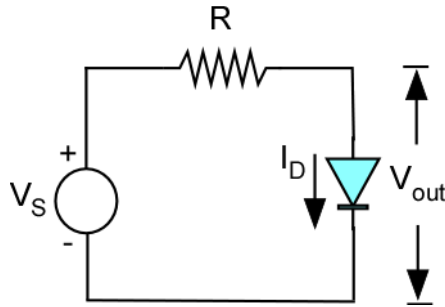


$$V_{out} = V_D$$

$$I_D = I_S \left(e^{V_D/V_T} - 1 \right)$$

$$V_S = RI_D + V_D = RI_D(V_D) + V_D$$

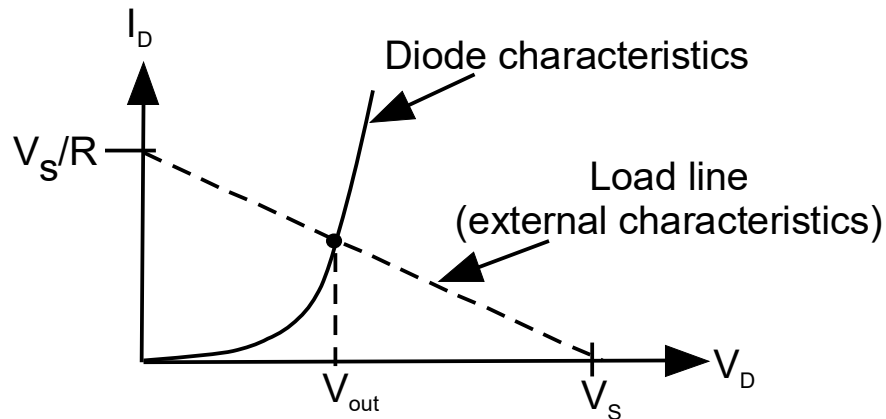Nonlinear transcendental system → Use graphical method



Solution is found at intersection of load line characteristics and diode characteristics

Diode Circuits – Iterative Methods

Newton-Raphson Method

Wish to solve $f(x)=0$ for x

$$\text{Use: } x_{k+1} = x_k - [f'(x_k)]^{-1} f(x_k)$$

$$x^{(k+1)} = x^{(k)} - [f'(x^{(k)})]^{-1} f(x^{(k)})$$

$$f(V_D) = \frac{V_D - V_S}{R} + I_S (e^{V_D/V_T} - 1) = 0$$
$$f'(V_D) = \frac{1}{R} + \frac{I_S}{V_T} e^{V_D/V_T}$$

$$V_D^{(k+1)} = V_D^{(k)} - \frac{\frac{V_D^{(k)} - V_S}{R} + I_S (e^{V_D^{(k)}/V_T} - 1)}{\frac{1}{R} + \frac{I_S}{V_T} e^{V_D^{(k)}/V_T}}$$

Where $V_D^{(k)}$ is the value of V_D at the k th iteration

Procedure is repeated until convergence to final (true) value of V_D which is the solution. Rate of convergence is quadratic.

