

ECE 342

Electronic Circuits

Lecture 9

Common Source Amplifiers - 1

Jose E. Schutt-Aine
Electrical & Computer Engineering
University of Illinois
jesa@Illinois.edu


Biasing of MOS Transistors

- **Bias Characteristics**

- Operation in saturation region
- Stable and predictable drain current

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)^2$$


Two-Supply MOS Bias

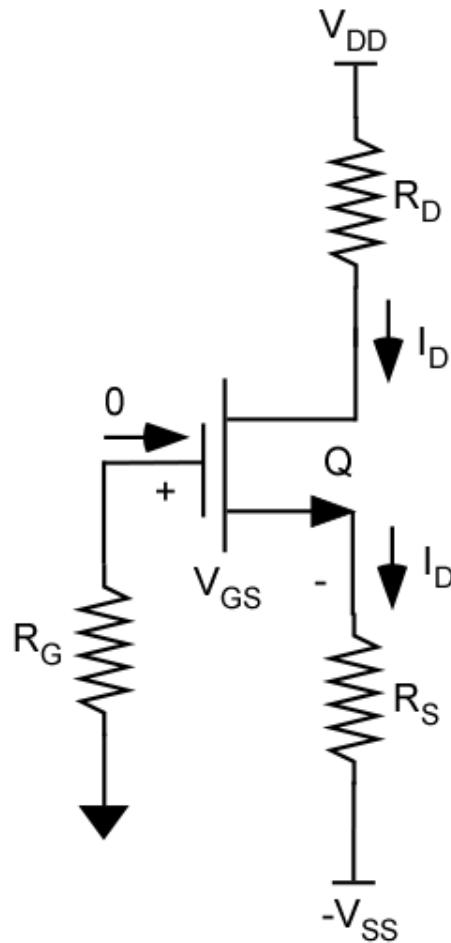

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)^2$$



R_G provides DC ground at gate and high input resistance to signal source.

Single-Supply MOS Bias

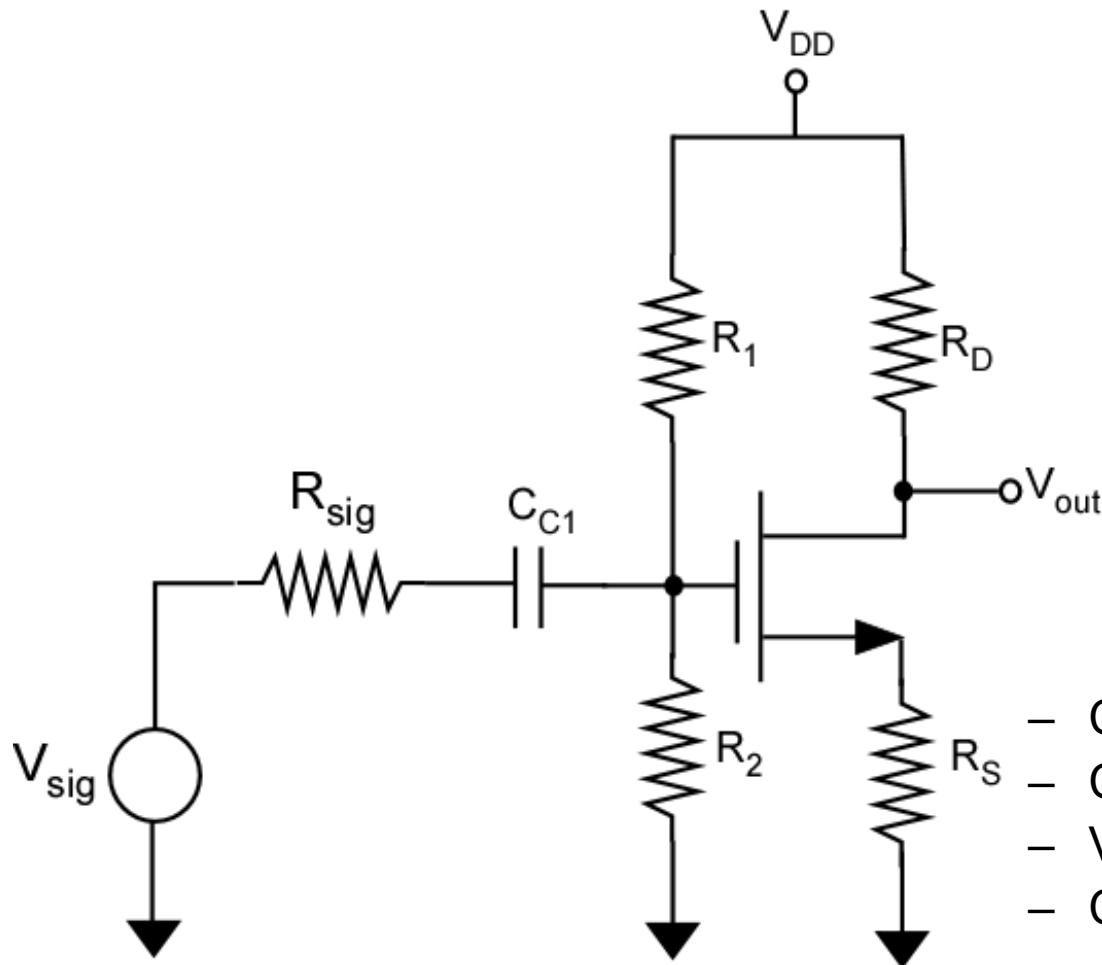

- Choose R_1 and R_2 to fix V_G
- Choose R_S and R_2 to fix V_s
- V_{GS} determines I_D
- Choose R_D to fix V_D

Common Source MOSFET Amplifier

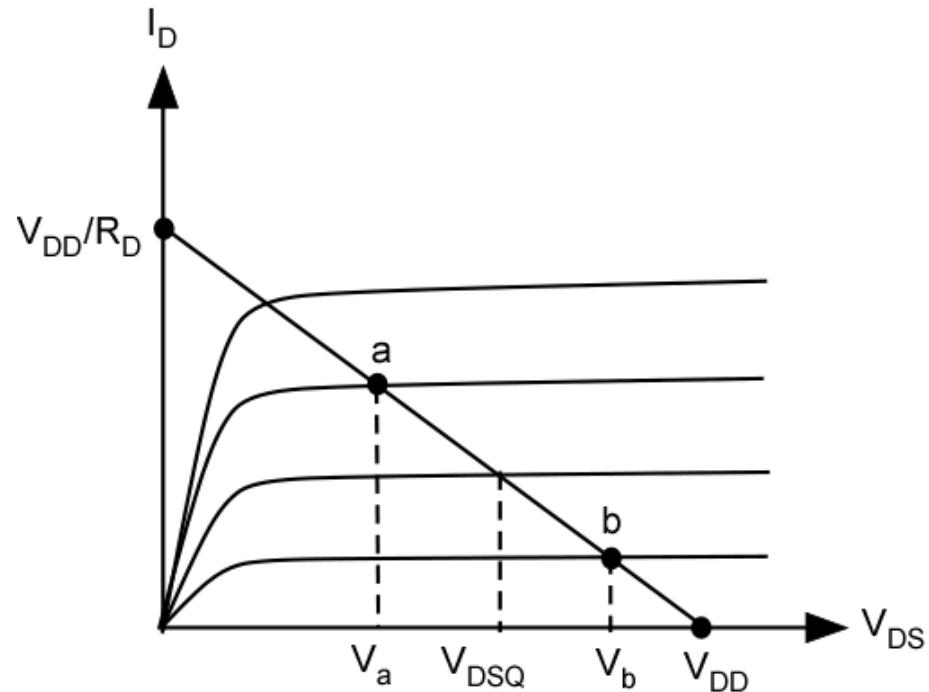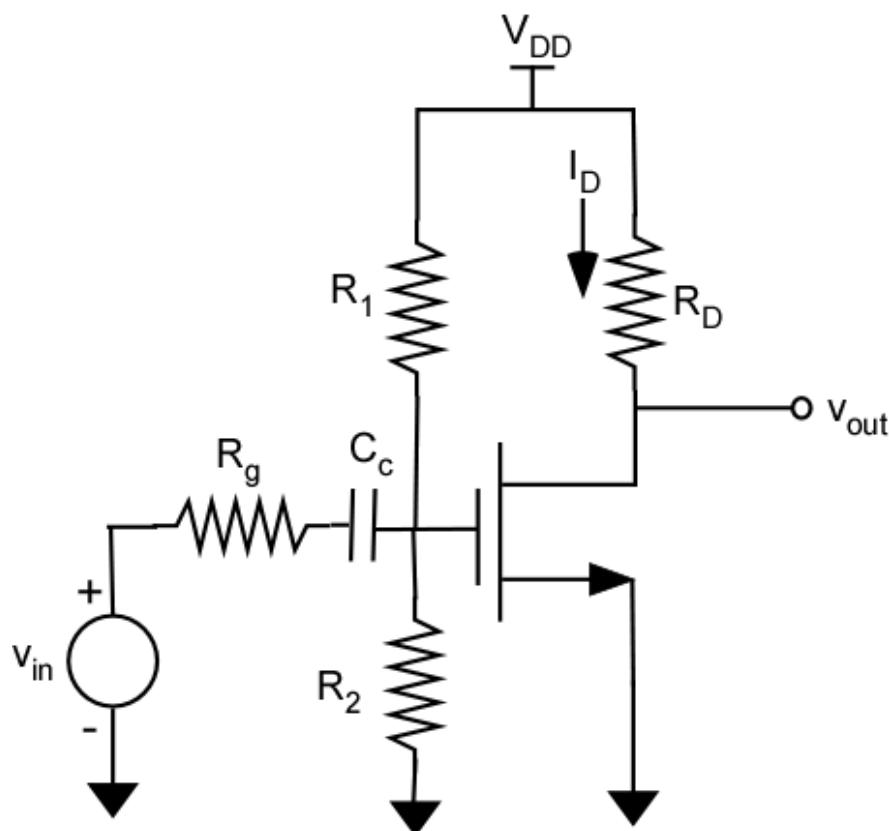

Bias is to keep MOS in saturation region


Common Source MOSFET Amplifier

$$V_{DS} = V_{DD} - I_D R_D$$

$$V_{GS} = V_{GSQ} + v_{in}$$

v_{in} is a sinusoid

$$V_{GS} = V_{GSQ} + B \sin \omega t$$

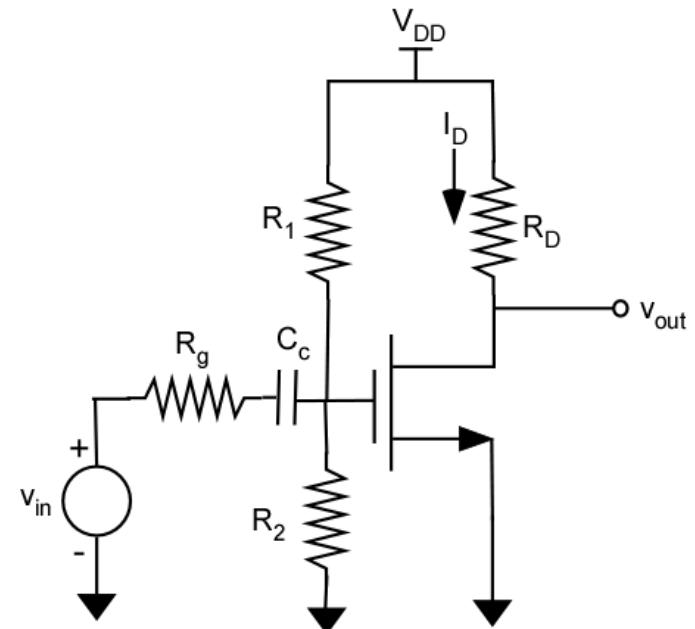

For small-signal operation,
the value of B must be much smaller than V_{GSQ}

CS Amplifier – DC Analysis

Find component values to establish a bias point of $I_D = 1 \text{ mA}$, $V_{DQ} = 5 \text{ V}$ and $V_{DS} = 3 \text{ V}$. $V_{DD} = 15 \text{ V}$ and $K = 500 \mu\text{A/V}^2$ and $V_T = 0.5 \text{ V}$


$$I_D = K(V_{GS} - V_T)^2$$

$$V_{GS} = V_T + \sqrt{\frac{I_D}{K}} = 0.5 + \sqrt{\frac{0.001}{0.0005}} = 1.91 \text{ V}$$

$$R_D = \frac{V_{DD} - V_{DQ}}{I_D} = \frac{15 - 5}{0.001} = \frac{10}{0.001} = 10 \text{ k}\Omega$$

$$V_S = V_{DQ} - V_{DS} = 5 - 3 = 2 \text{ V}$$
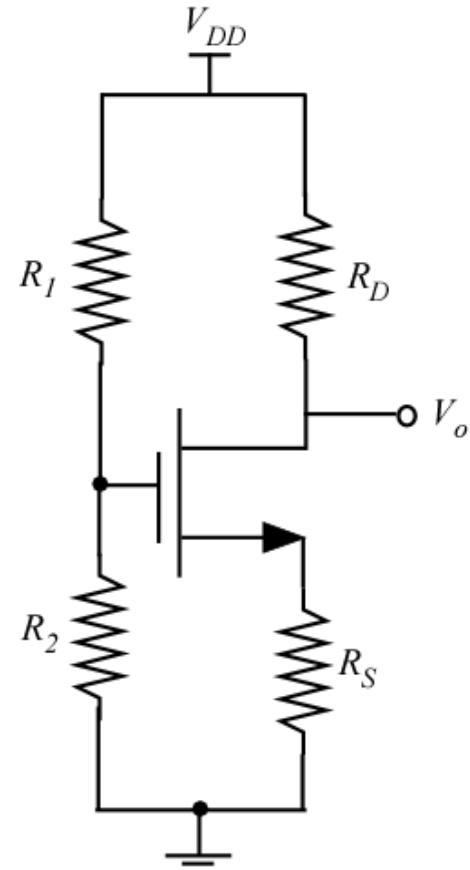
$$R_S = \frac{V_S}{I_D} = \frac{2}{0.001} = 2 \text{ k}\Omega$$



CS Amplifier – DC Analysis

Need to find R_1 and R_2 . First get V_{GQ}

$$V_{GQ} = V_{GS} + I_D R_S = 1.91 + 2 = 3.91V$$

Choose current through R_1 and R_2 to be 1 μ A. Then, we have

$$R_1 + R_2 = \frac{15}{10^{-6}} = 15 M\Omega$$

$$R_2 = (R_1 + R_2) \frac{V_{GQ}}{V_{DD}} = (15M) \frac{3.9}{15} = 3.9 M\Omega$$

$$R_1 = 11.1 M\Omega$$

