

# ECE 342


# Electronic Circuits

## Lecture 15


## BJT – DC Operation

Jose E. Schutt-Aine  
Electrical & Computer Engineering  
University of Illinois  
[jesa@illinois.edu](mailto:jesa@illinois.edu)


# BJT – Common-Emitter Characteristics

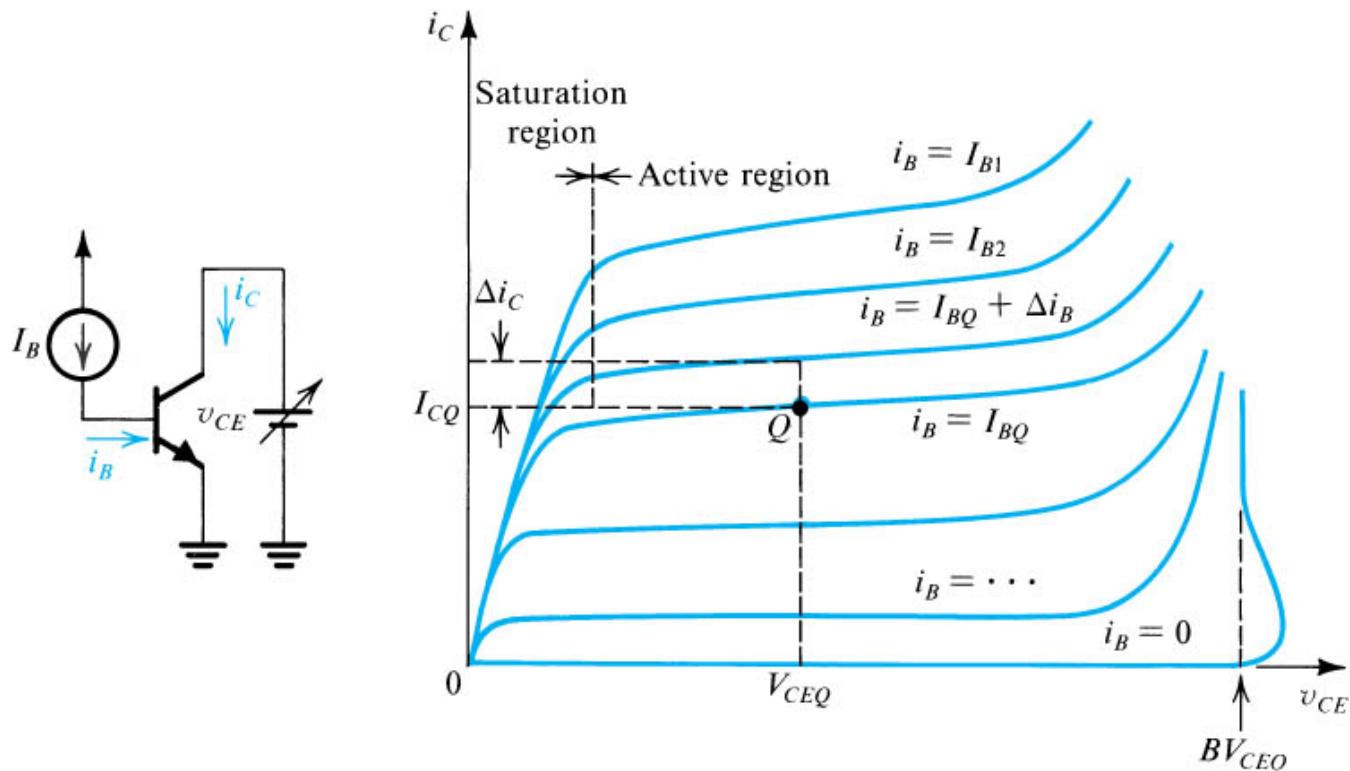

# BJT – Voltage-Current Characteristics

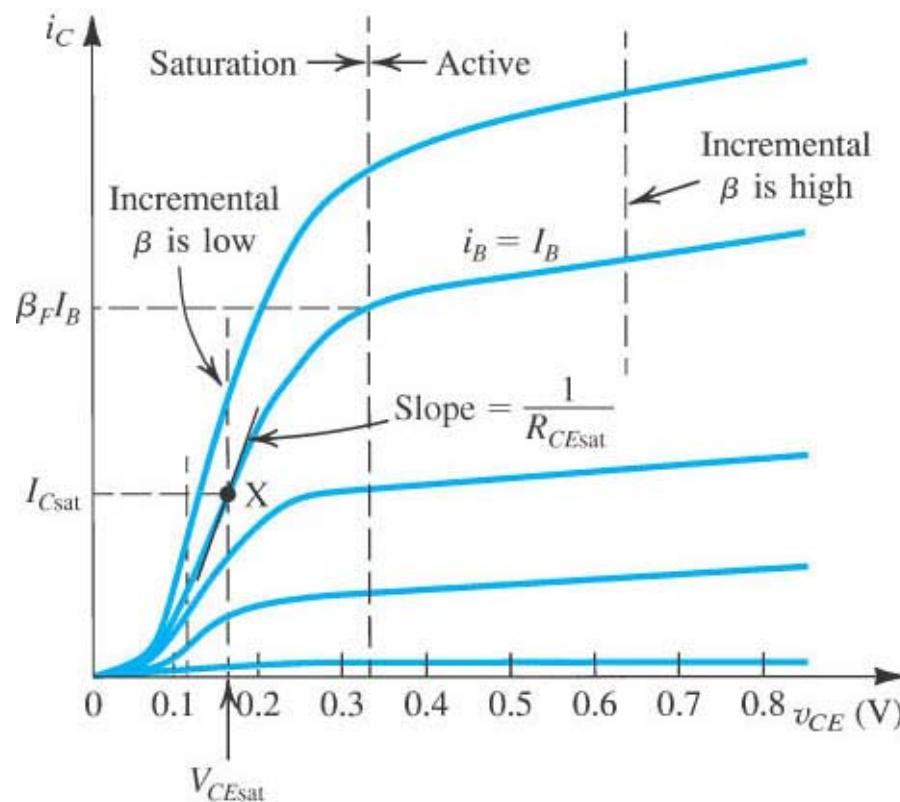



# Common Emitter Configuration

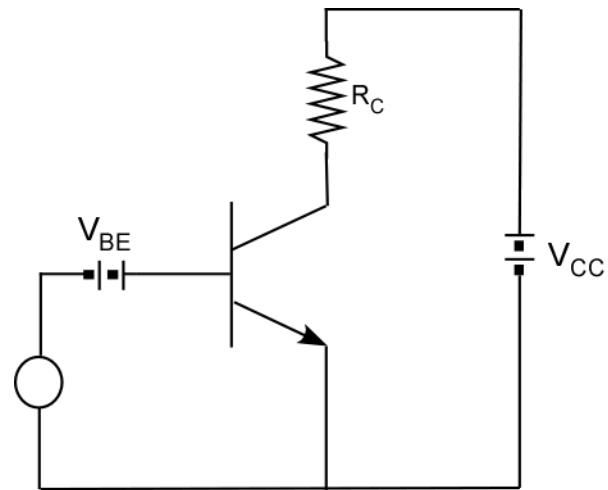



$$I_E = I_B + I_C$$

$$I_C = \alpha I_E$$

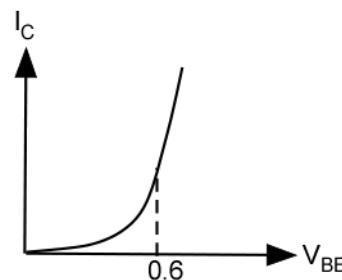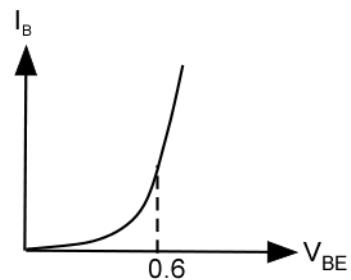
$$I_C = \frac{\alpha}{1-\alpha} I_B = \beta I_B$$



# Common Emitter I-V Characteristics

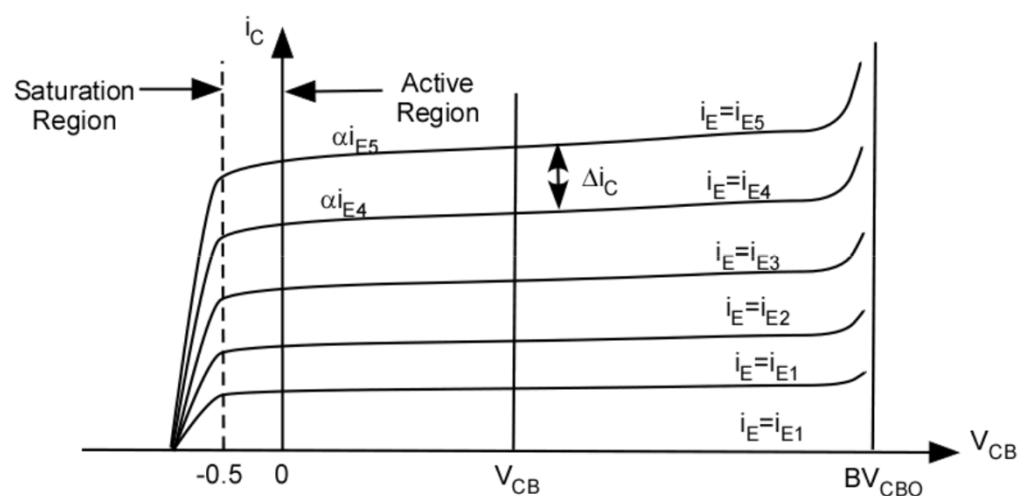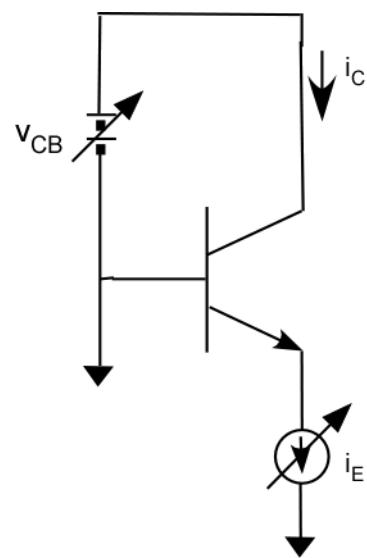

# Early Voltage

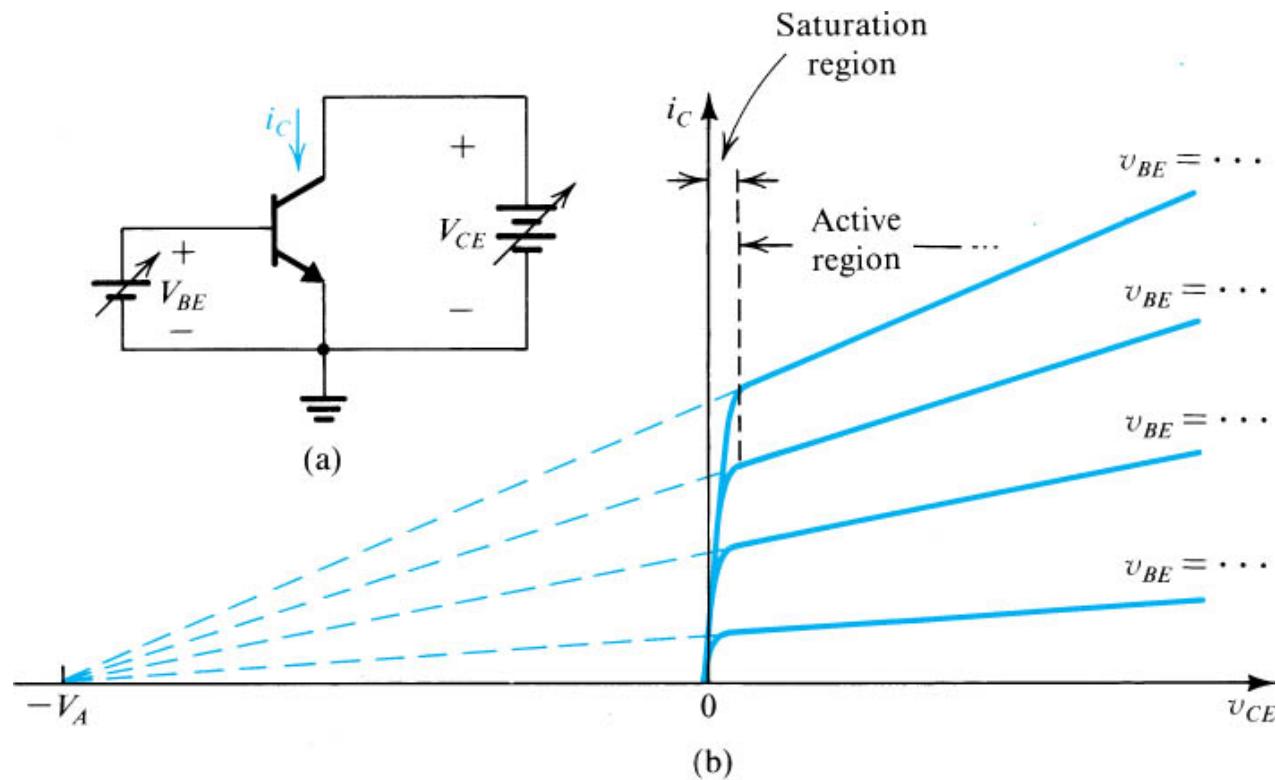

- **Early Voltage  $V_A$** 
  - Dependence of collector current on collector voltage
  - Increasing  $V_{CE}$  increases the width of the depletion region

# Output Resistance

$r_o$  is output resistance seen from collector terminal

$$i_C = I_s e^{V_{BE}/V_T} \left( 1 + \frac{V_{CE}}{V_A} \right)$$

$$r_o = \left[ \left. \frac{\partial i_C}{\partial V_{CE}} \right|_{V_{BE}=\text{constant}} \right]^{-1}$$

$$r_o = \frac{V_A + V_{CE}}{I_C}$$

Alternatively, neglecting the Early effect on the collector current, we define

$$\dot{I}_C = I_s e^{V_{BE}/V_T}$$


The output resistance then becomes

$$r_o = \frac{V_A}{\dot{I}_C}$$

# Problem

A transistor has  $\beta = 100$ ,  $v_{BE} = 0.7V$  with  $I_C = 1 \text{ mA}$ . Design a circuit such that a current of 2 mA flows through the collector and a voltage of 5V appears at the collector.

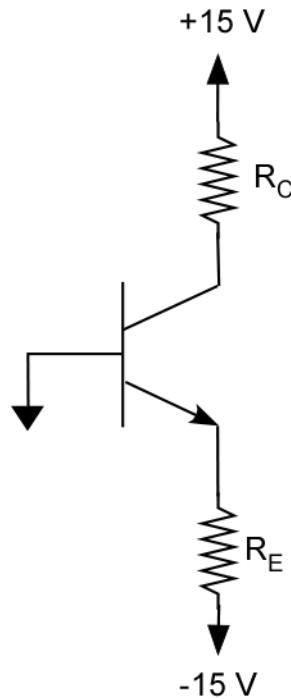**CBJ reversed biased  $\rightarrow$  FAR**



Voltage drop across  $R_C = 15 - 5 = 10V$   
 $I_C = 2 \text{ mA} \rightarrow R_C = 10V / 2 \text{ mA} = 5k\Omega$

Since  $v_{BE} = 0.7V$  at  $I_C = 1 \text{ mA}$

$$v_{BE} = 0.7 + V_T \ln\left(\frac{2}{1}\right) = 0.717 \text{ V at } 2 \text{ mA}$$

Since base is at 0V, emitter voltage is at  $-0.717 \text{ volts} = V_E$


For  $\beta = 100$ ,  $\alpha = 100/101 = 0.99 \rightarrow I_E = I_C/\alpha = 2/0.99 = 2.02 \text{ mA}$

$$\text{Now, } R_E = \frac{V_E - (-15)}{I_E} = \frac{-0.717 + 15}{2.02} = 7.07 \text{ k}\Omega$$


**This order of accuracy is not necessary**

# Operation in the Saturation Mode

## IV Characteristics

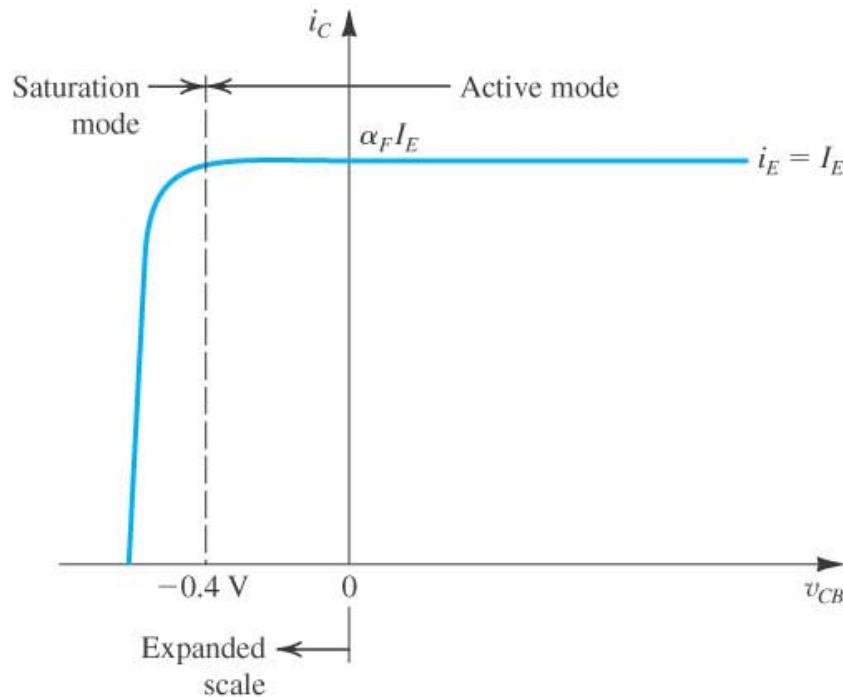

## Minority Carrier Profile

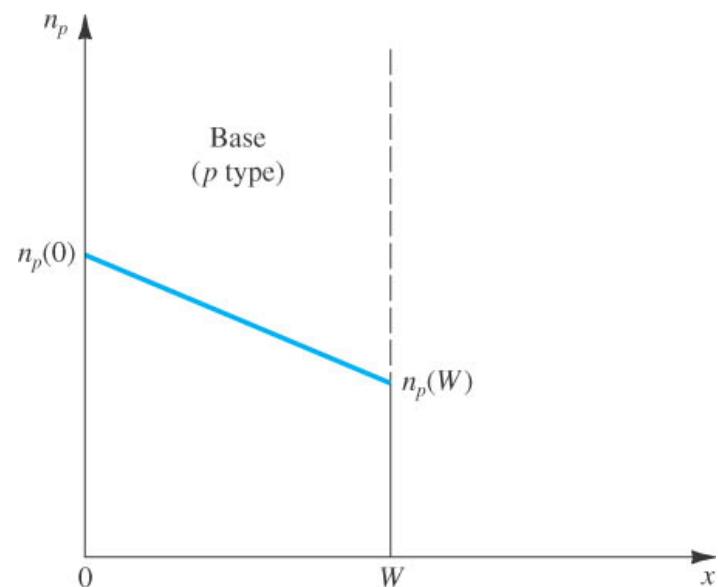

- Forward active region can be maintained for negative  $v_{CB}$  down to about -0.4V
- Beyond that point, the transistor enters the saturation mode and  $i_C$  decreases with decreasing  $v_{CB}$

# Operation in the Saturation Mode

If  $v_{BC}$  increases,  $i_C$  will decrease, as described by

$$i_C = I_S \left( e^{v_{BE}/V_T} - 1 \right) - \left( \frac{I_S}{\alpha_R} \right) \left( e^{v_{BC}/V_T} - 1 \right)$$

The base current  $i_B$  will decrease, as described by

$$i_B = \left( \frac{I_S}{\beta_F} \right) \left( e^{v_{BE}/V_T} - 1 \right) + \left( \frac{I_S}{\beta_R} \right) \left( e^{v_{BC}/V_T} - 1 \right)$$


The current gain will decrease to a value lower than  $\beta_F$  described as:

$$\beta_{forced} = \left. \frac{i_C}{i_B} \right|_{saturation} \leq \beta_F$$

We will also have:





$$V_{CEsat} = V_{BE} - V_{BC}$$

# Operation in the Saturation Mode

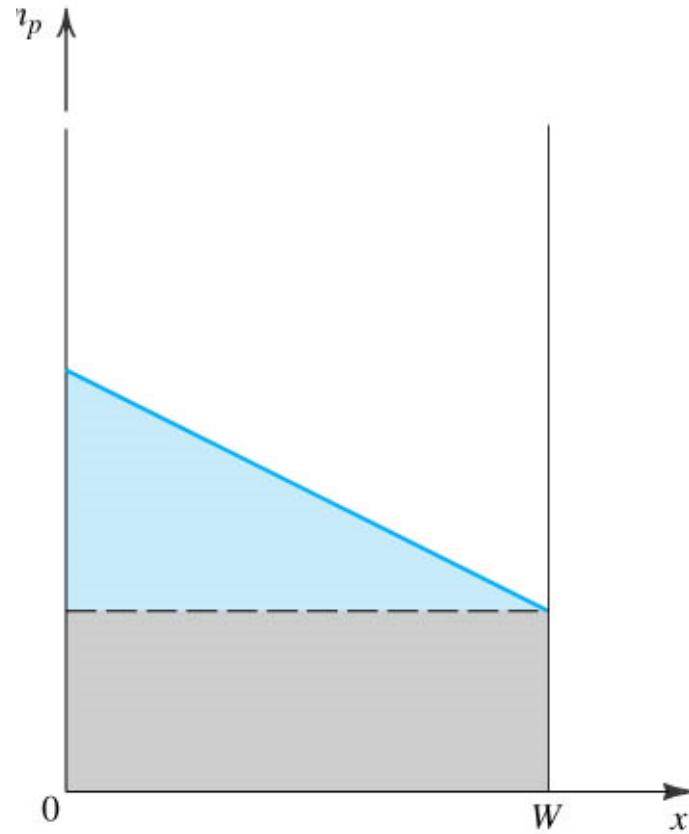


- Blue: Gradient that gives rise to diffusion current
- Gray: Minority carriers driving transistor deeper into saturation

# NPN in Saturation Mode

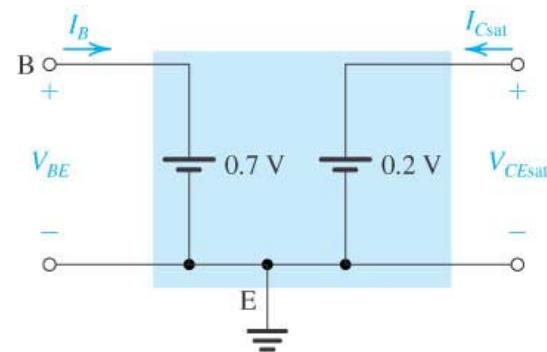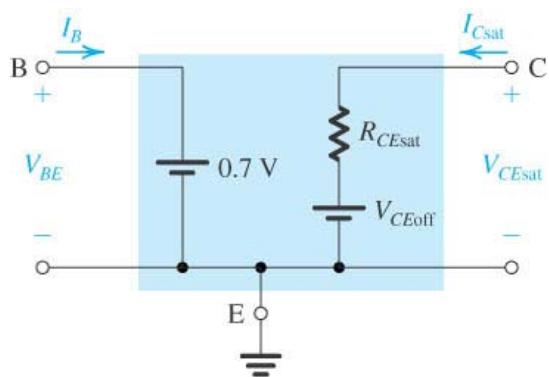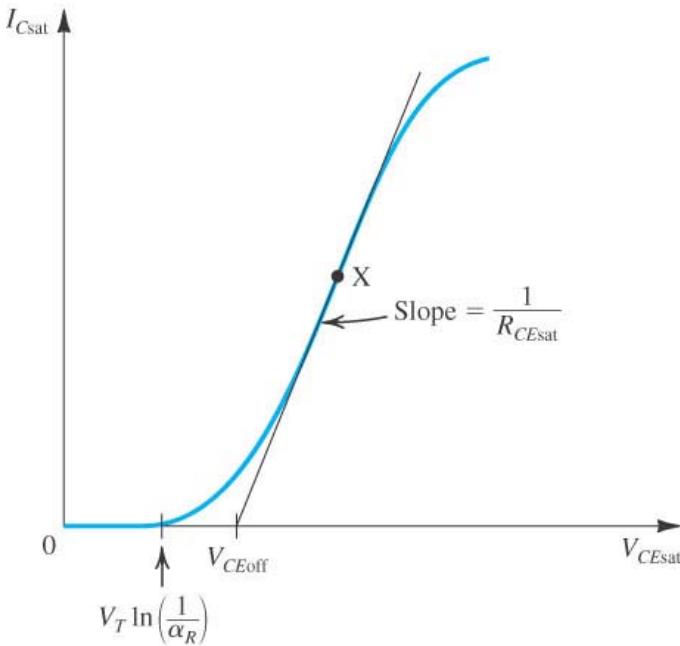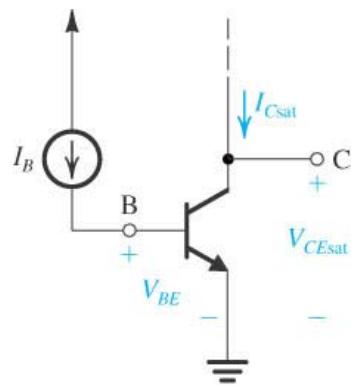


# Biasing Bipolar Transistors

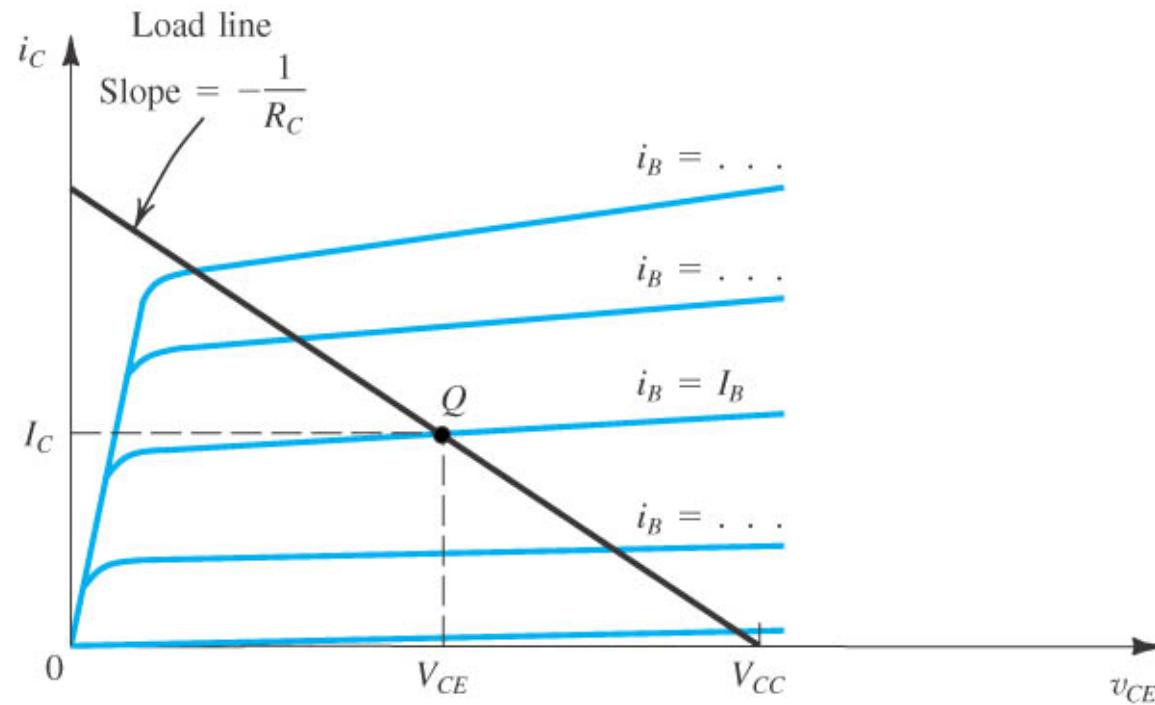

# BJT Bias

## 1. Base Current Bias

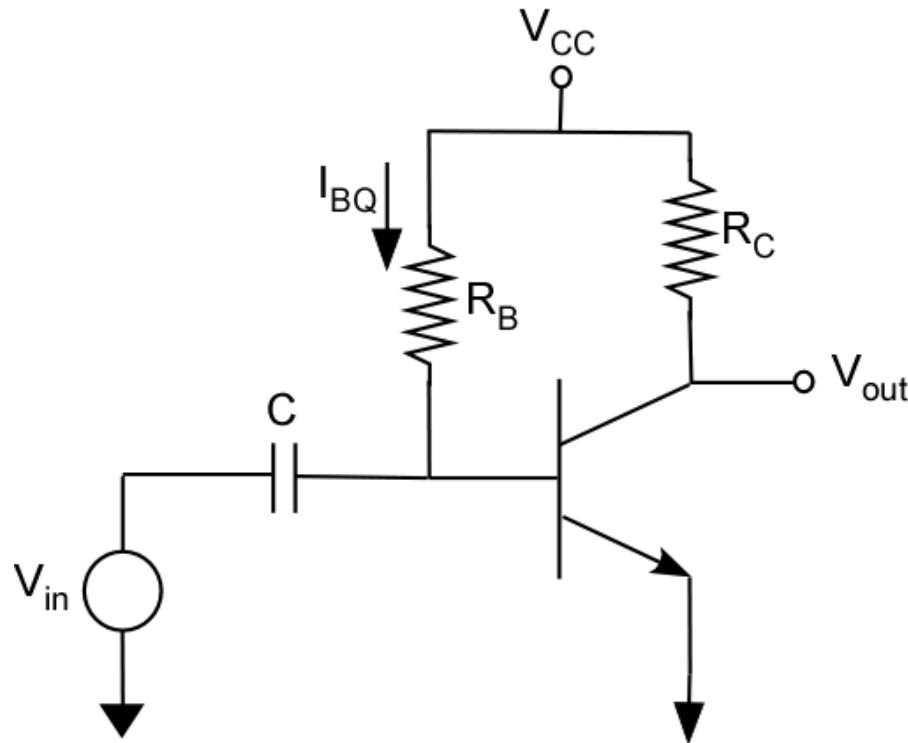


$$I_{BQ} = \frac{V_{CC} - V_{BE}}{R_B}$$

$$I_{BQ} = \frac{V_{CC} - 0.6}{R_B}$$


$$I_{BQ} \simeq \frac{V_{CC}}{R_B}$$

# BJT Bias

## 2. Emitter Bias

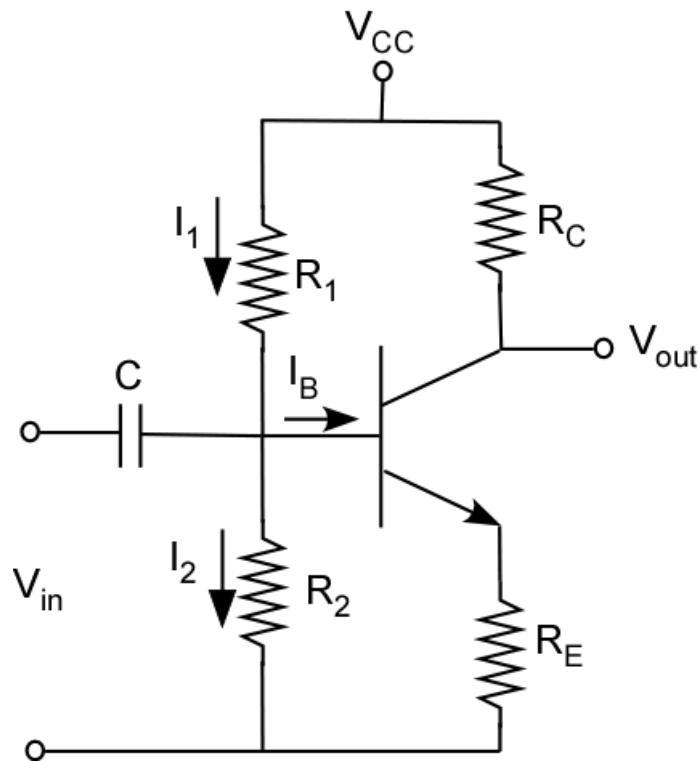


Thevenin Equivalent

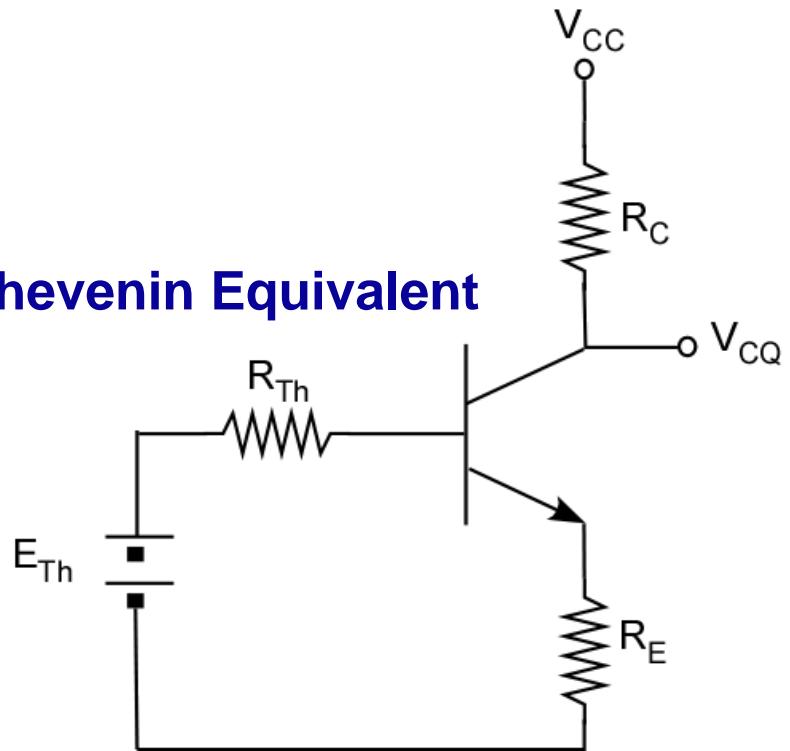

Provides good stability with respect to changes in  $\beta$  with temperature

# BJT Emitter Bias

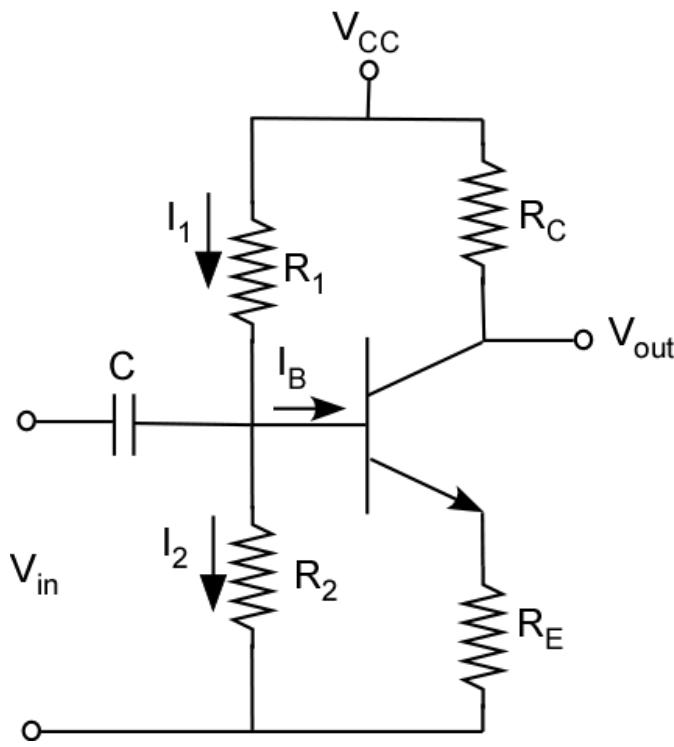

$$E_{th} = \frac{R_2}{R_1 + R_2} V_{CC}$$

$$R_{th} = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$$


$$E_{th} = R_{th} I_B + V_{BE} + R_E I_E$$

$$I_E = I_B + I_C = (\beta + 1) I_B$$

$$E_{th} - V_{BE} = R_{th} I_B + R_E (\beta + 1) I_B$$

$$I_B = I_{BQ} = \frac{E_{th} - V_{BE}}{R_{th} + (\beta + 1) R_E}$$

Thevenin Equivalent

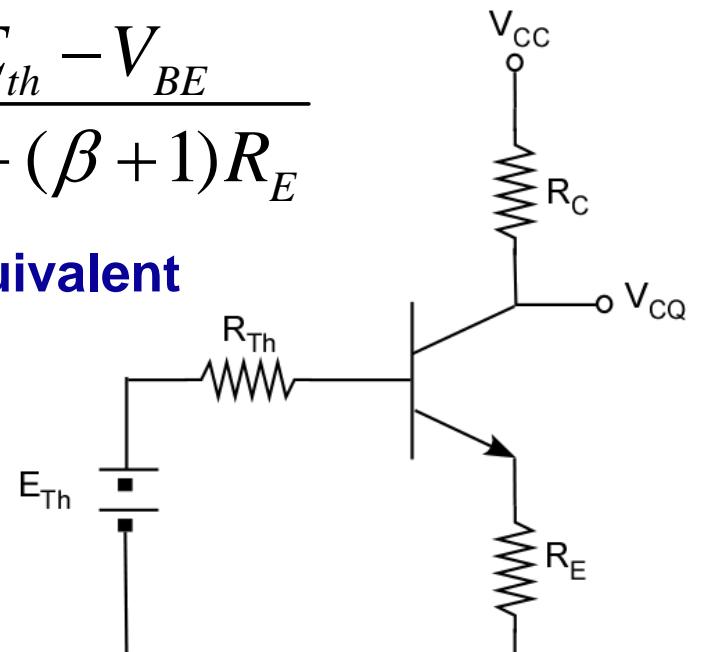


# Bipolar Biasing Approach

- **Methods**

- First method is to find  $R_1$  &  $R_2$  from  $E_{th}$  and  $R_{th}$  and  $I_{BQ}$
- Second method is to select  $R_2$  to be 10 times to 20 times  $R_E$  to provide good stability & then select  $R_1$  to give proper  $I_{BQ}$

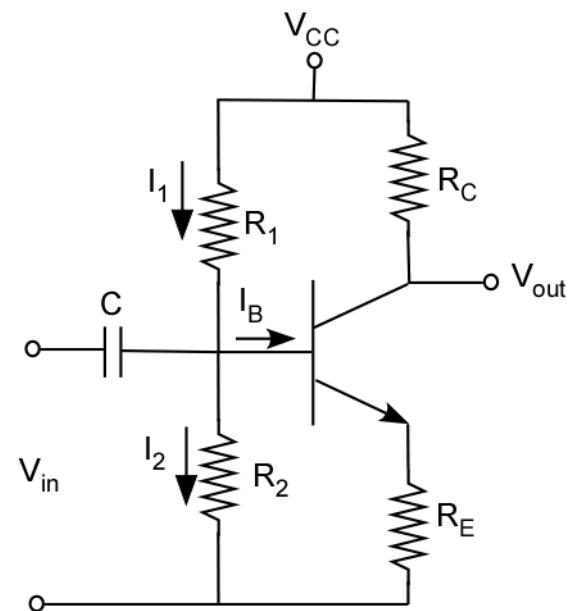**Remark: To keep collector voltage at the middle of the forward active region, use:**

$$V_{CQ} = \frac{V_{C\min} + V_{C\max}}{2} = \frac{V_{CC}}{2} \left( 1 + \frac{R_E}{R_E + R_C} \right)$$



# Stability Considerations

**Objective:** Minimize effect of variations in  $\beta$ . Circuit must be stable with respect to changes in  $\beta$ .


- Need to examine quiescent point in variations for interchanged BJT's

$$V_{CQ} = V_{CC} - I_{CQ}R_C = V_{CC} - \beta I_{BQ}R_C$$

$$R_{th}I_{BQ} + (\beta + 1)I_{BQ}R_E = E_{th} - V_{BE}$$

$$I_{BQ} = \frac{E_{th} - V_{BE}}{R_{th} + (\beta + 1)R_E}$$
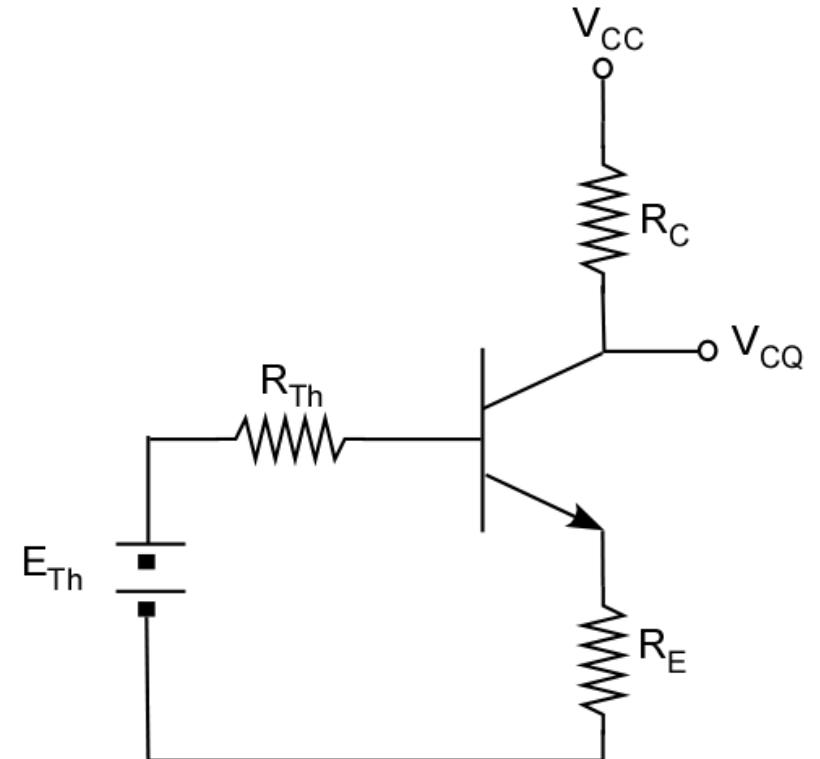
$$V_{CQ} = V_{CC} - \frac{\beta(E_{th} - V_{BE})R_C}{R_{th} + (\beta + 1)R_E}$$



# Stability Considerations

(A) If  $R_{th} \gg (\beta+1) R_E$

$$V_{CQ} \approx V_{CC} - \frac{\beta R_C}{R_{th}} (E_{th} - V_{BE})$$

Changes in  $\beta$  lead to significant changes in  $V_{CQ}$


(B) If  $(\beta+1) R_E \gg R_{th}$

$$V_{CQ} \approx V_{CC} - \frac{\beta R_C}{(\beta+1) R_E} (E_{th} - V_{BE})$$

$$V_{CQ} \approx V_{CC} - \frac{\alpha R_C}{R_E} (E_{th} - V_{BE})$$

$$\beta = 60 \Rightarrow \alpha = \frac{60}{61} = 0.983$$
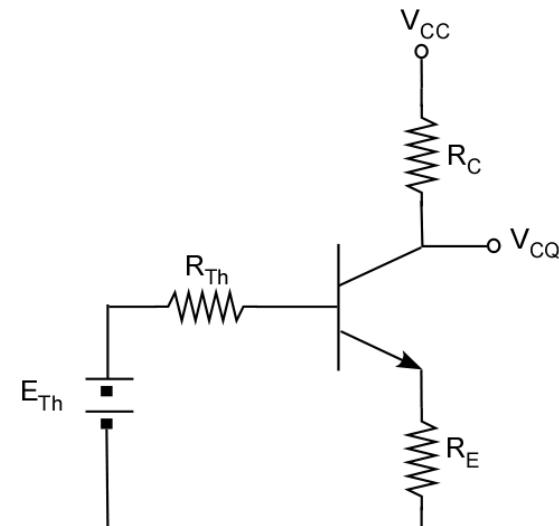
$$\beta = 100 \Rightarrow \alpha = \frac{100}{101} = 0.99$$




$\alpha$  varies only 1% to 2% for large  $\beta$  variations  $\rightarrow$  (B) is good choice.
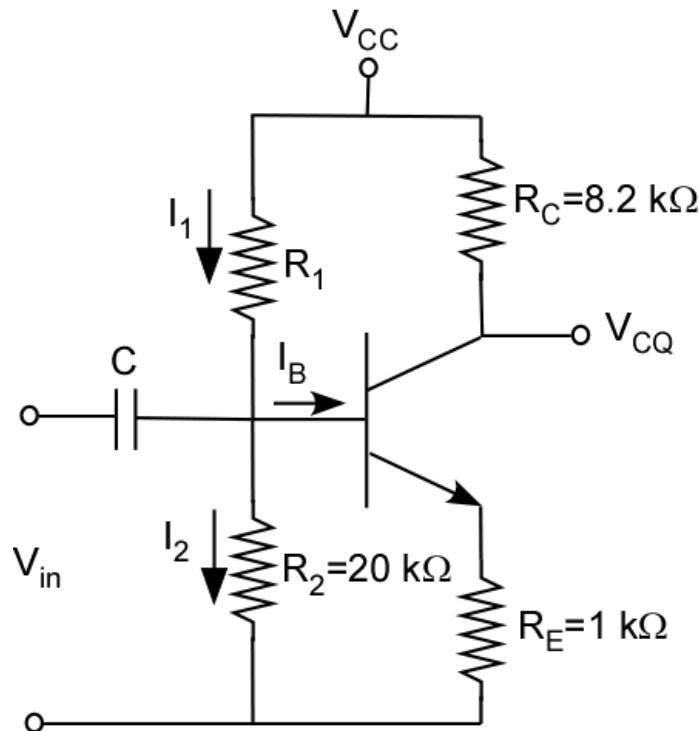
# Bias Example

The circuit shown below has  $R_C = 8.2 \text{ k}\Omega$ ,  $R_E = 1 \text{ k}\Omega$ ,  $R_2 = 20 \text{ k}\Omega$ ,  $V_{CC} = 12 \text{ V}$ ,  $\beta = 100$ ,  $V_{BE} = 0.7\text{V}$

- Select  $R_I$  to place  $V_{CQ}$  at midpoint of the (forward) active region.
- Find maximum symmetrical peak-to-peak output voltage that can be obtained before saturation or cutoff occurs.



# Bias Example - Solution

Minimum:

$$V_{CQ\min} = V_{CC} \frac{R_E}{R_E + R_C} = \frac{12}{1+8.2} = \frac{12}{9.2} = 1.3043 \text{ V}$$

Maximum:

$$V_{CQ\max} = V_{CC}$$

Midpoint:

$$V_{CQ} = \frac{V_{CQ\min} + V_{CQ\max}}{2} = \frac{13.3043}{2} = 6.65 \text{ V}$$

$$I_{CQ} = \frac{12 - 6.65}{R_C} = 0.652 \text{ mA}$$

$$I_{BQ} = \frac{0.652}{100} = 0.00652 \text{ mA} = 6.52 \mu\text{A}$$

# Bias Example (con't)

$$V_{BQ} = R_E I_E + 0.7 = 0.652 + 0.7 = 1.35 \text{ V}$$

$$I_2 = \frac{1.35 \text{ V}}{20 \text{ k}\Omega} = 0.0676 \text{ mA} = 67.6 \mu\text{A}$$

$$I_1 = I_2 + I_B = 67.6 \mu\text{A} + 6.82 \mu\text{A} = 74.1 \mu\text{A}$$

$$R_1 = \frac{V_{CC} - 1.35}{I_1} = \frac{12 - 1.35}{74.1 \mu\text{A}} = 143.6 \text{ k}\Omega$$

$$V_{\max} = 12 - 6.65 = 5.35 \text{ V}$$

$$\boxed{\begin{aligned} R_1 &= 143.6 \text{ k}\Omega \\ V_{\max} &= 5.35 \text{ V} \end{aligned}}$$