

# ECE 342

# Electronic Circuits


  

## Lecture 20


## Transfer Functions - 1

Jose E. Schutt-Aine  
Electrical & Computer Engineering  
University of Illinois  
jesa@Illinois.edu


# What is Capacitance?

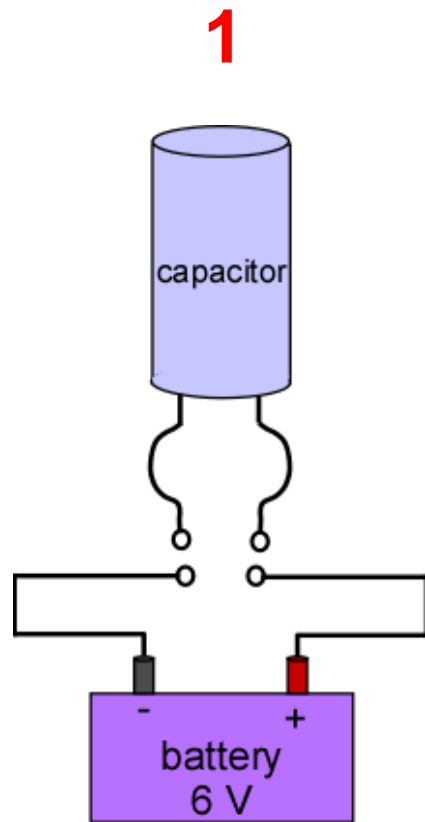

Voltage=0  
No Charge  
No Current

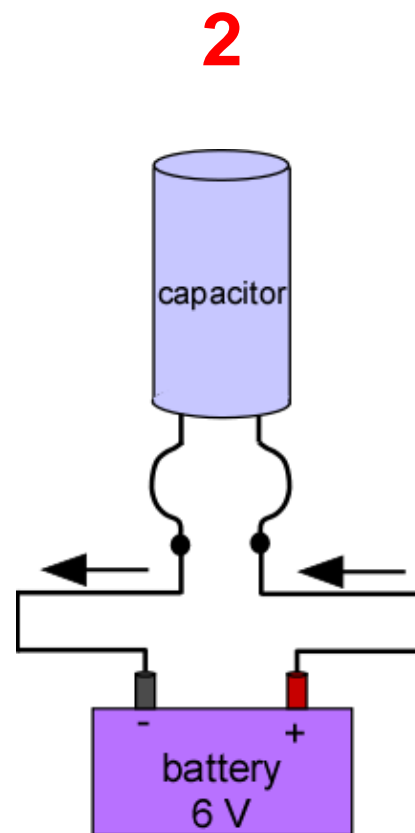


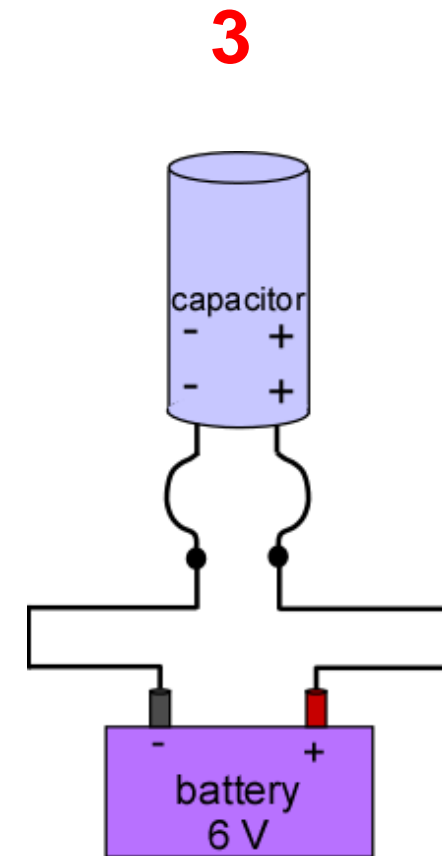Voltage build up  
Charge build up  
Transient Current




Voltage = 6V  
Charge=Q  
No Current


# What is Capacitance?

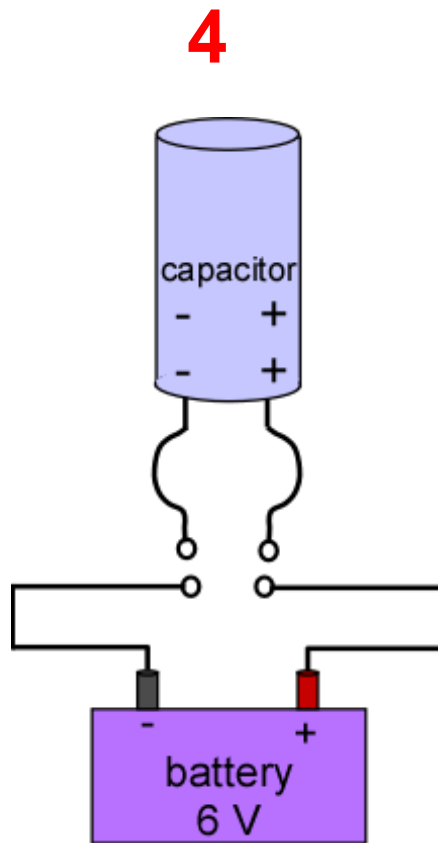

Voltage=6V  
Charge=Q  
No Current

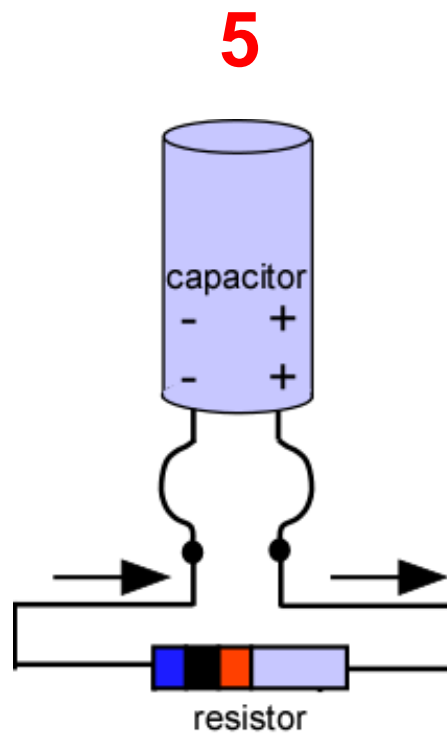

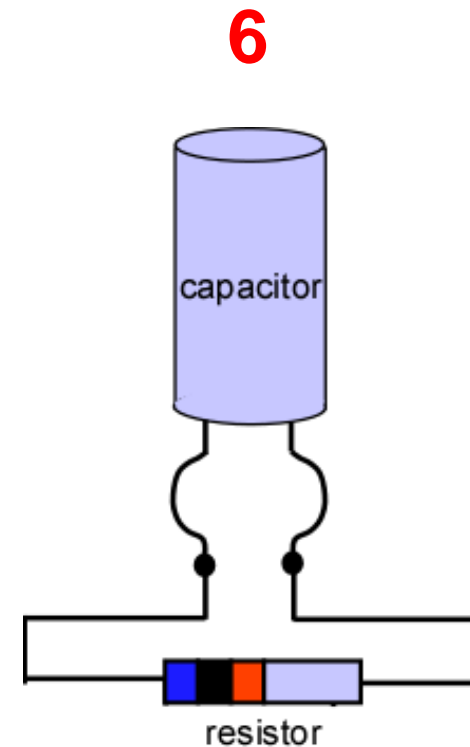Voltage decaying  
Charge decaying  
Transient Current



Voltage=0  
No Charge  
No Current

# Capacitance

Relation:  $Q = Cv$

$Q$ : charge stored by capacitor



$C$ : capacitance

$v$ : voltage across capacitor

$i$ : current into capacitor


$$i(t) = C \frac{dv}{dt} = \frac{dQ}{dt}$$
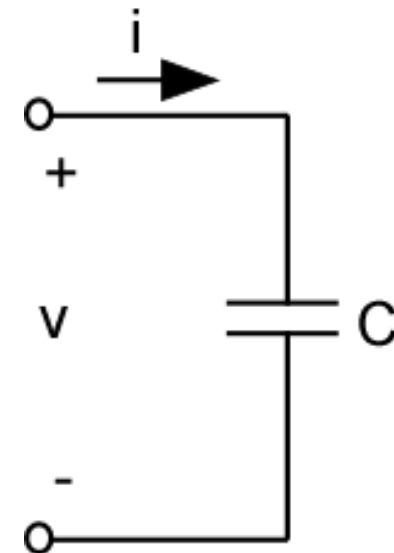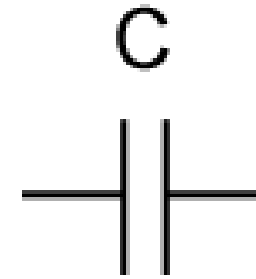
$$v(t) = \frac{1}{C} \int_0^t i(\tau) d\tau$$



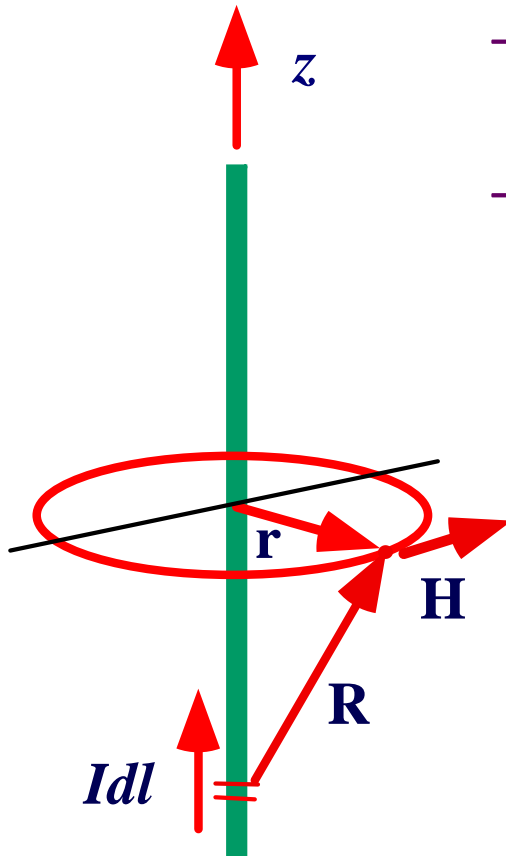
# What is Inductance?

- *Current in wire produces magnetic field*
- *Flux is magnetic field integrated over area*



$$\text{Inductance} = \frac{\text{Total Flux Linked}}{\text{Current}}$$

# Inductance

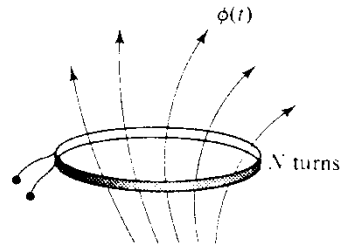

$$L = N \frac{d\Psi}{di}$$

$$L = \frac{\Psi}{I}$$

$$L = \int_v \frac{\vec{B} \cdot \vec{H} dv}{I^2}$$

# Inductance

Relation:  $\Psi = Li$

$\Psi$ : flux stored by inductor


$L$ : inductance

$i$ : current through inductor

$v$ : voltage across inductor

$$v(t) = L \frac{di}{dt} = \frac{d\Psi}{dt}$$
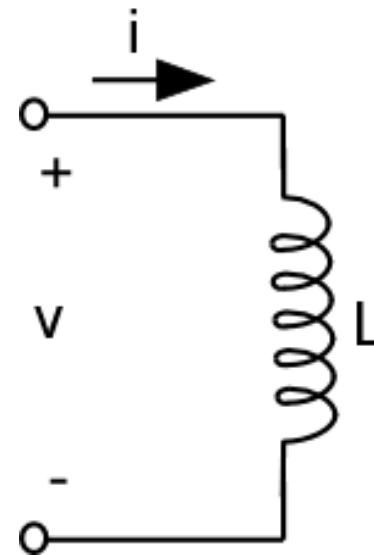
$$i(t) = \frac{1}{L} \int_0^t v(\tau) d\tau$$




# Low-Pass Circuit

$$i_R(t) = C \frac{dv_o}{dt} = i_C(t)$$

$$v_i(t) = Ri_R(t) + v_o(t)$$

$$v_i(t) = RC \frac{dv_o}{dt} + v_o(t)$$

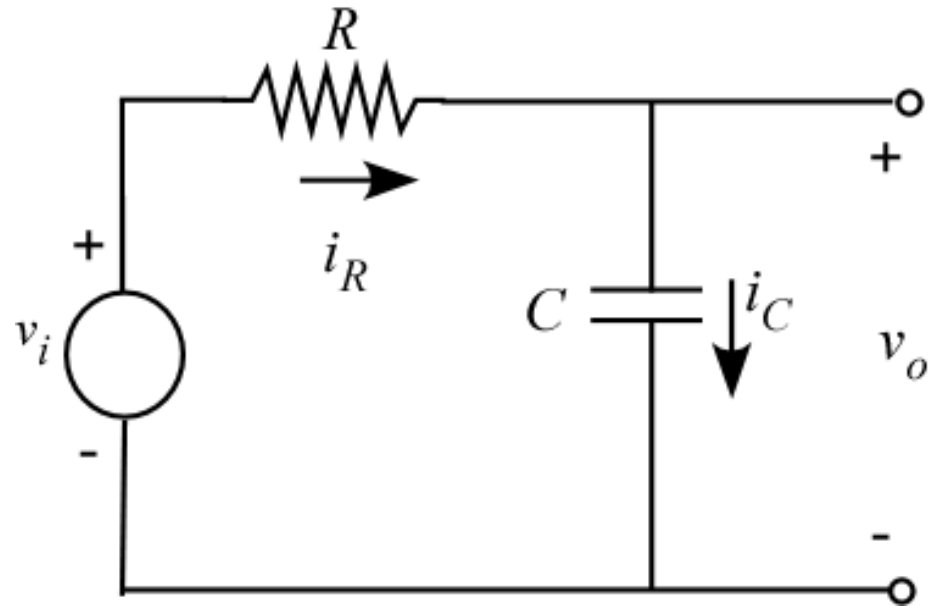

**Need to solve for  $v_o(t)$**




# Low-Pass Circuit

$$i_R(t) = C \frac{dv_o}{dt} = i_C(t)$$


$$v_i(t) = Ri_R(t) + v_o(t)$$

$$v_i(t) = RC \frac{dv_o}{dt} + v_o(t)$$

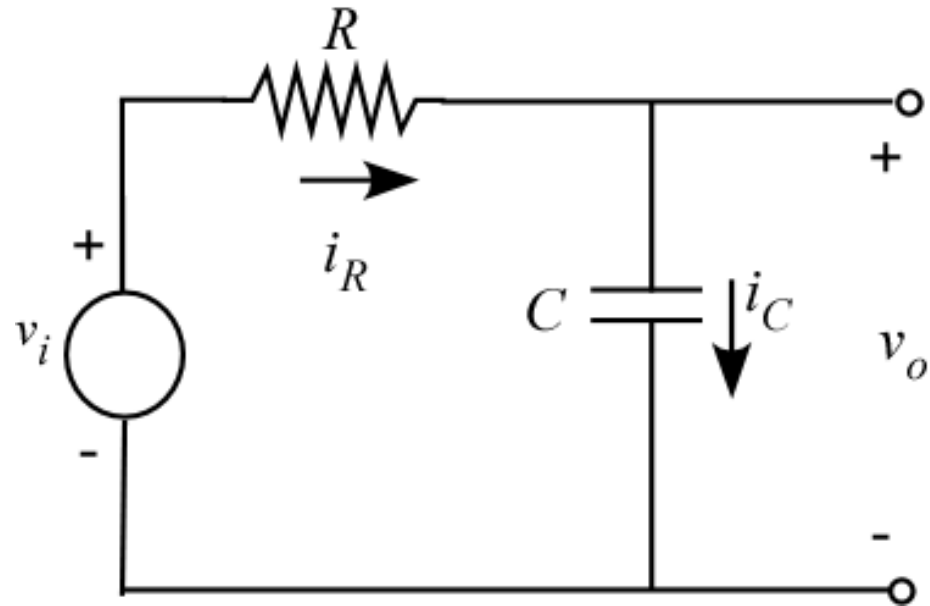

**Need to solve for  $v_o(t)$**

# Reactive Circuit

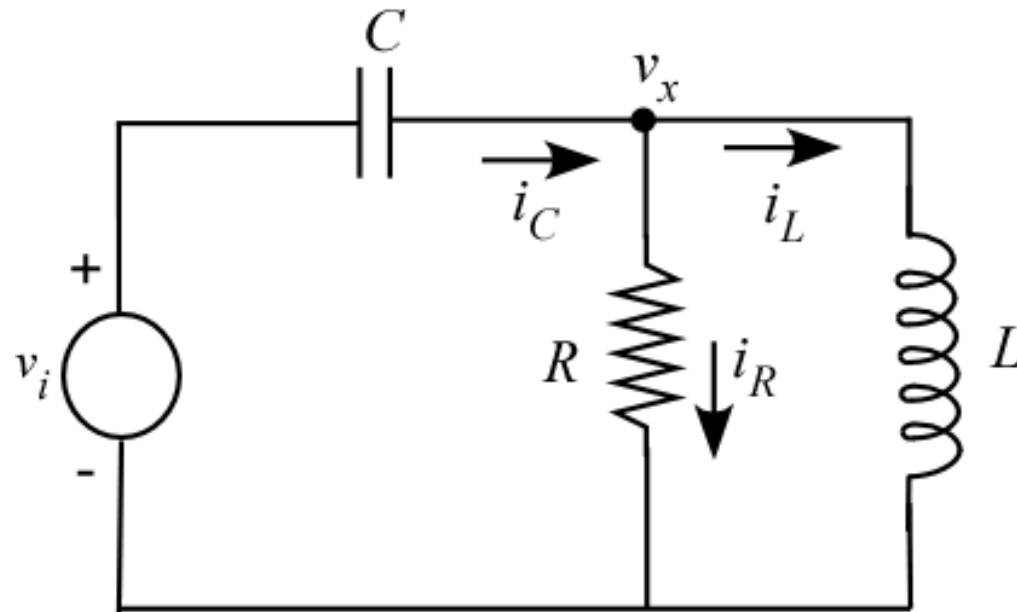

$$i_C(t) = i_R(t) + i_L(t)$$

**Need to solve for  $v_x(t)$**

$$v_x = L \frac{di_L}{dt} \quad i_C = C \frac{d(v_i - v_x)}{dt}$$

# Laplace Transforms

The Laplace transform  $F(s)$  of a function  $f(t)$  is defined as:

$$L\{f(t)\} = \int_0^{\infty} f(t)e^{-st} dt = F(s)$$

To a mathematician, this is very meaningful; however circuit engineers seldom use that integral

The Laplace transform provides a conversion from the time domain into a new domain, the  $s$  domain

# Laplace Transforms


The Laplace transform of the derivative of a function  $f(t)$  is given by

$$L\left\{\frac{df(t)}{dt}\right\} = \int_0^{\infty} \frac{df(t)}{dt} e^{-st} dt = sF(s)$$

**Differentiation in the time domain becomes a multiplication in the s domain. That is why Laplace transforms are useful to circuit engineers**

$$s = j\omega$$

# Low-Pass Circuit

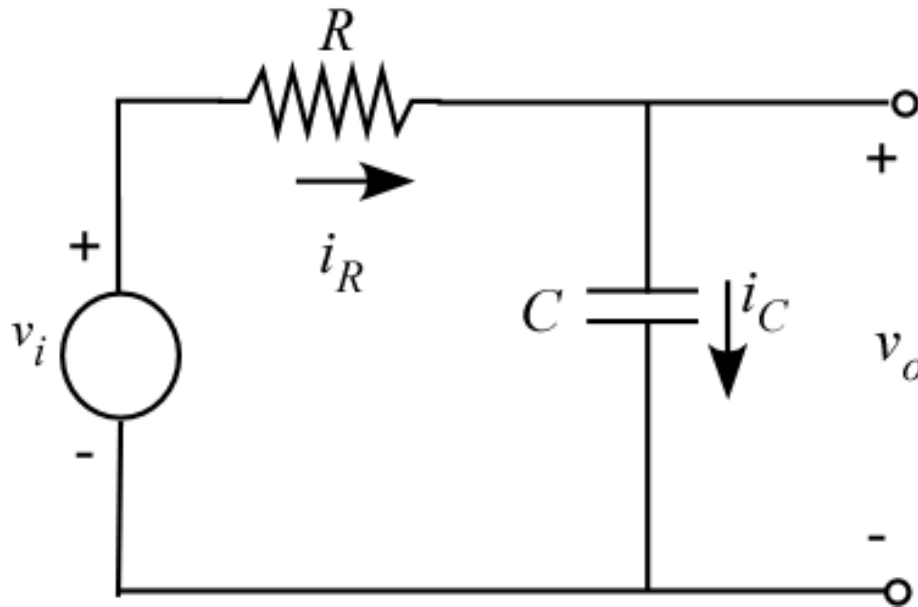

Time domain      s domain

$$v_o(t) \leftrightarrow V_o(s)$$

$$\frac{dv_o(t)}{dt} \leftrightarrow sV_o(s)$$

Time domain

s domain

$$v_i(t) = RC \frac{dv_o}{dt} + v_o(t) \longleftrightarrow V_i(s) = sRCV_o(s) + V_o(s)$$

# Low-Pass Circuit - Solution

$$V_o(s) = \frac{V_i(s)}{1 + sRC} \Rightarrow \frac{V_o(s)}{V_i(s)} = \frac{1}{1 + sRC}$$

Pole exists at  $s = -1/RC$

Assume that  $V_i(s) = V_d/s$


$$V_o(s) = \frac{V_d}{s(1 + sRC)} = \frac{A}{s} + \frac{B}{(s + 1/RC)}$$

Inversion



$$v_o(t) = Au(t) + Be^{-t/RC}$$

# Reactive Circuit

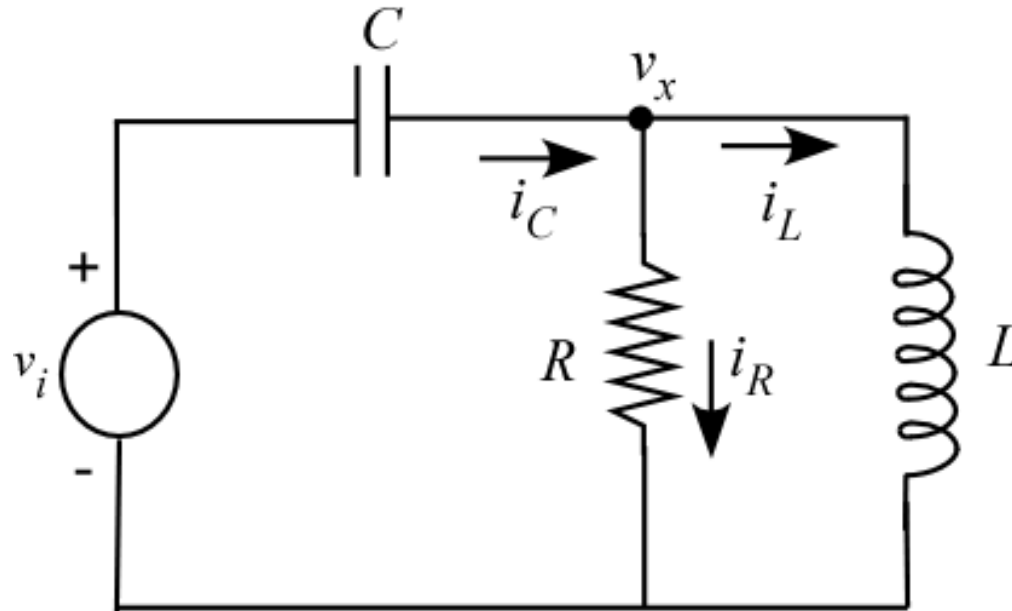

$$v_x = L \frac{di_L}{dt}$$

$$V_x(s) = sLI_L$$

$$i_C = C \frac{d(v_i - v_x)}{dt}$$

$$I_C = sC(V_i - V_x)$$

## Reactive Circuit - Solution

$$sC(V_i - V_x) = \frac{V_x}{R} + \frac{V_x}{sL}$$

$$sCV_i = V_x \left( sC + \frac{1}{R} + \frac{1}{sL} \right)$$

$$V_x = \frac{sCV_i}{\left( sC + \frac{1}{R} + \frac{1}{sL} \right)} = \frac{V_i}{\left( 1 + \frac{1}{sRC} + \frac{1}{s^2LC} \right)}$$

**Exercise: Use inversion to solve for  $v_x(t)$**



# Table of Laplace Transforms

Function	Transform
$u(t - \alpha)$	$\frac{1}{s} e^{-\alpha s}$
$e^{-\alpha t}$	$\frac{1}{s + \alpha}$
$\cos(\alpha t)$	$\frac{s}{s^2 + \alpha^2}$

# Capacitance – s Domain


Assume time-harmonic behavior of voltage and current variables  $j\omega = s$

$$i(t), v(t) \sim e^{j\omega t}$$

$$i(t) \leftrightarrow I(s)$$

$$v(t) \leftrightarrow V(s)$$

$$\frac{d}{dt} \leftrightarrow s$$

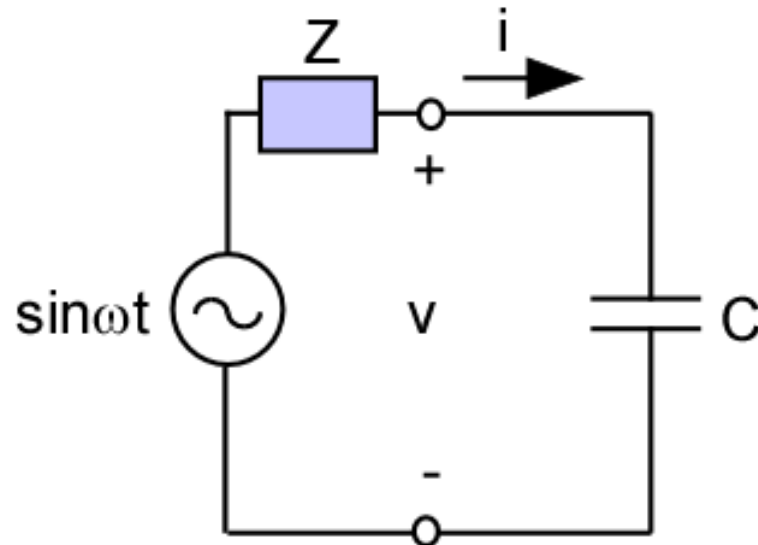

$$I(s) = sCV(s)$$

**The capacitor is a reactive element**

$$\text{Reactance : } X_C = \frac{1}{sC}$$

# Inductance – s Domain


Assume time-harmonic behavior of voltage and current variables  $j\omega = s$

$$i(t), v(t) \sim e^{j\omega t}$$

$$i(t) \leftrightarrow I(s)$$

$$v(t) \leftrightarrow V(s)$$

$$\frac{d}{dt} \leftrightarrow s$$

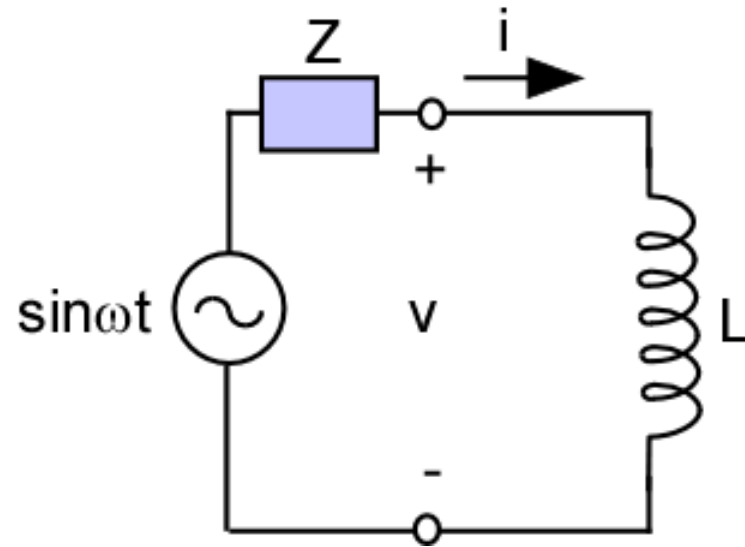


$$V(s) = sLI(s)$$

**The inductor is a reactive element**

$$\text{Reactance: } X_L = sL$$

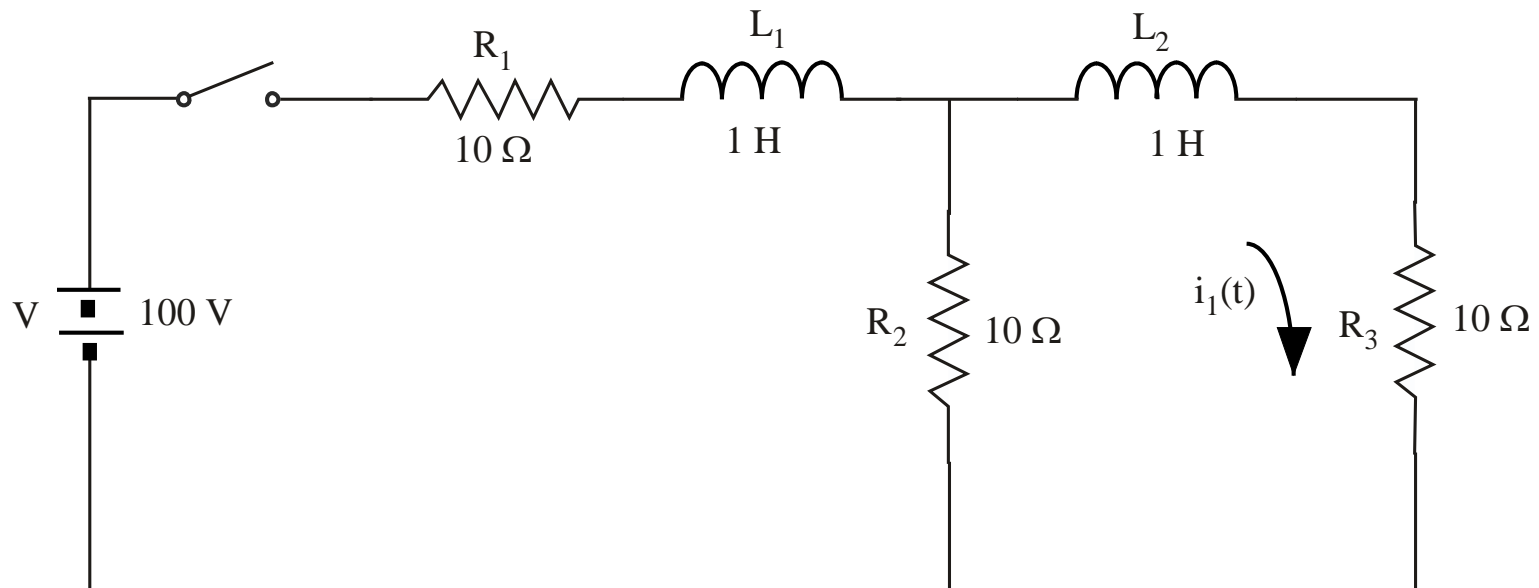
# Transfer Function

Need to find the current  $i_1(t)$  in resistor  $R_3$



# Transfer Function


## Thevenin voltage calculation

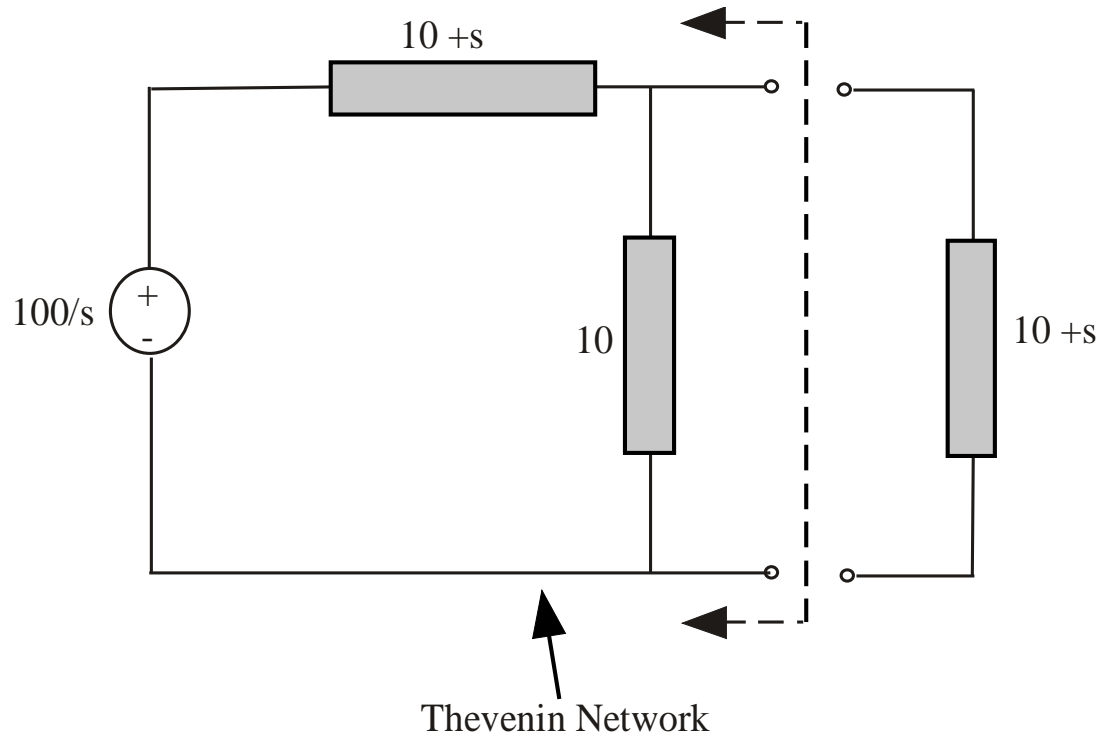

$$V_{th} = \frac{10(100/s)}{10 + s + 10} = \frac{1,000}{s(s + 20)}$$


# Transfer Function

## Calculating the impedance

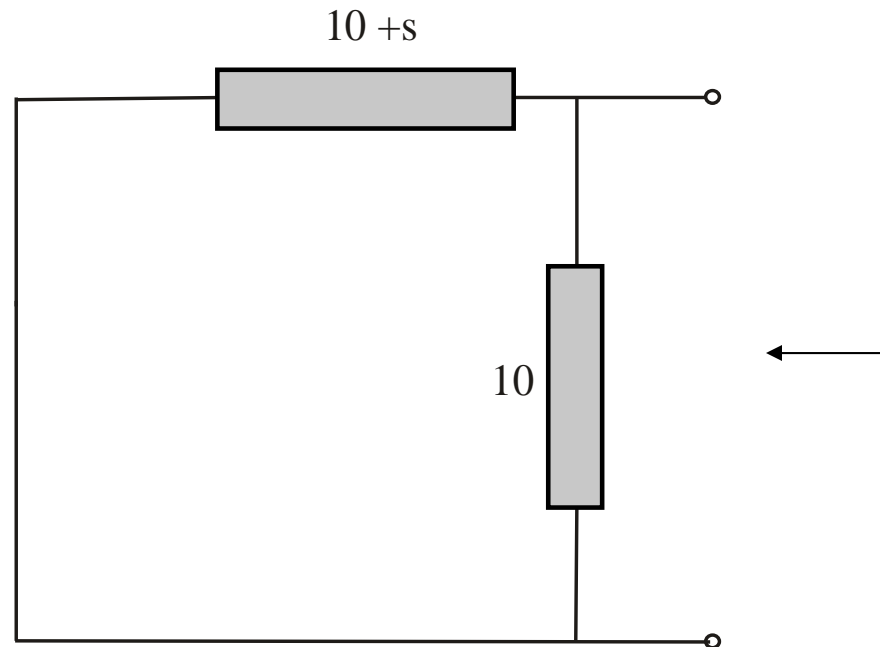

$$Z_{th} = \frac{10(s + 10)}{(s + 20)}$$

# Transfer Function

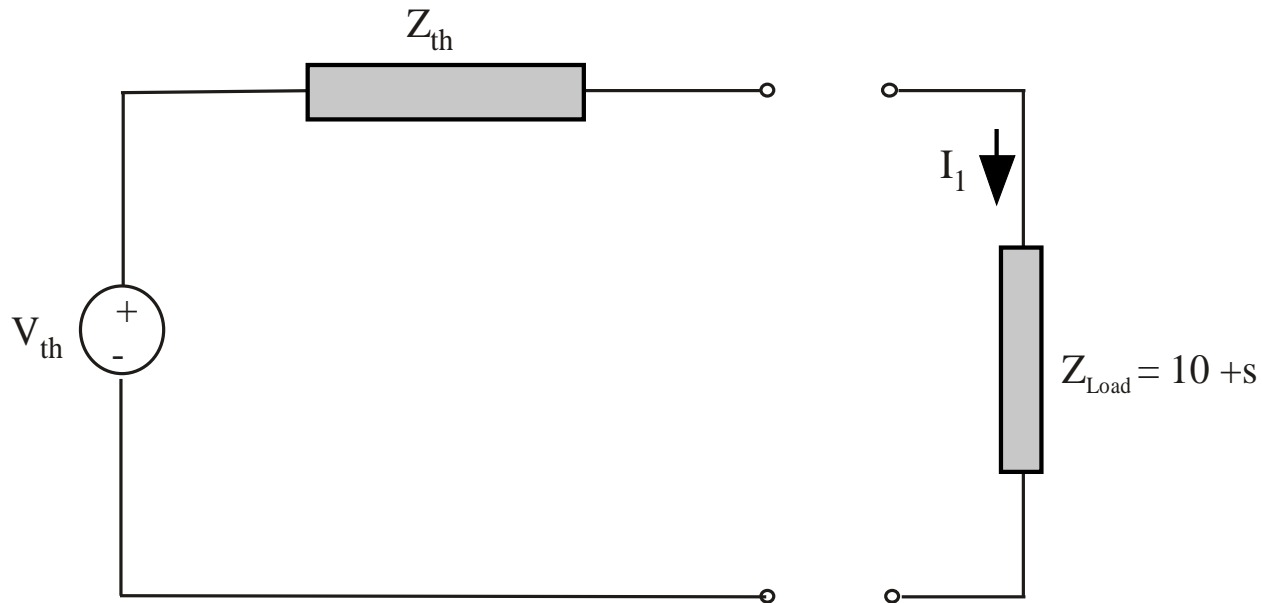

$$I_1(s) = \frac{V_{th}(s)}{Z_{th}(s) + Z_{Load}} = \frac{1,000}{\frac{10(s+10)}{s+20} + (s+10)}$$

$$I_1(s) = \frac{1,000}{s(s^2 + 40s + 300)}$$

## Expanding using partial fraction

$$I_1(s) = \frac{K_1}{s} + \frac{K_2}{(s+10)} + \frac{K_3}{(s+30)}$$

With  $K_1 = 3.33$ ,  $K_2 = -5$ ,  $K_3 = 1.67$

The time-domain current  $i_1(t)$  is:

$$i_1(t) = 3.33 - 5e^{-10t} + 1.67e^{-30t} \quad A$$



# Octave & Decade

If  $f_2 = 2f_1$ , then  $f_2$  is one octave above  $f_1$

If  $f_2 = 10f_1$ , then  $f_2$  is one decade above  $f_1$


$$\# \text{ of octaves} = \log_2 \frac{f_2}{f_1} = 3.32 \log_{10} \frac{f_2}{f_1}$$

$$\# \text{ of decades} = \log_{10} \frac{f_2}{f_1}$$

2 GHz is one octave above 1 GHz

10 GHz is one decade above 1 GHz

# Low-Pass Circuit

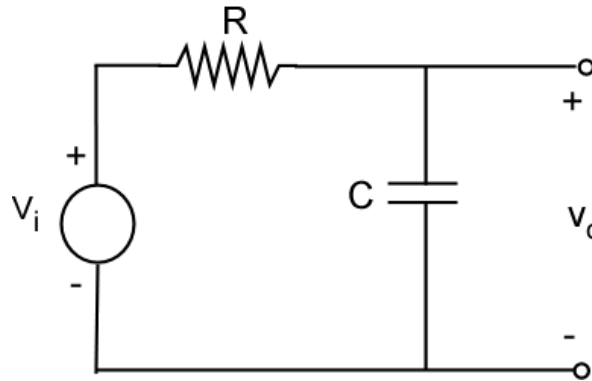

In frequency domain:

$$V_o = \frac{V_i}{R + \frac{1}{j\omega C}} \cdot \frac{1}{j\omega C}$$

$$V_o = \frac{V_i}{1 + j\omega RC} \Rightarrow A_v = \frac{V_o}{V_i} = \frac{1}{1 + j\omega RC}$$

$$A_v = \frac{1}{1 + j\omega RC} = \frac{1}{1 + jf / f_o}$$

# Low-Pass Circuit

$$f_o = \frac{1}{2\pi RC} = \frac{1}{2\pi\tau}$$


$\tau = RC =$  time constant

At very high frequencies, the single time constant (STC) transfer function goes as

$$G = -20 \log \sqrt{1 + (\omega / \omega_o)^2}$$

$$G \simeq -20 \log(\omega / \omega_o) = -20X$$



where  $X = \log(\omega / \omega_o)$

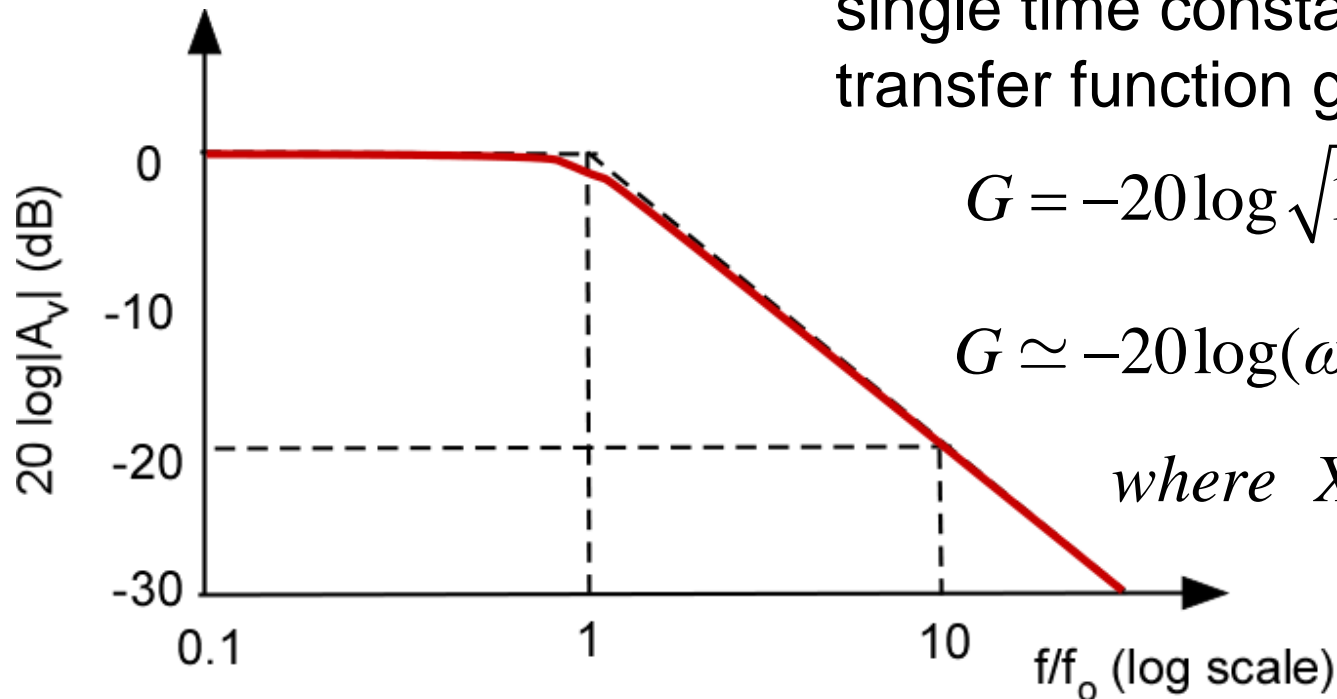

At high frequencies, slope of curve is  $-20$  dB

if  $X = 1$  ( $\omega = 10\omega_o$ ), decrease is  $-20$  dB  $\Rightarrow -20$  dB / decade

# High-Pass Circuit

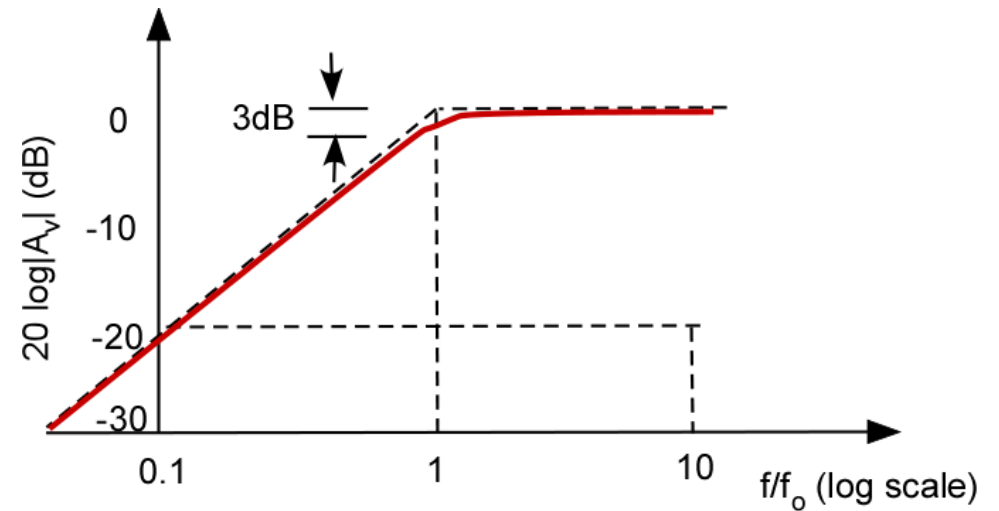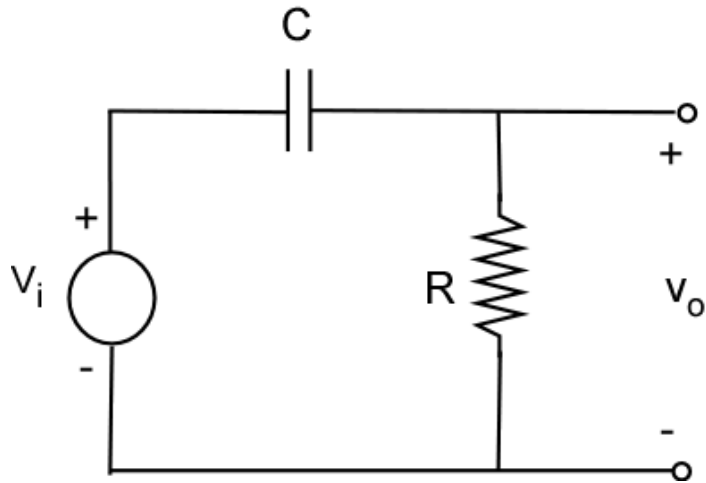

$$V_o = \frac{V_i R}{R + \frac{1}{j\omega C}} = \frac{V_i}{1 + \frac{1}{j\omega RC}}$$

$$A_v = \frac{V_o}{V_i} = \frac{1}{1 - j \frac{1}{2\pi f RC}} = \frac{1}{1 - j f_o / f}$$

# Frequency Response

3-dB points are points where the magnitude is divided by  $2^{1/2}$  (power is halved)  $|1+j|= 2^{1/2}$

$$A_{dB} = 20 \log 1.414 = 3 \text{ dB}$$


Amplifier has intrinsic gain  $A_o$

Low-pass characteristics is: 
$$\frac{1}{1 + jf / f_{hi}}$$

High-pass characteristics is: 
$$\frac{jf / f_{lo}}{1 + jf / f_{lo}}$$

Overall gain  $A(f)$  is 
$$A_o \cdot \frac{jf / f_{lo}}{1 + jf / f_{lo}} \cdot \frac{1}{1 + jf / f_{hi}}$$

# Frequency Response

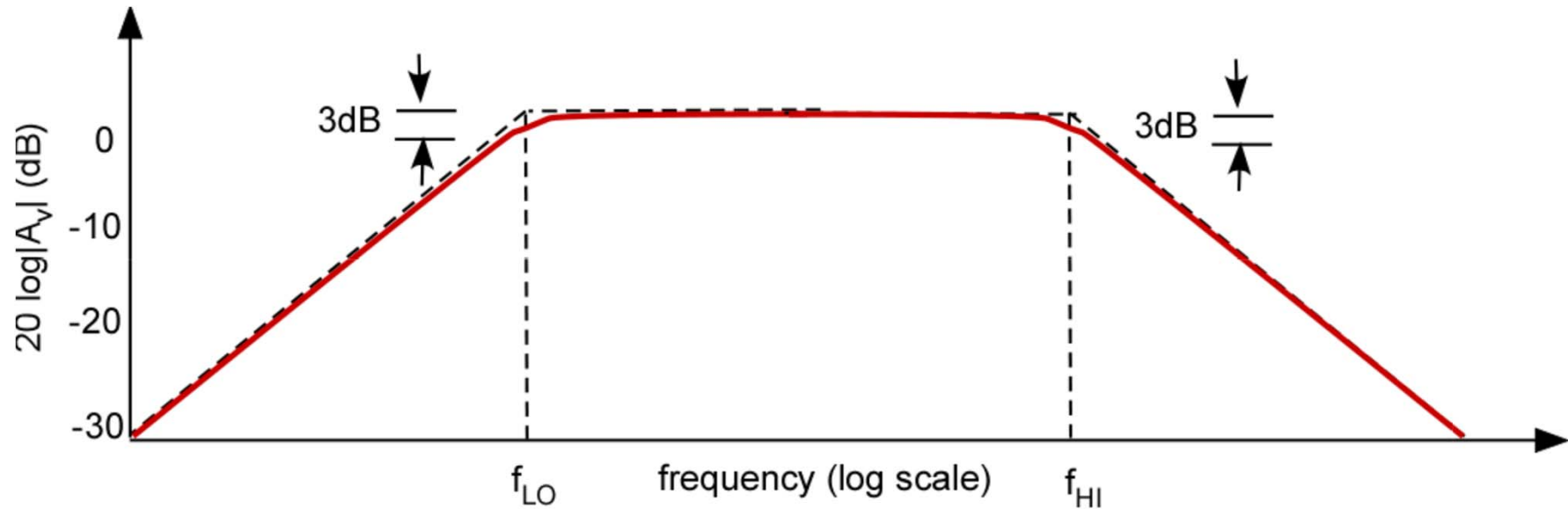

Overall gain  $A(f)$  is

$$A(f) = A_o \cdot \frac{jf / f_{lo}}{1 + jf / f_{lo}} \cdot \frac{1}{1 + jf / f_{hi}}$$