

ECE 342

Electronic Circuits

Lecture 22



Transistor Capacitances

Jose E. Schutt-Aine
Electrical & Computer Engineering
University of Illinois
jesa@illinois.edu

Model for general Amplifying Element


C_{c1} and C_{c2} are coupling capacitors (large) $\rightarrow \mu\text{F}$

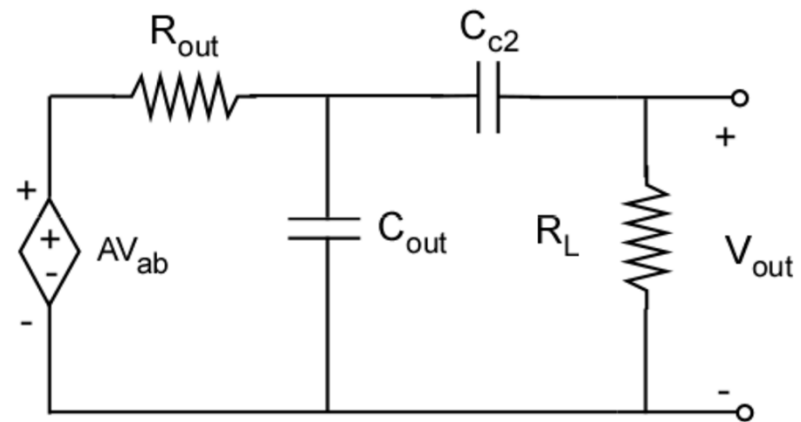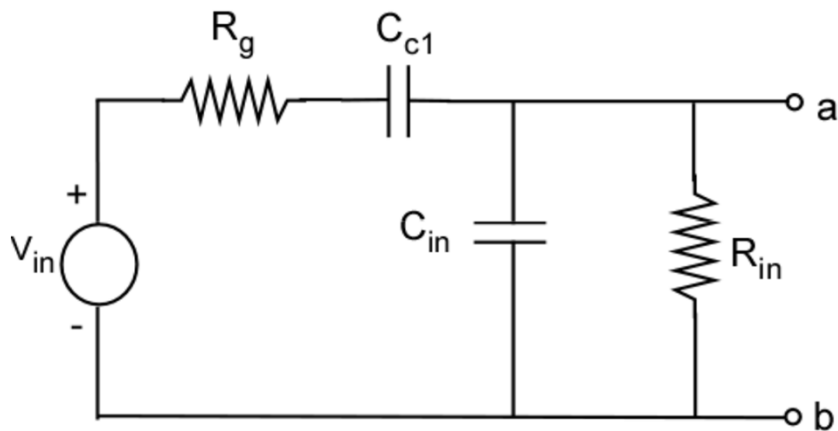C_{in} and C_{out} are parasitic capacitors (small) $\rightarrow \text{pF}$



Midband Frequencies

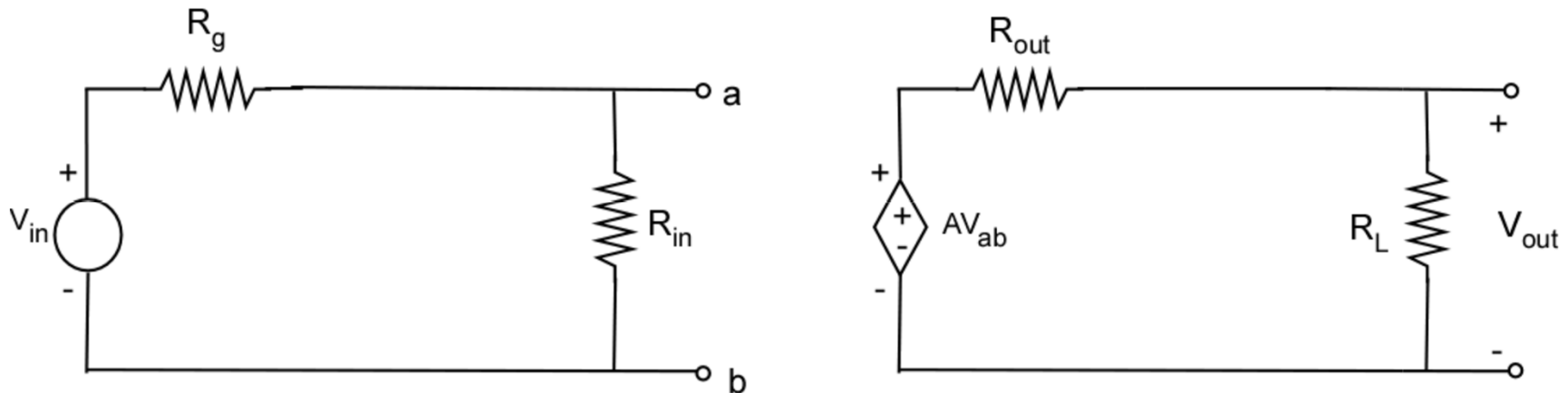
- Coupling capacitors are short circuits
- Parasitic capacitors are open circuits



$$A_{MB} = \frac{v_{out}}{v_{in}} = \frac{R_{in}}{R_g + R_{in}} A \frac{R_L}{R_{out} + R_L}$$

Low Frequency Model

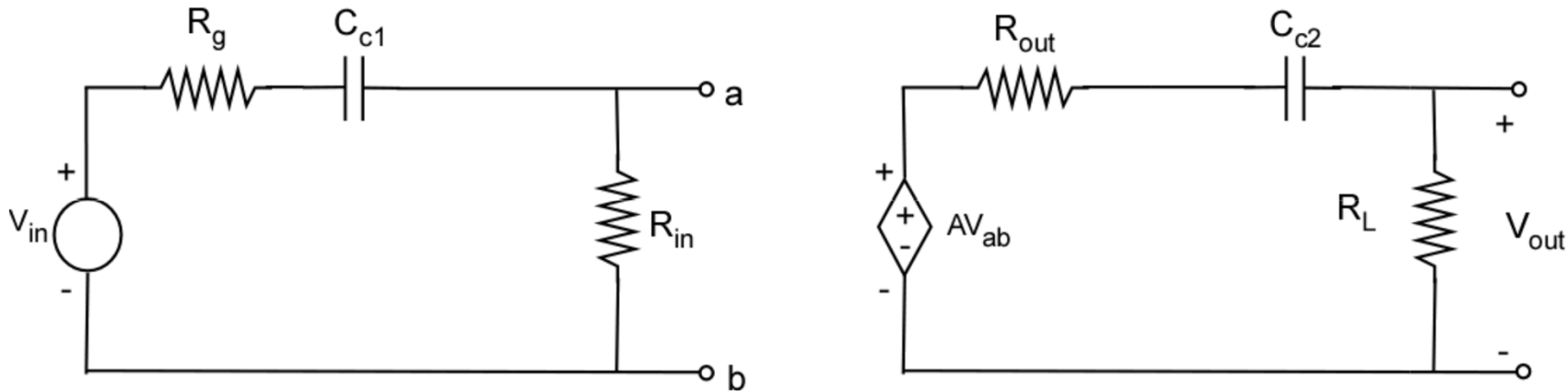- Coupling capacitors are present
- Parasitic capacitors are open circuits



$$V_{ab} = \frac{v_{in} R_{in}}{R_g + R_{in} + \frac{1}{j\omega C_{c1}}} = \frac{v_{in} j\omega C_{c1} R_{in}}{1 + j\omega C_{c1} (R_g + R_{in})}$$

$$V_{ab} = v_{in} \frac{R_{in}}{R_g + R_{in}} \cdot \frac{j\omega C_{c1} (R_g + R_{in})}{\left[1 + j\omega C_{c1} (R_g + R_{in}) \right]}$$

Low Frequency Model

$$\text{define } f_{l1} = \frac{1}{2\pi(R_g + R_{in})C_{c1}} \text{ and } f_{l2} = \frac{1}{2\pi(R_L + R_{out})C_{c2}}$$

$$V_{ab} = V_{in} \frac{R_{in}}{R_g + R_{in}} \cdot \frac{jf / f_{l1}}{1 + jf / f_{l1}}$$

$$\text{Similarly, } v_{out} = Av_{ab} \frac{R_L}{R_L + R_{out}} \cdot \frac{jf / f_{l2}}{1 + jf / f_{l2}}$$

Low Frequency Model

$$\text{Overall gain} = \frac{v_{out}}{v_{in}} = \frac{R_{in}}{R_g + R_{in}} \cdot A \cdot \frac{R_L}{R_L + R_{out}} \cdot \frac{jf / f_{l1}}{1 + jf / f_{l1}} \cdot \frac{jf / f_{l2}}{1 + jf / f_{l2}}$$

$$\frac{v_{out}}{v_{in}} = A_{MB} \cdot \frac{jf / f_{l1}}{1 + jf / f_{l1}} \cdot \frac{jf / f_{l2}}{1 + jf / f_{l2}}$$

Example


$R_{out} = 3 \text{ k}\Omega$, $R_g = 200 \text{ }\Omega$, $R_{in} = 12 \text{ k}\Omega$, $R_L = 10 \text{ k}\Omega$
 $C_{c1} = 5 \text{ }\mu\text{F}$ and $C_{c2} = 1 \text{ }\mu\text{F}$

$$f_{l1} = \frac{1}{2\pi(12,200 \times 5 \times 10^{-6})} = 2.61 \text{ Hz}$$


$$f_{l2} = \frac{1}{2\pi(13,000 \times 10^{-6})} = 12.2 \text{ Hz}$$

High Frequency Model

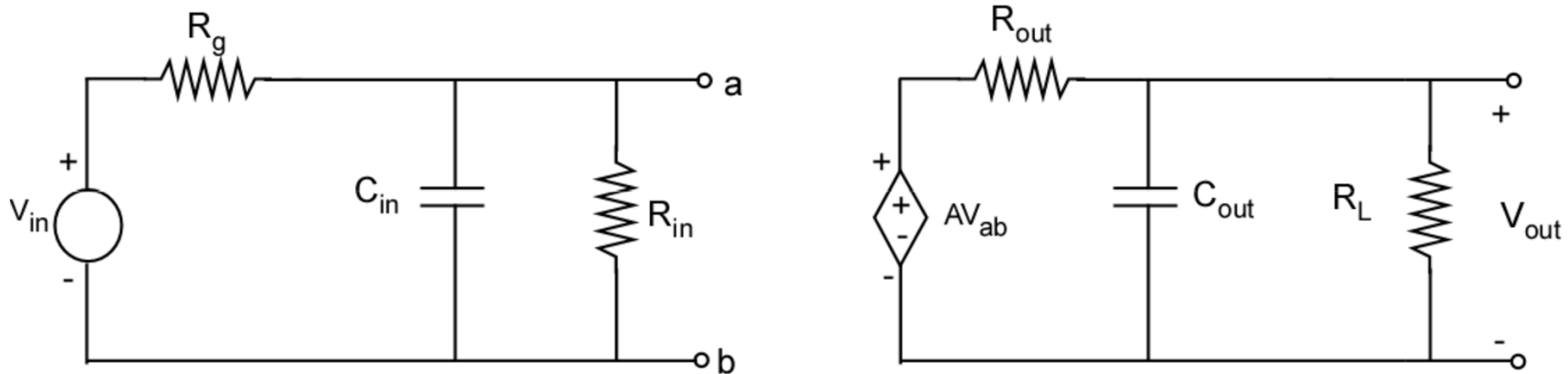- Assume coupling capacitors are short
- Account for parasitic capacitors



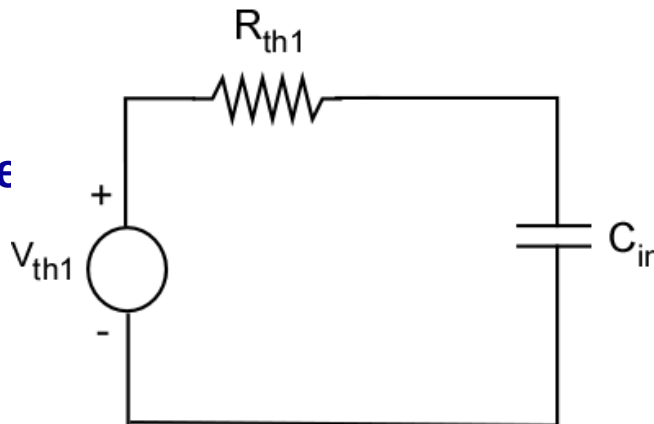Potential Thevenin equivalent for input as seen by C_{in}



$$V_{th1} = \frac{v_{in} R_{in}}{R_g + R_{in}}$$

$$R_{th1} = R_g \parallel R_{in}$$

High Frequency Model

$$v_{ab} = \frac{v_{in} R_{in}}{R_g + R_{in}} \cdot \frac{1}{1 + j\omega C_{in} R_{th1}}$$

$$v_{ab} = \frac{v_{in} R_{in}}{R_g + R_{in}} \cdot \frac{1}{1 + jf / f_{h1}} \quad \text{where} \quad f_{h1} = \frac{1}{2\pi R_{th1} C_{in}}$$

$$\text{Likewise } v_{out} = \frac{Av_{ab} R_L}{R_{out} + R_L} \cdot \frac{1}{1 + j\omega C_{out} R_{th2}}$$

$$\text{with } R_{th2} = R_{out} \parallel R_L$$

$$v_{out} = \frac{Av_{ab} R_L}{R_L + R_{out}} \cdot \frac{1}{1 + jf / f_{h2}} \quad \text{where} \quad f_{h2} = \frac{1}{2\pi R_{th2} C_{out}}$$

High Frequency

Overall gain is:

$$\frac{v_o}{v_i} = A \cdot \frac{R_{in}}{R_{in} + R_g} \cdot \frac{R_L}{R_L + R_{out}} \cdot \frac{1}{1 + jf / f_{h1}} \cdot \frac{1}{1 + jf / f_{h2}}$$

or

$$\frac{v_o}{v_i} = A_{MB} \cdot \frac{1}{1 + jf / f_{h1}} \cdot \frac{1}{1 + jf / f_{h2}}$$

Example

Example: $R_{out} = 3 \text{ k}\Omega$, $R_g = 200 \text{ }\Omega$, $R_{in} = 12 \text{ k}\Omega$, $R_L = 10 \text{ k}\Omega$
 $C_{in} = 200 \text{ pF}$ and $C_{out} = 40 \text{ pF}$

$$f_{h1} = \frac{1}{2\pi \times 2 \times 10^{-10} \times (12,200 \parallel 200)} = 4.05 \text{ MHz}$$

$$f_{h2} = \frac{1}{2\pi \times 40 \times 10^{-12} \times (10,000 \parallel 3,000)} = 1.72 \text{ MHz}$$

Summary: low-frequency < 12.2 Hz, High frequency > 1.72 MHz

$$\log\left(\frac{4.05 \times 10^6}{12.2}\right) = 5.52 \simeq 5 \text{ decades}$$

MOSFET - Gate Capacitance Effect

Triode region: $C_{gs} = C_{gd} = \frac{1}{2}WLC_{ox}$

Saturation region: $C_{gs} = \frac{2}{3}WLC_{ox}$ $C_{gd} = 0$

Cutoff: $C_{gd} = C_{gs} = 0$


$$C_{gb} = WLC_{ox}$$

MOSFET – Junction Capacitances


Overlap capacitance (gate-to-source): $C_{ov} = WL_{ov}C_{ox}$

$$C_{sb} = \frac{C_{sbo}}{\sqrt{1 + \frac{V_{SB}}{V_o}}}$$
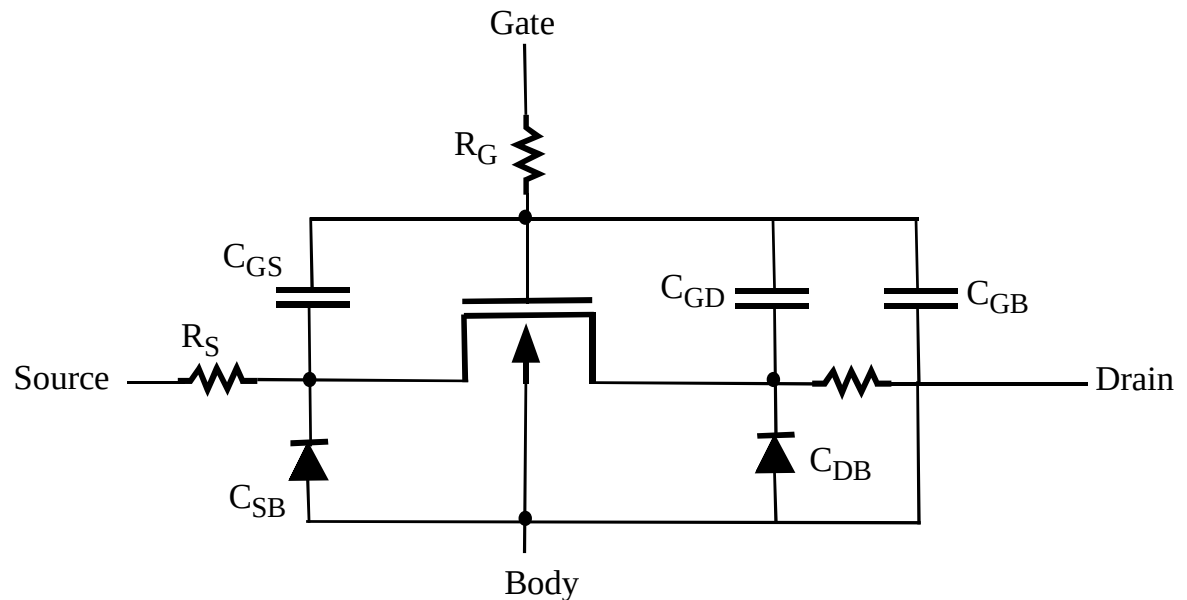
$$C_{db} = \frac{C_{dbo}}{\sqrt{1 + \frac{V_{DB}}{V_o}}}$$



MOSFET High-Frequency Model

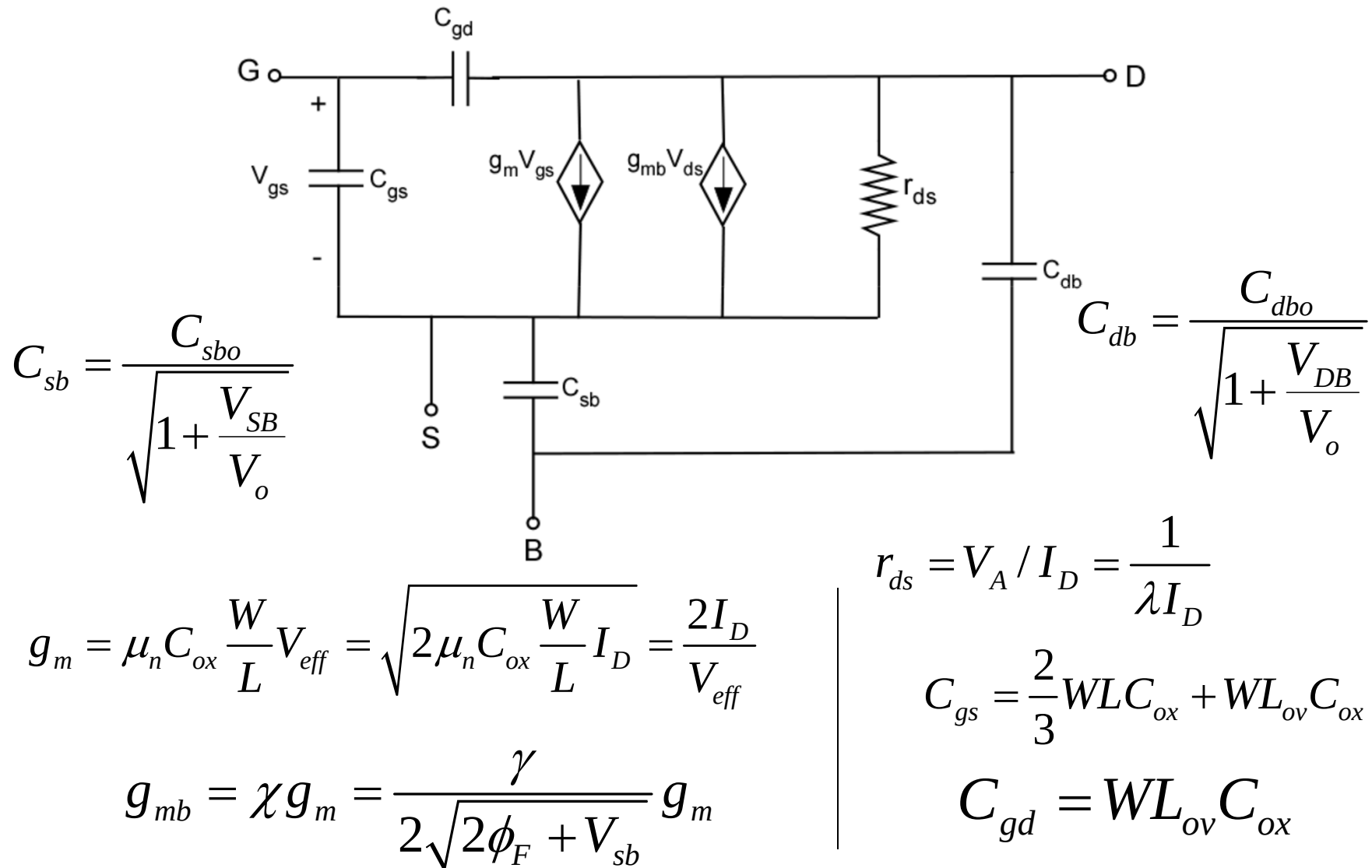

BJT Capacitances

Base: Diffusion Capacitance: C_{de} (small signal)

$$C_{de} \equiv \frac{dQ_n}{dv_{BE}}$$

where Q_n is minority carrier charge in base

$$C_{de} = \tau_F \frac{di_C}{dv_{BE}} = \tau_F g_m = \frac{\tau_F}{V_T}$$

where τ_F is the forward transit time (time spent crossing base)

BJT Capacitances

Base-emitter junction capacitance:

$$C_{je} = \frac{C_{je0}}{\left(1 - \frac{V_{BE}}{V_{oe}}\right)^m}$$

C_{je0} is C_{je} at 0 V. V_{oe} is EBJ built in voltage ~ 0.9 V

BJT Capacitances

In hybrid pi model, $C_{de} + C_{je} = C_{\pi}$

Collector-base junction capacitance


$$C_{\mu} = \frac{C_{\mu 0}}{\left(1 + \frac{V_{CB}}{V_{oe}}\right)^m}$$

$C_{\mu 0}$ is C_{μ} at 0 V. V_{oc} is CBJ built in voltage ~ 0.9 V

C_{π} is around a few tens of pF

C_{μ} is around a few pF



High-Frequency Hybrid- π Model

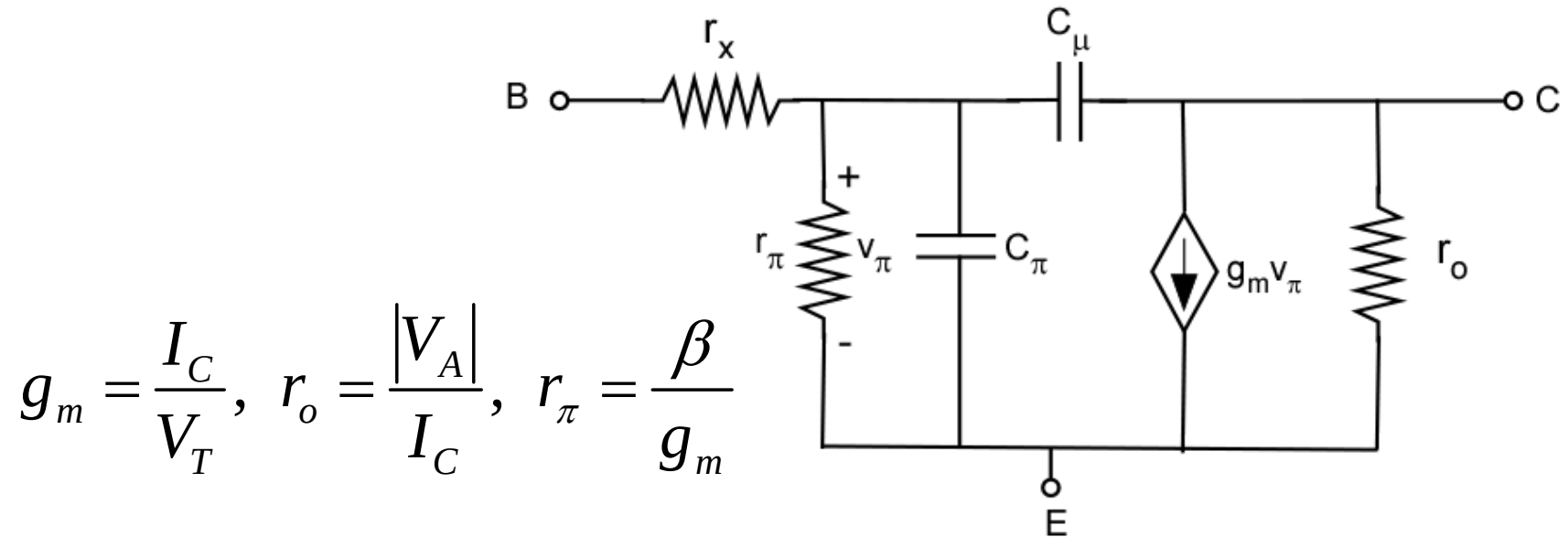



$$C_\pi + C_\mu = \frac{g_m}{2\pi f_T}, \quad C_\pi = C_{de} + C_{je}, \quad C_{de} = \tau_F g_m$$

$$C_\mu = \frac{C_{jco}}{\left(1 + \frac{V_{CB}}{V_{oe}}\right)^m}, \quad m = 0.3 - 0.5 \quad f_T = \frac{g_m}{2\pi (C_\pi + C_\mu)}$$

CS - Three Frequency Bands

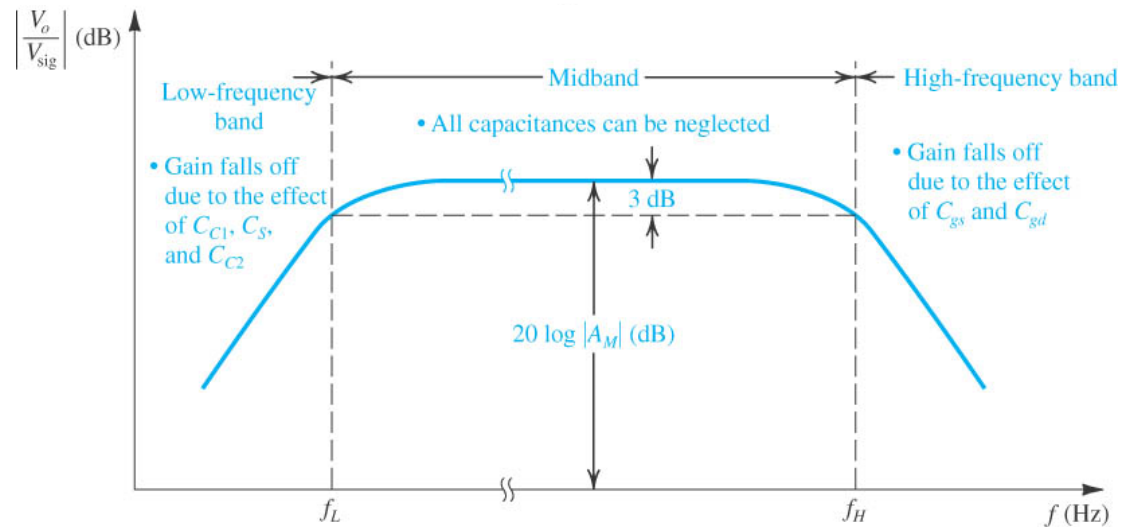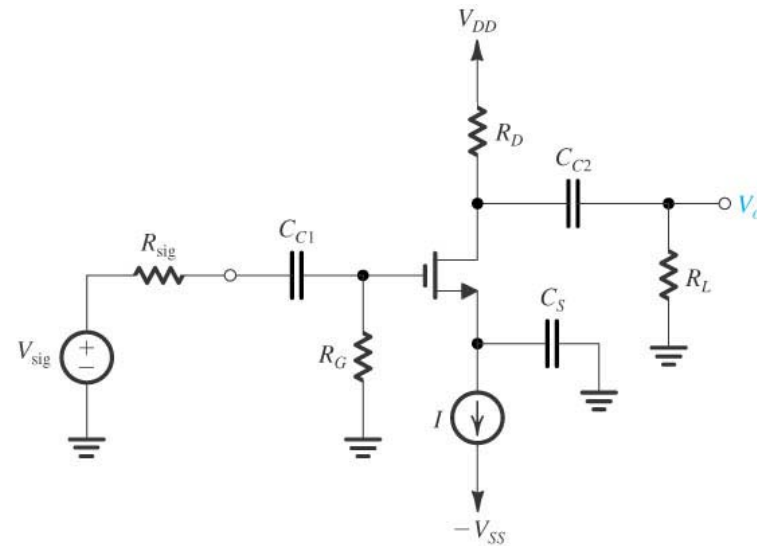


CE - Three Frequency Bands

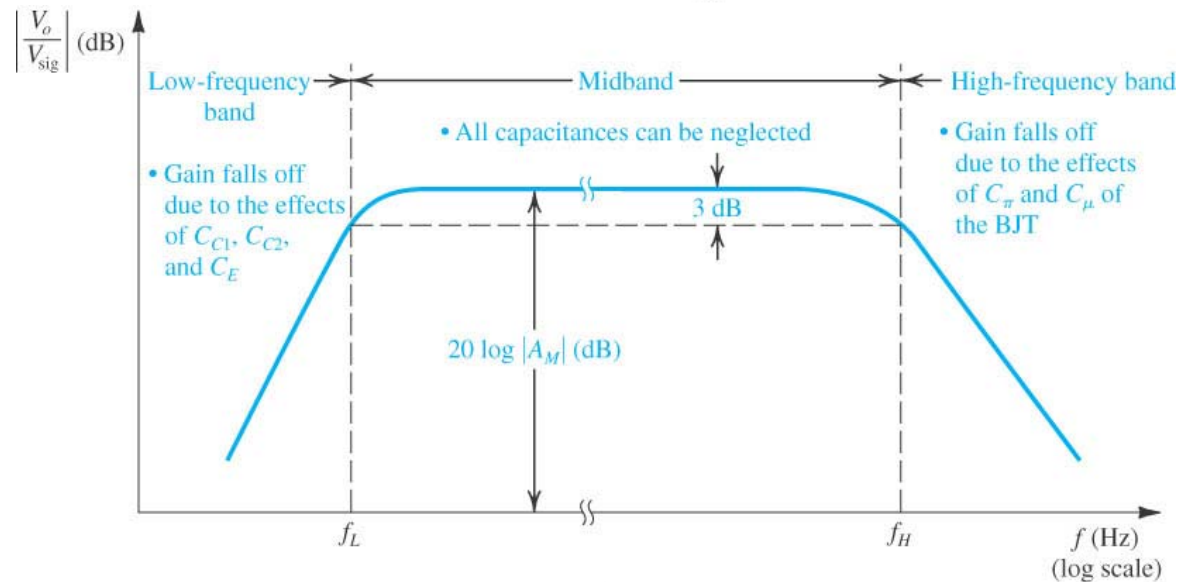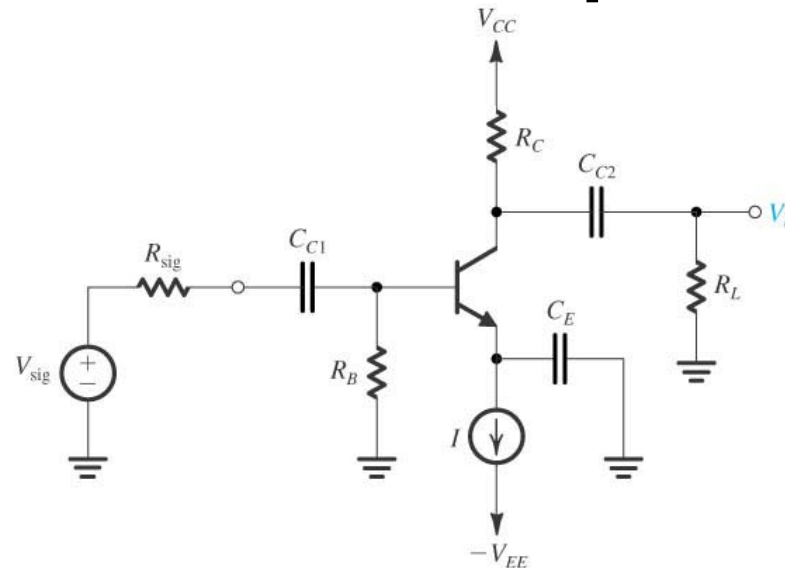

Unity-Gain Frequency f_T

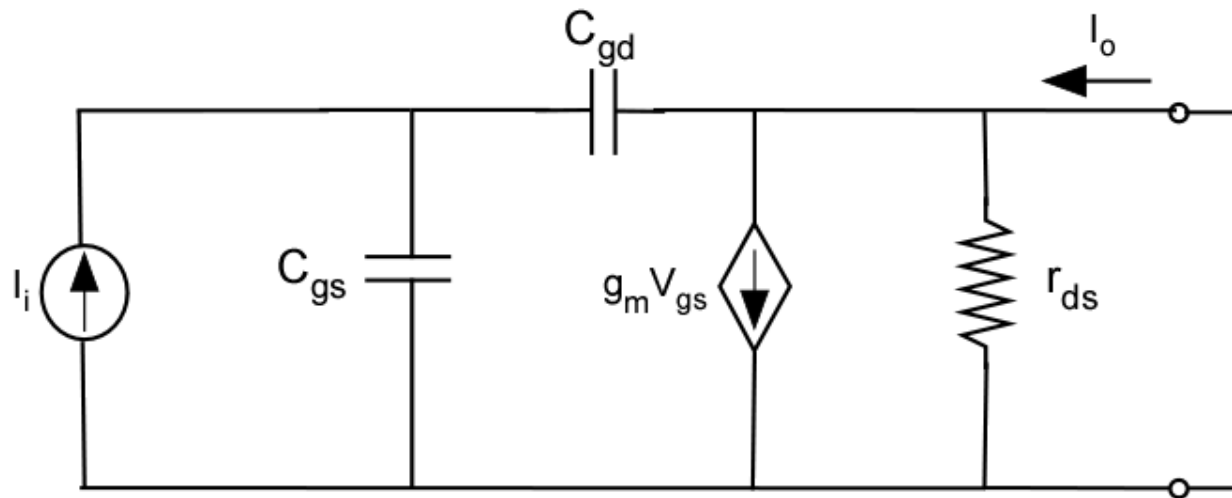f_T is defined as the frequency at which the short-circuit current gain of the common source configuration becomes unity



Define:

$$s = j\omega$$

(neglect $sC_{gd}V_{gs}$ since C_{gd} is small)

$$I_o = g_m V_{gs} - sC_{gd} V_{gs}$$

$$\frac{I_o}{I_i} = \frac{g_m}{s(C_{gs} + C_{gd})}$$

$$I_o \approx g_m V_{gs} \quad V_{gs} = \frac{I_i}{s(C_{gs} + C_{gd})}$$


Calculating f_T

For $s=j\omega$, magnitude of current gain becomes unity at

$$\omega_T = \frac{g_m}{C_{gs} + C_{gd}} \Rightarrow f_T = \frac{g_m}{2\pi(C_{gs} + C_{gd})}$$

$f_T \sim 100$ MHz for $5\text{-}\mu\text{m}$ CMOS, $f_T \sim$ several GHz for $0.13\mu\text{m}$ CMOS

BJT - Short-Circuit Current Gain

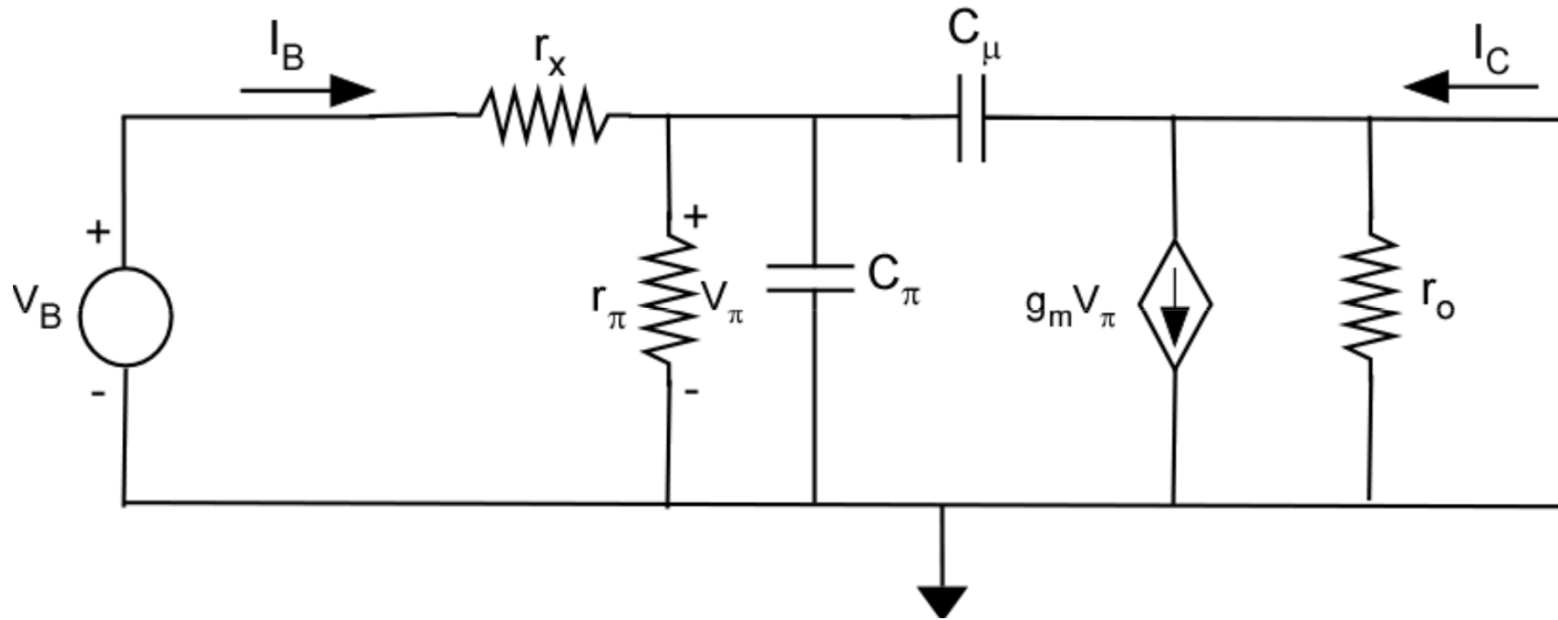

$$I_C = (g_m - sC_\mu) v_\pi$$

$$v_\pi = \frac{I_B}{\frac{1}{r_\pi} + sC_\mu + sC_\pi}$$

BJT - Short-Circuit Current Gain

Define h_{fe} as short-circuit current gain

$$h_{fe} = \frac{I_C}{I_B} = \frac{g_m - sC_\mu}{\frac{1}{r_\pi} + s(C_\pi + C_\mu)}$$

$g_m \gg sC_\mu$ at freq. of interest

$$h_{fe} = \frac{I_C}{I_B} = \frac{g_m r_\pi}{1 + s(C_\pi + C_\mu)r_\pi}$$

BJT - Short-Circuit Current Gain

$$h_{fe} = \frac{\beta_o}{1 + s(C_\pi + C_\mu)r_\pi}$$

Define h_{fe} has a single pole (or STC) response.
Unity gain bandwidth is for:

$$h_{fe} = \frac{g_m r_\pi}{1 + s(C_\pi + C_\mu)r_\pi} = 1 \quad \text{or} \quad \frac{g_m}{2\pi f_T (C_\pi + C_\mu)} = 1$$

In some cases, if C_μ is known, then

BJT - Short-Circuit Current Gain

$$f_T = \frac{g_m}{2\pi(C_\pi + C_\mu)}$$

From which we get

$$C_\pi + C_\mu = \frac{g_m}{2\pi f_T} = \frac{g_m}{\omega_T}$$

$$\text{Thus, } C_\pi + C_\mu = \frac{g_m}{\omega_T} \Rightarrow C_\pi = \frac{g_m}{\omega_T} - C_\mu$$