

# ECE 342


# Electronic Circuits

## Lecture 23


## Miller Effect

Jose E. Schutt-Aine  
Electrical & Computer Engineering  
University of Illinois  
[jesa@illinois.edu](mailto:jesa@illinois.edu)


# MOSFET High-Frequency Model

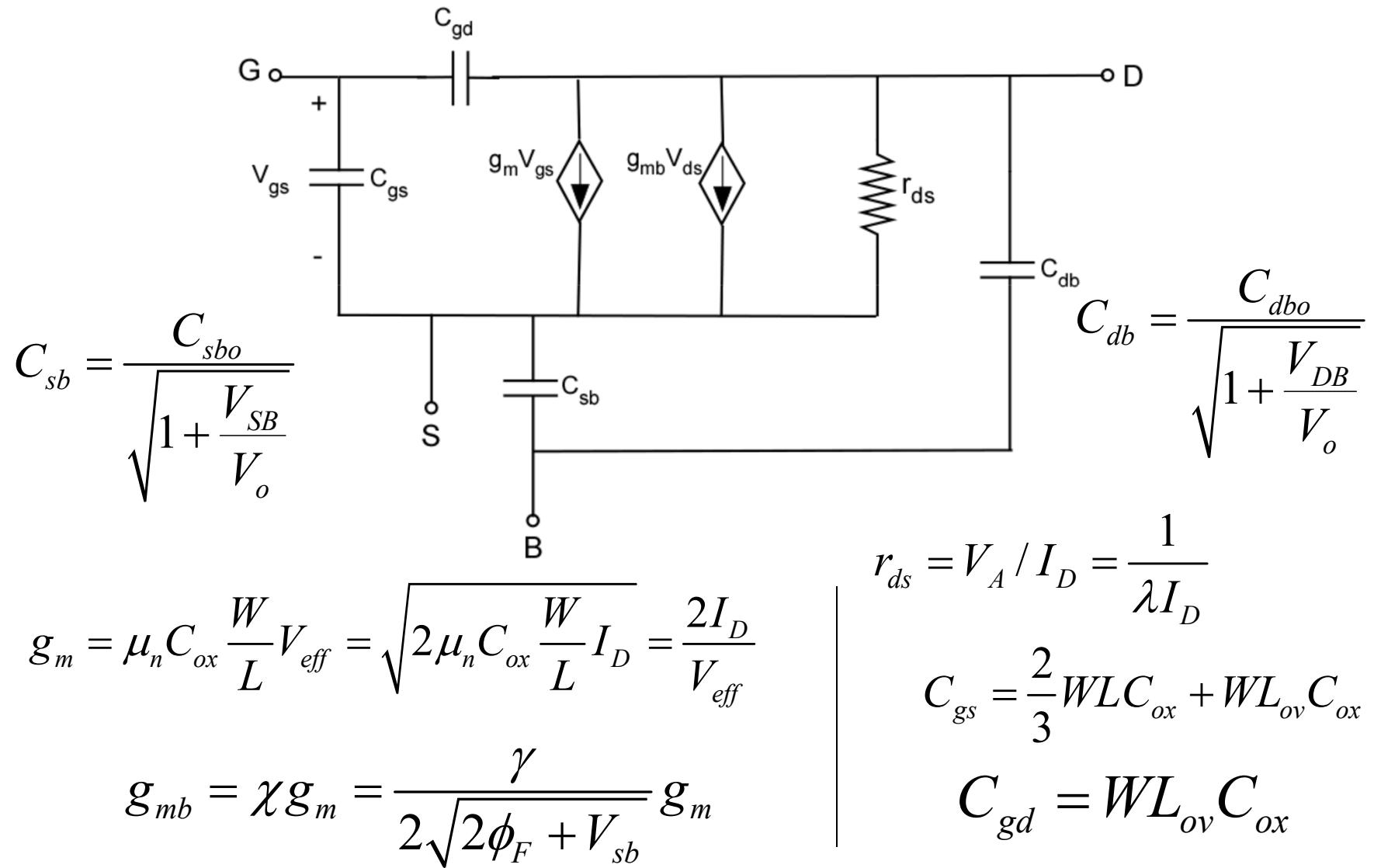

# CS - High-Frequency Response

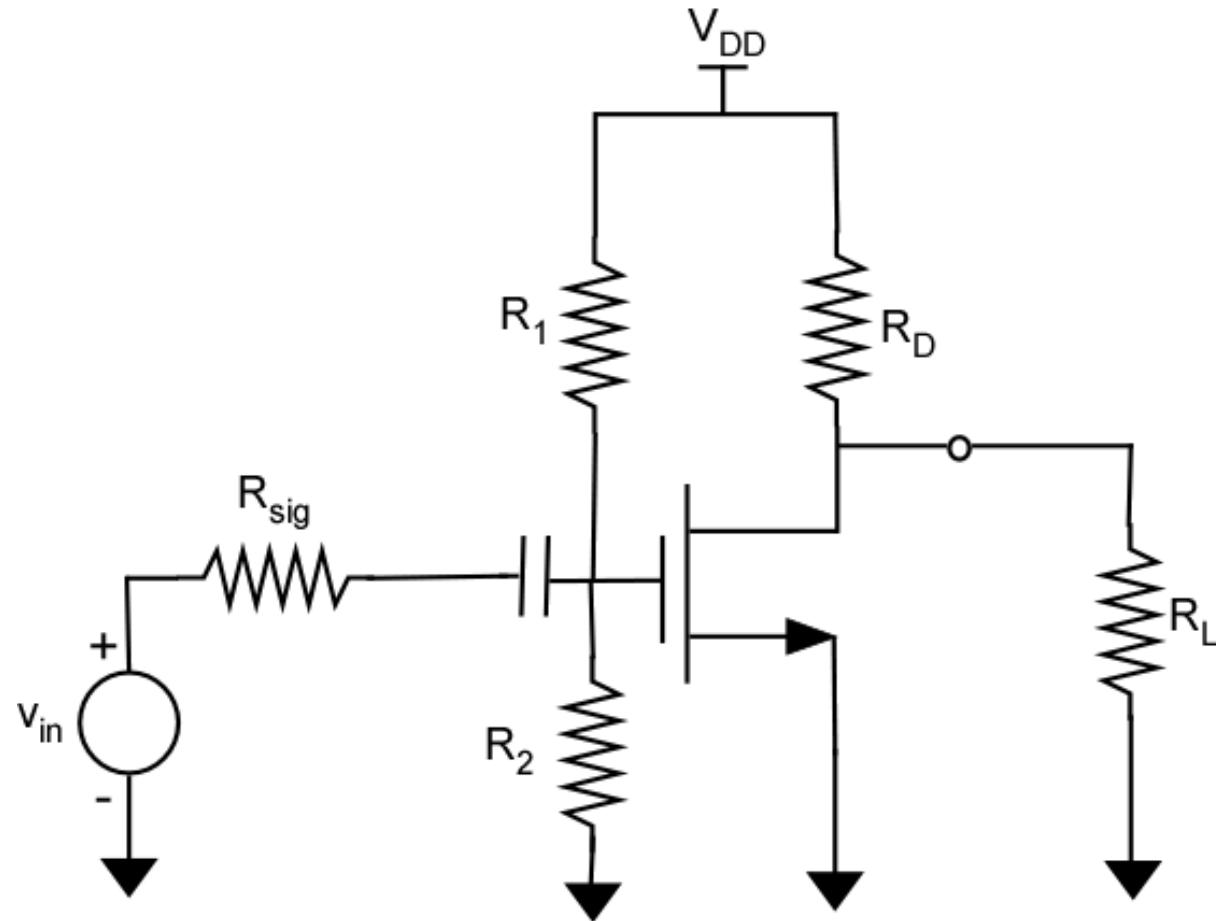


# CS - High-Frequency Response

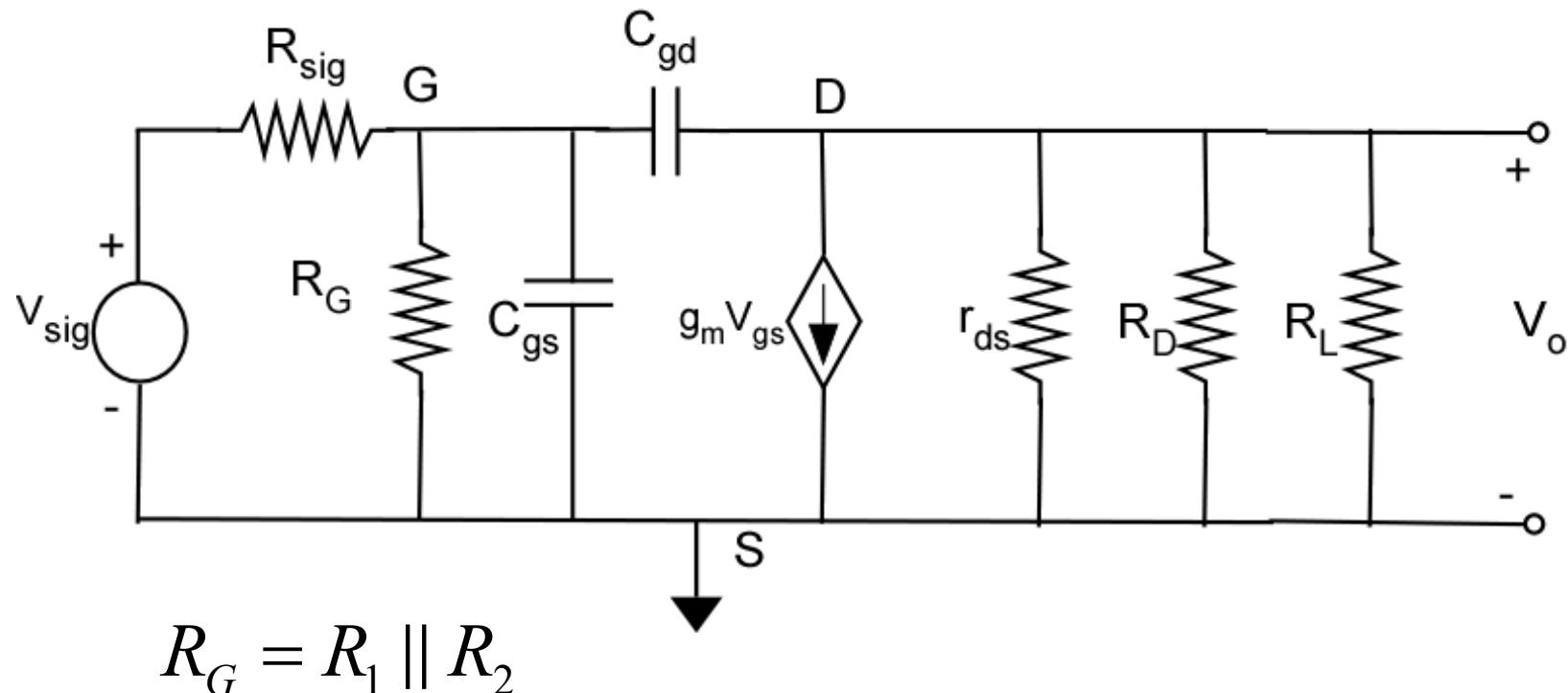
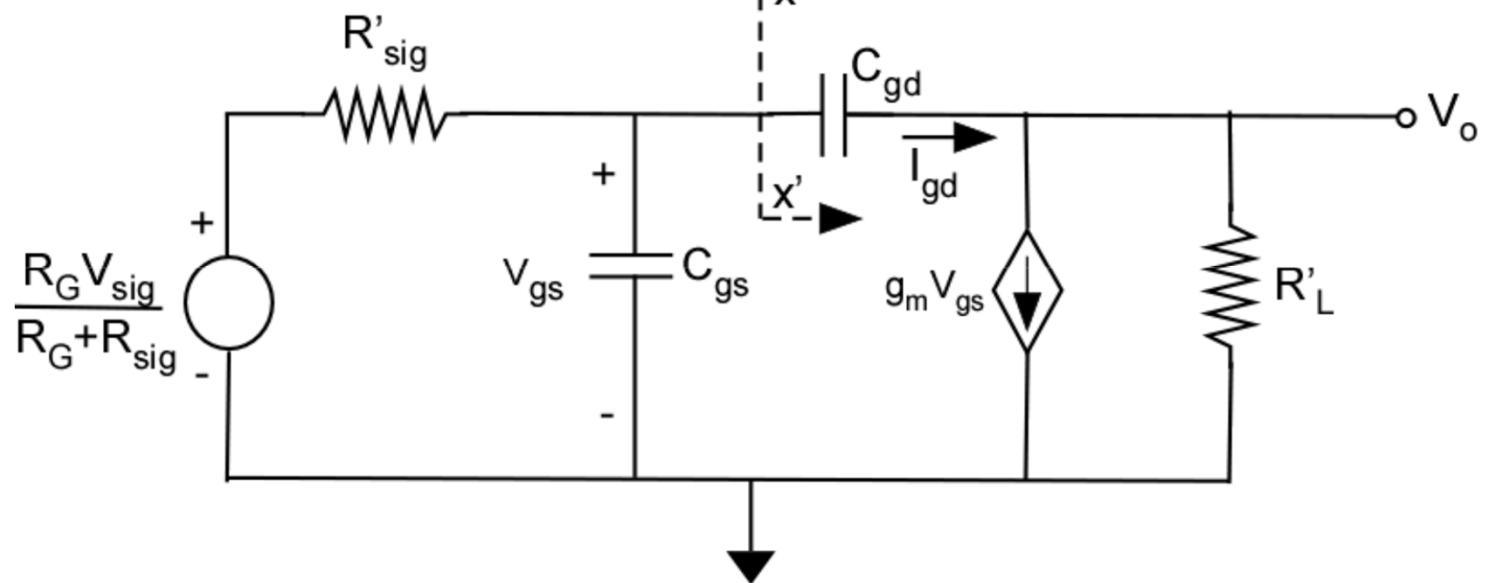
# CS - High-Frequency Response

$$R'_{sig} = R_{sig} \parallel R_G$$

$$R'_L = r_{ds} \parallel R_D \parallel R_L$$



$$I_{gd} = sC_{gd} (V_{gs} - V_o) = sC_{gd} [V_{gs} - (-g_m R'_L V_{gs})]$$

$$I_{gd} = sC_{gd} (1 + g_m R'_L) V_{gs}$$

# CS – Miller Effect


Define  $C_{eq}$  such that

$$sC_{eq}V_{gs} = sC_{gd} \left(1 + g_m R'_L\right) V_{gs}$$

$$V_o = -g_m R'_L V_{gs}$$

$$C_{eq} = C_{gd} \left(1 + g_m R'_L\right) = \text{Miller Capacitance}$$
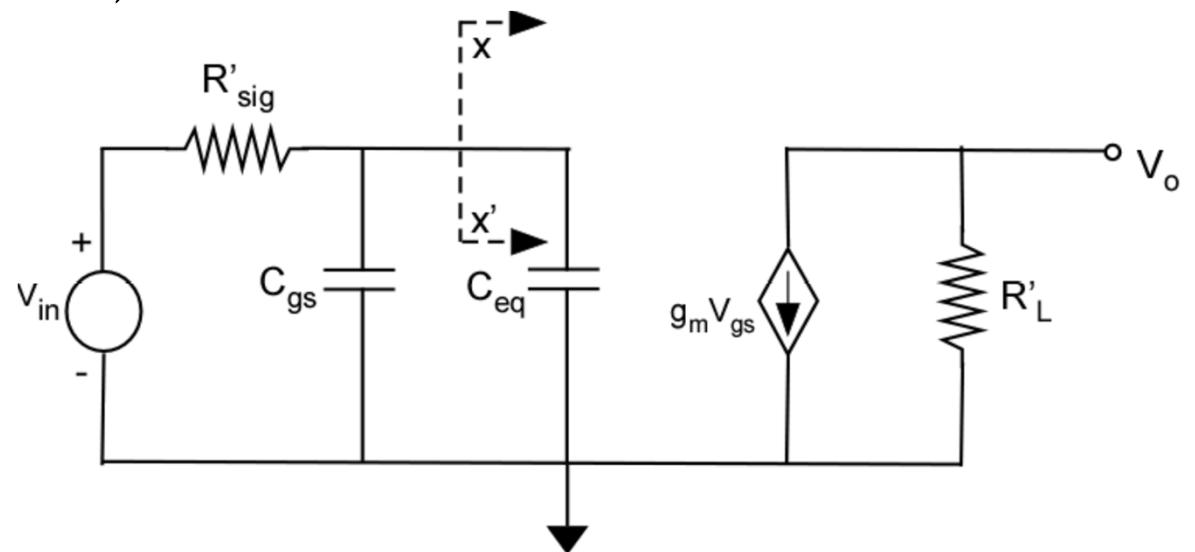
$$v_{in} = \frac{R_g V_{sig}}{R_g + R_{sig}}$$



# CS – Miller Effect

$$V_{gs} = \left( \frac{R_G V_{sig}}{R_G + R_{sig}} \right) \frac{1}{1 + jf / f_o}$$

$f_o$  is the corner frequency of the STC circuit

$$f_o = \frac{1}{2\pi C_{in} R'_{sig}}$$

$$C_{in} = C_{gs} + C_{eq} = C_{gs} + \overbrace{C_{gd} \left( 1 + g_m R'_L \right)}^{Miller}$$

# CS – Miller Effect

$$\frac{V_o}{V_{sig}} = - \left( \frac{R_G}{R_G + R_{sig}} \right) g_m R_L' \frac{1}{1 + jf / f_o}$$

$$\frac{V_o}{V_{sig}} = \frac{A_M}{1 + jf / f_H}$$

$$f_H = f_o = \frac{1}{2\pi C_{in} R_{sig}'}$$

# Example

$R_{sig} = 100 \text{ k}\Omega$ ,  $R_G = 4.7 \text{ M}\Omega$ ,  $R_D = 15 \text{ k}\Omega$ ,  $g_m = 1 \text{ mA/V}$ ,  
 $r_{ds} = 150 \text{ k}\Omega$ ,  $R_L = 10 \text{ k}\Omega$ ,  $C_{gs} = 1 \text{ pF}$  and  $C_{gd} = 0.4 \text{ pF}$

$$R' = r_{ds} \parallel R_D \parallel R_L = 150 \parallel 15 \parallel 15 = 7.14 \text{ k}\Omega$$

$$A_M = -\frac{R_G}{R_G + R_{sig}} g_m R' = -\frac{4.7}{4.7 + 0.1} \times 1 \times 7.14 = -7$$

$$\text{Miller Cap : } C_{eq} = C_M = (1 + g_m R') C_{gd}$$

$$C_M = 0.4 \times (1 + 7.14) = 3.26 \text{ pF}$$

# Example (cont')

$$C_{in} = 1.0 + 3.26 = 4.26 \text{ pF}$$


Upper 3 dB frequency is at:

$$f_H = \frac{1}{2\pi C_{in} (R_{sig} \parallel R_G)}$$


$$f_H = \frac{1}{2\pi \times 4.26 \times 10^{-12} \times (0.1 \parallel 4.7) \times 10^6} = 3.82 \text{ kHz}$$

$$f_H = 3.82 \text{ kHz}$$


# CE High-Frequency Model

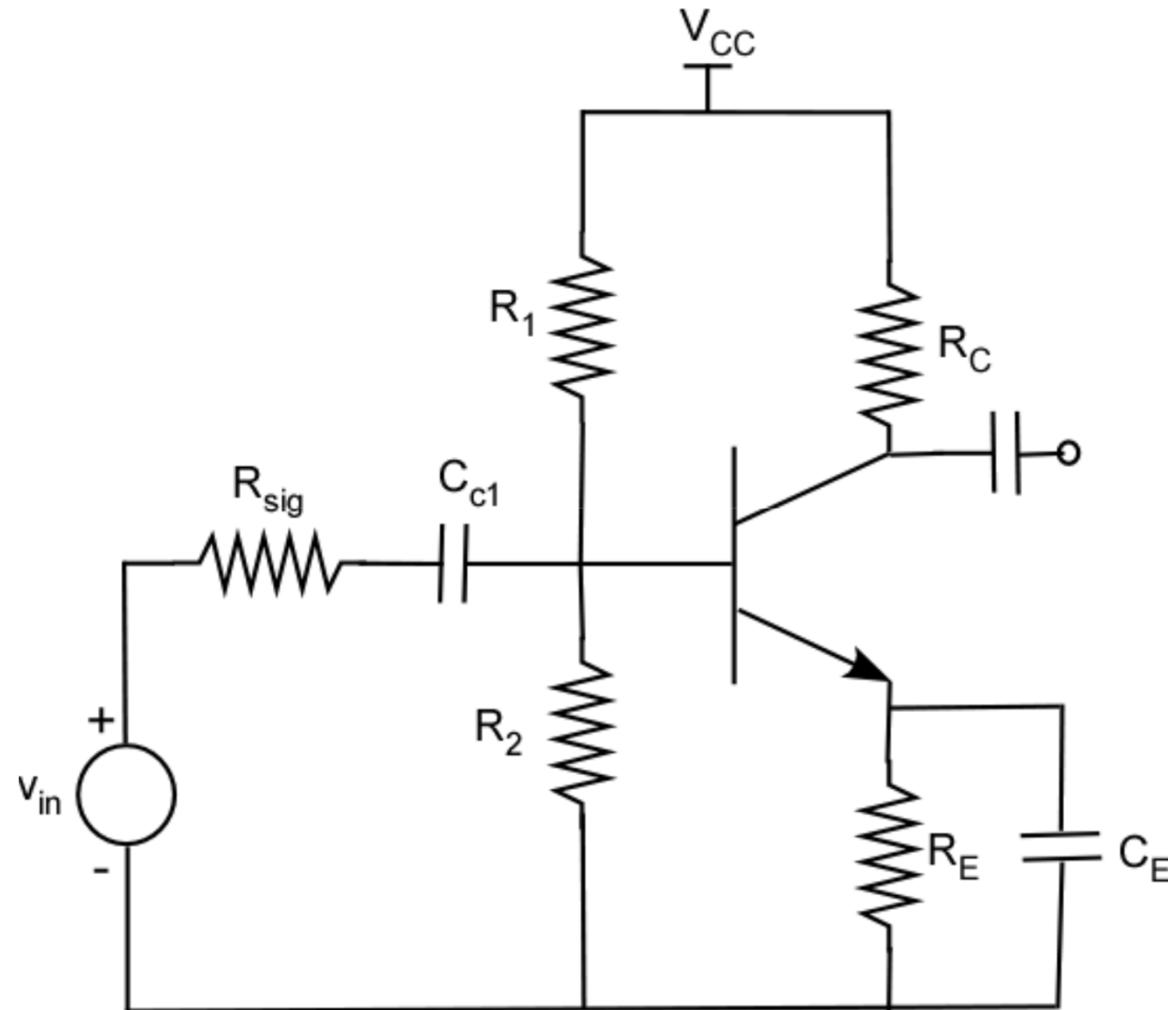

# CE High-Frequency Model

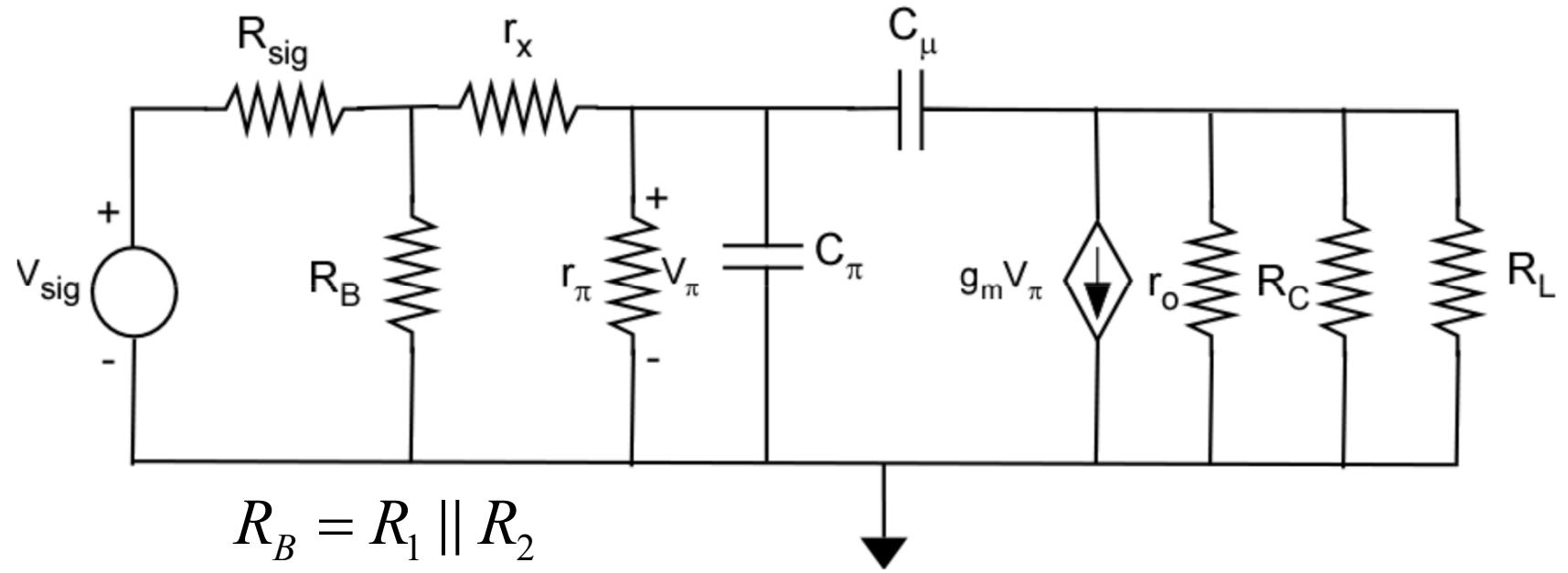

# CE High-Frequency Model

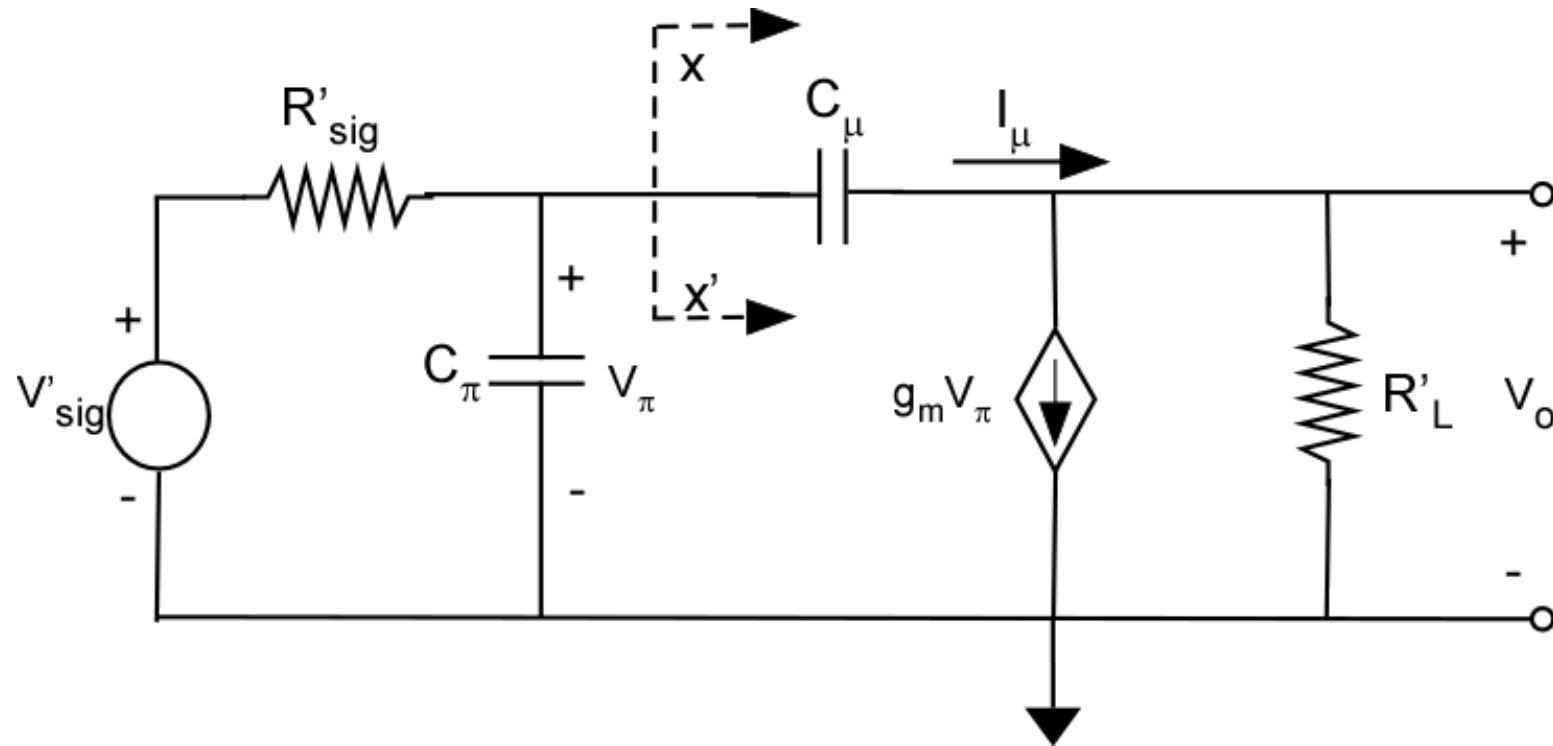

$$V'_{sig} = V_{sig} \cdot \frac{R_B}{R_B + R_{sig}} \cdot \frac{r_\pi}{r_\pi + r_x + (R_{sig} \parallel R_B)}$$


# CE High-Frequency Model

$$R'_{sig} = r_\pi \parallel \left[ r_x + \left( R_{sig} \parallel R_B \right) \right]$$

$$R'_L = r_o \parallel R_C \parallel R_L$$

$$V_o \simeq -g_m v_\pi R'_L$$

# Bipolar Miller Effect

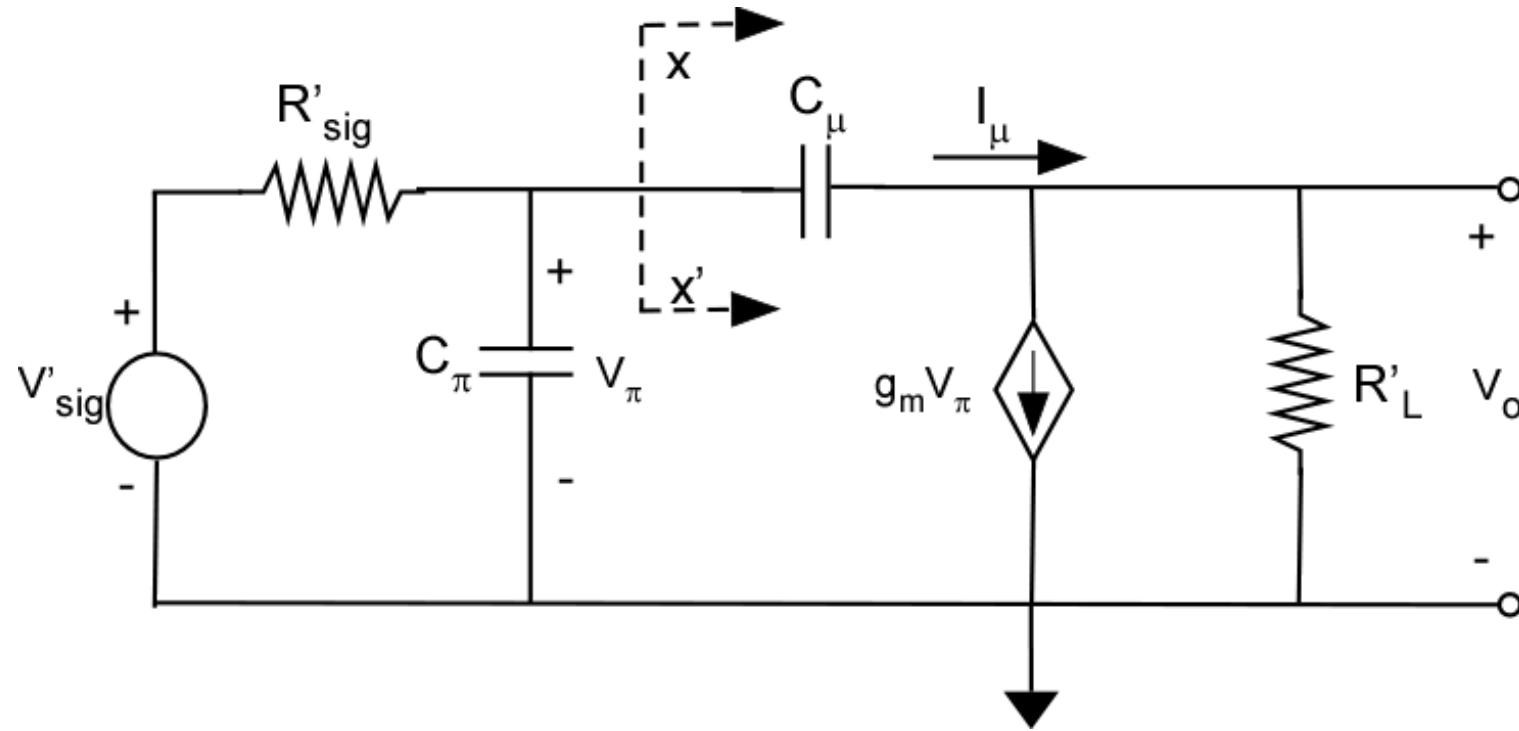

The left hand side of the circuit at XX' knows the existence of  $C_\mu$  only through the current  $I_\mu \rightarrow$  replace  $C_\mu$  with  $C_{eq}$  from base to ground

# Bipolar Miller Effect


$$I_\mu = sC_\mu(v_\pi - v_o) = sC_\mu \left[ v_\pi - \left( -g_m R'_L v_\pi \right) \right]$$

$$I_\mu = sC_\mu \left( 1 + g_m R'_L \right) v_\pi$$

$$sC_{eq}v_\pi = I_\mu = sC_\mu \left( 1 + g_m R'_L \right) v_\pi$$

$C_{eq} = C_\mu \left( 1 + g_m R'_L \right)$ , Miller capacitance for BJT

# Bipolar Miller Effect

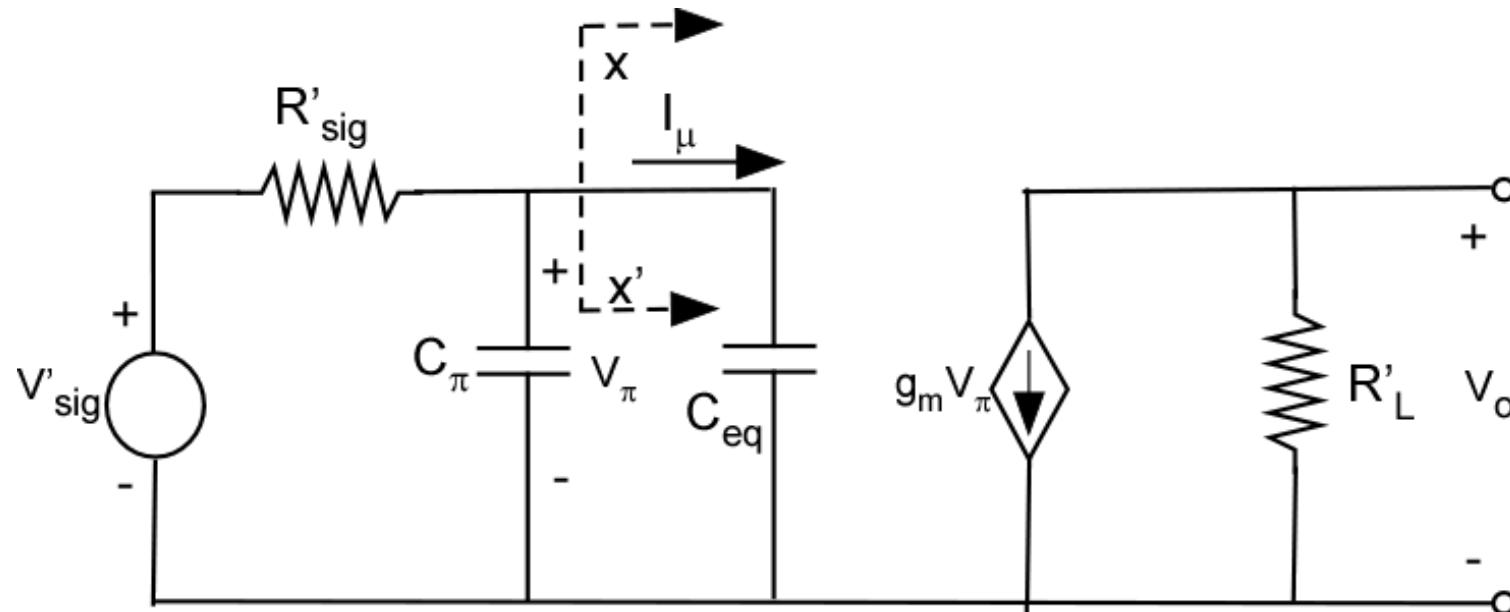

$$V_{\pi} = V'_{sig} \frac{1}{1 + jf / f_o}$$

$$f_o = \frac{1}{2\pi C_{in} R'_{sig}}$$

# Bipolar Miller Effect (cont')


where  $C_{in} = C_\pi + C_{eq} = C_\pi + C_\mu \left(1 + g_m R_L' \right)$

$$\frac{V_o}{V_{sig}} = \left[ \frac{R_B}{R_B + R_{sig}} \cdot \frac{r_\pi g_m R_L'}{r_\pi + r_x + (R_{sig} \parallel R_B)} \right] \left[ \frac{1}{1 + jf / f_o} \right]$$


$$\frac{V_o}{V_{sig}} = A_M \frac{1}{1 + jf / f_o}$$

$$f_H = f_o = \frac{1}{2\pi C_{in} R_{sig}'}$$

# CS – Miller Effect – Exact Analysis

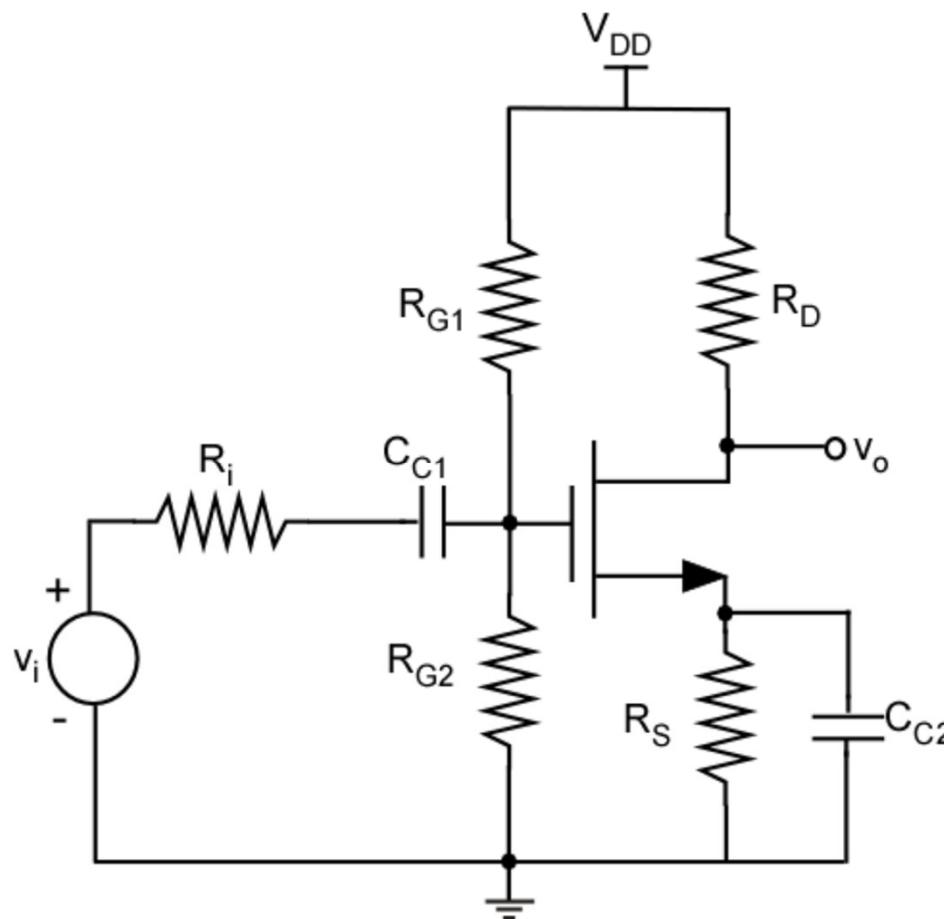

# CS – Miller Effect – Exact Analysis

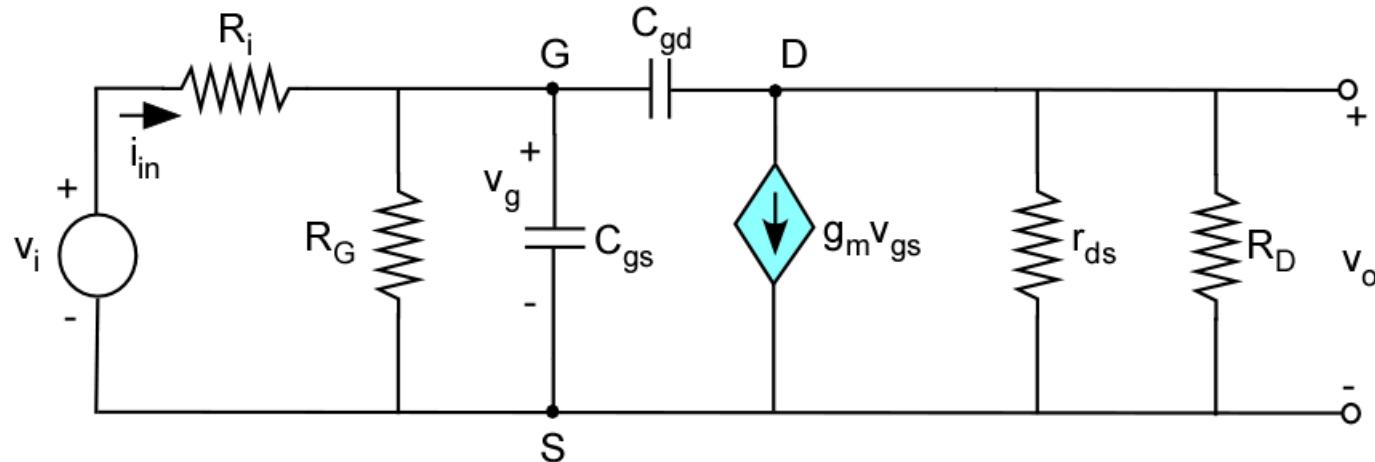

$$G_i = \frac{1}{R_i} \quad G_D = \frac{1}{R_D} \quad G_g = \frac{1}{R_g} \quad g_{ds} = \frac{1}{r_{ds}} \quad R'_D = R_D \parallel r_{ds} = \frac{1}{G_D + g_{ds}}$$

$$\frac{v_o}{v_i} = -\frac{G_i R'_D (g_m - sC_{gd})}{G_i + G_g + s[C_{gs} + C_{gd}] + sC_{gd} R'_D [G_i + G_g] + sC_{gd} g_m R'_D + s^2 C_{gd} C_{gs} R'_D}$$

# CS – Miller Effect – Exact Analysis

We neglect the terms in  $s^2$  since

$$|s^2 C_{gd} C_{gs} R'_D| \ll |s C_{gd} g_m R'_D| \quad \text{or} \quad |s C_{gs}| \ll |g_m|$$

$$\frac{v_o}{v_i} = -\frac{G_i R'_D (g_m - s C_{gd})}{G_i + G_g + s [C_{gs} + C_{gd} (1 + g_m R'_D) + C_{gd} R'_D (G_i + G_g)]}$$

↑  
Miller

If we multiply through by  $R_i = \frac{1}{G_i}$

# CS – Miller Effect – Exact Analysis

$$\frac{v_o}{v_i} = -\frac{R'_D (g_m - sC_{gd})}{1 + R_i G_g + s \left\{ R_i \left[ C_{gs} + C_{gd} (1 + g_m R'_D) \right] + C_{gd} R'_D (1 + R_s G_g) \right\}}$$

From which we extract the 3-dB frequency point

$$f_H = \frac{1 + R_i G_g}{2\pi \left\{ R_i \left[ C_{gs} + C_{gd} (1 + g_m R'_D) \right] + C_{gd} R'_D (1 + R_i G_g) \right\}}$$

# CS – Miller Effect – Exact Analysis


If  $G_g$  is negligible

$$f_H \simeq \frac{1}{2\pi \left\{ R_i \left[ C_{gs} + C_{gd} \left( 1 + g_m R'_D \right) \right] + C_{gd} R'_D \right\}}$$

If  $R_i = 0$

$$f_H \simeq \frac{1}{2\pi C_{gd} R'_D}$$
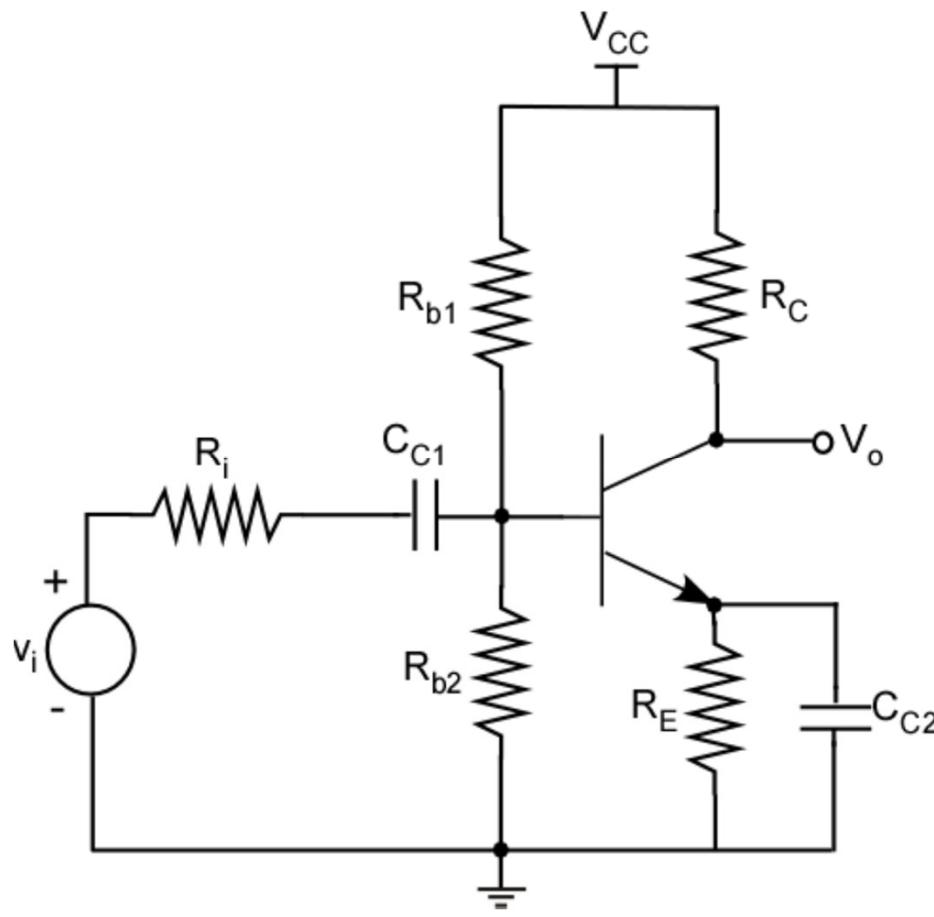
# BJT-CE – Miller Effect – Exact Analysis




$$G_i = \frac{1}{R_i} \quad G_C = \frac{1}{R_C}$$

$$g_\pi = \frac{1}{r_\pi} \quad g_o = \frac{1}{r_o}$$

$$R'_C = R_C // r_o = \frac{1}{G_C + g_o}$$
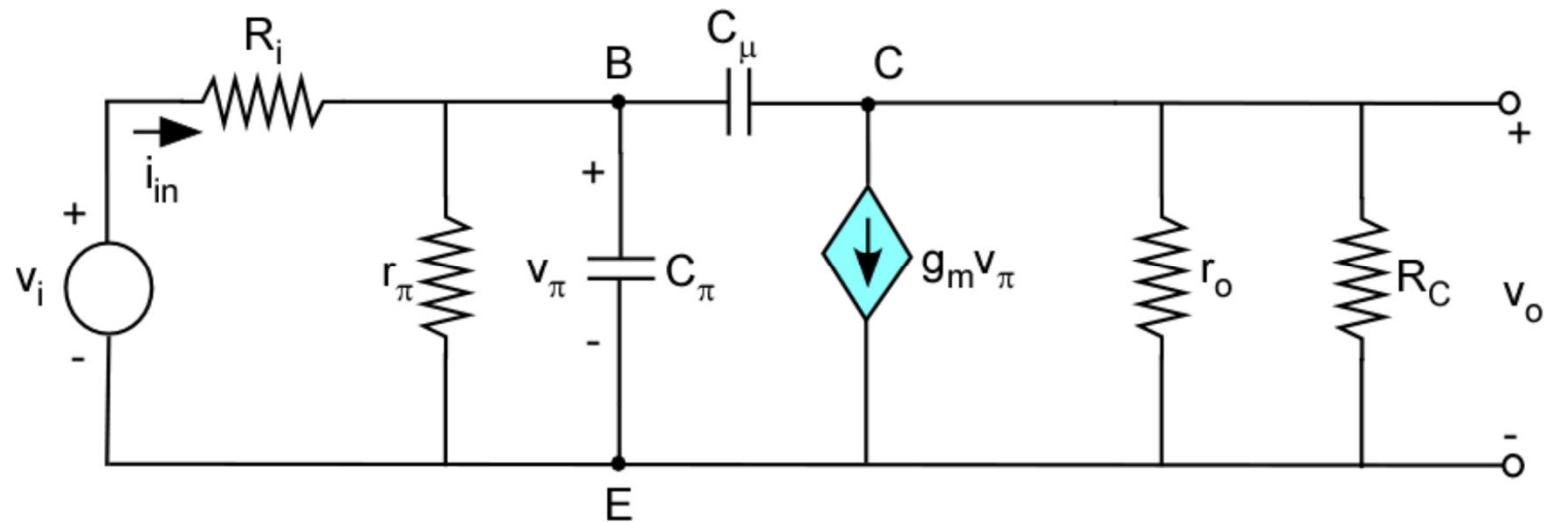
# BJT-CE – Miller Effect – Exact Analysis



$$\frac{v_o}{v_i} = -\frac{G_s R'_C (g_m - sC_\mu)}{G_i + g_\pi + s[C_\pi + C_\mu] + sC_\mu R'_C [G_i + g_\pi] + sC_\mu g_m R'_C + s^2 C_\mu C_\pi R'_C}$$

# BJT-CE – Miller Effect – Exact Analysis

We neglect the terms in  $s^2$  since

$$|s^2 C_\mu C_\pi R'_C| \ll |s C_\mu g_m R'_C| \quad \text{or} \quad |s C_\pi| \ll |g_m|$$

$$\frac{v_o}{v_i} = -\frac{G_i R'_C (g_m - s C_\mu)}{G_i + g_\pi + s \left[ C_\pi + C_\mu (1 + g_m R'_C) + C_\mu R'_C (G_i + g_\pi) \right]}$$

↑  
Miller

If we multiply through by  $R_i = \frac{1}{G_i}$

$$\frac{v_o}{v_i} = -\frac{R'_C (g_m - s C_\mu)}{1 + R_i g_\pi + s \left\{ R_i \left[ C_\pi + C_\mu (1 + g_m R'_D) \right] + C_\mu R'_C (1 + R_i g_\pi) \right\}}$$

# BJT-CE – Miller Effect – Exact Analysis


$$f_H = \frac{1 + R_i g_\pi}{2\pi \left\{ R_i \left[ C_\pi + C_\mu (1 + g_m R'_C) \right] + C_\mu R'_C (1 + R_i g_\pi) \right\}}$$

If  $R_i = 0$

$$f_H \simeq \frac{1}{2\pi C_\mu R'_C}$$
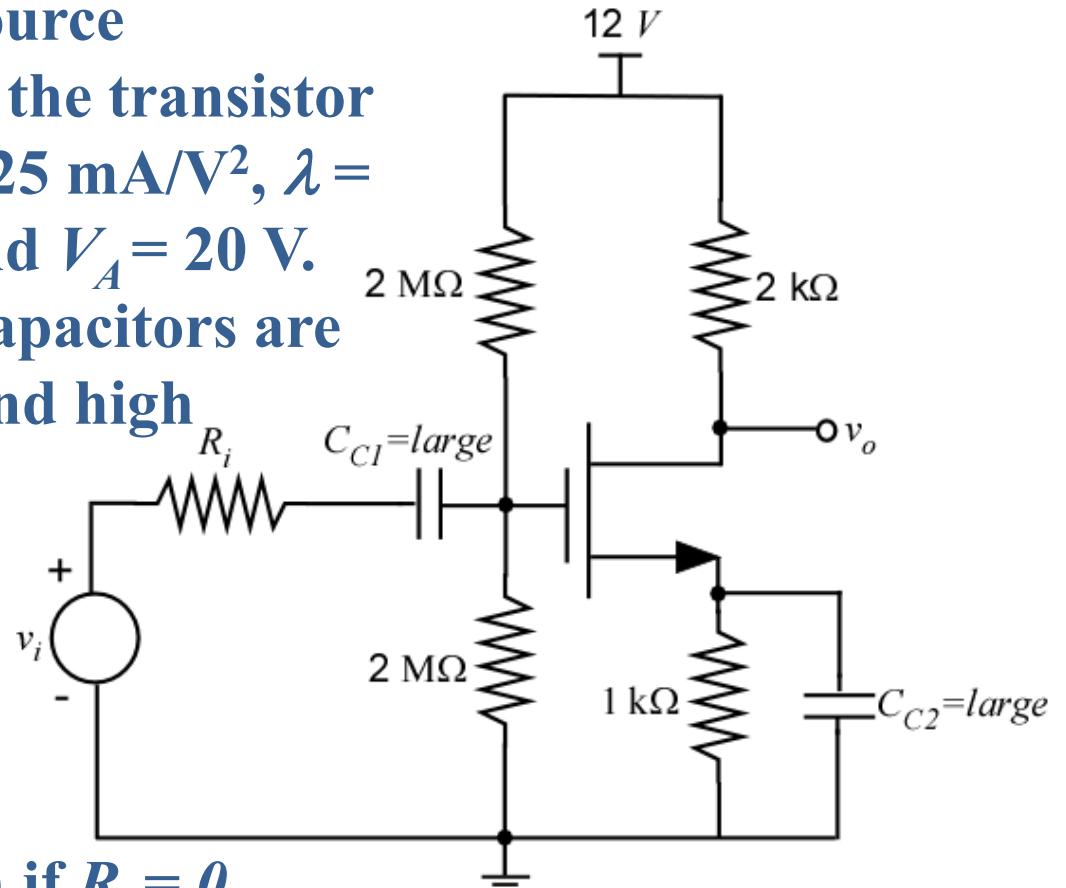
# Example


For the discrete common-source MOSFET amplifier shown, the transistor has  $V_T = 1\text{V}$ ,  $\mu C_{ox}(W/L) = 0.25 \text{ mA/V}^2$ ,  $\lambda = 0$ ,  $C_{gs} = 3 \text{ pF}$ ,  $C_{gd} = 2.7 \text{ pF}$  and  $V_A = 20 \text{ V}$ . Assume that the coupling capacitors are short circuits at midband and high frequencies.



(a) Find the 3dB bandwidth if  $R_i = 0$

(b) Find the 3dB bandwidth if  $R_i = 50 \text{ k}\Omega$

# Example – Part (a)

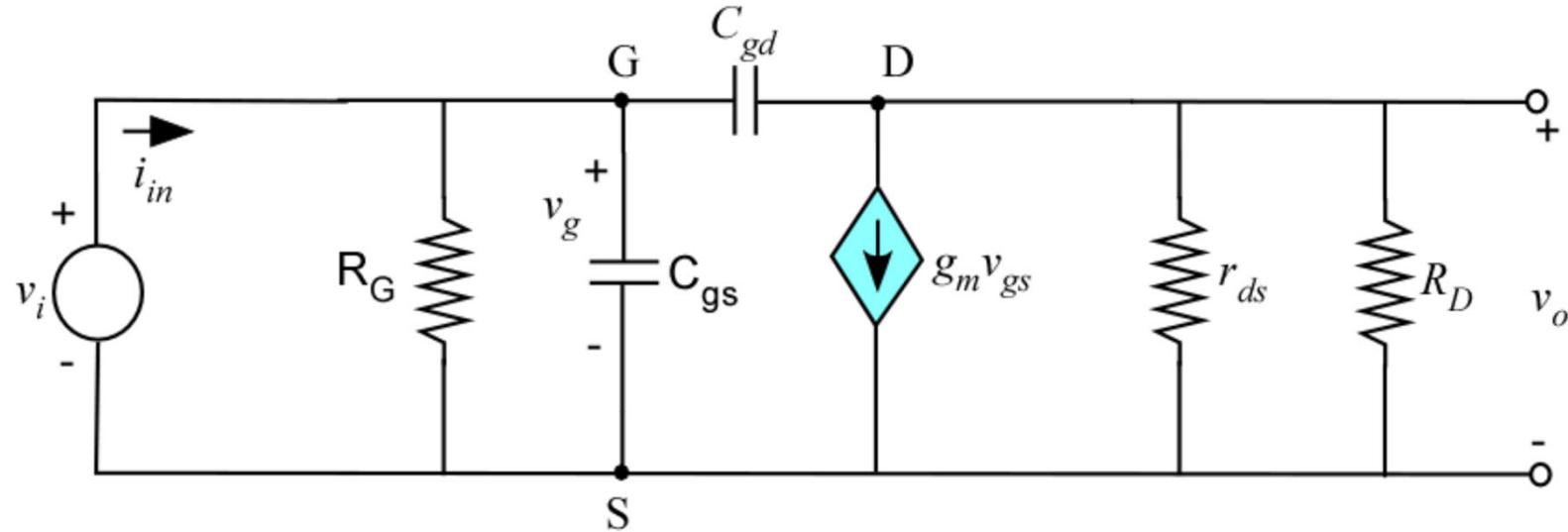


$$\text{If } R_i = 0, \quad f_{3dB} = \frac{1}{2\pi C_{gd} R_D} \quad r_{ds} = \frac{|V_A|}{I_D} = \frac{20}{1.516} = 13 \text{ k}\Omega$$

$$R' = R_D \parallel r_{ds} = 13 \parallel 2 = 1.736 \text{ k}\Omega$$

$$f_{3dB} = \frac{1}{2\pi 2.7 \times 10^{-12} \times 1.736 \times 10^3} = 33.95 \text{ MHz}$$

# Example Part (b)

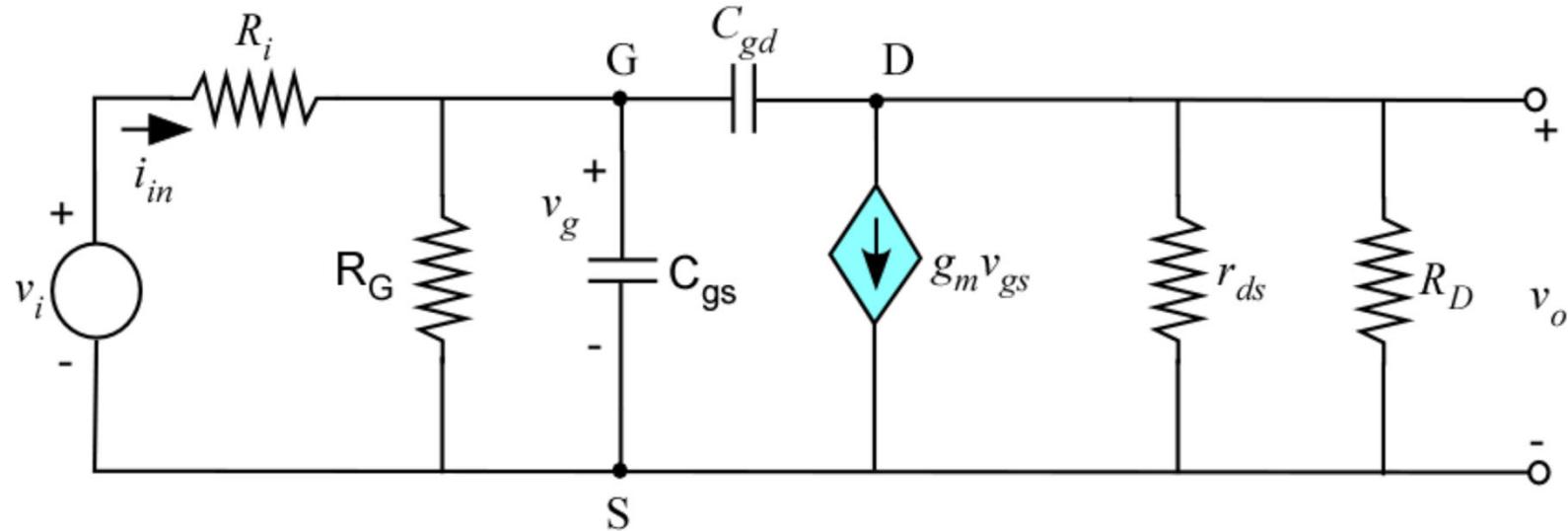

$$\text{If } R_i = 50 \text{ k}\Omega, \quad g_m R'_D = 0.870 \times 1.736 = 1.51$$

$$f_H \simeq \frac{1}{2\pi \left\{ R_i \left[ C_{gs} + C_{gd} (1 + g_m R'_D) \right] + C_{gd} R'_D \right\}}$$

$$f_H \simeq \frac{1}{2\pi \left\{ 50 \left[ 3 + 2.7(1 + 1.51) \right] + 2.7 \times 1.736 \right\}} = 32.27 \text{ kHz}$$