

## Experiment 09 - Advanced Technique

### 1 Introduction

In many S-parameter measurements, one wishes to obtain data for only a subsection of the entire system under test. A test fixture may be required between the normal coaxial calibration planes and the DUT; it may be useful to see the DUT performance with a certain matching network in place, it may be desired to see what the subsystem performance would be when the given DUT is inserted, etc.. In such cases, direct measurements of the DUT can not be performed. Figure 1 shows a simple yet concise illustration of the scenario. Here is an interesting work, measuring and modeling an on-wafer CMOS inductor, closely related to what is described in this Experiment: <http://ieeexplore.ieee.org/document/5498302/>

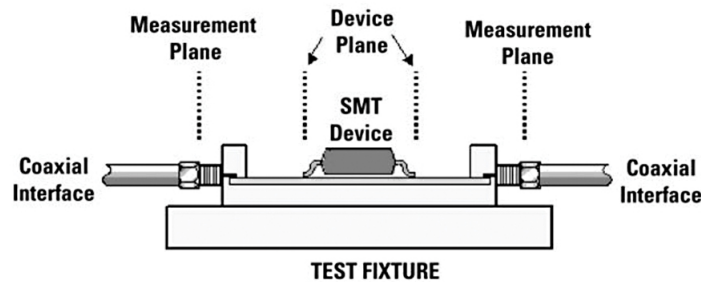


Figure 1: In-fixture measurement. Image originally from [1]

In the previous Experiment, you learned to use TRL calibration to remove the effects of all discontinuities between the so-called *measurement plane* and the *device plane* shown in Figure 1. In this Experiment, we will investigate more techniques that allows to separate and extract the data. The technique is *port extension*.

You will practice port extension on the microstrip student unknown, which you are much familiar with by now; an impedance transformer embedded exactly the same way as the microstrip student unknown shown in Figure 2.

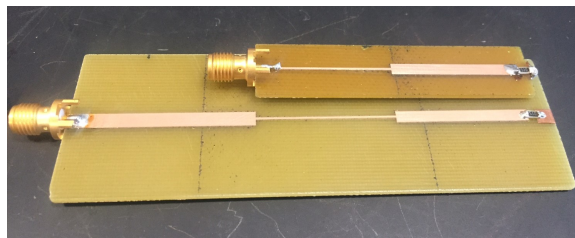


Figure 2: Embedded and non-embedded impedance transformer

### 2 Background

#### Port-extension

The classical de-embedding problem is the removal of the effects of a fixture or wafer probe. If one can treat the fixture/probe as a simple length of 50 ohm transmission line, then the problem reduces to one of shifting the reference planes, known as port extension. The familiar SOLT calibration is performed with coaxial standards, an *electrical*

*delay* is then added to effectively extend the measurement plane through the connector and out to the desired point on the microstrip line where the device plane is, thereby obviating the need for difficult-to-build microstrip standards. This has two potentially serious drawbacks: (1) the coax-to-microstrip transition discontinuity, and (2) non ideal transmission line characteristics of the microstrip line, such as attenuation and dispersion. Neither of these effects are characterized and removed by this technique. Hence, this simple technique usually works best in measurements where the frequencies involved are not too high.

### S-parameter De-embedding

Figure 3 shows de-embedding workflow with Agilent VNA.

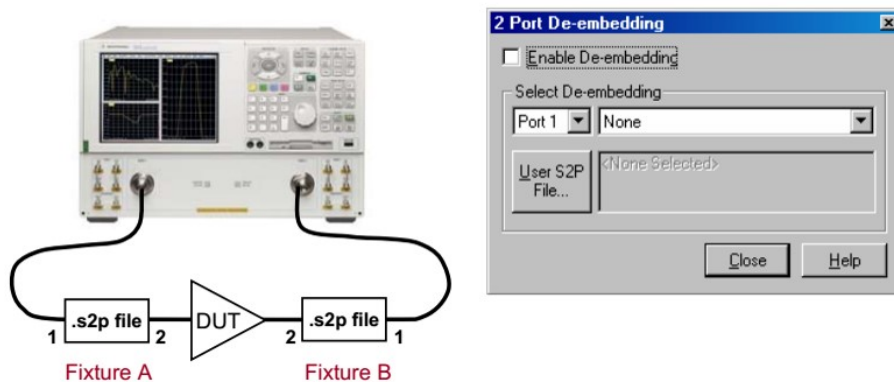


Figure 3: De-embedding technique with Keysight/Agilent VNA. Chart originally from [2]

De-embedding technique is based on cascading different blocks of S-parameters. It is known from the nature of S-parameter that it can **not** be cascaded directly. The most common way to deal with cascaded blocks of S-parameters is to convert them to T-parameter. T-parameter of the DUT is then computed and converted back to S-parameter as shown in Figure 4.

Multi-port de-embedding techniques make use of more complicated formulas and hence, will not be discussed here.

### 3 Pre-lab

1. If the microstrip student unknown were embedded after a 1.5in 100Ω microstrip line, would the port extension method be able to shift the reference plane?
2. Write conversion formulas between S- and T-parameter? Why cannot S-parameter be used to cascade multiple blocks while T-parameter can?
3. Use Problem 4, Homework 2 or your intuition to prove that a 50-ohm ideal transmission line measured at frequency  $f$  under a 50-ohm system has S-parameters as

$$S = \begin{bmatrix} 0 & e^{-j2\pi f\tau} \\ e^{-j2\pi f\tau} & 0 \end{bmatrix}$$

where  $\tau$  is the delay by which signal propagates along the line. Plot  $\text{phase}(S_{21})$  versus frequency  $f$  **qualitatively** and show where  $\tau$  appears in your plot.

### 4 Equipment

- Agilent E8358A VNA.
- Agilent 85052D 3.5mm SOLT calibration kit.
- Embedded 1-port microstrip student unknown, 1-port impedance transformer.

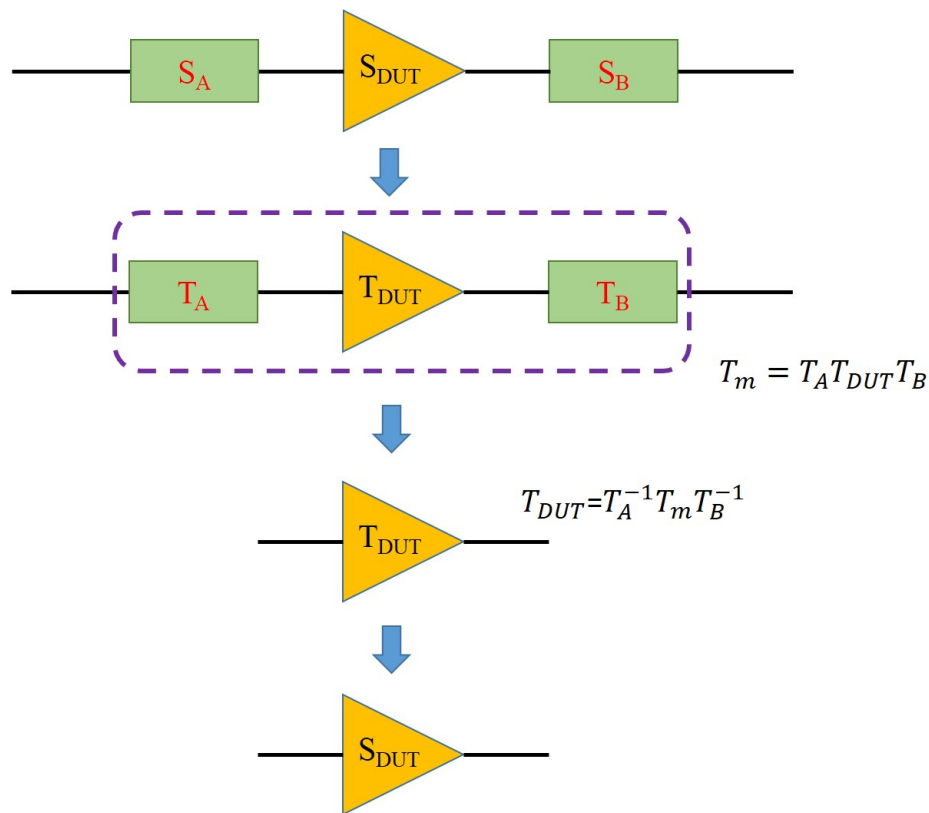


Figure 4: 2-port de-embedding formulation

- 3.5mm cables.
- N-type to 3.5mm adaptors.

## 5 Procedure

### Part I - Port extension: 300kHz - 4GHz

The microstrip student unknown and the impedance transformer will be measured first. In order to bypass the 1.5-in microstrip line embedded between the actual DUT and the SMA port using port extension, we need to know the electrical corresponding to that 1.5-in microstrip line. We will measure it in 2 different ways.

1. Calibrate the VNA from 300kHz to 4GHz using SOLT.
2. Connect the TRL REFLECT standard to Port 1. Set display to “SMITH CHART”. Dial in the appropriate amount of ELECTRICAL DELAY so that the displayed impedance is “balled up” around that of an open (somewhere between 350 and 500 picoseconds should work). You now have determine the electrical delay of the 1.5in microstrip line. Explain why is this true? What is the value you found?
3. With the electrical delay added, you now can connect the DUTs and measure them. If it is the microstrip student unknown, make sure you have the same one you used last time. Save the data and compare it against your measurement in the previous Experiment. If it is the impedance transformer, you have the non-embedded one as shown in Figure 2 to compare with.
4. You will now measure the electrical delay of the 1.5in microstrip line by a different way. Reset any electrical delay on any port (if any) to 0. Connect the THRU standard to 2 ports of the VNA. Set display of S21 to “PHASE”. Use question 3, *pre-lab*, put 2 markers at any two points to collect data and compute the electrical delay. Note that since the THRU is 3in, two times longer than the REFLECT, or the “obstacle” between the DUT and SMA connectors, the electrical delay found in this step should be halved to give the effective value for shifting the reference plane.

5. With the delay corresponding to 1.5in microstrip line added to port 1, you can now measure your micrstrip student unknown again. Collect the data.
6. Compare the electrical delay values found in step 2 vs step 4? Compare the microstrip student unknown measurement in step 3 and step 5? Which one do you think is more accurate? Which one is more convenient? Why?

## Part II - Model Extraction: Inductor & Capacitor

Using measured data that was obtained from probe station measurements, students must build proper models and extract necessary parameters in the models. Students will start with .s2p Touchstone files containing the measurement data and with a suggested model for the inductor and for the capacitor and then will find the appropriate parameters to simulate a response of that model that will match the measured data with high accuracy. This model could then be used to help with later designs or other simulations.

The DUTs (Device Under Test) are an inductor and a capacitor on a GaAs substrate. To accurately simulate the response of our inductor under test, we use the model shown in Figure 5.  $C_2$  and  $C_3$  represent the capacitances occurred at the ports, and  $C_1$  represents the coupling capacitance between the spiral inductor lines.  $R$  is corresponding to the loss. Larger  $R$  means higher loss in the substrate.  $L_1$  is, of course, the inductance of the inductor.

It is easy to represent this model using “PI” network and  $[Y]$  matrix, as shown in Figure 6.

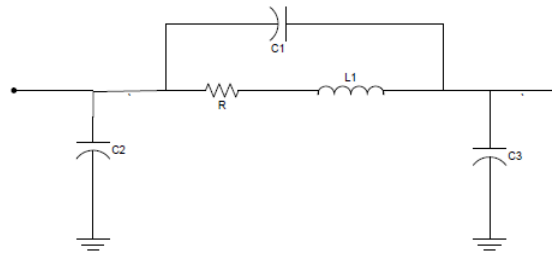


Figure 5: Suggested Inductor Model

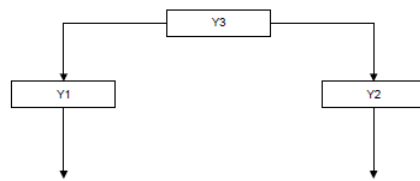


Figure 6: Y-matrix PI network

Using  $Y_1$  and  $Y_2$ , you can extract parameter  $C_2$  and  $C_3$ .  $Y_3$  contains  $R$ ,  $L_1$  and  $C_1$ 's information. At low frequency,  $C_1$  provide an open branch. If  $Z_3=1/Y_3$ , the real part of  $Z_3$  at low frequency will be quite close to  $R$  while the imaginary part of  $Z_3$  will provide us  $L_1$ . From the curves of  $Y_3$ , we can find a resonance frequency point that is corresponding to the resonance frequency of the paralleled LC circuits. Using that point and  $L_1$  we got before, we can get  $C_1$ .

For a capacitor under test, a similar model (Figure 7) can be used. But the  $Y_3$  branch now is a serial circuit. Using the same concepts from the inductor model extraction, we can extract all the parameters needed for this “PI” network.

We only can measure  $[S]$  parameters using the network analyzer. To get  $[Y]$ , we have to change  $[S]$  to  $[Y]$  using standard transformation. These formulas are provided below.

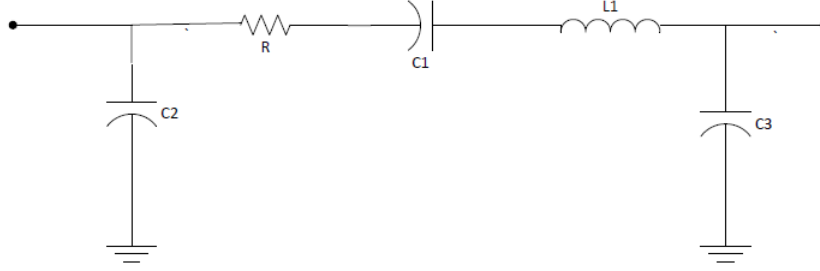


Figure 7: Y-matrix PI network

$$\begin{aligned}
 Y_{Y11} &= 1/50 * ((1 - S_{11}) * (1 + S_{22}) + S_{12} * S_{21}) / ((1 + S_{11}) * (1 + S_{22}) - S_{12} * S_{21}) \\
 Y_{Y12} &= -1/50 * 2 * S_{12} / ((1 + S_{11}) * (1 + S_{22}) - S_{12} * S_{21}) \\
 Y_{Y21} &= -1/50 * 2 * S_{21} / ((1 + S_{11}) * (1 + S_{22}) - S_{12} * S_{21}) \\
 Y_{Y22} &= 1/50 * ((1 + S_{11}) * (1 - S_{22}) + S_{12} * S_{21}) / ((1 + S_{11}) * (1 + S_{22}) - S_{12} * S_{21})
 \end{aligned} \tag{1}$$

$$\begin{aligned}
 Y_1 &= Y_{Y11} + Y_{Y21} & Z_1 &= 1/Y_1 \\
 Y_2 &= Y_{Y22} + Y_{Y12} & Z_2 &= 1/Y_2 \\
 Y_3 &= (Y_{Y21} + Y_{Y12}) / 2.0 & Z_3 &= -1/Y_3
 \end{aligned} \tag{2}$$

1. Using the given inductor .s2p file, build the model and extract the parameters of a PI network. Please demonstrate all necessary steps in the plots and print them in one page. NOTE: .ds files can be imported into ADS the same way you have imported .s2p files before (they are in Touchstone format).
2. Using the given capacitor.s2p file to build the model and extract the parameters of a PI network. Please demonstrate all necessary steps in the plots and print them in one page.
3. Required plots/tables for this part:
  - Plots of Real  $[Y_1]$ , Imag  $[Y_1]$ , Real  $[Y_2]$ , Imag  $[Y_2]$ , Real  $[Y_3]$ , Imag  $[Y_3]$  vs. frequency with appropriate markers to show how you calculated  $C_1$ ,  $C_2$ ,  $C_3$ ,  $L_1$ , and R.
  - Smith Charts of  $S_{11}$  and  $S_{21}$  with measured and simulated data using the extracted values.
  - Table of values of  $C_1$ ,  $C_2$ ,  $C_3$ ,  $L_1$ , and R for both the inductor and the capacitor.

## 6 Conclusion

1. What are pros and cons of the de-embedding technique?
2. Does your direct measurement of DUTs (both 1-port and 2-port) agree very well? If not, what could be the sources of discrepancies?

## References

- [1] Hiroyuki Maehara. *Using VNA Calibration Capabilities to Achieve Extremely Accurate Built-in Spectrum Measurements*. <http://www.mpdigest.com/2016/11/22/using-vna-calibration-capabilities-to-achieve-extremely-accurate-built-in-spectrum-measurements/>. [Online; accessed 30-Mar-2017]. Nov. 2016.
- [2] Agilent Technologies, Inc. *Modern Measurement Techniques for Testing Advanced Military Communications and Radars*. 2006.