

1. Consider the transmission line system shown in the figure above.

(a) Find the input impedance  $Z_{in}$ .

$$\Gamma_R = \frac{Z_R - Z_o}{Z_R + Z_o} = \frac{30 + j40 - 50}{30 + j40 + 50} = 0.5\angle 90^\circ$$

$$\Gamma(d=l) = \Gamma_R e^{-2j\beta l} = 0.5\angle 90^\circ e^{-j\frac{4\pi}{\lambda}0.725\lambda} = 0.5\angle -72^\circ$$

$$Z_{in} = Z_o \left[ \frac{1 + \Gamma(l)}{1 - \Gamma(l)} \right] = 50 \left[ \frac{1 + 0.5\angle -72^\circ}{1 - 0.5\angle -72^\circ} \right]$$

$$Z_{in} = 64.36\angle -51.73^\circ$$

$$Z_{in} = (39.86 - j50.54) \Omega$$

$$Z_{in} = (39.86 - j50.54) \Omega$$

(b) Find the current drawn from the generator

$$I_g = \frac{V_g}{Z_g + Z_{in}} = \frac{100\angle 0^\circ}{(10 + j10)(39.86 - j50.54)}$$

$$I_g = \frac{100\angle 0^\circ}{(49.86 - j40.54)} = \frac{100\angle 0^\circ}{64.26\angle -39.11^\circ}$$

$$I_g = 1.552\angle 39.11^\circ$$

$$I_g = 1.207 + j0.981$$

(c) Find the time-average power delivered to the load

$$V(l) = Z_{in} I_g = 64.36 \angle -51.73^\circ \times 1.552 \angle 39.11^\circ = 100.159 \angle -12.62^\circ$$


$$\langle P \rangle = \frac{1}{2} \operatorname{Re} [V(l) I_g^*] = \frac{1}{2} \operatorname{Re} [100.159 \angle -12.62^\circ \times 1.552 \angle -39.11^\circ]$$

$$\langle P \rangle = \frac{1}{2} \operatorname{Re} [V(l) I_g^*] = \frac{1}{2} \operatorname{Re} [100.159 \times 1.552 \times \cos 51.73^\circ] = 48.26W$$

$$\underline{\langle P \rangle = 48.26W}$$

2. A lossless transmission line of characteristic impedance  $75 \Omega$  is terminated by some complex load,  $Z_L$ . If the distance from the load to the location of the first impedance minimum is measured to be  $.304\lambda$  and the impedance at that point is  $22.5 \Omega$ , using the Smith Chart find:

- a) The SWR.
  - i. Find  $z_{min}=Z_{min}/Z_0=.3$  on the Smith Chart
  - ii. Draw constant SWR circle
  - iii. Locate real crossing on  $r>1$  side of Smith Chart
  - iv. Read off  $r_{max} = \text{SWR} = 3.3$
- b) The load impedance,  $Z_L$ .
  - i. Rotate from  $z_{min}$  towards the load by  $0.304\lambda$
  - ii. Draw line from point to origin of Smith Chart
  - iii. Read off  $z_L = 1.6 + j1.5$
  - iv.  $Z_L = z_L Z_0 = 120 + j112.5 \Omega$
- c) The reflection coefficient,  $\bar{\Gamma}_L$ .
  - i. Read off  $\theta = 38.5^\circ$
  - ii. Measure normalized linear distance from origin to  $Z_L$ :  $|\Gamma_L| = .53$
- d) Distance to the first voltage maximum.
  - i. Rotate from  $z_L$  towards generator to real crossing on  $r>1$  side
  - ii.  $d_{max} = .054\lambda$
- e) Value of the line impedance at this point.
  - i. Read off  $z_{max} = 3.3$
  - ii.  $Z_{max} = z_{max} Z_0 = 247.5 \Omega$
- f) The distance to the closest point to the load where the real part of the line impedance is  $75 \Omega$ .
  - i. Find intersection of SWR circle with  $r = 1$  circle
  - ii. Read off distance towards the generator =  $.134\lambda$
- g) Is the impedance at the point located in part f inductive or capacitive?
  - i. Point is on bottom portion of Smith Chart so it is capacitive.

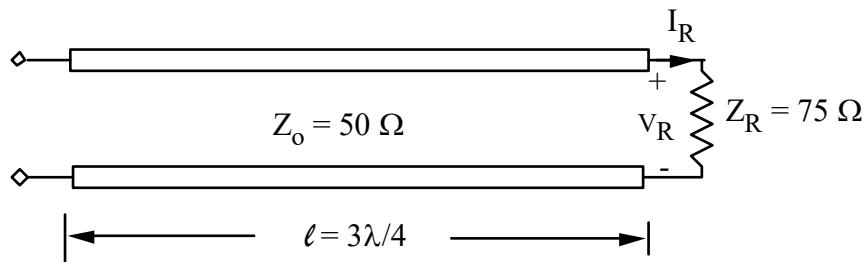


3. Given the lossless transmission line shown above,

- (a) Find the reflection coefficient  $\Gamma_R$  and the standing wave ratio (SWR) for this loaded transmission line.
- (b) Sketch the standing wave patterns for the magnitude of the voltage along this transmission line in terms of  $V_R$ .
- (c) Determine the impedance at the input of this loaded transmission line.
- (d) If a sinusoidal generator  $10 \angle 0^\circ$  V, which has a source impedance of  $100 \Omega$  is connected to this loaded transmission line, what is the time average power delivered to the  $75\Omega$  load.

$$(a) \Gamma_R = \frac{Z_R - Z_0}{Z_R + Z_0} = \frac{75 - 50}{75 + 50} = 0.2$$

$$\text{SWR} = \frac{1+0.2}{1-0.2} = 1.5$$

(b)

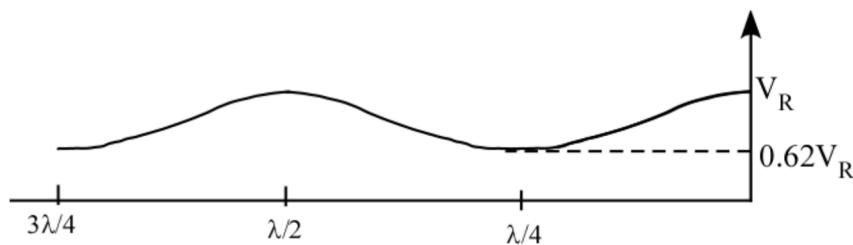

$$(c) Z_{in} = \frac{Z_0^2}{Z_R} = \frac{(50)^2}{75} = \frac{2500}{75} = 33.33 \Omega$$


$$(d) \langle P \rangle = \frac{1}{2} \operatorname{Re} [V_{in} I_{in}^*] = \frac{|V_s|^2 Z_{in}}{2(Z_s + Z_{in})^2} = \frac{(100)(33.33)}{2(100+33.33)^2}, \langle P \rangle = 0.0937 \text{ watts}$$


4. Answer the following questions using a Smith chart. Clearly identify significant features on the chart. A transmission line with characteristic impedance  $50 \Omega$  is terminated by a load of impedance  $Z_r = 40 + j50 \Omega$ .

- (a) What is the SWR? *Solution: The normalized  $z_r$  is  $0.8 + j 1.0$ . Find this point on the Smith Chart, draw the constant SWR circle, read off the SWR=3.0*
- (b) What is the phase of  $\Gamma_r$ ? *72 degrees, from the Smith Chart.*
- (c) What is the normalized admittance at the load?  *$0.5-j0.6$ , from the Smith Chart.*
- (d) What is the normalized admittance at  $d = 12.2\lambda$  toward the generator from the load?  *$0.5+j0.6$ , from the Smith Chart.*
- (e) What is the phase of  $\Gamma$  at  $d = 12.2\lambda$  toward the generator from the load? (10 pts) - *72 degrees, from the Smith Chart. Be sure to read the phase of Gamma from the impedance side of the constant SWR circle.*
- (f) What is the shortest distance from the load at which a short-circuited stub could be attached to achieve an impedance match? *0.265 wavelengths, from the Smith Chart.*
- (g) What would the normalized input admittance of the stub be? *-j1.1*

IMPEDANCE OR ADMITTANCE COORDINATES

$$T_r = 0.5 \angle 32^\circ$$

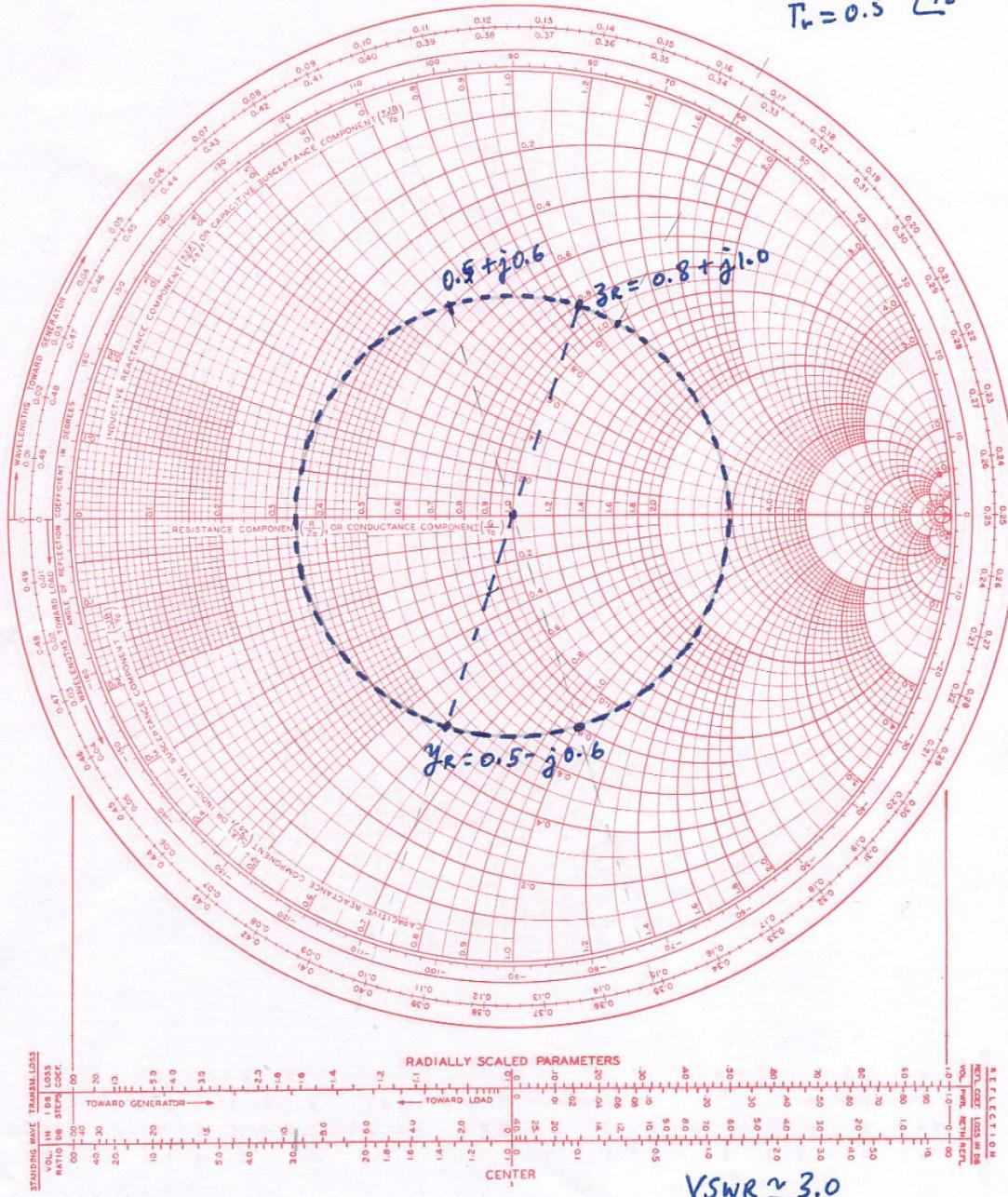

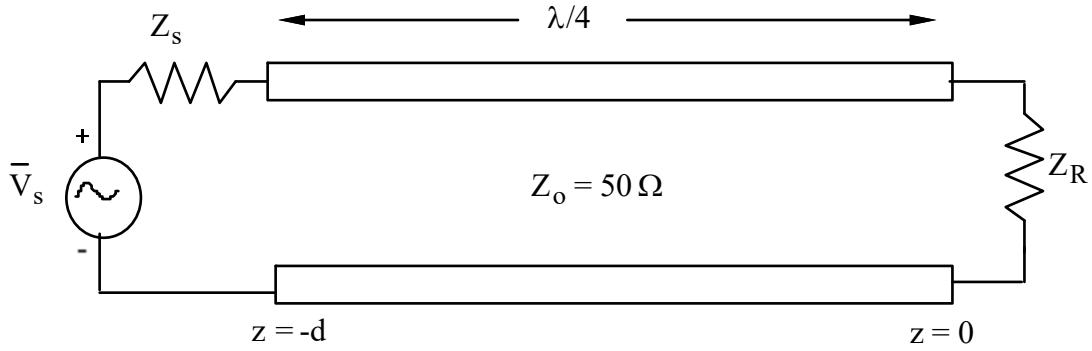

5. For the above figure, let  $\bar{V}_s = 1$  volt,  $Z_s = 30 \Omega$ , and  $Z_R = 40 \Omega$ .

(a) What is the impedance at the input of the line ( $z = -d$ )?

$$Z_{in} = \frac{Z_o^2}{Z_R} = \frac{(50)^2}{40} = 62.5 \Omega$$

(b) What is the phasor current through  $Z_s$ ?

$$I_{in} = \frac{1}{Z_s + Z_{in}} = \frac{1}{30 + 62.5} = 0.01081 A$$

(c) What is the phasor current through  $Z_R$ ?

$$T_s = 5/8, \Gamma_s = -2/8, \Gamma_R = -1/9, ,$$

$$V+ = -j0.608 V, = \frac{-j0.608}{50} [1 - (-0.111)]$$

$$I_R = -j13.51 \text{ mA}$$

(d) What is the time-average power delivered to the load?

$$P = \frac{1}{2} \operatorname{Re} \{ V_{in} I_{in}^* \} = \frac{1}{2} \operatorname{Re} \{ 62.5 \times 0.01081 \times 0.01081 \}$$

$$P = 3.65 \text{ mW}$$