


ECE 451

Advanced Microwave Measurements

Review

Jose E. Schutt-Aine
Electrical & Computer Engineering
University of Illinois
jesa@illinois.edu

Generalized Impedance

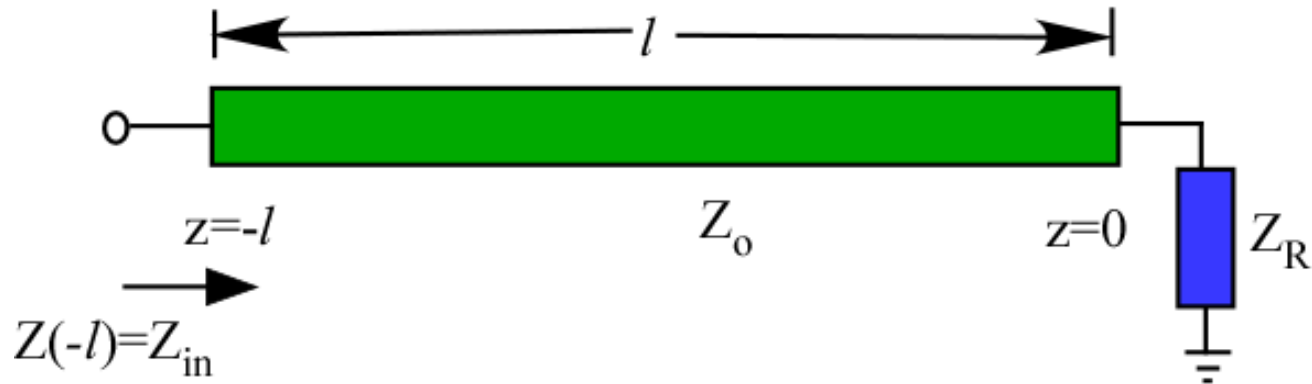


$$Z(z) = \frac{V(z)}{I(z)} = Z_o \left[\frac{e^{-j\beta z} + \Gamma_R e^{+j\beta z}}{e^{-j\beta z} - \Gamma_R e^{+j\beta z}} \right]$$

$$Z(-l) = Z_o \left[\frac{Z_R + jZ_o \tan \beta l}{Z_o + jZ_R \tan \beta l} \right]$$

Impedance
transformation
equation

Generalized Impedance

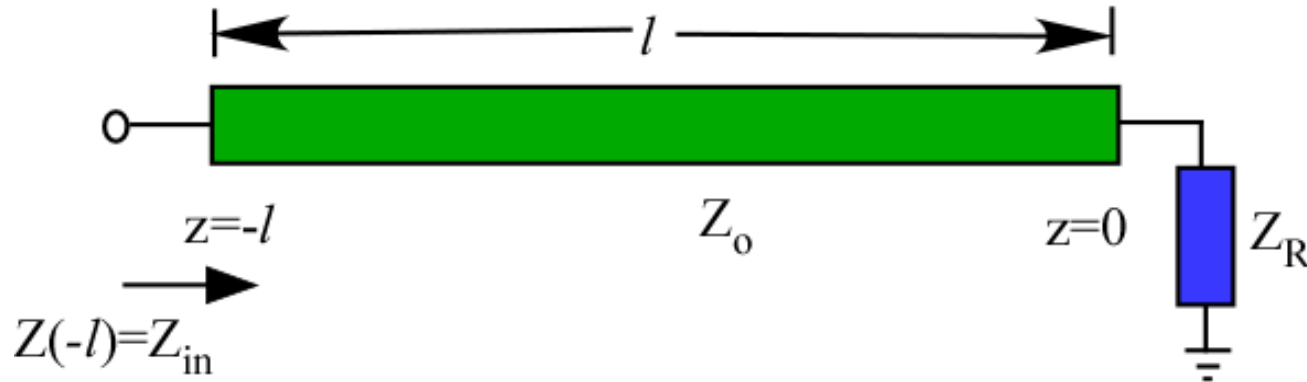

- Short circuit $Z_R=0$, line appears inductive for $0 < l < \lambda/2$

$$Z(-l) = jZ_o \tan \beta l$$

- Open circuit $Z_R \rightarrow \text{inf}$, line appears capacitive for $0 < l < \lambda/2$

$$Z(-l) = \frac{Z_o}{j \tan \beta l}$$

- If $l = \lambda/4$, the line is a quarter-wave transformer

$$Z(-l) = \frac{Z_o^2}{Z_R}$$

Generalized Reflection Coefficient

$$\Gamma(z) = \frac{\text{Backward traveling wave at } z}{\text{Forward traveling wave at } z} = \frac{V_b(z)}{V_f(z)}$$

$$\Gamma(z) = \frac{V_- e^{+j\beta z}}{V_+ e^{-j\beta z}} = \frac{V_-}{V_+} e^{+2j\beta z} = \Gamma_R e^{+2j\beta z}$$

**Reflection coefficient
transformation equation**



$$\Gamma(-l) = \Gamma_R e^{-2j\beta l}$$


$$Z(z) = Z_o \frac{1 + \Gamma(z)}{1 - \Gamma(z)}$$

$$\Gamma(z) = \frac{Z(z) - Z_o}{Z(z) + Z_o}$$

Voltage Standing Wave Ratio (VSWR)


Define Voltage Standing Wave Ratio as:

$$VSWR = \frac{V_{\max}}{V_{\min}} = \frac{1 + |\Gamma_R|}{1 - |\Gamma_R|}$$

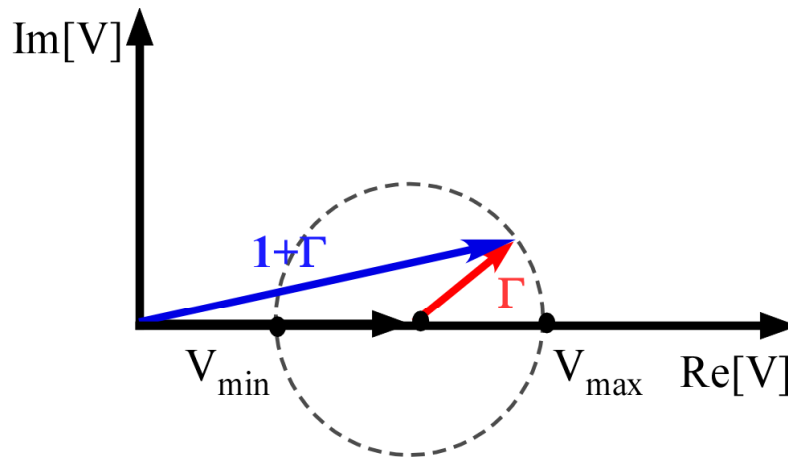


It is a measure of the interaction between forward and backward waves

Application: Slotted-Line Measurement

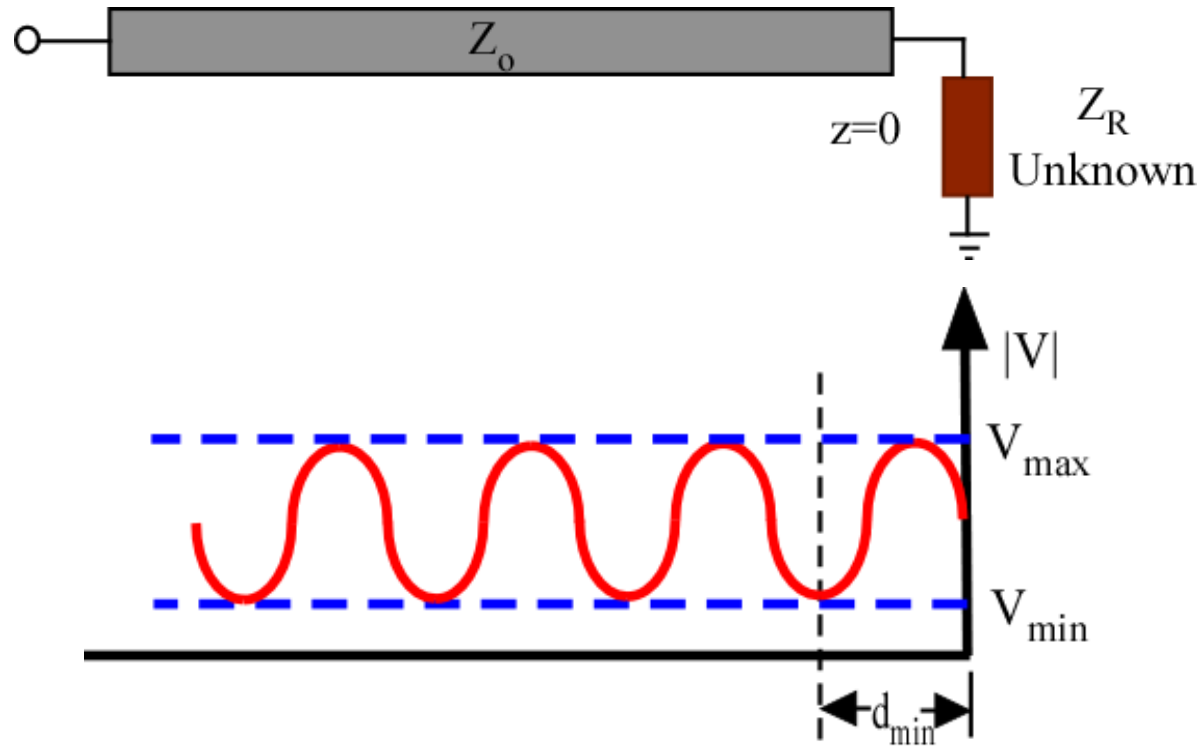

- Measure $VSWR = V_{\max}/V_{\min}$
- Measure location of first minimum

Application: Slotted-Line Measurement

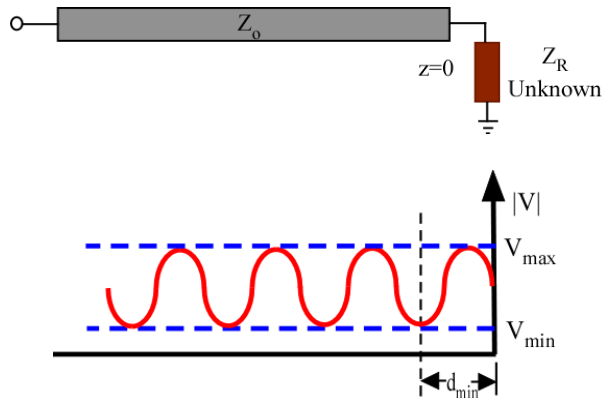

At minimum, $\Gamma(z) = \text{pure real} = -|\Gamma_R|$

Therefore, $\Gamma(-d_{\min}) = \Gamma_R e^{-2j\beta d_{\min}} = -|\Gamma_R|$

So, $\Gamma_R = -|\Gamma_R| e^{+2j\beta d_{\min}}$

Since $|\Gamma_R| = \frac{VSWR - 1}{VSWR + 1}$ **then** $\Gamma_R = -\left(\frac{VSWR - 1}{VSWR + 1}\right) e^{+2j\beta d_{\min}}$

and $Z_R = Z_o \left(\frac{1 + \Gamma_R}{1 - \Gamma_R} \right)$

Summary of TL Equations

Voltage

$$V(z) = V_+ e^{-j\beta z} \left[1 + \Gamma_R e^{+2j\beta z} \right]$$

Current

$$I(z) = \frac{V_+}{Z_o} e^{-j\beta z} \left[1 - \Gamma_R e^{+2j\beta z} \right]$$


Impedance Transformation → $Z(-l) = Z_o \left[\frac{Z_R + jZ_o \tan \beta l}{Z_o + jZ_R \tan \beta l} \right]$

Reflection Coefficient Transformation → $\Gamma(-l) = \Gamma_R e^{-2j\beta l}$

Reflection Coefficient – to Impedance → $Z(z) = Z_o \frac{1 + \Gamma(z)}{1 - \Gamma(z)}$

Impedance to Reflection Coefficient → $\Gamma(z) = \frac{Z(z) - Z_o}{Z(z) + Z_o}$

Determining V_+

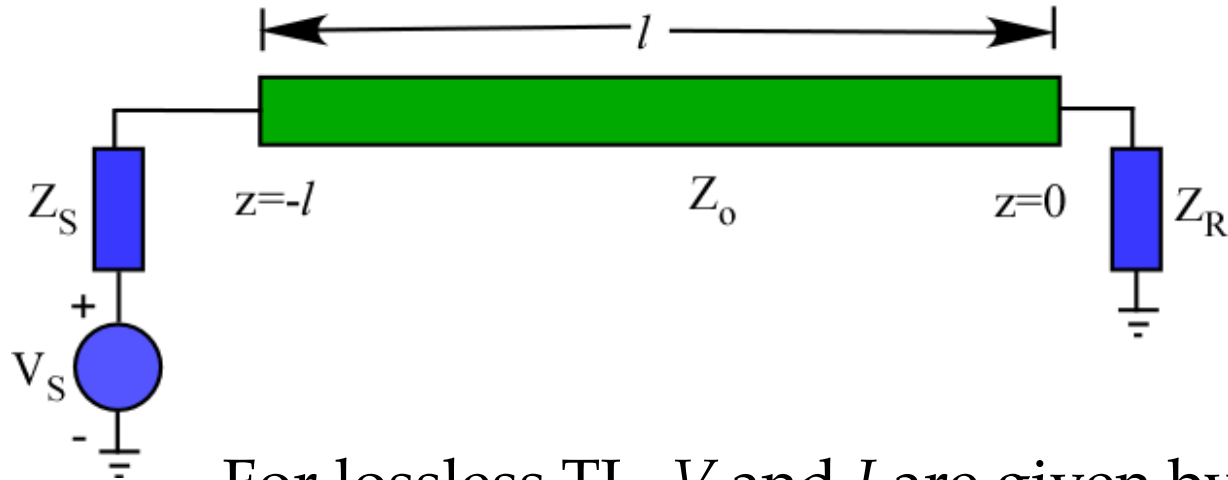

For lossless TL, V and I are given by

$$V(z) = V_+ e^{-j\beta z} \left[1 + \Gamma_R e^{+2j\beta z} \right]$$

reflection coefficient
at the load


$$\Gamma_R = \frac{Z_R - Z_o}{Z_R + Z_o}$$

$$I(z) = \frac{V_+ e^{-j\beta z}}{Z_o} \left[1 - \Gamma_R e^{+2j\beta z} \right]$$

$$\text{At } z = -l, \quad V_s = Z_s I(-l) + V(-l)$$

Determining V_+
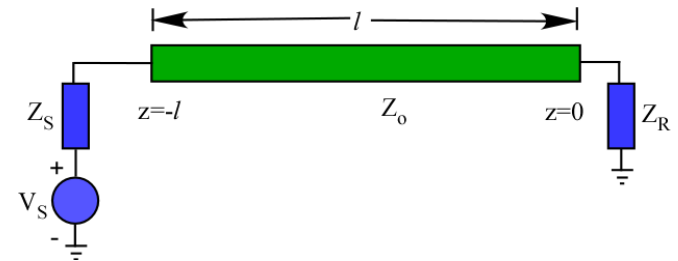
$$V_+ \left(e^{+j\beta l} - \Gamma_S \Gamma_R e^{-j\beta l} \right) = T_S V_S$$




$$\text{with } T_S = \left(1 + \frac{Z_S}{Z_o} \right)^{-1} = \frac{Z_o}{Z_S + Z_o} \quad \text{and} \quad \Gamma_S = \frac{Z_S - Z_o}{Z_S + Z_o}$$

From which

$$V_+ = \frac{T_S V_S e^{-j\beta l}}{1 - \Gamma_S \Gamma_R e^{-2j\beta l}}$$

Example 1

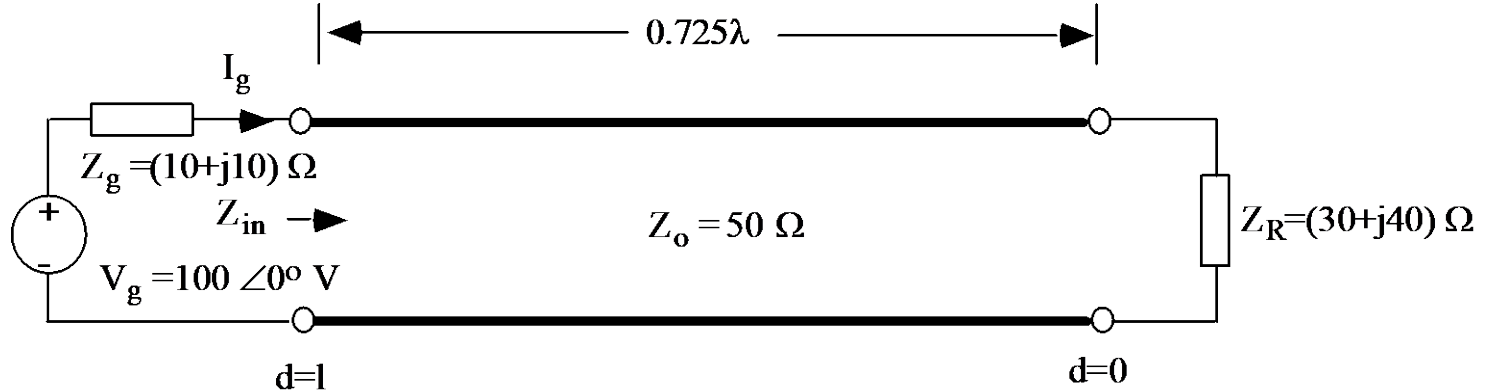

Consider the transmission line system shown in the figure above.

(a) Find the input impedance Z_{in} .

$$\Gamma_R = \frac{Z_R - Z_o}{Z_R + Z_o} = \frac{(30 + j40) - 50}{(30 + j40) + 50} = 0.5 \angle 90^\circ$$

$$\Gamma(d = l) = \Gamma_R e^{-2j\beta l} = 0.5 \angle 90^\circ e^{-j\frac{4\pi}{\lambda} \cdot 0.725\lambda} = 0.5 \angle -72^\circ$$

Example 1 – Cont'

$$Z_{in} = Z_o \left[\frac{1 + \Gamma(l)}{1 - \Gamma(l)} \right] = 50 \left[\frac{1 + 0.5 \angle -72^\circ}{1 - 0.5 \angle -72^\circ} \right] \Omega$$

$$Z_{in} = 64.361 \angle -51.738^\circ \Omega = (39.86 - j50.54) \Omega$$

(b) Find the current drawn from the generator

$$I_g = \frac{V_g}{Z_g + Z_{in}} = \frac{100 \angle 0^\circ}{(10 + j10)(39.86 - j50.54)} = 1.552 \angle 39.11^\circ A$$

$$I_g = 1.207 + j0.981 A$$

Example 1 – Cont'


c) Find the time-average power delivered to the load

$$V(l) = Z_{in} I_g = 64.361 \angle 51.73^\circ \times 1.5562 \angle 39.11^\circ = 100.159 \angle -12.62^\circ \frac{1}{2}$$

$$\langle P \rangle = \frac{1}{2} \text{Real} [V(l) I_g^*] = \frac{1}{2} \text{Real} [100.159 \angle -12.62^\circ \times 1.5562 \angle -39.11^\circ]$$

$$\langle P \rangle = \frac{1}{2} \text{Real} [V(l) I_g^*] = 48.26 \text{ W}$$

Example 1 – Cont'

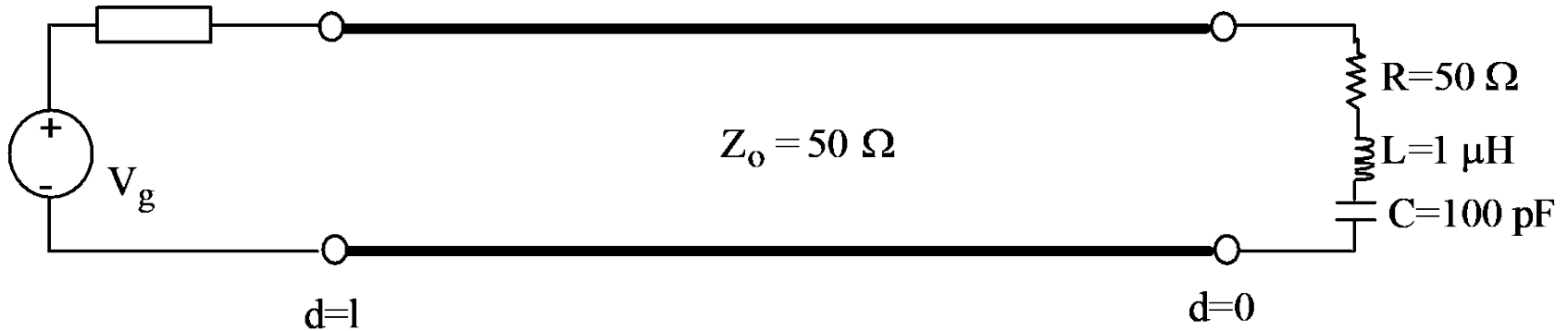

In the system shown above, a line of characteristic impedance 50Ω is terminated by a series R, L, C circuit having the values $R = 50 \Omega$, $L = 1 \mu\text{H}$, and $C = 100 \text{ pF}$.


(d) Find the source frequency f_o for which there are no standing waves on the line.

Example 1 – Cont'

No standing wave on the line if $Z_R = R = Z_0$ which occurs at the resonant frequency of the RLC circuit. Thus,

$$f_o = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{10^{-6} \times 10^{-10}}} = \frac{10^8}{2\pi} \text{ Hz} = 15.92 \text{ MHz}$$

Lossy Transmission Line

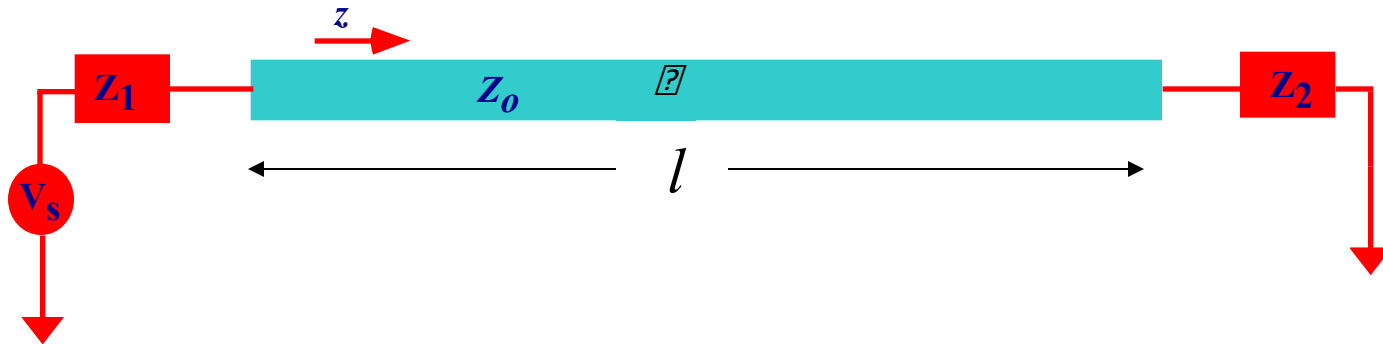


$$V(z) = Ae^{-\alpha z}e^{-j\beta z} + Be^{+\alpha z}e^{+j\beta z}$$

$$I(z) = \frac{1}{Z_o} \left[Ae^{-\alpha z}e^{-j\beta z} - Be^{+\alpha z}e^{+j\beta z} \right]$$

$$Z_o = \sqrt{\frac{(R(\omega) + j\omega L)}{(G + j\omega C)}}$$

$$\gamma = \alpha + j\beta = \sqrt{(R(\omega) + j\omega L)(G + j\omega C)}$$

Wave Approach

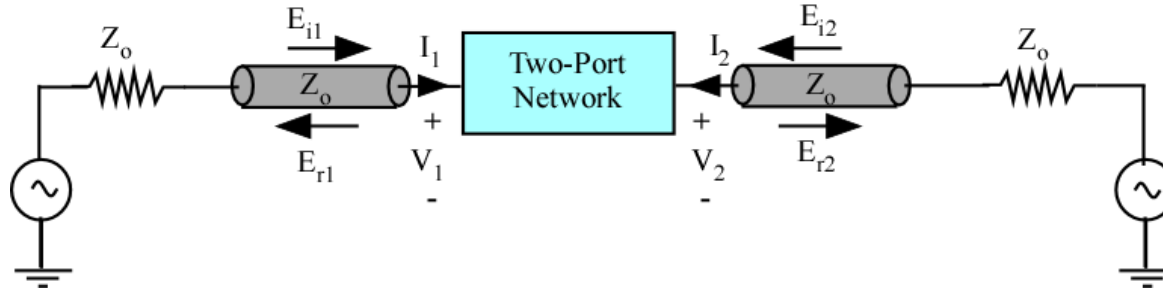

$$a_1 = \frac{E_{i1}}{\sqrt{Z_o}}$$

$$a_2 = \frac{E_{i2}}{\sqrt{Z_o}}$$

$$b_1 = \frac{E_{r1}}{\sqrt{Z_o}}$$

$$b_2 = \frac{E_{r2}}{\sqrt{Z_o}}$$

Z_o is the reference impedance of the system

$$b_1 = S_{11} a_1 + S_{12} a_2$$

$$b_2 = S_{21} a_1 + S_{22} a_2$$

N-Port S Parameters

$$\begin{bmatrix} b_1 \\ b_2 \\ \cdot \\ b_n \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} & \cdot & \cdot \\ S_{21} & S_{22} & \cdot & \cdot \\ \cdot & \cdot & \cdot & \cdot \\ \cdot & \cdot & \cdot & S_{nn} \end{bmatrix} \begin{bmatrix} a_1 \\ a_2 \\ \cdot \\ a_n \end{bmatrix}$$

$$\mathbf{b} = \mathbf{S}\mathbf{a}$$

If $b_i = 0$, then no reflected wave on port $i \rightarrow$ port is matched

$$a_i = \frac{V_i^+}{\sqrt{Z_{oi}}}$$

V_i^+ : incident voltage wave in port i

V_i^- : reflected voltage wave in port i

$$b_i = \frac{V_i^-}{\sqrt{Z_{oi}}}$$

Z_{oi} : impedance in port i

Dissipated Power

$$P_d = \frac{1}{2} \mathbf{a}^T (\mathbf{U} - \mathbf{S}^T \mathbf{S}^*) \mathbf{a}^*$$

The dissipation matrix $\mathbf{D}$ is given by:

$$\mathbf{D} = \mathbf{U} - \mathbf{S}^T \mathbf{S}^*$$

Passivity insures that the system will always be stable provided that it is connected to another passive network

For passivity

- (1) the determinant of $\mathbf{D}$ must be ≥ 0
- (2) the determinant of the principal minors must be ≥ 0

Dissipated Power

When the dissipation matrix is 0, we have a lossless network →

$$\mathbf{S}^T \mathbf{S}^* = \mathbf{U}$$

The $\mathbf{S}$ matrix is unitary.

For a lossless two-port:

$$|S_{11}|^2 + |S_{21}|^2 = 1$$

$$|S_{22}|^2 + |S_{12}|^2 = 1$$

If in addition the network is reciprocal, then

$$S_{12} = S_{21} \quad \text{and} \quad |S_{11}| = |S_{22}| = \sqrt{1 - |S_{12}|^2}$$

Scattering Transfer Parameters

In T-Parameters, traveling waves at the input are related to those at the output

$$b_1 = S_{11}a_1 + S_{12}a_2$$

$$b_1 = T_{11}a_2 + T_{12}b_2$$

$$b_2 = S_{21}a_1 + S_{22}a_2$$


$$a_1 = T_{21}a_2 + T_{22}b_2$$

$$\begin{pmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{pmatrix} = \begin{pmatrix} T_{12}T_{22}^{-1} & T_{11} - T_{12}T_{21}T_{22}^{-1} \\ T_{22}^{-1} & -T_{21}T_{22}^{-1} \end{pmatrix}$$

$$\begin{pmatrix} T_{11} & T_{12} \\ T_{21} & T_{22} \end{pmatrix} = \begin{pmatrix} S_{12} - S_{11}S_{22}S_{21}^{-1} & S_{11}S_{21}^{-1} \\ -S_{22}S_{21}^{-1} & S_{21}^{-1} \end{pmatrix}$$

T parameters can be cascaded $\mathbf{T} = \mathbf{T}_A \cdot \mathbf{T}_B$

High-Frequency Characterization

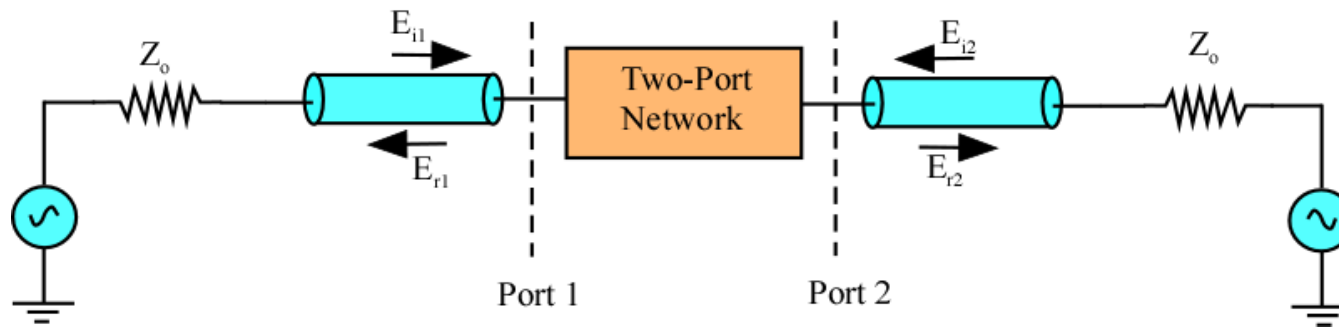

Transmission-Line Scattering Parameters

$$S_{21} = \frac{(1 - \Gamma^2)X}{1 - \Gamma^2 X^2} \quad S_{11} = \frac{(1 - X^2)\Gamma}{1 - \Gamma^2 X^2}$$

$$X = e^{-\gamma d}$$

$$Z_c = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

$$\Gamma = \frac{Z_c - Z_o}{Z_c + Z_o}$$

$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)}$$

TL Extraction Formulas

$$X = e^{-\gamma d} = e^{-j\beta d} e^{-\alpha d} \quad X = e^{-\gamma d} = \frac{(S_{11} + S_{21}) - \Gamma}{1 - (S_{11} + S_{21})\Gamma}$$

$$\Gamma = Q \pm \sqrt{Q^2 - 1}$$

$$Q = \frac{\{S_{11}^2 - S_{21}^2\} + 1}{2S_{11}}$$

$$R = \operatorname{Re}\{\gamma Z_c\}$$

$$G = \operatorname{Re}\left\{\frac{\gamma}{Z_c}\right\}$$

$$L = \frac{1}{\omega} \operatorname{Im}\{Z_c \gamma\}$$

$$C = \frac{1}{\omega} \operatorname{Im}\left\{\frac{\gamma}{Z_c}\right\}$$


Modeling Interconnections

Low Frequency




Short

Mid-range
Frequency

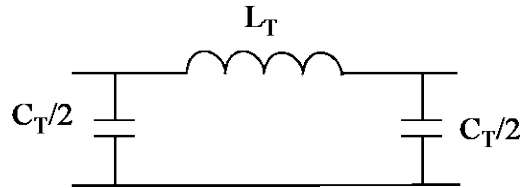


or

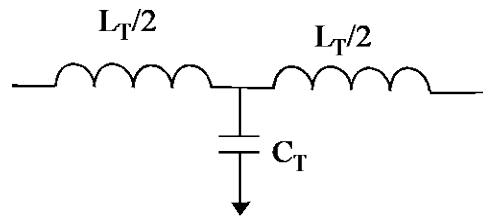

Lumped
Reactive CKT

High Frequency

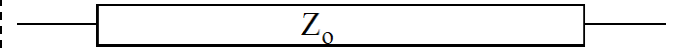

Transmission
Line