

# ECE 451

# Advanced Microwave Measurements

## The Smith Chart

Jose E. Schutt-Aine  
Electrical & Computer Engineering  
University of Illinois  
[jschutt@emlab.uiuc.edu](mailto:jschutt@emlab.uiuc.edu)

# Derivation of the Smith Chart

The relationship between impedance and reflection coefficient is given by:

$$Z(z) = Z_o \left[ \frac{1 + \Gamma(z)}{1 - \Gamma(z)} \right]$$

where  $Z_o$  is the characteristic impedance of the system.  
The normalized impedance is

$$Z_n(z) = \frac{1 + \Gamma(z)}{1 - \Gamma(z)} = \frac{1 + \Gamma}{1 - \Gamma}$$

The reflection coefficient and the normalized impedance have the form:

$$\Gamma = \Gamma_r + j\Gamma_i \quad \text{and} \quad Z_n = r + jx$$

# Derivation of the Smith Chart

Therefore

$$r + jx = \frac{1 + \Gamma_r + j\Gamma_i}{1 - \Gamma_r - j\Gamma_i} = \frac{[(1 + \Gamma_r) + j\Gamma_i][(1 - \Gamma_r) + j\Gamma_i]}{(1 - \Gamma_r)^2 + \Gamma_i^2}$$

Separating real and imaginary components,

$$r + jx = \frac{1 - \Gamma_r^2 + j\Gamma_i(1 + \Gamma_r) + j\Gamma_i(1 - \Gamma_r) - \Gamma_i^2}{(1 - \Gamma_r)^2 + \Gamma_i^2}$$

Isolating the real part from both sides

$$r = \frac{1 - \Gamma_r^2 - \Gamma_i^2}{(1 - \Gamma_r)^2 + \Gamma_i^2}$$

# Derivation of the Smith Chart

Multiplying through by the denominator,

$$r \left[ 1 + \Gamma_r^2 - 2\Gamma_r + \Gamma_i^2 \right] = 1 - \Gamma_r^2 - \Gamma_i^2$$

$$\Gamma_r^2(r+1) + \Gamma_i^2(r+1) - 2r\Gamma_r = 1 - r$$

$$\Gamma_r^2 + \Gamma_i^2 - \frac{2r\Gamma_r}{1+r} + \frac{r^2}{(1+r)^2} = \frac{1-r}{1+r} + \frac{r^2}{(1+r)^2}$$

Completing the square


$$\Gamma_r^2 + \Gamma_i^2 - \frac{2r\Gamma_r}{1+r} = \frac{1-r}{1+r} \quad \text{or} \quad \left( \Gamma_r - \frac{r}{1+r} \right)^2 + \Gamma_i^2 = \frac{1}{(1+r)^2}$$

# Derivation of the Smith Chart

$$\left( \Gamma_r - \frac{r}{1+r} \right)^2 + \Gamma_i^2 = \frac{1}{(1+r)^2}$$

This is the equation of a circle centered at
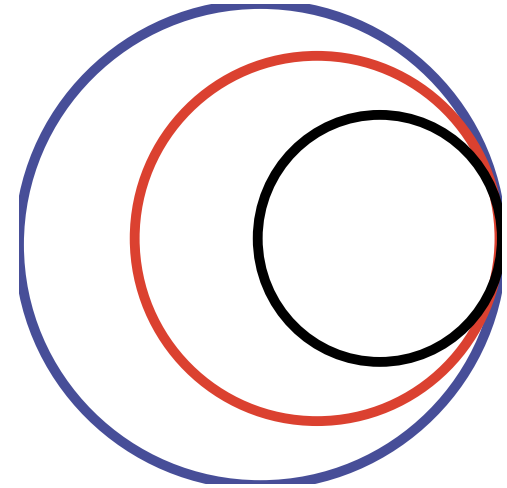
$$\left( \frac{r}{1+r}, 0 \right) \text{ and of radius } \frac{1}{1+r}$$



Equating the imaginary parts gives

$$x = \frac{2\Gamma_i}{(1 - \Gamma_r)^2 + \Gamma_i^2}$$

$$x \left[ 1 + \Gamma_r^2 - 2\Gamma_r + \Gamma_i^2 \right] = 2\Gamma_i \quad \text{or} \quad \Gamma_r^2 x - 2x\Gamma_r + x\Gamma_i^2 - 2\Gamma_i = -x$$


# Derivation of the Smith Chart

$$\Gamma_r^2 - 2\Gamma_r + 1 + \Gamma_i^2 - \frac{2\Gamma_i}{x} + \frac{1}{x^2} = \frac{1}{x^2} - 1 + 1$$

$$(\Gamma_r - 1)^2 + \left(\Gamma_i - \frac{1}{x}\right)^2 = \frac{1}{x^2}$$

This is the equation of a circle centered at
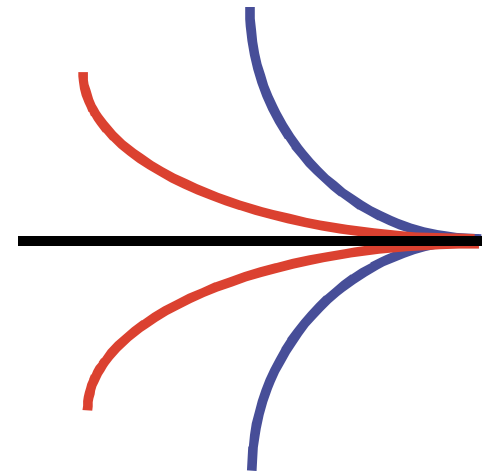
$$\left(1, \frac{1}{x}\right) \text{ of radius } \frac{1}{x}$$



# The Smith Chart

The reflection coefficient is given by


$$\Gamma = \frac{Z_n - 1}{Z_n + 1} = \frac{r - 1 + jx}{r + 1 + jx}$$

We also have

$$|\Gamma| = \left[ \frac{(r - 1)^2 + x^2}{(r + 1)^2 + x^2} \right]^{1/2} \leq 1$$

$$Z_n = \frac{1 + \Gamma(z)}{1 - \Gamma(z)}$$
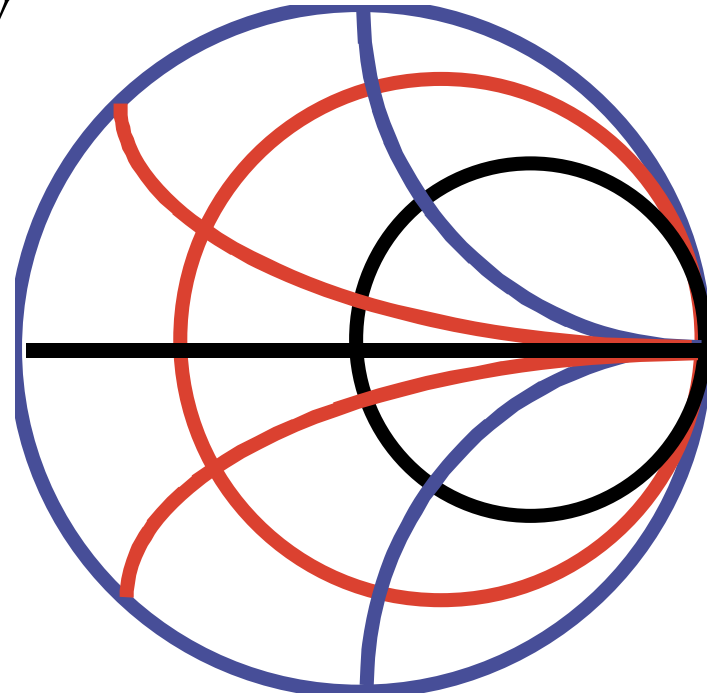
$$y = \frac{1}{Z_n} = \frac{1 - \Gamma(z)}{1 + \Gamma(z)}$$



Thus, going from normalized impedance to normalized admittance corresponds to a 180 degree shift.


# The Smith Chart

## 3 ways to move on the Smith chart


- Constant SWR circle → displacement along TL
- Constant resistance (conductance) circle → addition of reactance (susceptance)
- Constant reactance (susceptance) arc → addition of resistance (conductance)



# The Smith Chart

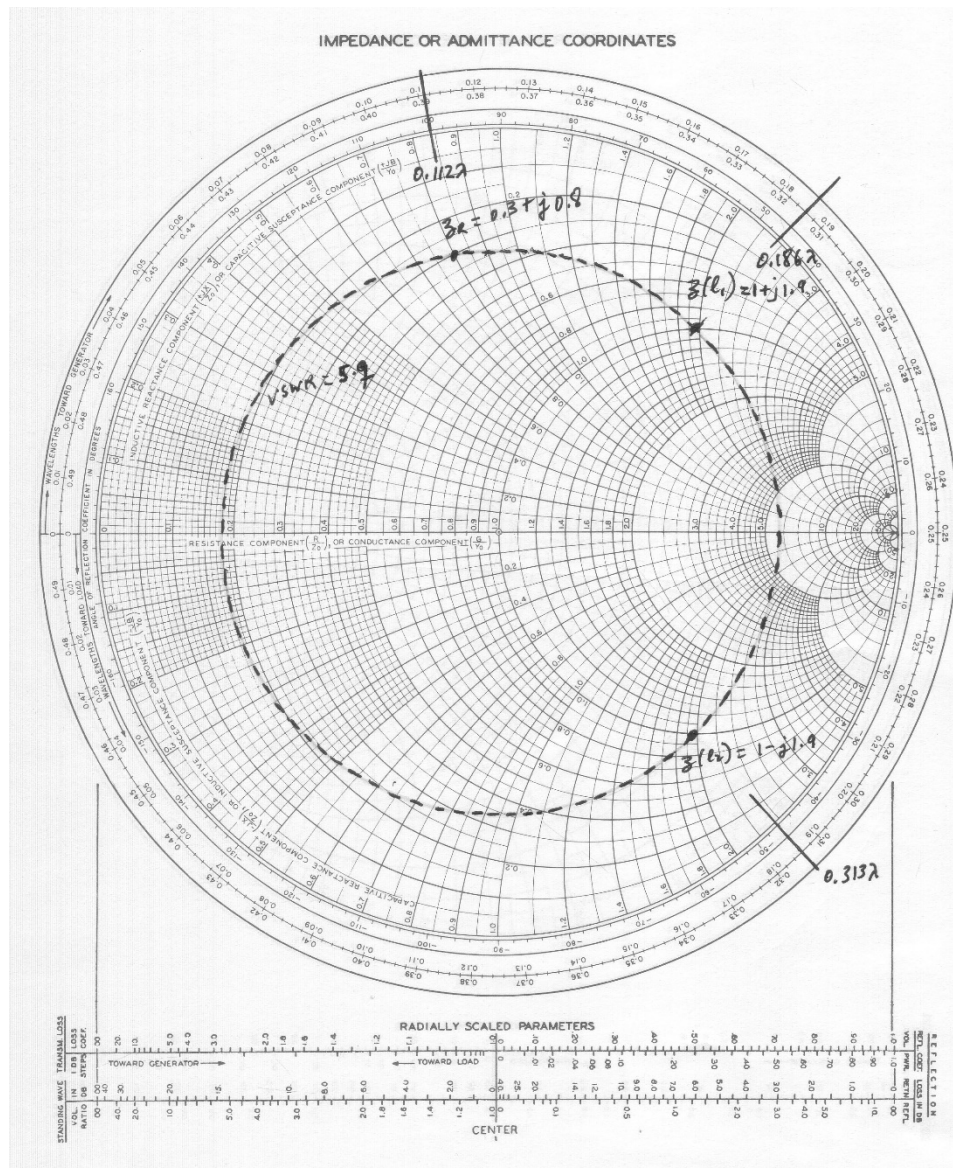

# Smith Chart Example

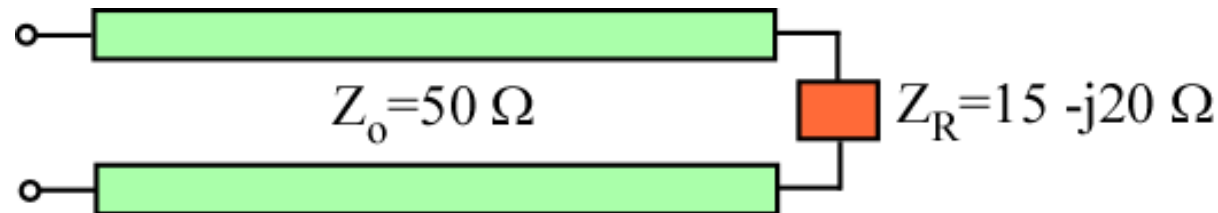

**FIND:**


1. Reflection coefficient at load

$$z_R = 0.3 - j0.4 \Rightarrow \Gamma_R = 0.6e^{j227^\circ}$$


2. SWR on the line  
SWR=4.0

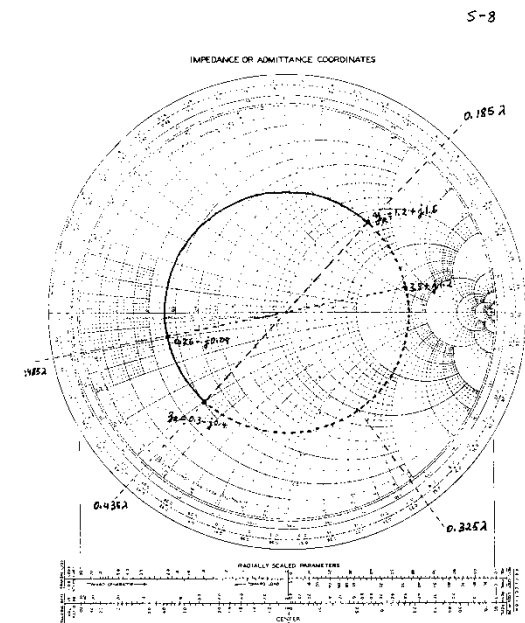3.  $d_{min}$

$$d_{min} = (0.5 - 0.435)\lambda = 0.065\lambda$$




# Smith Chart Example

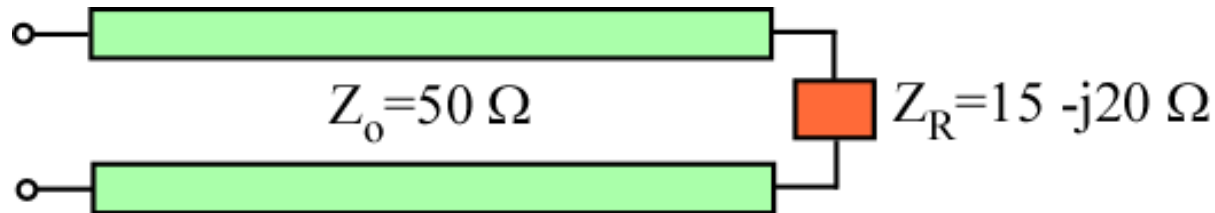

4. Line impedance at  $0.05\lambda$  to the left  
 $50(0.26 - j0.09) = 13 - j4.5\Omega$

5. Line admittance at  $0.05\lambda$   
 $(3.5 + j1.2) / 50 = 0.068 + j0.025 \text{ S}$

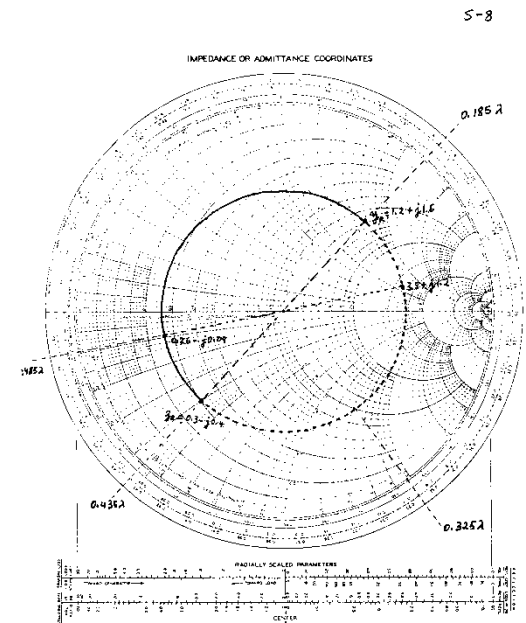6. Location nearest to load where  $\text{Real}[y]=1$   
 $0.14\lambda = 0.325\lambda - j0.185\lambda = 0.14\lambda$



# Smith Chart Example<sub>3</sub>

