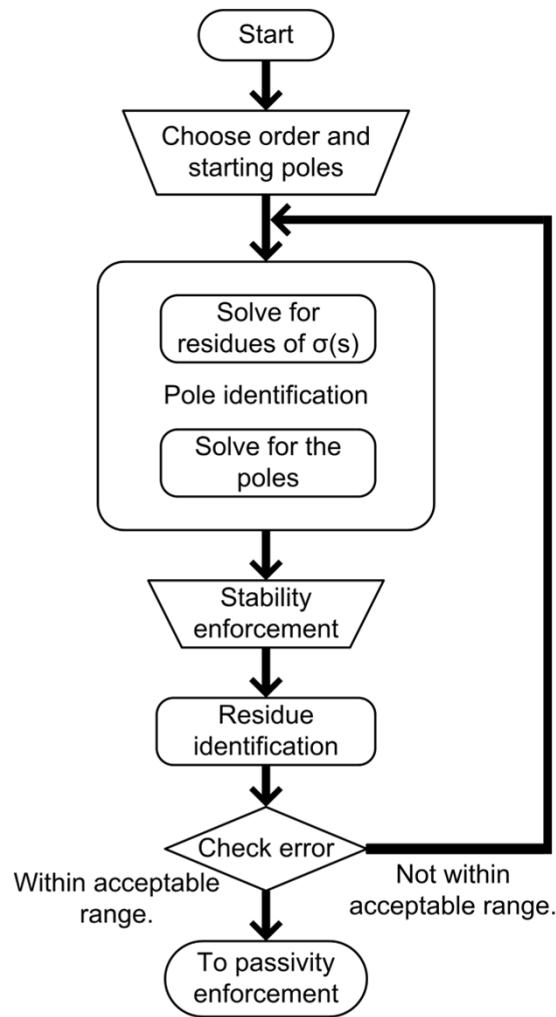


ECE 451

Circuit Synthesis

Jose E. Schutt-Aine
Electrical & Computer Engineering
University of Illinois
jesa@illinois.edu

MOR via Vector Fitting



- Rational function approximation:


$$f(s) \approx \sum_{n=1}^N \frac{c_n}{s - a_n} + d + sh$$

- Introduce an unknown function $\sigma(s)$ that satisfies:


$$\begin{bmatrix} \sigma(s)f(s) \\ \sigma(s) \end{bmatrix} \approx \begin{bmatrix} \sum_{n=1}^N \frac{c_n}{s - \tilde{a}_n} + d + sh \\ \sum_{n=1}^N \frac{\tilde{c}_n}{s - \tilde{a}_n} + 1 \end{bmatrix}$$

- Poles of $f(s)$ = zeros of $\sigma(s)$:
- Flip unstable poles into the left half plane.
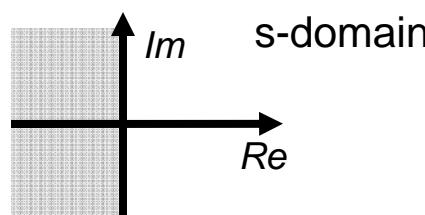
$$f(s) \approx \frac{\sum_{n=1}^N \frac{c_n}{s - \tilde{a}_n} + d + sh}{\sum_{n=1}^N \frac{\tilde{c}_n}{s - \tilde{a}_n} + 1} = \frac{\prod_{n=1}^{N+1} (s - z_n)}{\prod_{n=1}^N (s - \tilde{z}_n)}$$



Passivity Enforcement

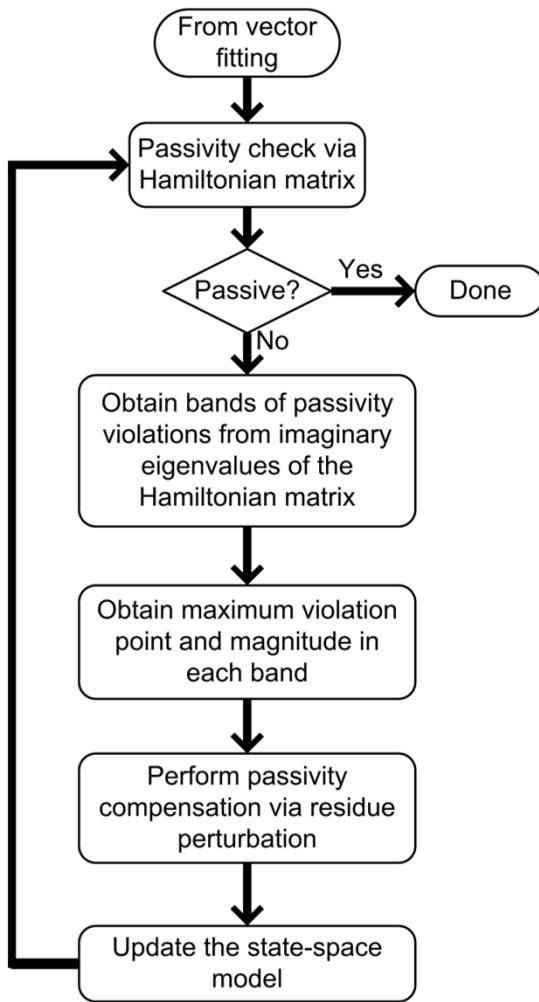

- State-space form:

$$\dot{x} = Ax + Bu$$

$$y = Cx + Du$$


- Hamiltonian matrix:

$$M = \begin{bmatrix} A + BKD^T C & BKB^T \\ -C^T LC & -A^T -C^T DKB^T \end{bmatrix}$$

$$K = (I - D^T D)^{-1} \quad L = (I - DD^T)^{-1}$$

- Passive if M has no imaginary eigenvalues.

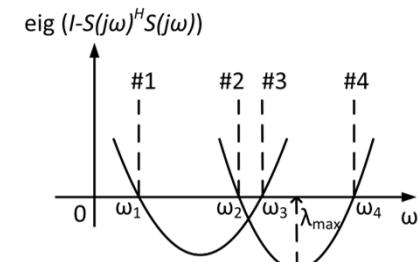- Sweep: $eig(I - S(j\omega)^H S(j\omega))$



- Quadratic programming:

– Minimize (*change in response*) subject to (*passivity compensation*).

$$\min(\text{vec}(\Delta C)^T H \text{vec}(\Delta C)) \quad \text{subject to} \quad \Delta \lambda = G \cdot \text{vec}(\Delta C).$$

Macromodel Circuit Synthesis

Use of Macromodel

- Time-Domain simulation using recursive convolution
- Frequency-domain circuit synthesis for SPICE netlist

Macromodel Circuit Synthesis

Objective: Determine equivalent circuit from macromodel representation*

Motivation

- Circuit can be used in SPICE

Goal

- Generate a netlist of circuit elements

*Giulio Antonini "SPICE Equivalent Circuits of Frequency-Domain Responses", IEEE Transactions on Electromagnetic Compatibility, pp 502-512, Vol. 45, No. 3, August 2003.

Circuit Realization

Circuit realization consists of interfacing the reduced model with a general circuit simulator such as SPICE

Model order reduction gives a transfer function that can be presented in matrix form as

$$S(s) = \begin{bmatrix} s_{11}(s) & \cdot & s_{1N}(s) \\ \cdot & \cdot & \cdot \\ s_{N1}(s) & \cdot & s_{NN}(s) \end{bmatrix}$$

or

$$Y(s) = \begin{bmatrix} y_{11}(s) & \cdot & y_{1N}(s) \\ \cdot & \cdot & \cdot \\ y_{N1}(s) & \cdot & y_{NN}(s) \end{bmatrix}$$

Y-Parameter - Circuit Realization


Each of the Y-parameters can be represented as

$$y_{ij}(s) = d + \sum_{k=1}^L \frac{a_k}{s - p_k}$$

where the a_k 's are the residues and the p_k 's are the poles. d is a constant

Y-Parameter - Circuit Realization

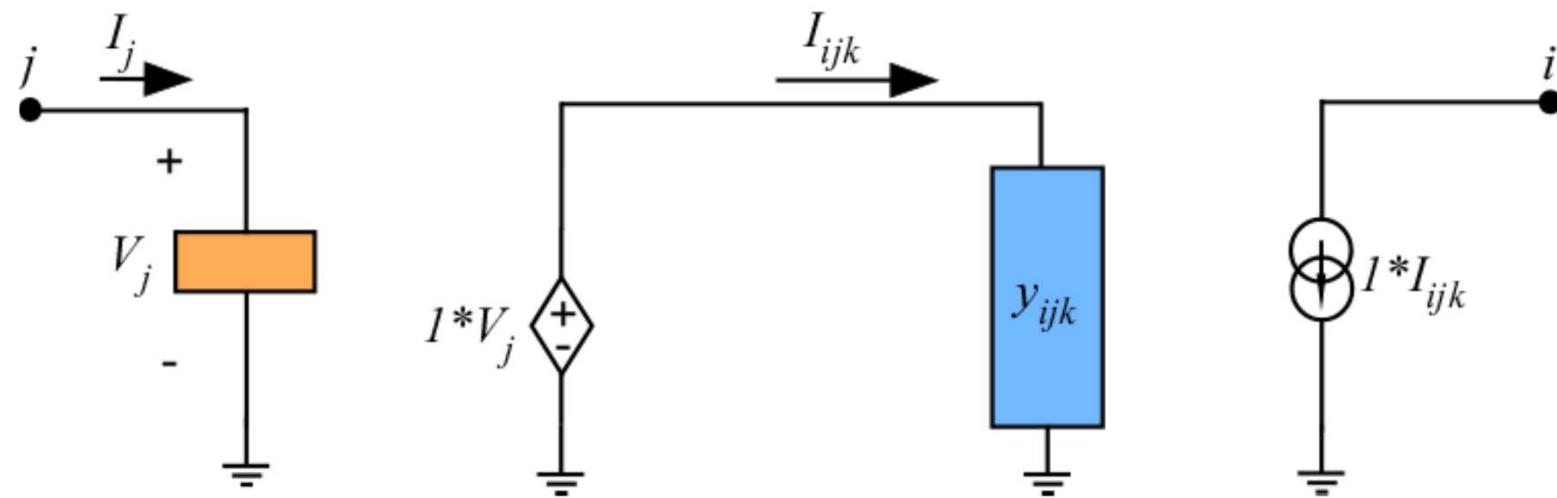The realized circuit will have the following topology:



We need to determine the circuit elements within y_{ijk}

Y-Parameter - Circuit Realization

We try to find the circuit associated with each term:

$$y_{ij}(s) = d + \sum_{k=1}^L \frac{a_k}{s - p_k}$$

1. Constant term d

$$y_{ijd}(s) = d$$

2. Each pole-residue pair

$$y_{ijk}(s) = \frac{a_k}{s - p_k}$$

Y-Parameter - Circuit Realization

In the pole-residue case, we must distinguish two cases


(a) Pole is real $y_{ijk}(s) = \frac{a_k}{s - p_k}$

(b) Complex conjugate pair of poles

$$y_{ijk}(s) = \frac{\alpha_k + j\beta_k}{s - \sigma_k - j\omega_k} + \frac{\alpha_k - j\beta_k}{s - \sigma_k + j\omega_k}$$


In all cases, we must find an equivalent circuit consisting of lumped elements that will exhibit the same behavior

Circuit Realization – Constant Term

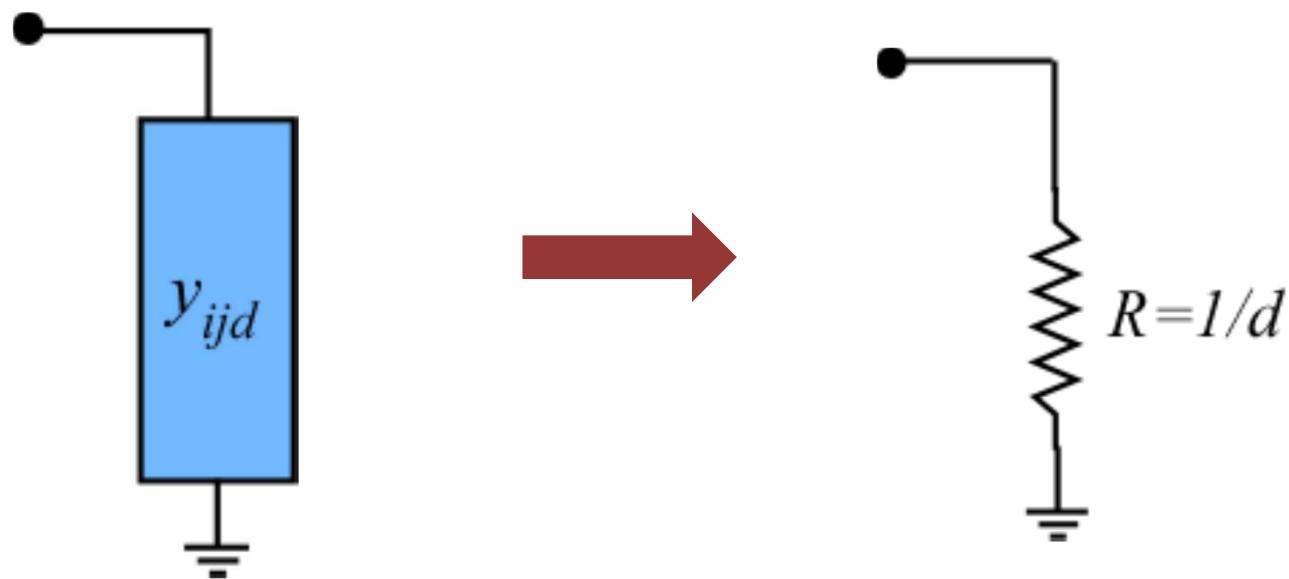

$$R = \frac{1}{d}$$

Circuit Realization - Real Pole

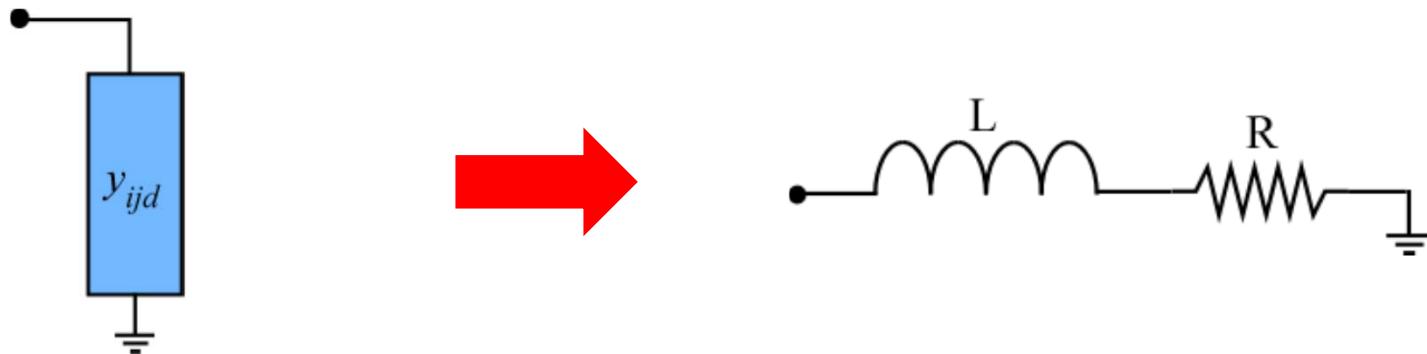


Consider the circuit shown above. The input impedance Z as a function of the complex frequency s can be expressed as:

$$Z = sL + R \quad Y(s) = \frac{1/L}{s + R/L} \quad y_{ijk}(s) = \frac{a_k}{s - p_k}$$

$$L = 1/a_k$$

$$R = -p_k/a_k$$

Circuit Realization - Complex Poles

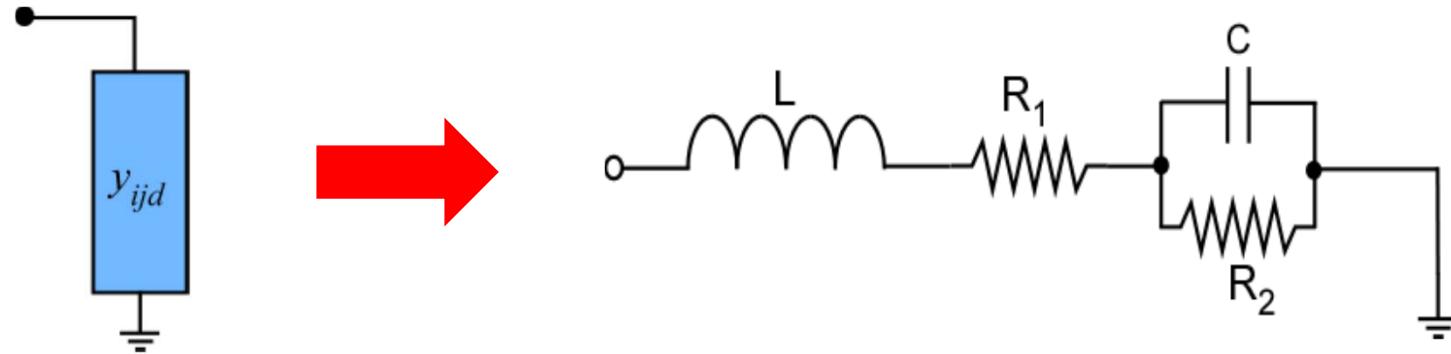


Consider the circuit shown above. The input impedance Z as a function of the complex frequency s can be expressed as:

$$Z = sL + R_1 + \frac{1}{1/R_2 + sC} = sL + R_1 + \frac{R_2}{1 + sCR_2}$$

$$Z = \frac{(R_1 + sL)(1 + sCR_2) + R_2}{1 + sCR_2}$$

Circuit Realization - Complex Poles

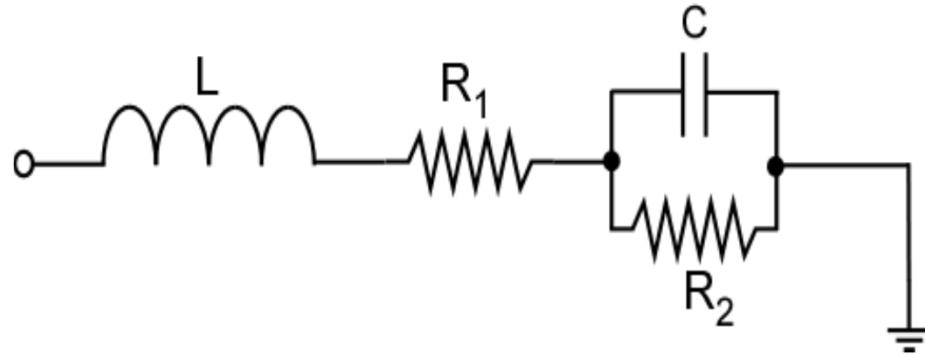

$$Y = \frac{CR_2(s + 1/CR_2)}{LCR_2 \left[s^2 + s \left(\frac{L + CR_1R_2}{LR_2C} \right) + \frac{(R_1 + R_2)}{LR_2C} \right]}$$

$$Y = \frac{1}{L} \frac{(s + 1/CR_2)}{\left[s^2 + s \left(\frac{L + CR_1R_2}{LR_2C} \right) + \frac{(R_1 + R_2)}{LR_2C} \right]}$$

Circuit Realization - Complex Poles

Each term associated with a complex pole pair in the expansion gives:

$$\hat{Y} = \frac{r_1}{s - p_1} + \frac{r_2}{s - p_2}$$

Where r_1 , r_2 , p_1 and p_2 are the complex residues and poles.
They satisfy: $r_1 = r_2^*$ and $p_1 = p_2^*$

It can be re-arranged as:

$$\hat{Y} = (r_1 + r_2) \frac{\left[s - (r_1 p_2 + r_2 p_1) / (r_1 + r_2) \right]}{s^2 - s(p_1 + p_2) + p_1 p_2}$$

Circuit Realization - Complex Poles

We next compare

$$Y = \frac{1}{L} \frac{(s + 1/CR_2)}{s^2 + s \left(\frac{L + CR_1R_2}{LR_2C} \right) + \frac{(R_1 + R_2)}{LR_2C}}$$

and


$$\hat{Y} = (r_1 + r_2) \frac{s - (r_1 p_2 + r_2 p_1) / (r_1 + r_2)}{s^2 - s(p_1 + p_2) + p_1 p_2}$$

DEFINE

$$p = p_1 p_2 \text{ product of poles} \quad a = r_1 + r_2 \text{ sum of residues}$$

$$g = p_1 + p_2 \text{ sum of poles} \quad x = r_1 p_2 + r_2 p_1 \text{ cross product}$$

Circuit Realization - Complex Poles

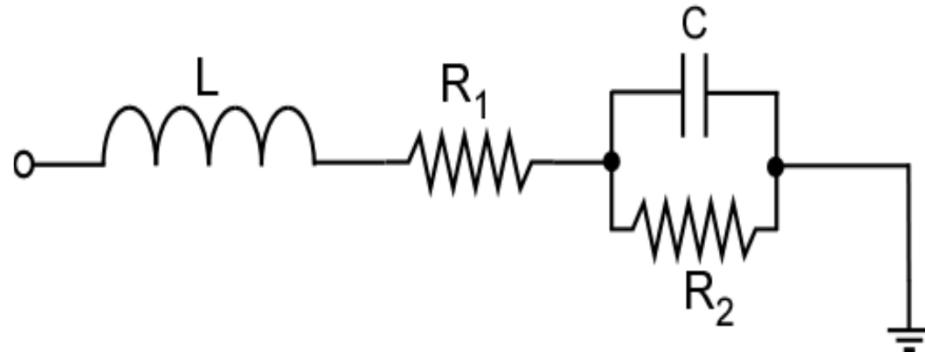

We can identify the circuit elements

$$L = 1/a$$

$$R_1 = \frac{x}{a^2} - \frac{g}{a}$$

$$R_2 = -\frac{p}{x} - \frac{x}{a^2} + \frac{g}{a}$$

$$C = \frac{pa}{x^2} + \frac{1}{a} - \frac{g}{x}$$

Circuit Realization - Complex Poles

In the circuit synthesis process, it is possible that some circuit elements come as negative. To prevent this situation, we add a contribution to the real parts of the residues of the system. In the case of a complex residue, for instance, assume that

$$\hat{Y} = \frac{r_1}{s - p_1} + \frac{r_2}{s - p_2}$$
$$\hat{Y} = \underbrace{\frac{r_1 + \Delta}{s - p_1} + \frac{r_2 + \Delta}{s - p_2}}_{\text{Augmented Circuit}} - \underbrace{\left(\frac{\Delta}{s - p_1} + \frac{\Delta}{s - p_2} \right)}_{\text{Compensation Circuit}}$$

Can show that both augmented and compensation circuits will have positive elements

S-Parameter - Circuit Realization


Each of the S-parameters can be represented as

$$s_{ij}(s) = d + \sum_{k=1}^L \frac{a_k}{s - p_k}$$

where the a_k 's are the residues and the p_k 's are the poles. d is a constant

Realization from S-Parameters

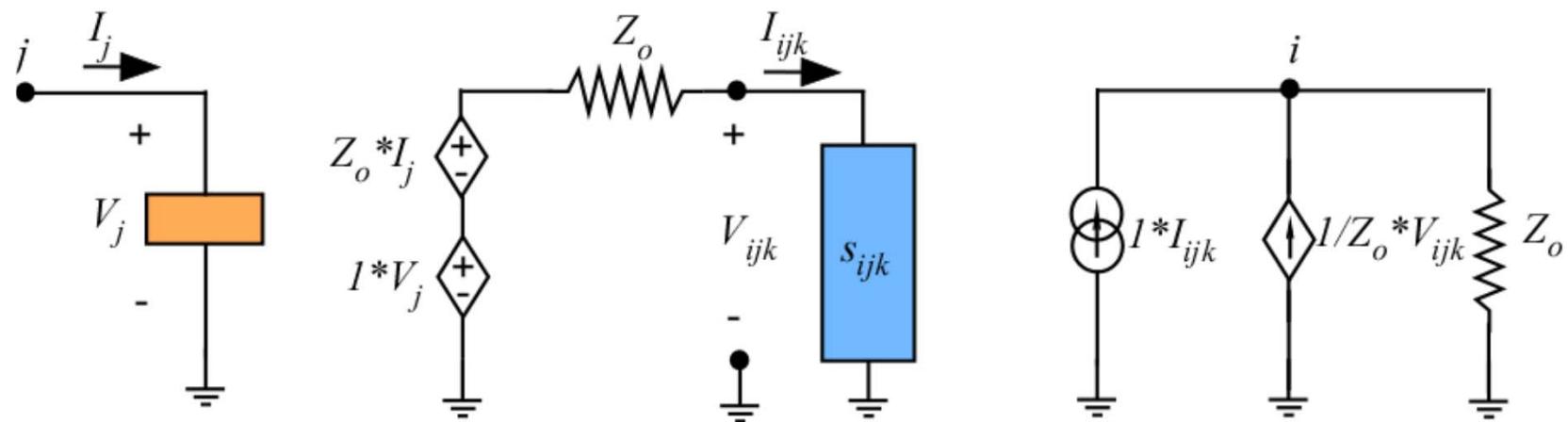The realized circuit will have the following topology:



We need to determine the circuit elements within s_{ijk}

S-Parameter - Circuit Realization

We try to find the circuit associated with each term:

$$s_{ij}(s) = d + \sum_{k=1}^L \frac{a_k}{s - p_k}$$

1. Constant term d

$$s_{ijd}(s) = d$$

2. Each pole and residue pair

$$s_{ijk}(s) = \frac{a_k}{s - p_k}$$

S-Parameter - Circuit Realization

In the pole-residue case, we must distinguish two cases


(a) Pole is real $s_{ijk}(s) = \frac{a_k}{s - p_k}$

(b) Complex conjugate pair of poles

$$s_{ijk}(s) = \frac{\alpha_k + j\beta_k}{s - \sigma_k - j\omega_k} + \frac{\alpha_k - j\beta_k}{s - \sigma_k + j\omega_k}$$


In all cases, we must find an equivalent circuit consisting of lumped elements that will exhibit the same behavior

S- Circuit Realization – Constant Term

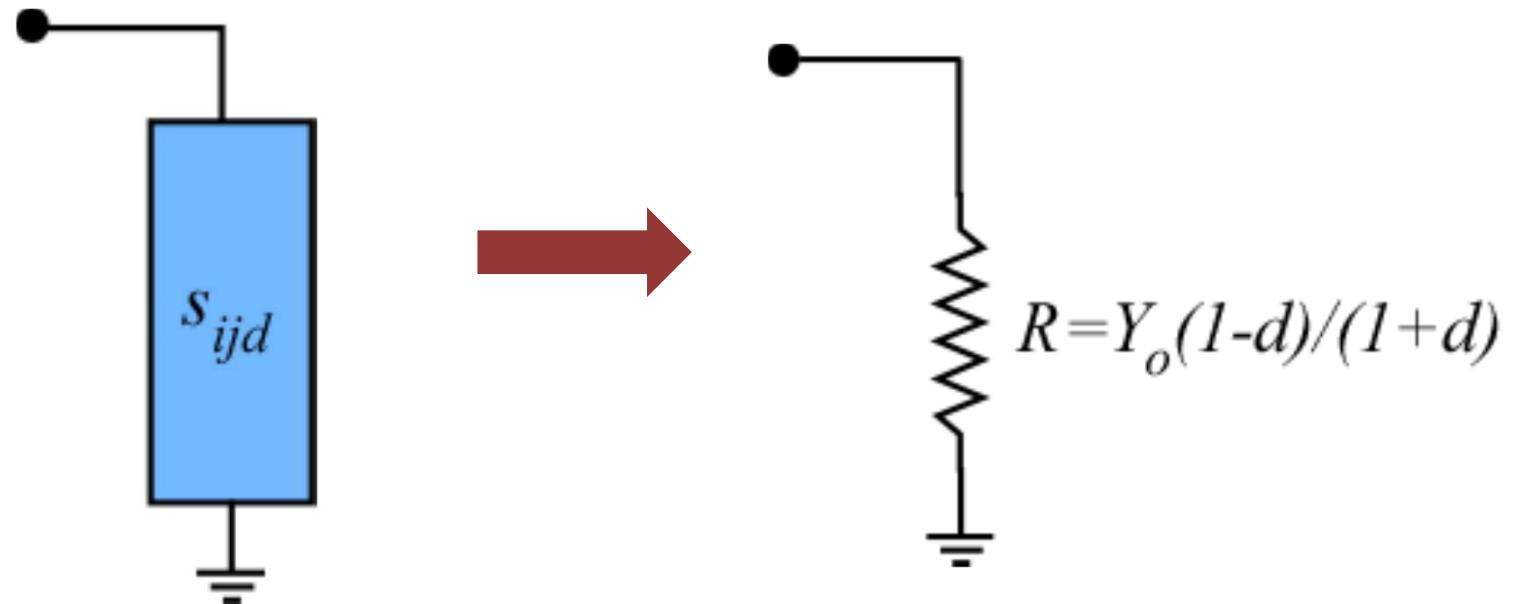


$$R = Y_o \left(\frac{1-d}{1+d} \right)$$

S-Realization – Real Poles

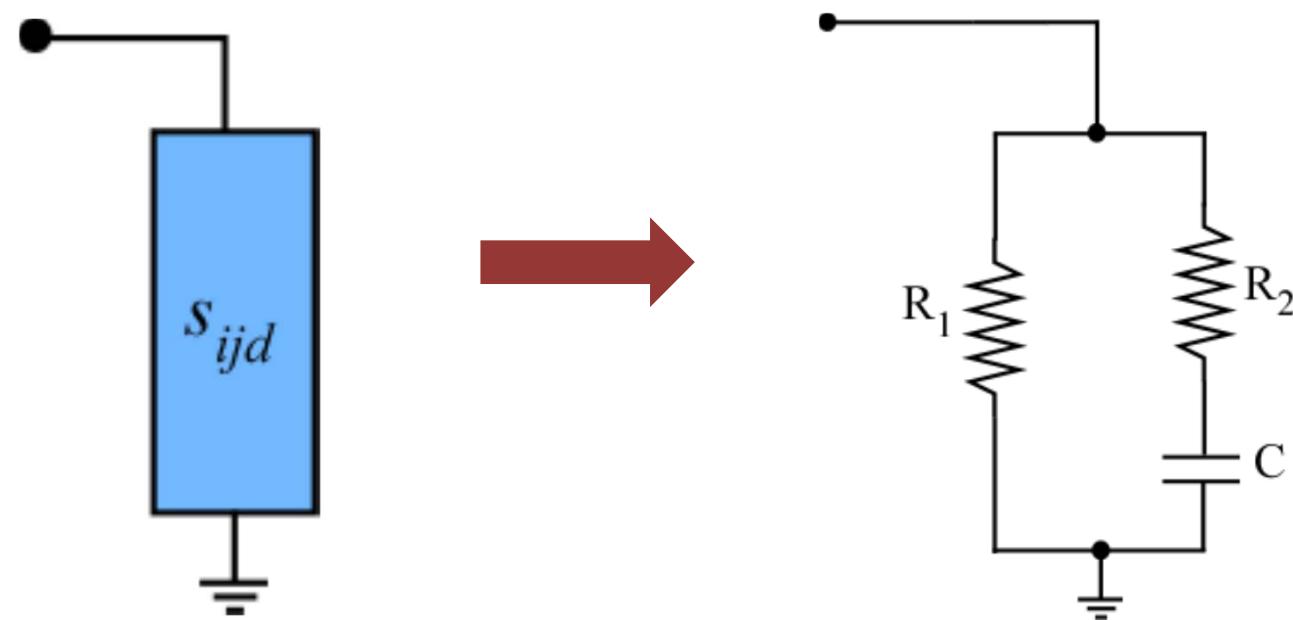

S-Realization – Real Poles

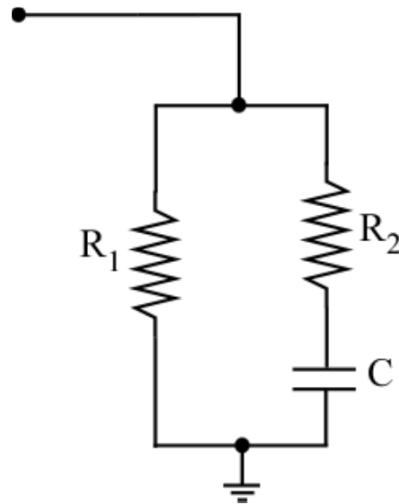

Admittance of proposed model is given by:

$$Y = \frac{(R_1 + R_2)}{R_1 R_2} \left[\frac{s + \frac{1}{(R_1 + R_2)C}}{s + \frac{1}{R_2 C}} \right]$$


S-Realization – Real Poles

From S-parameter expansion we have:

$$s_{ijk}(s) = \frac{r_k}{s - p_k}$$

which corresponds to:
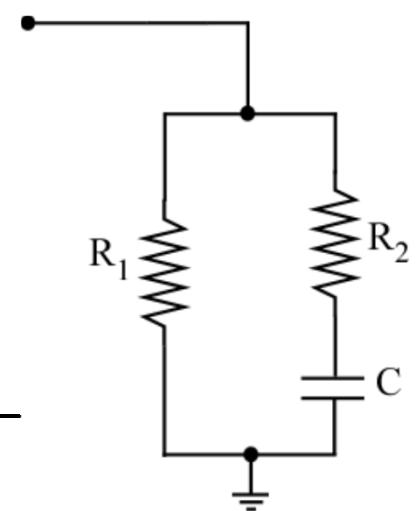
$$\hat{Y} = Y_o \left(\frac{s - a}{s - b} \right) \text{ where } a = p_k + r_k, \text{ and } b = p_k -$$



from which

$$Y_o = \frac{R_1 + R_2}{R_1 R_2}$$


$$C = -\frac{(b - a)}{b^2 Z_o}$$

$$R_2 = \frac{-1}{bC}$$

$$R_1 = -R_2 - \frac{1}{aC}$$

Realization – Complex Poles

Proposed model

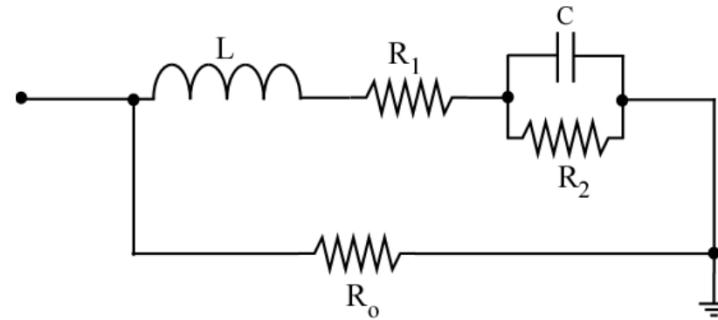

$$Y = Y_a + \frac{1}{R_o} = \frac{1 + sCR_2}{s^2 LCR_2 + s(L + R_1 R_2 C) + (R_1 + R_2)} + \frac{1}{R_o}$$

which can be re-arranged as:

$$Y = \frac{1}{R_o} \left[\frac{s^2 + s \left(\frac{L + R_1 R_2 C + R_o R_2 C}{LCR_2} \right) + \frac{R_o + R_1 + R_2}{LCR_2}}{s^2 + s \left(\frac{L + R_1 R_2 C}{LCR_2} \right)_o + \frac{R_1 + R_2}{LCR_2}} \right]$$

Realization – Complex Poles

From the S-parameter expansion, the complex pole pair gives:

$$\hat{S} = \frac{r_1}{s - p_1} - \frac{r_2}{s - p_2} = \frac{s(r_1 + r_2) - (r_1 p_2 + r_2 p_1)}{s^2 - s(p_1 + p_2) + p_1 p_2}$$

which corresponds to an admittance of:

$$\hat{Y} = Y_o \left(\frac{1 - \hat{S}}{1 + \hat{S}} \right) = \left(\frac{1 - \frac{sa - x}{s^2 - sg + p}}{1 + \frac{sa - x}{s^2 - sg + p}} \right) Y_o$$

Realization – Complex Poles

The admittance expression can be re-arranged as

$$\hat{Y} = \left(\frac{s^2 - sg + p - sa + x}{s^2 - sg + p + sa - x} \right) Y_o = \left(\frac{s^2 - s(g + a) + p + x}{s^2 - s(g - a) + p - x} \right) Y_o$$

WE HAD DEFINED

$$p = p_1 p_2 \text{ product of poles} \quad a = r_1 + r_2 \text{ sum of residues}$$

$$g = p_1 + p_2 \text{ sum of poles} \quad x = r_1 p_2 + r_2 p_1 \text{ cross product}$$

Realization – Complex Poles

Matching the terms with like coefficients gives

$$R_o = \frac{1}{Y_o}$$


$$p + x = \frac{R_o + R_1 + R_2}{LCR_2}$$

$$p - x = \frac{R_1 + R_2}{LCR_2}$$

$$2p = \frac{R_o + 2R_1 + 2R_2}{LCR_2}$$

$$2x = \frac{R_o}{LCR_2}$$

Realization from S-Parameters

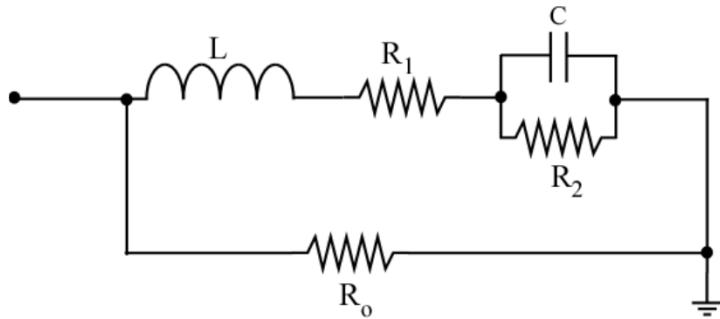

Solving gives

$$L = -\frac{R_o}{2a}$$

$$R_2 = \frac{R_o \left(\frac{p}{x} - 1 \right)}{2} - R_1$$


$$R_1 = \frac{1}{2} \left(\frac{gR_o}{a} + \frac{2Lx}{a} - R_o \right)$$

$$C = \frac{-a}{R_2 x}$$


Typical SPICE Netlist

```
* 32 -pole approximation
*This subcircuit has 16 pairs of complex poles and 0 real poles
.subckt sample 8000 9000
vsens8001 8000 8001 0.0
vsens9001 9000 9001 0.0
*subcircuit for s[1][1]
*complex residue-pole pairs for k= 1 residue: -6.4662e-002 8.1147e-002 pole: -4.4593e-001 -2.4048e+001
elc1 1 0 8001 0 1.0
hc2 2 1 vsens8001 50.0
rtersc3 2 3 50.0
vp4 3 4 0.0
l1cd5 4 5 1.933e-007
rocd5 4 0 5.000e+001
r1cd6 5 6 5.895e+003
c1cd6 6 0 3.474e-015
r2cd6 6 0 -9.682e+003
:
*constant term 2 2 -6.192e-003
edee397 397 0 9001 0 1.0e+000
hdee398 398 397 vsens9001 50.0
rterdee399 398 399 50.0
vp400 399 400 0.0
rdee400 400 0 49.4
*current sources
fs4 0 8001 vp4 -1.0
gs4 0 8001 4 0 0.020
fs10 0 8001 vp10 -1.0
gs10 0 8001 10 0 0.020
fs16 0 8001 vp16 -1.0
gs16 0 8001 16 0 0.020
fs22 0 8001 vp22 -1.0
gs22 0 8001 22 0 0.020
fs28 0 8001 vp28 -1.0
gs28 0 8001 28 0 0.020
```

Realization from Y-Parameters

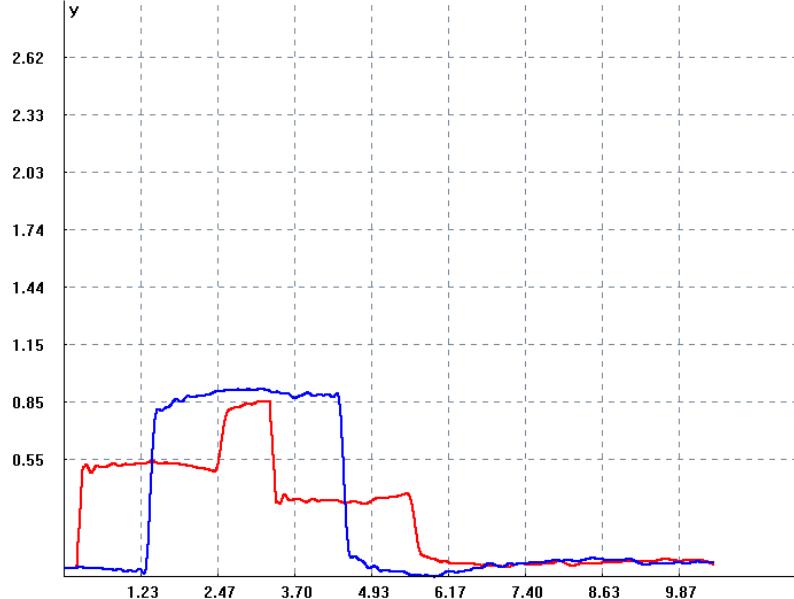

Recursive convolution

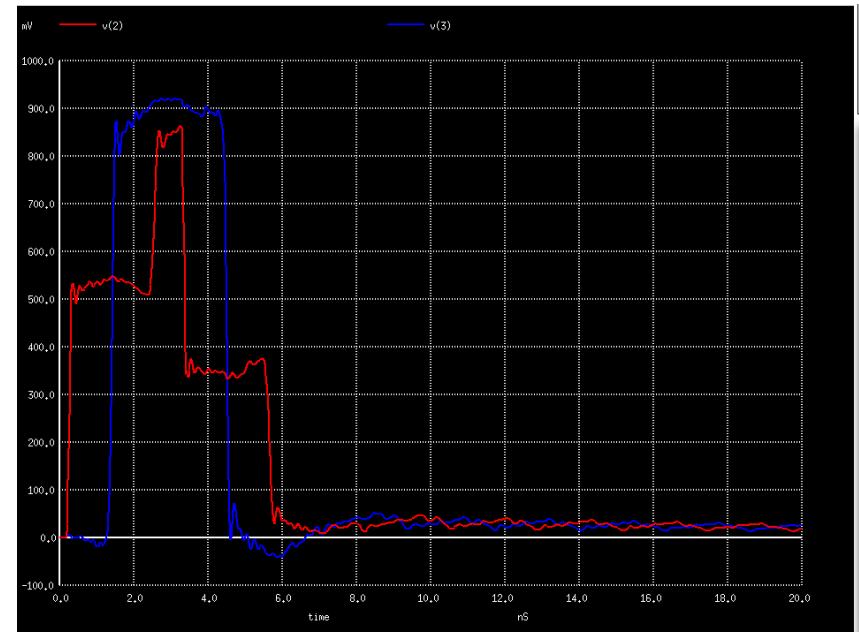


SPICE realization

Realization from S-Parameters



Recursive convolution

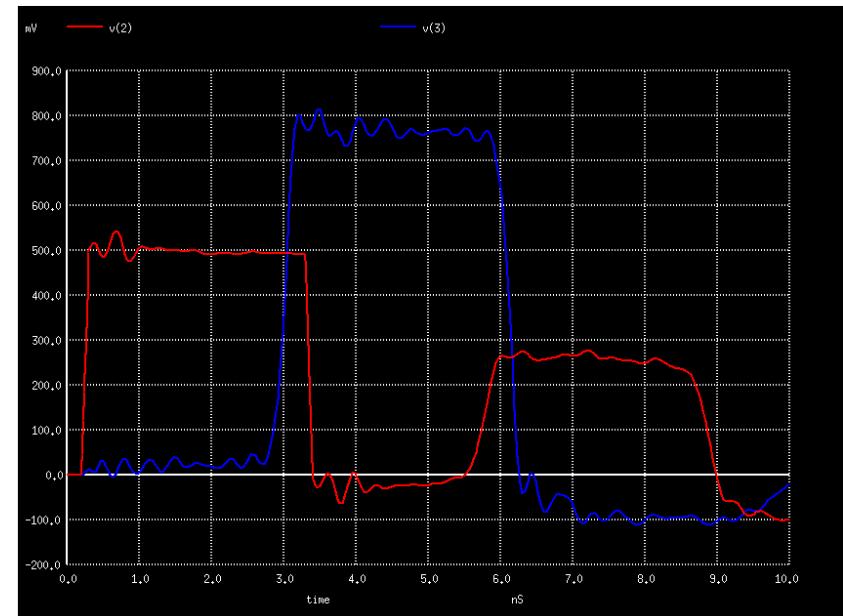

SPICE realization