

ECE 453

Wireless Communication Systems

Mixers


Jose E. Schutt-Aine
Electrical & Computer Engineering
University of Illinois
jesa@illinois.edu

Mixers

Frequency translation modules used in receivers to produce baseband signals

- Frequency can be higher (up-conversion) or lower (down-conversion)
- Make use of nonlinearities in devices
- Can be based on passive or active devices
- Used in receivers, transmitters and instrumentation
- Superheterodyne receivers combines RF and LO signals to produce IF


Nonlinear Behavior

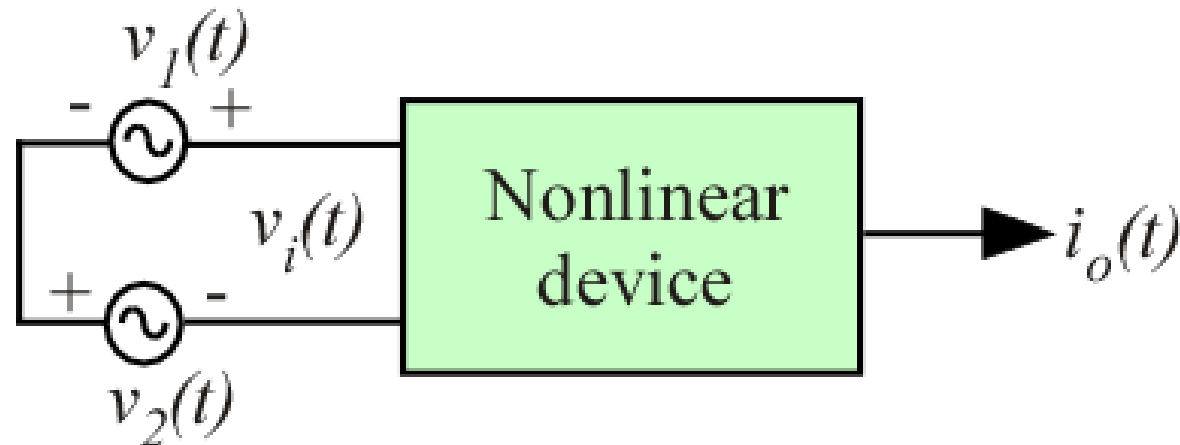

$$i_o(t) = I_0 + av_i(t) + b[v_i(t)]^2 + c[v_i(t)]^3 + \dots$$

- If input has one frequency, harmonics will be generated
- If several input frequencies are used, sum and difference frequencies are generated

Nonlinear Behavior

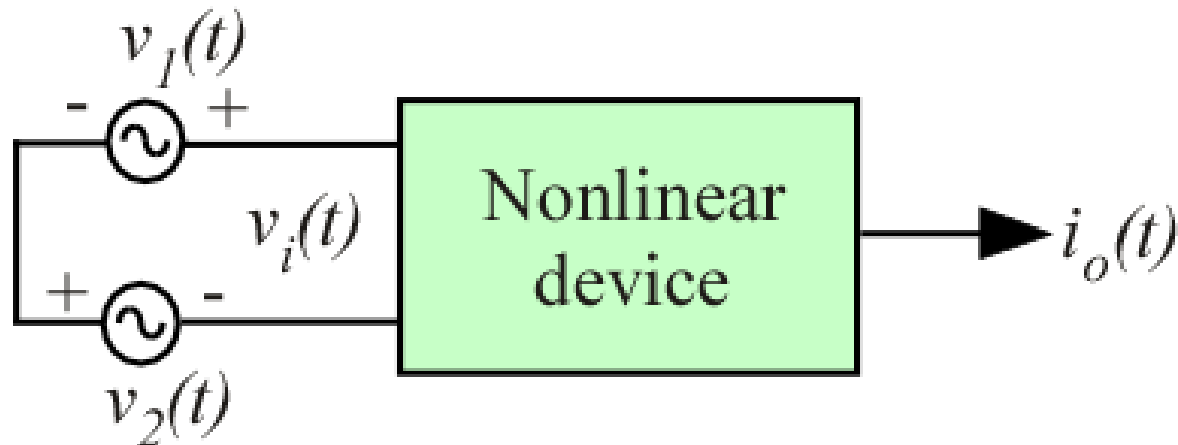

Square-law behavior is ideal for mixer since the least number of undesired frequencies are produced

$$i_o(t) = av_i(t) + b[v_i(t)]^2$$

Mixer Principles

$$v_i(t) = V_1 \cos \omega_1 t + V_2 \cos \omega_2 t$$

$$i_o(t) = aV_1 \cos \omega_1 t + aV_2 \cos \omega_2 t + bV_1^2 \cos^2 \omega_1 t \\ + bV_2^2 \cos^2 \omega_2 t + 2bV_1V_2 \cos \omega_1 t \cos \omega_2 t$$

- The final term (or *product term*) yields the desired output

$$2bV_1V_2 \cos \omega_1 t \cos \omega_2 t =$$

$$bV_1V_2 \left[\cos(\omega_1 - \omega_2)t + \cos(\omega_1 + \omega_2)t \right]$$

Mixer Principles

If filter is used to remove unwanted terms:


$\omega_1 \rightarrow \omega_{LO}$: local oscillator frequency

$\omega_2 \rightarrow \omega_{RF}$: RF frequency

$$i_o(t) = bV_1V_2 \left[\underbrace{\cos(\omega_{LO} - \omega_{RF})t}_{\omega_{IFL}} + \underbrace{\cos(\omega_{LO} + \omega_{RF})t}_{\omega_{IFH}} \right]$$

Filter can be used to choose IF frequency



Single-Ended Mixer

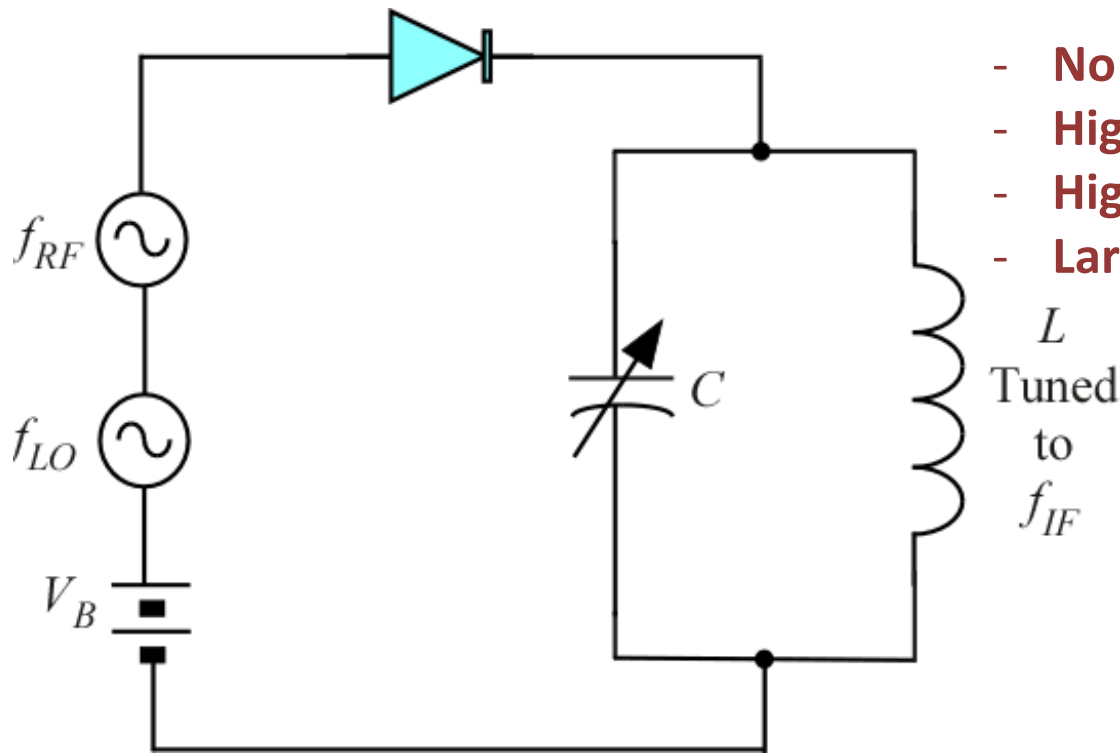

Limitations


- No isolation between LO and RF
- High-order nonlinearities
- High noise figure
- Large output LO current

Single-Ended Mixer

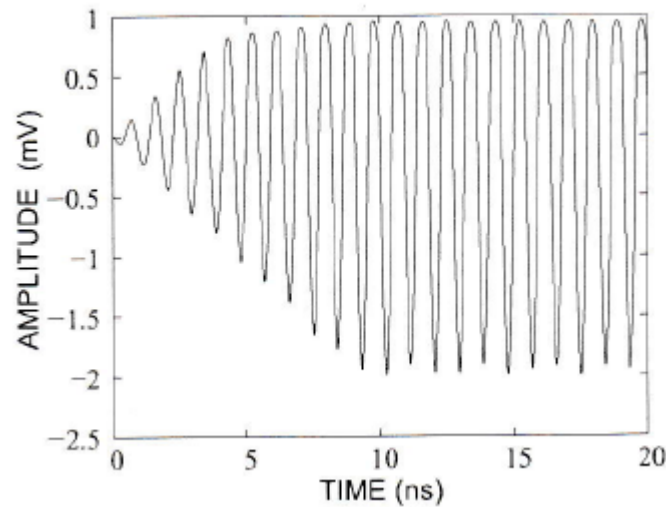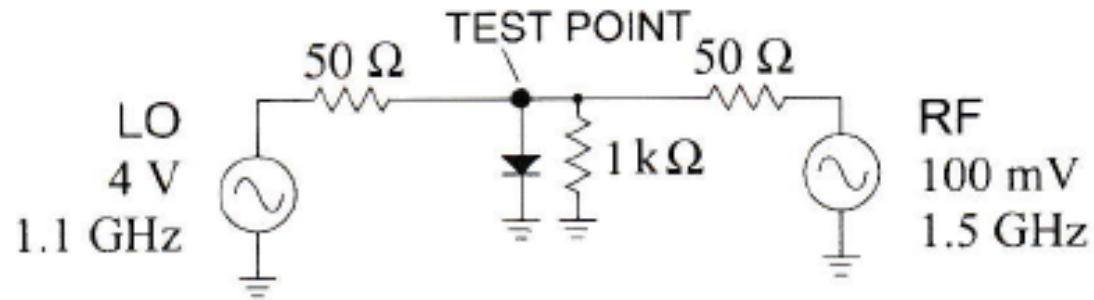


Waveform at
test point

Single-Ended Mixer

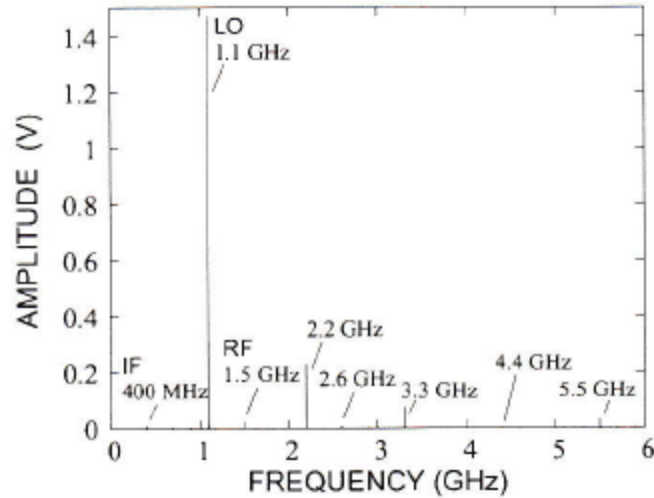


Spectrum at
test point

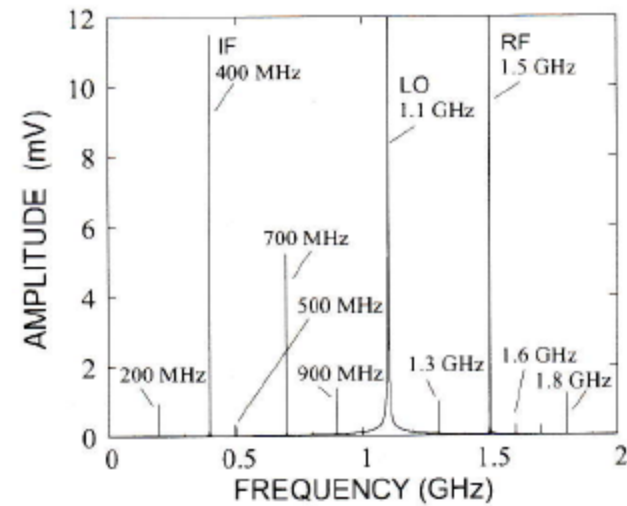

Expanded spectrum
at test point

Desired signal is IF at 400 MHz

Switching Principle

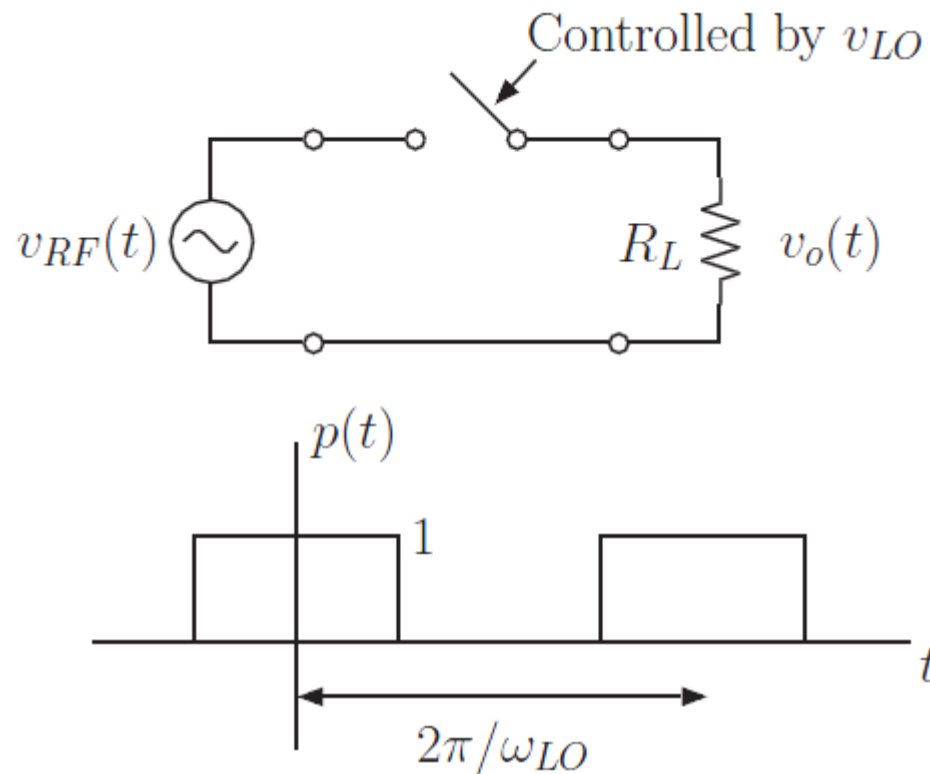

Simple switch exhibits strong nonlinearities

Switching Principle

$$S(t) = \frac{1}{2} + \sum_{n=1}^{\infty} \frac{\sin n\pi / 2}{n\pi / 2} \cos n\omega_{LO}t$$


$$v_{RF}(t) = V_{RF} \cos \omega_{RF}t$$

$$v_o(t) = v_{RF}(t) \times S(t) = V_{RF} \cos \omega_{RF}t \left(\frac{1}{2} + \sum_{n=1}^{\infty} \frac{\sin n\pi / 2}{n\pi / 2} \cos n\omega_{LO}t \right)$$

- Even harmonics of f_{LO} disappear since $\sin(n\pi/2)/n\pi/2 = 0$ when n is even
- No frequency terms in f_{LO} and its odd harmonics
- Only terms due to $\cos\omega_{RF}t \times \cos n\omega_{LO}t$ with n odd


Filter can be used to select $|f_{RF} \pm f_{LO}|$

Single-Balanced Diode Mixer


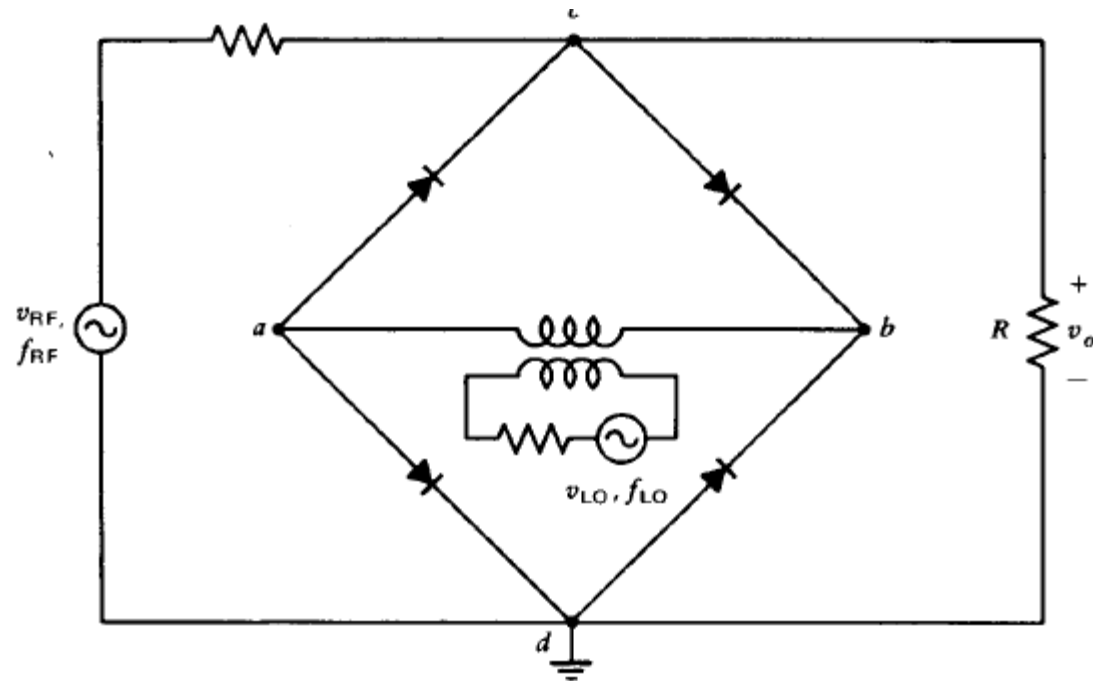


- $v_{LO} \gg v_{RF}$ so LO signal controls diode states
- Diodes act like switches


Single-Balanced Diode Mixer Operation

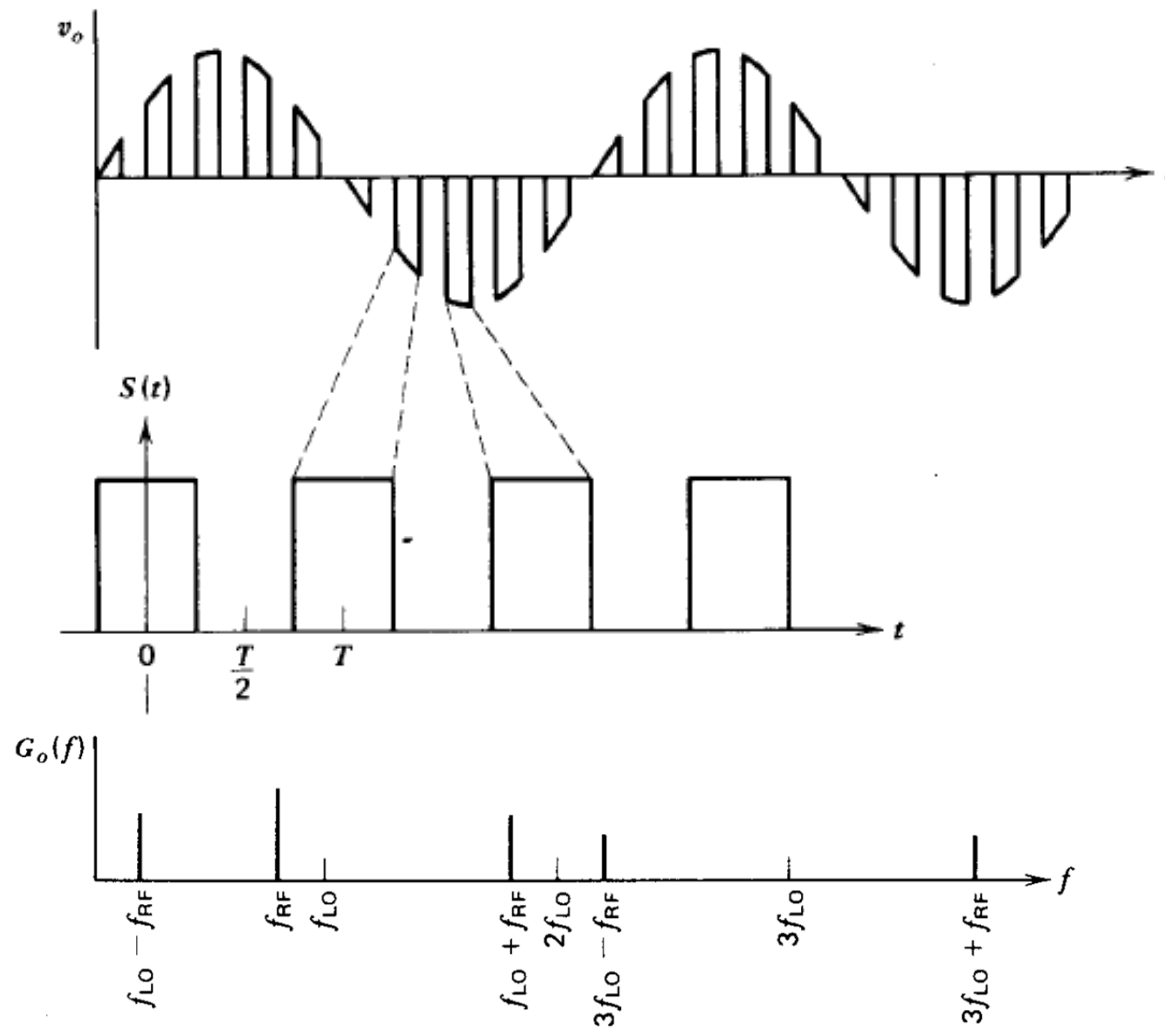


Double-Balanced Diode Mixer

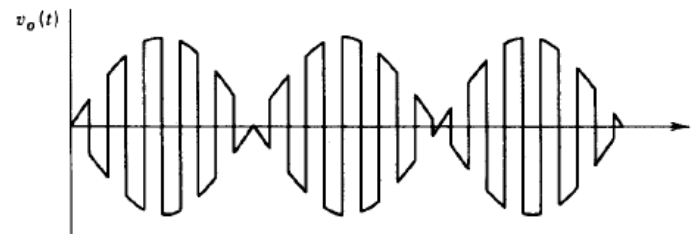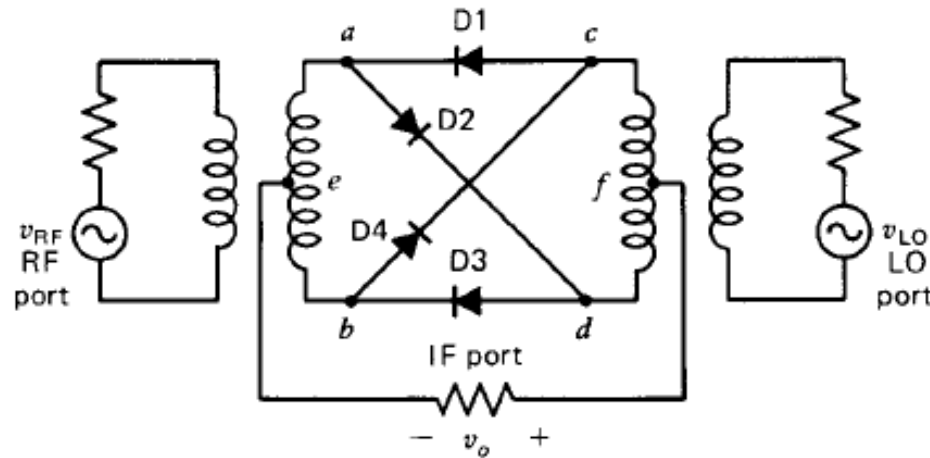

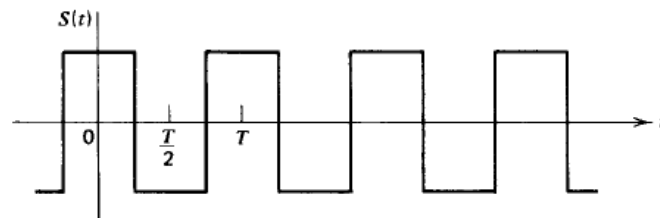Currents due to v_{RF} are small compared to those due to v_{LO} .



Balanced BJT Mixer

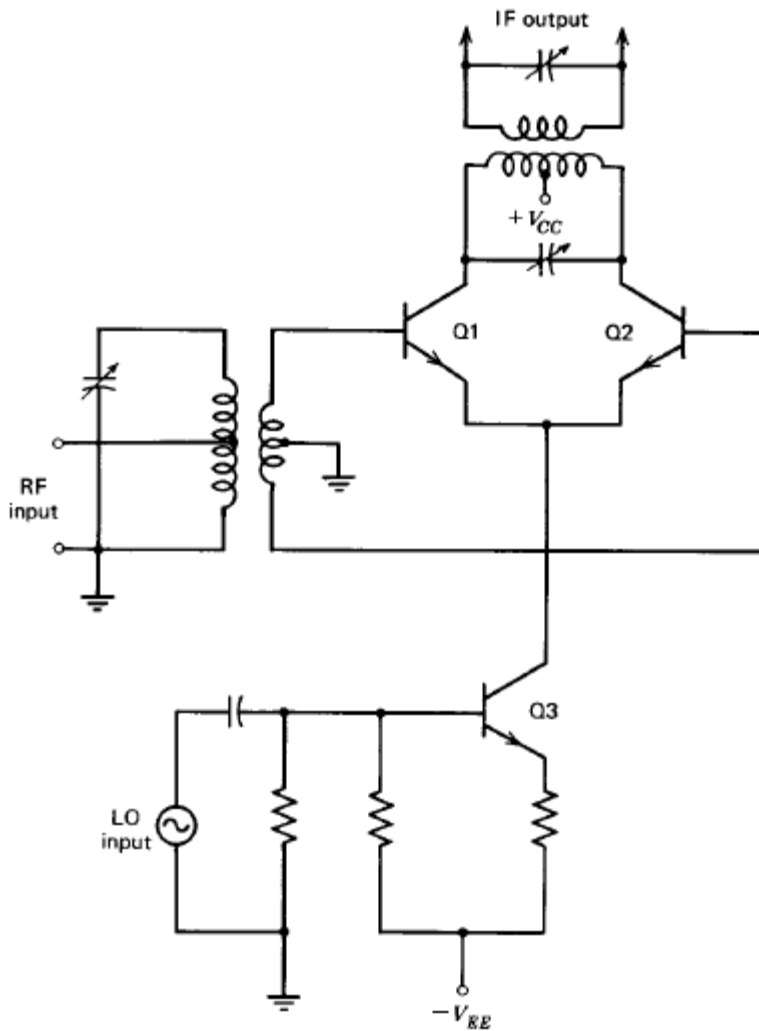


If transistors are matched, LO signal does not reach RF or IF ports.

Mixer Performance

- Conversion Gain (Loss) – ratio of IF power to RF power
- Noise Figure - ratio of SNR_{in} to SNR_{out}
- Isolation - amount of leakage or feedthrough between mixer ports
- Conversion Compression - deviation of IF output power from linearity
- Dynamic Range – amplitude range over which mixer can operate
- Two-Tone, Third-Order Intermodulation Distortion – distortion caused by second received RF signal
- Intercept Point – measures third-order suppression
- Desensitization – compression of signal at adjacent frequency
- Harmonic Intermodulation Distortion – mixing of harmonics
- Cross-Modulation Distortion – transfer from modulated to unmodulated carrier

Mixer Performance Terminology

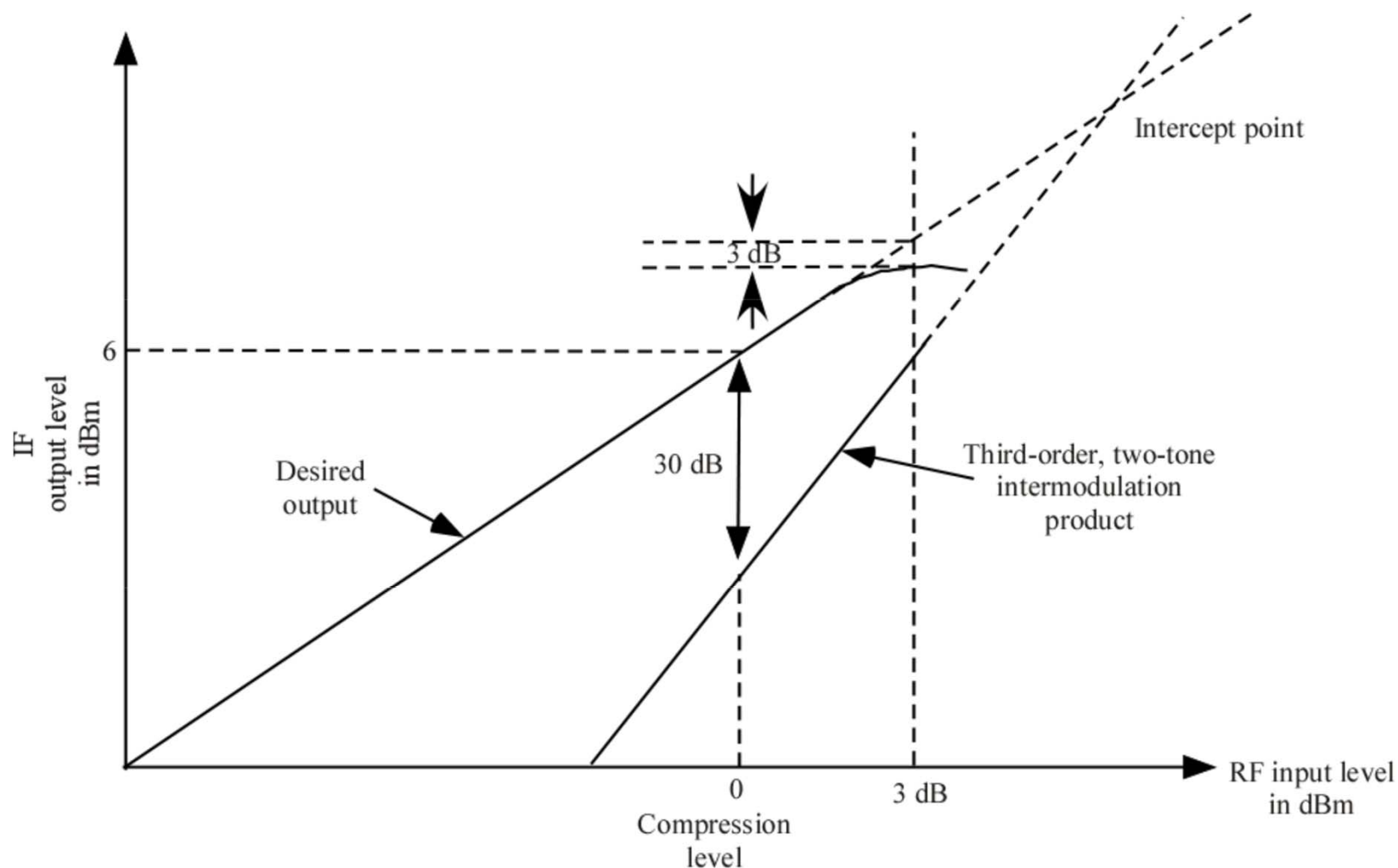

Mixer Topologies

Mixer type	Advantages	Disadvantages
Active (vs. passive)	<ul style="list-style-type: none"> • Conversion gain • Better linearity • Lower LO power • Simpler to implement 	<ul style="list-style-type: none"> • Typically higher noise figure • Less-predictable performance • Limited to lower frequencies
Unbalanced (active)	<ul style="list-style-type: none"> • Lowest noise figure • All ports single-ended 	<ul style="list-style-type: none"> • Poor port-to-port isolation • Poor linearity • Difficult to implement
Single-balanced (active)	<ul style="list-style-type: none"> • LO-to-RF isolation • RF-to-IF isolation • Best linearity • Good noise figure 	<ul style="list-style-type: none"> • Differential IF output • LO-to-IF feed-through
Double-balanced (active)	<ul style="list-style-type: none"> • LO-to-RF, LO-to-IF and RF-to-IF isolation • Good spurious product rejection • Good linearity • Simple to implement 	<ul style="list-style-type: none"> • High noise figure • High power consumption