


ECE 453

Wireless Communication Systems

Network Parameters


Jose E. Schutt-Aine
Electrical & Computer Engineering
University of Illinois
jesa@illinois.edu

Transfer Function Representation

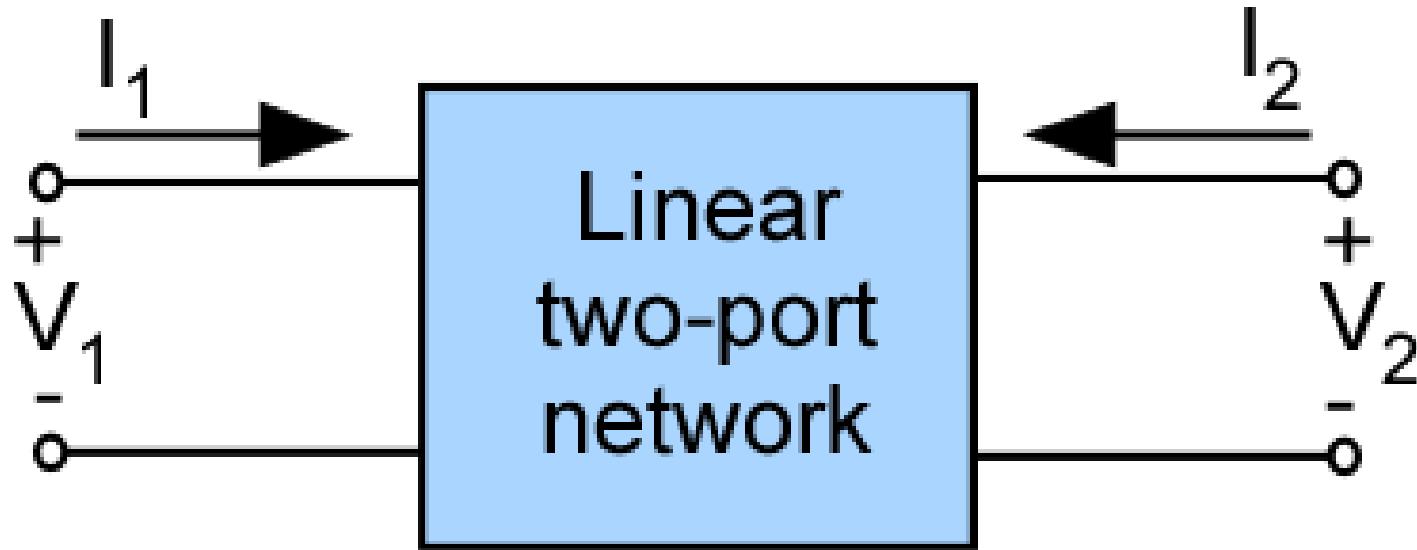

Use a two-terminal representation of system for input and output


Y-parameter Representation

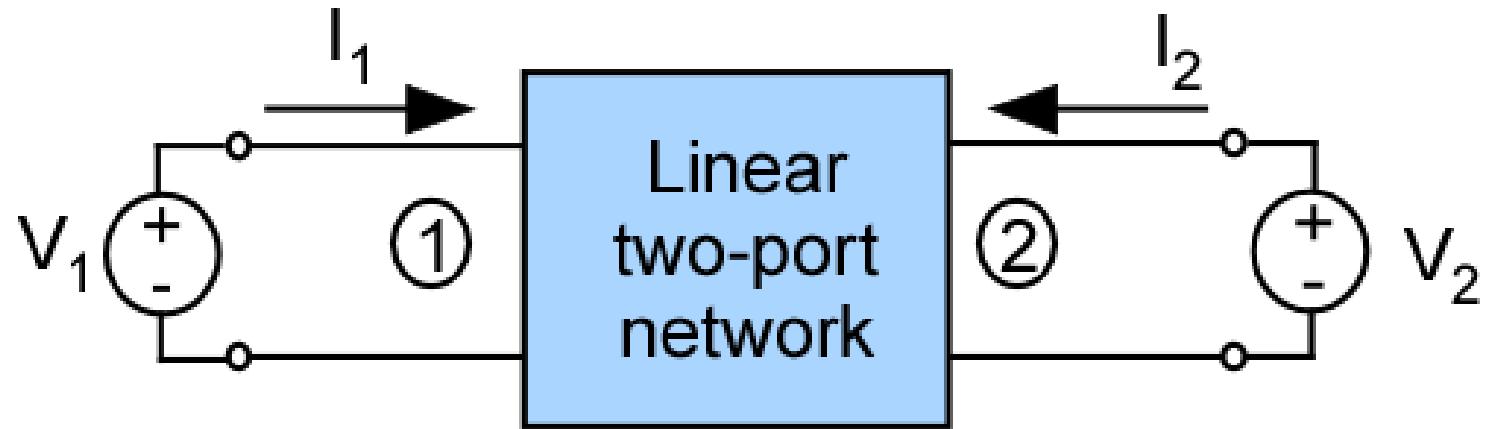

$$I_1 = y_{11}V_1 + y_{12}V_2$$

$$I_2 = y_{21}V_1 + y_{22}V_2$$


Y Parameter Calculations

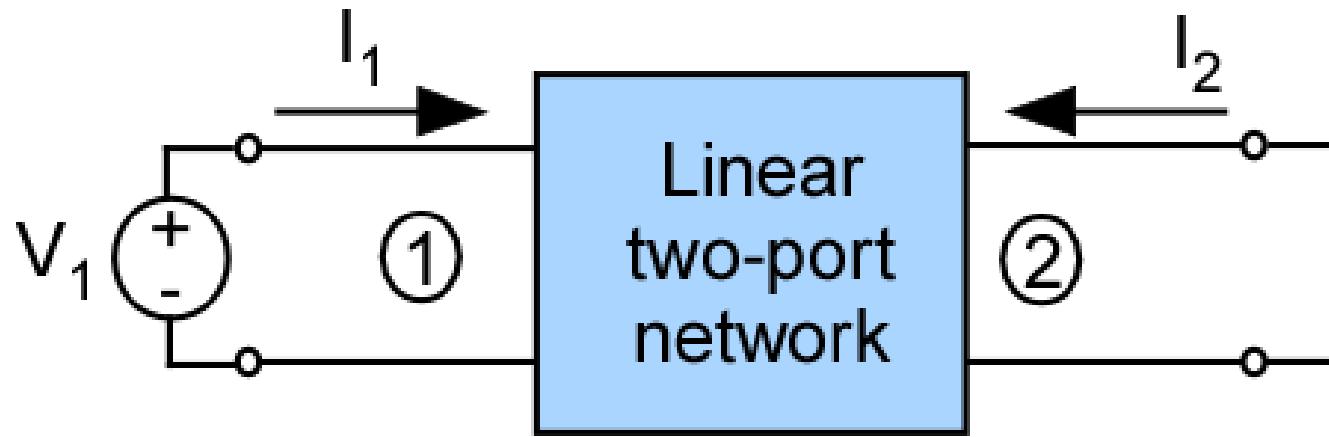

$$y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0}$$
$$y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0}$$

To make $V_2=0$, place a short at port 2


Z Parameters

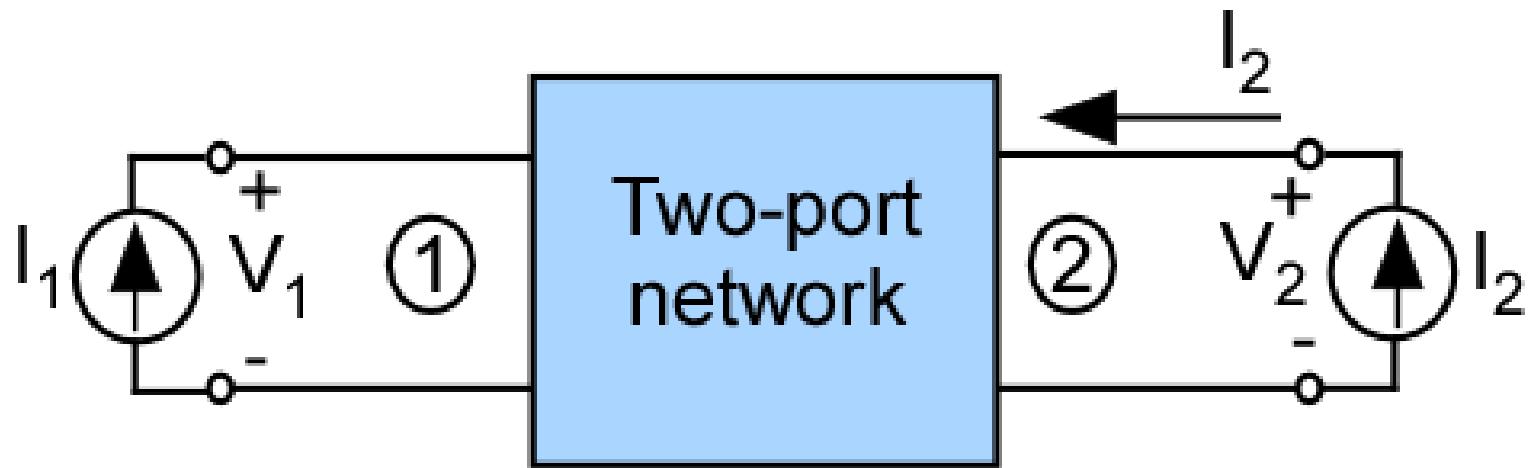

$$V_1 = z_{11}I_1 + z_{12}I_2$$

$$V_2 = z_{21}I_1 + z_{22}I_2$$

Z-parameter Calculations

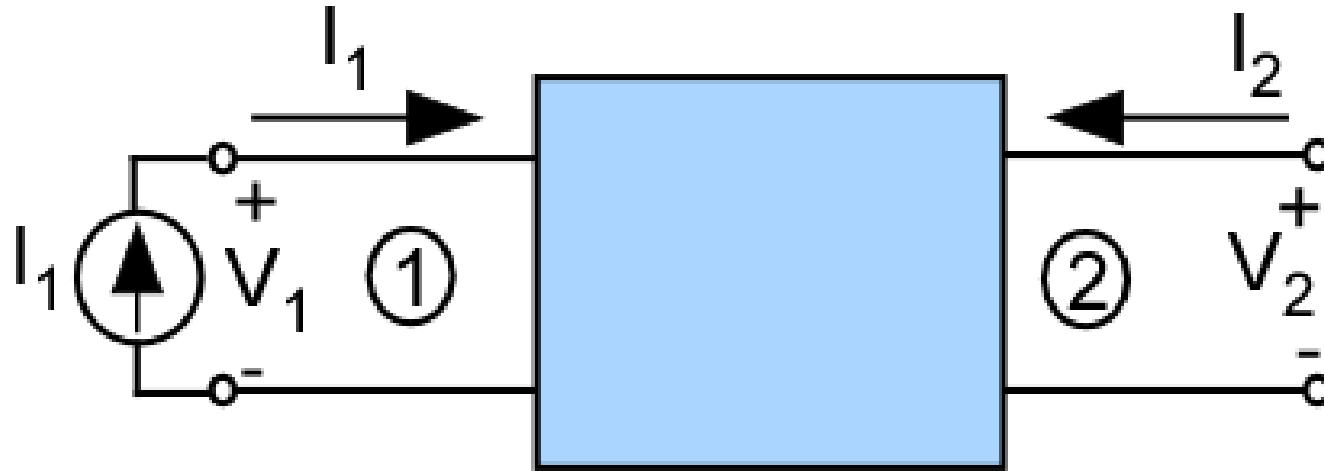


$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0}$$

$$z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$

To make $I_2=0$, place an open at port 2


H Parameters

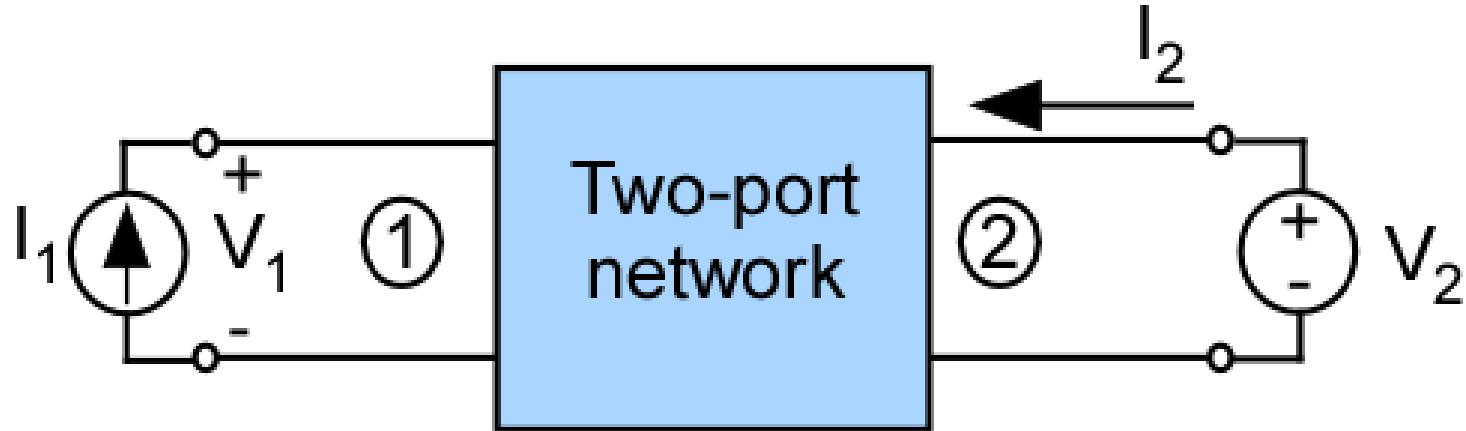

$$V_1 = h_{11}I_1 + h_{12}V_2$$

$$I_2 = h_{21}I_1 + h_{22}V_2$$

H Parameter Calculations

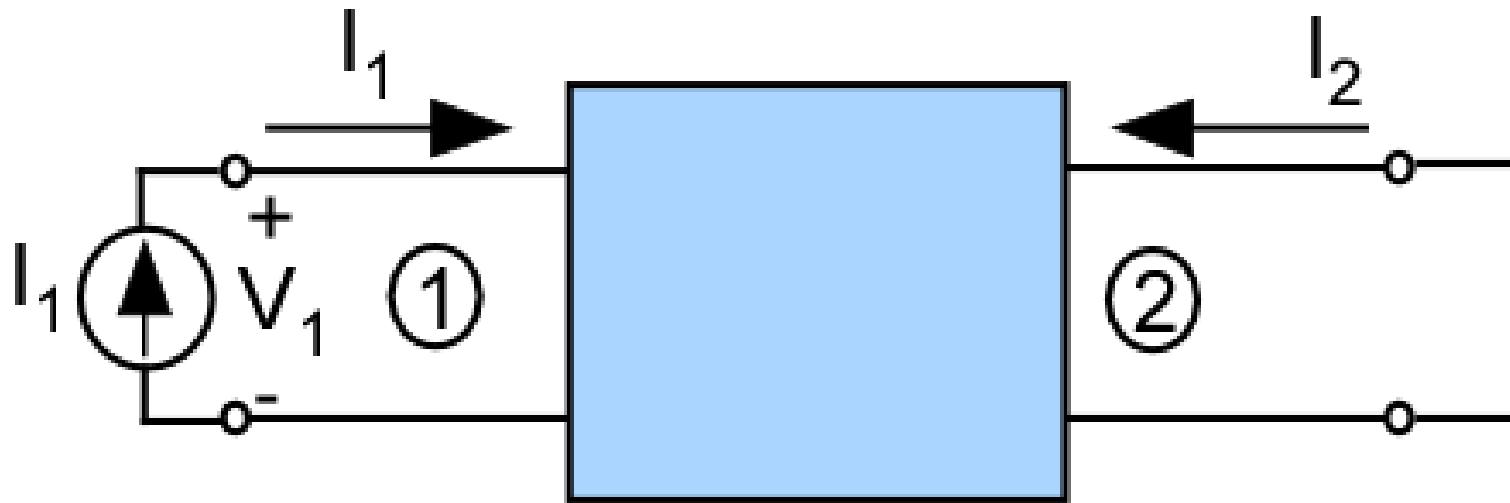


$$h_{11} = \frac{V_1}{I_1} \Big|_{V_2=0}$$

$$h_{21} = \frac{I_2}{I_1} \Big|_{V_2=0}$$

To make $V_2=0$, place a short at port 2


G Parameters

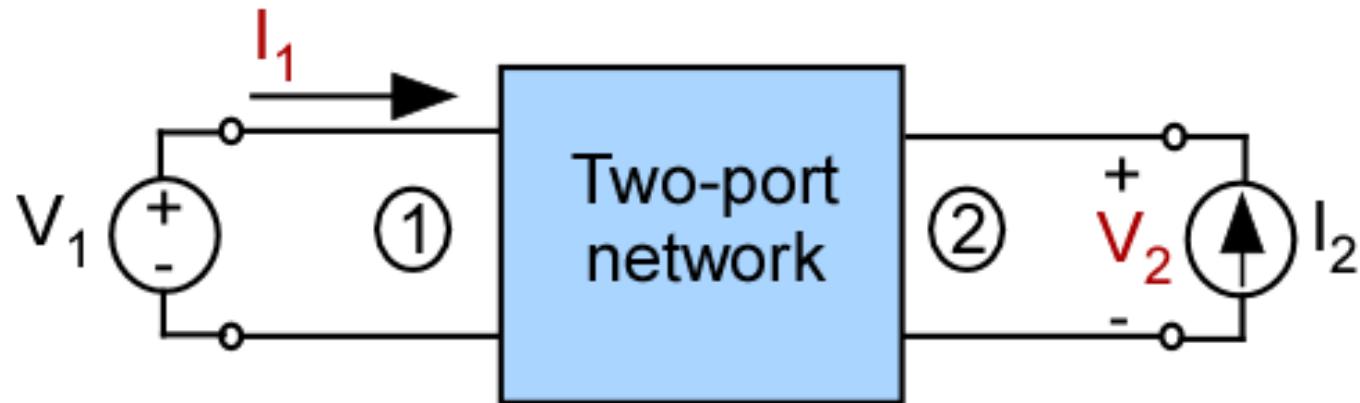

$$I_1 = g_{11}V_1 + g_{12}I_2$$

$$V_2 = g_{21}V_1 + g_{22}I_2$$


G-Parameter Calculations

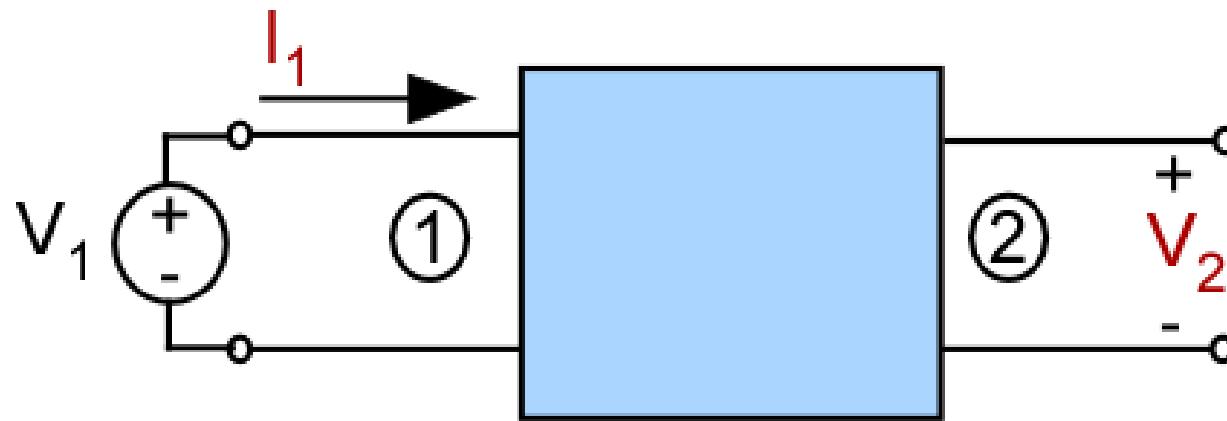

$$g_{11} = \left. \frac{I_1}{V_1} \right|_{I_2=0} \quad g_{21} = \left. \frac{V_2}{V_1} \right|_{I_2=0}$$

To make $I_2 = 0$, place an open at port 2

Y-Parameters of TL

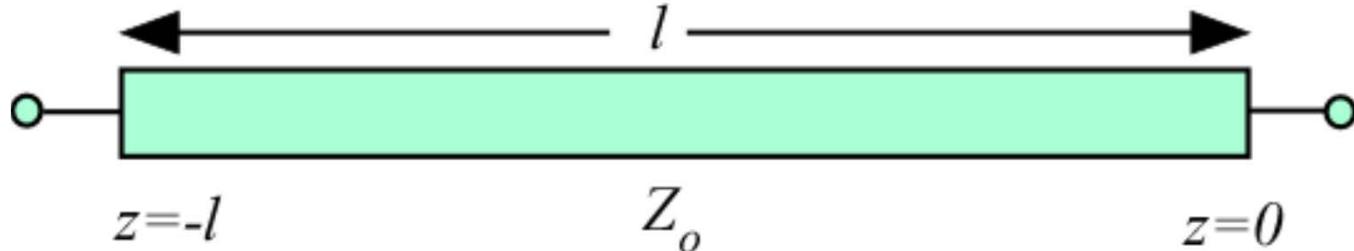


Find the Y-parameters of a lossless transmission line with propagation constant β and characteristic impedance Z_o (admittance Y_o)

$$V(z) = V_+ e^{-j\beta z} + V_- e^{+j\beta z}$$

$$I(z) = Y_o (V_+ e^{-j\beta z} - V_- e^{+j\beta z})$$

Let port 1 be at $z = -l$ and port 2 at $z = 0$

Y-Parameters of TL

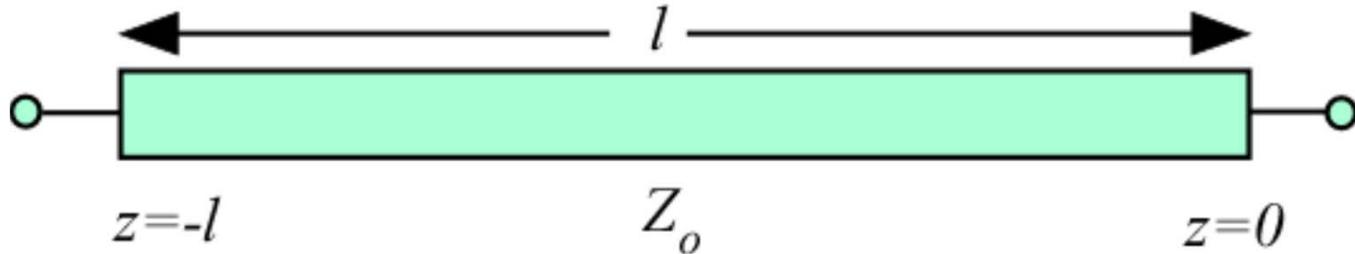

at port 1

$$V_1 = V_+ e^{+j\beta l} + V_- e^{-j\beta l}$$

$$I_1 = Y_o (V_+ e^{+j\beta l} - V_- e^{-j\beta l})$$


at port 2 ($z = 0$)

$$V_2 = V_+ + V_-$$

$$I_2 = -Y_o (V_+ - V_-)$$

$$V_+ = \frac{V_2 - Z_o I_2}{2} \quad \text{and} \quad V_- = \frac{V_2 + Z_o I_2}{2}$$

Y-Parameters of TL

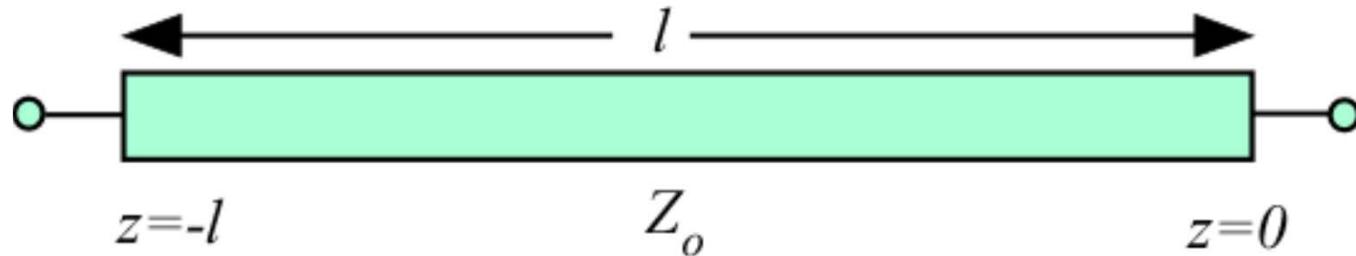

So that

$$V_1 = \left(\frac{V_2 - Z_o I_2}{2} \right) e^{+j\beta l} + \left(\frac{V_2 + Z_o I_2}{2} \right) e^{-j\beta l}$$


$$I_1 = Y_o \left(\frac{V_2 - Z_o I_2}{2} \right) e^{+j\beta l} - Y_o \left(\frac{V_2 + Z_o I_2}{2} \right) e^{-j\beta l}$$

and

$$V_1 = V_2 \cos \beta l - Z_o I_2 j \sin \beta l$$

$$I_1 = +Y_o V_2 j \sin \beta l - I_2 \cos \beta l$$

Y-Parameters of TL

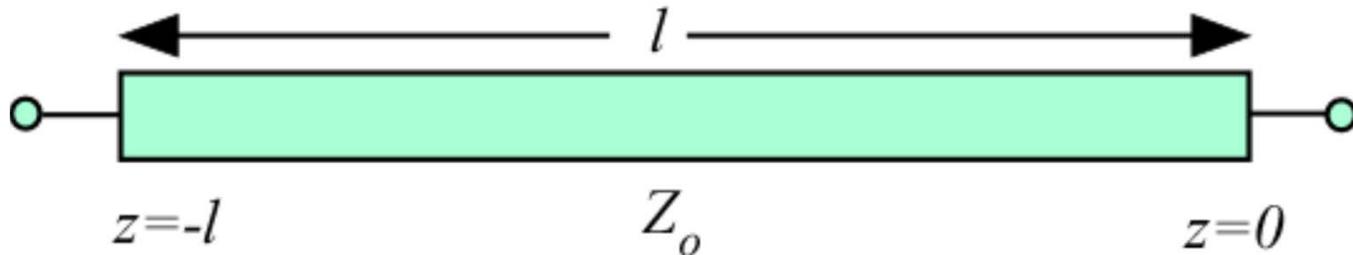

Using definitions for Y_{11}

$$Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} = \frac{-I_2 \cos \beta l}{-jZ_o I_2 \sin \beta l} = \frac{-jY_o \cos \beta l}{\sin \beta l}$$

and

$$Y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0} = \frac{-I_2}{-jZ_o I_2 \sin \beta l} = \frac{+jY_o}{\sin \beta l}$$

$$Y_{22} = Y_{11} \text{ by symmetry}$$

$$Y_{12} = Y_{21} \text{ by reciprocity}$$