

# ECE 546

## Lecture - 05

# Transmission Lines

Spring 2024

Jose E. Schutt-Aine  
Electrical & Computer Engineering  
University of Illinois  
[jesa@illinois.edu](mailto:jesa@illinois.edu)

# Maxwell's Equations

$$\nabla \times E = -\frac{\partial B}{\partial t}$$

**Faraday's Law of Induction**

$$\nabla \times H = J + \frac{\partial D}{\partial t}$$

**Ampère's Law**

$$\nabla \cdot D = \rho$$

**Gauss' Law for electric field**

$$\nabla \cdot B = 0$$


**Gauss' Law for magnetic field**

**Constitutive Relations**

$$B = \mu H$$

$$D = \epsilon E$$

# Why Transmission Line?

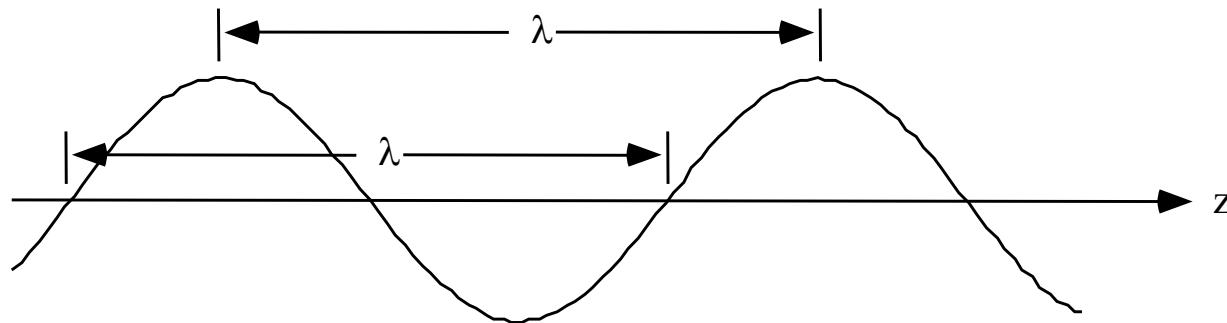

Wavelength :  $\lambda$

$$\lambda = \frac{\text{propagation velocity}}{\text{frequency}}$$

# Why Transmission Line?

**In Free Space**


**At 10 KHz :  $\lambda = 30 \text{ km}$**

**At 10 GHz :  $\lambda = 3 \text{ cm}$**

Transmission line behavior is prevalent when the structural dimensions of the circuits are comparable to the wavelength.

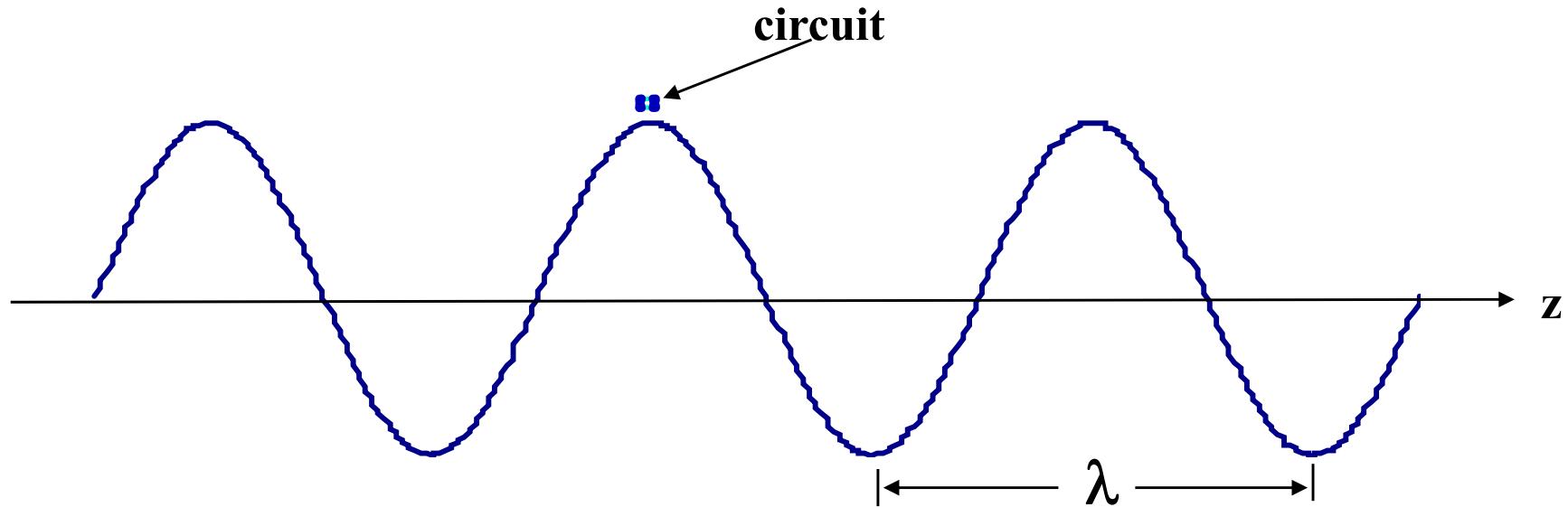
# Justification for Transmission Line

Let  $d$  be the largest dimension of a circuit



If  $d \ll \lambda$ , a lumped model for the circuit can be used

# Justification for Transmission Line

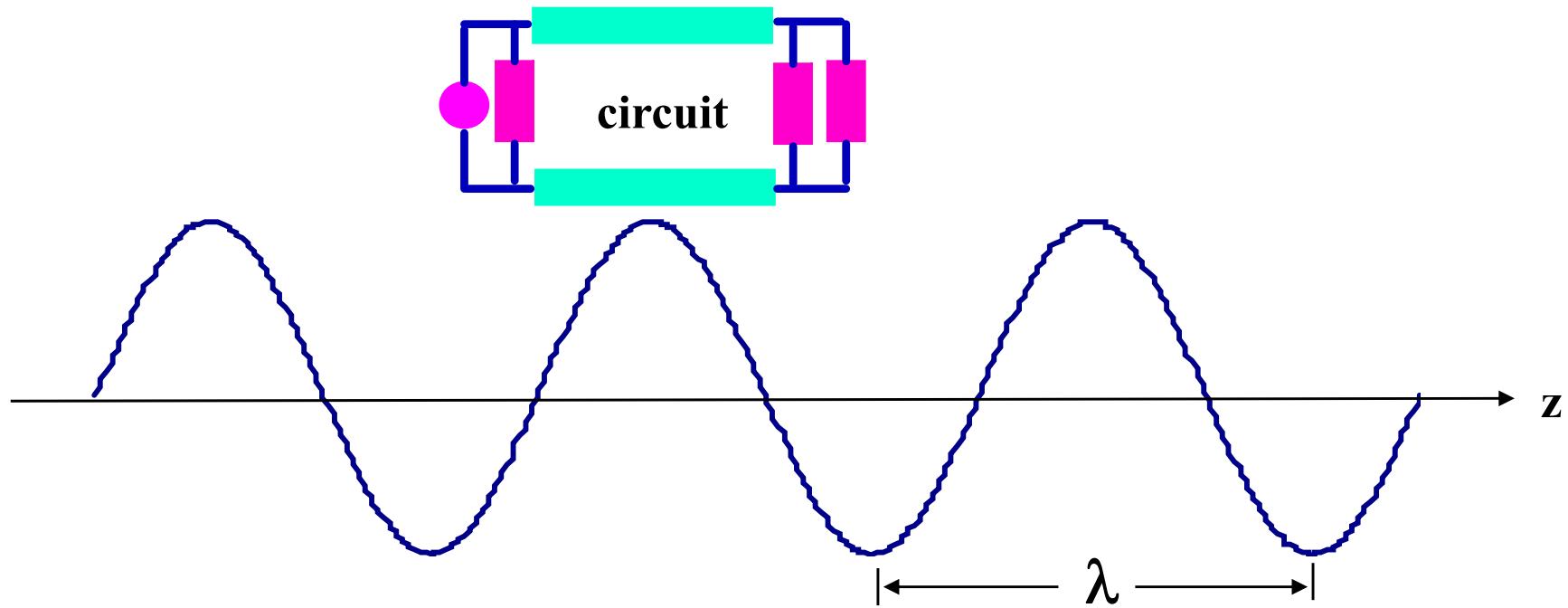


If  $d \approx \lambda$ , or  $d > \lambda$  then use transmission line model

# Modeling Interconnections

Low Frequency


Mid-range  
Frequency

High Frequency

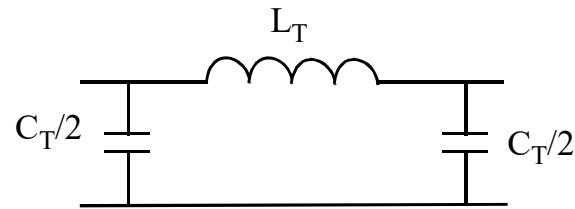

Short


or

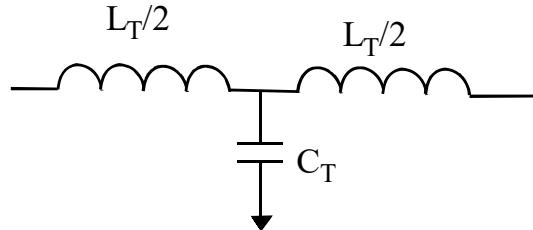

Lumped  
Reactive CKT

Transmission  
Line

# Single wire near ground

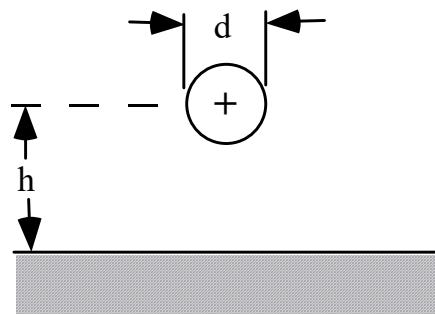


$$\text{for } d \ll h, \quad Z_o = \frac{1}{2\pi} \sqrt{\frac{\mu}{\epsilon}} \ln \left( \frac{4h}{d} \right)$$

$$Z_o = 120 \cosh^{-1}(D/d)$$

$$C = \frac{2\pi\epsilon}{\ln \left( \frac{4h}{d} \right)}$$


$$L = \frac{\mu}{2\pi} \ln \frac{4h}{d}$$
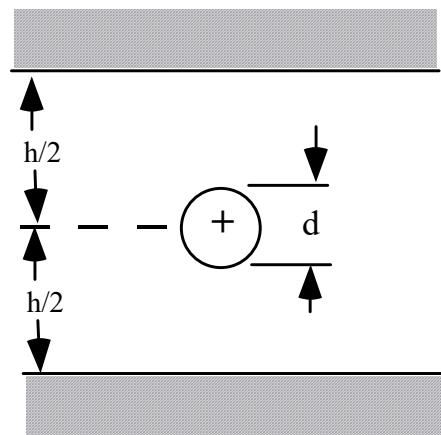
# Single wire between grounded parallel planes ground return



$$Z_o = \frac{1}{2\pi} \sqrt{\frac{\mu}{\epsilon}} \ln\left(\frac{4h}{\pi d}\right)$$


# Wires in parallel near ground

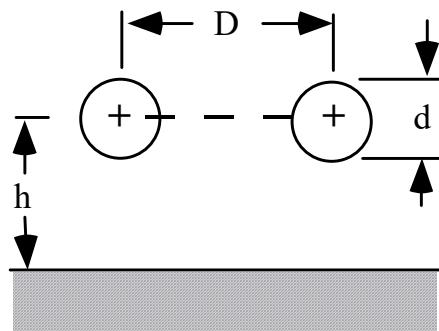

for  $d \ll D, h$

$$Z_O = \left( 69 / \sqrt{\epsilon_r} \right) \log_{10} \left\{ \left( 4h/d \right) \sqrt{1 + \left( 2h/D \right)^2} \right\}$$


# Balanced, near ground

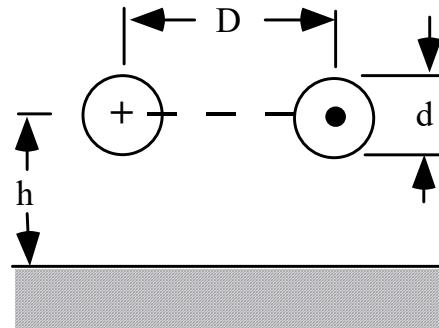

for  $d \ll D, h$


$$Z_o = \left( 276 / \sqrt{\epsilon_r} \right) \log_{10} \left\{ \frac{(2D/d)}{\sqrt{1 + (D/2h)^2}} \right\}$$

# Open 2-wire line in air

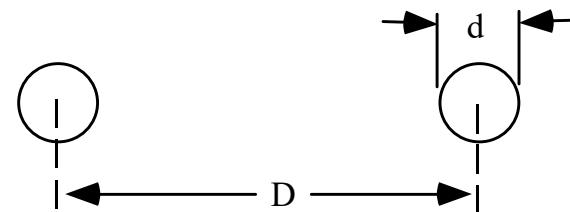

$$Z_o = 120 \cosh^{-1}(D/d)$$


# Parallel-plate Transmission Line

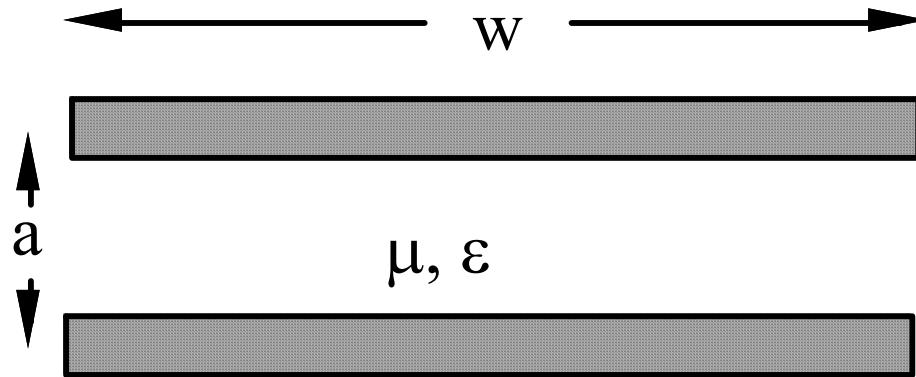

$$L = \frac{\mu a}{w}$$

$$C = \frac{\epsilon w}{a}$$


# Types of Transmission Lines

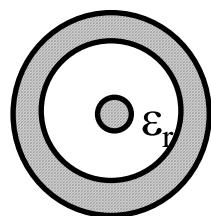


Coaxial line




Waveguide

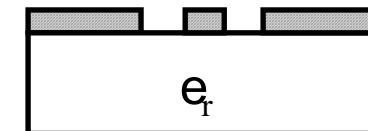


Coplanar line

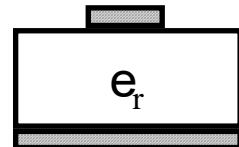

Microstrip

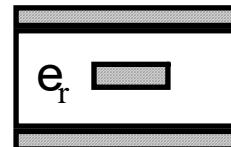


Stripline

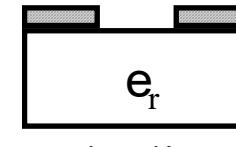

Slot line

# Coaxial Transmission Line

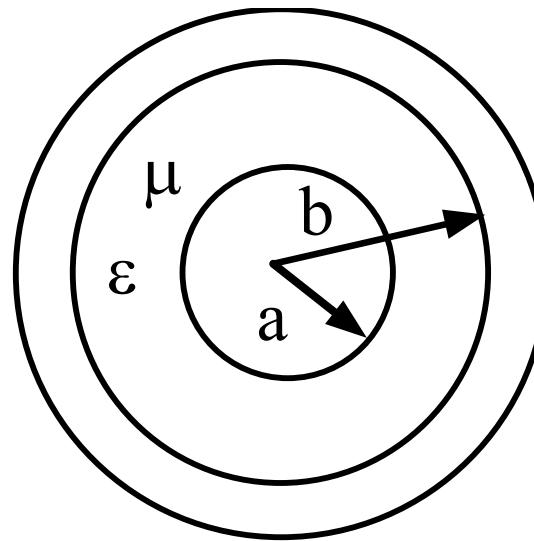


**TEM Mode of Propagation**

$$L = \mu \ln \frac{b}{a}$$

$$C = \frac{2\pi\epsilon}{\ln(b/a)}$$

# Coaxial Air Lines

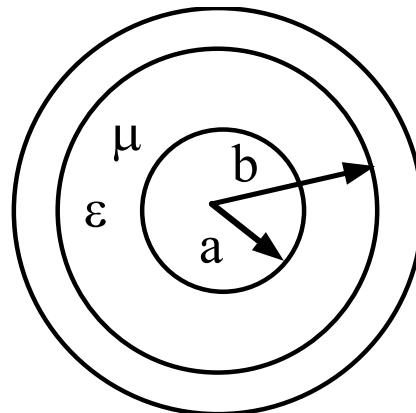


Infinite Conductivity

$$Z_o = \frac{\sqrt{\mu/\epsilon}}{2\pi} \ln(b/a)$$

Finite Conductivity


$$Z_o = \frac{\sqrt{\mu/\epsilon}}{2\pi} \ln(b/a) \left[ 1 + \frac{(1/a + 1/b)}{4\sqrt{\pi f \mu \sigma} \ln(b/a)} (1 - j) \right]$$

# Coaxial Connector Standards

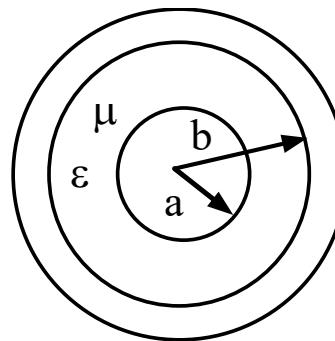


<u>Connector</u>	<u>Frequency Range</u>
14 mm	DC - 8.5 GHz
GPC-7	DC - 18 GHz
Type NDC - 18 GHz	
3.5 mm	DC - 33 GHz
2.92 mm	DC - 40 GHz
2.4 mm	DC - 50 GHz
1.85 mm	DC - 65 GHz
1.0 mm	DC - 110 GHz

# Microstrip

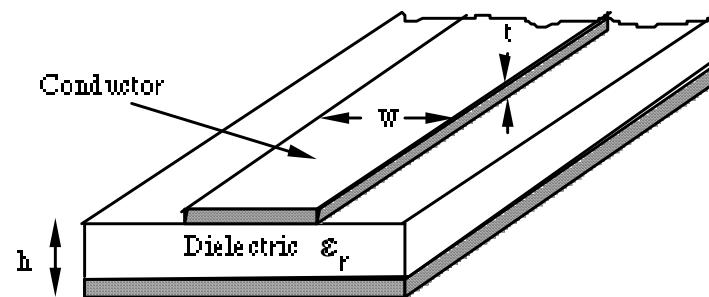


(a)

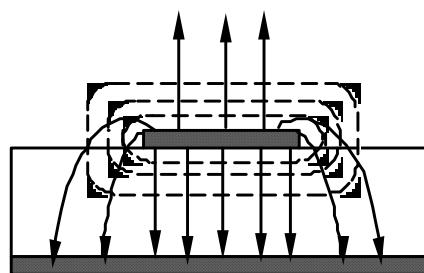

\_\_\_\_\_ Electric field lines  
\_\_\_\_\_ Magnetic field lines


(b)

# Microstrip

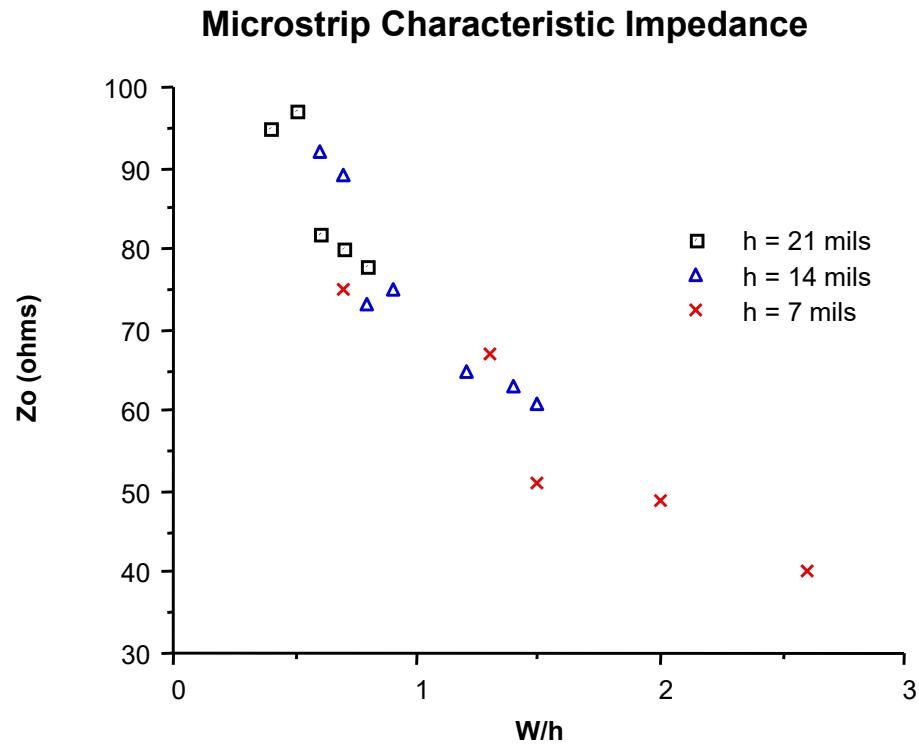

dielectric constant : 4.3.

# Telegraphers' Equations

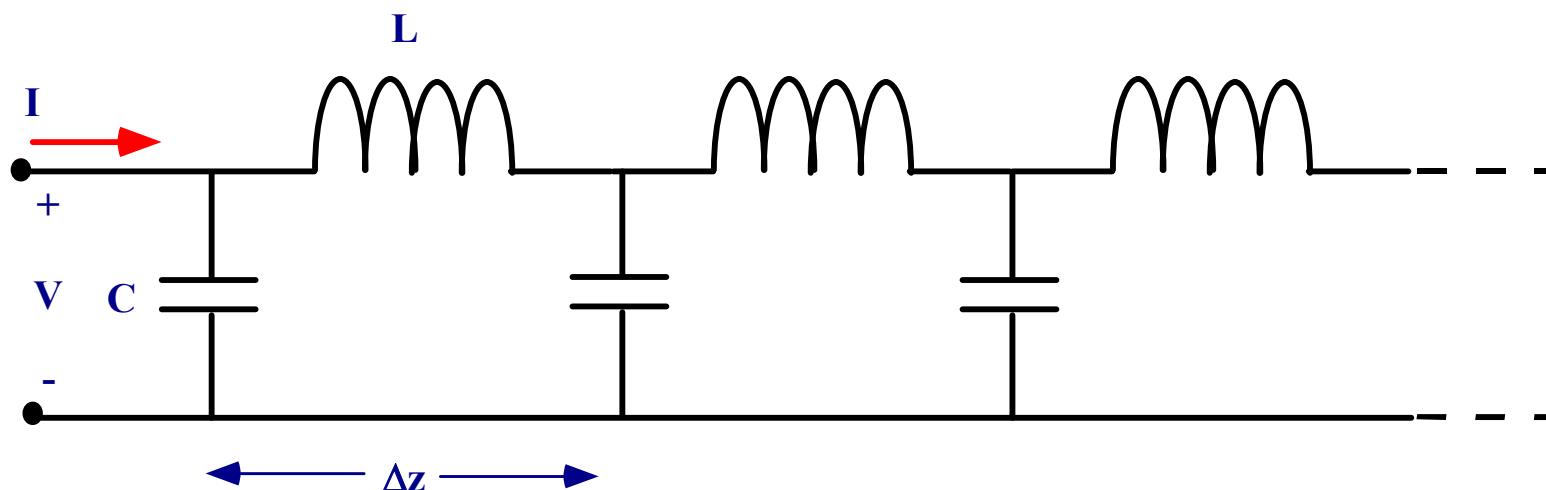

**$L$ : Inductance per unit length.**

**$C$ : Capacitance per unit length.**

$$-\frac{\partial V}{\partial z} = L \frac{\partial I}{\partial t}$$

Assume  
time-harmonic  
dependence

$$-\frac{\partial V}{\partial z} = j\omega LI$$


$$-\frac{\partial I}{\partial z} = C \frac{\partial V}{\partial t}$$

$$V, I \sim e^{j\omega t}$$



$$-\frac{\partial I}{\partial z} = j\omega CV$$

# TL Solutions

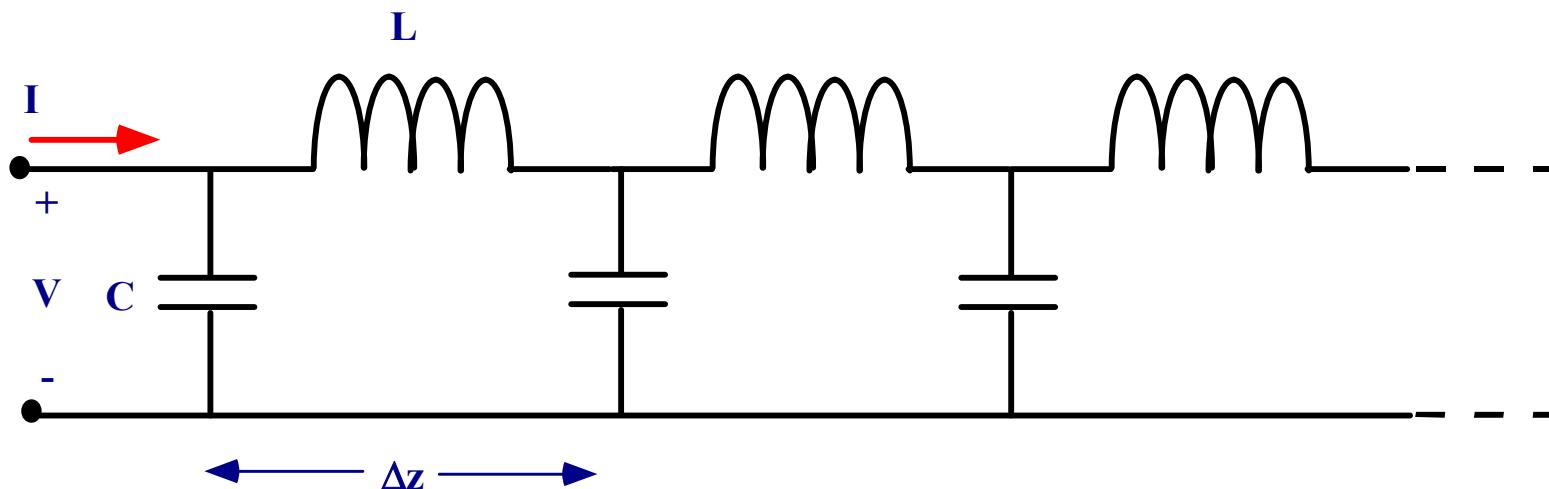


$$-\frac{\partial}{\partial z} \left( \frac{\partial V}{\partial z} \right) = -\frac{\partial^2 V}{\partial z^2} = j\omega L \frac{\partial I}{\partial z} = -j\omega L j\omega C V \quad \rightarrow \quad \frac{\partial^2 V}{\partial z^2} = -\omega^2 L C V$$

$$-\frac{\partial}{\partial z} \left( \frac{\partial I}{\partial z} \right) = -\frac{\partial^2 I}{\partial z^2} = j\omega C \frac{\partial V}{\partial z} = -j\omega L j\omega C I \quad \rightarrow \quad \frac{\partial^2 I}{\partial z^2} = -\omega^2 C L I$$

# TL Solutions

(Frequency Domain)

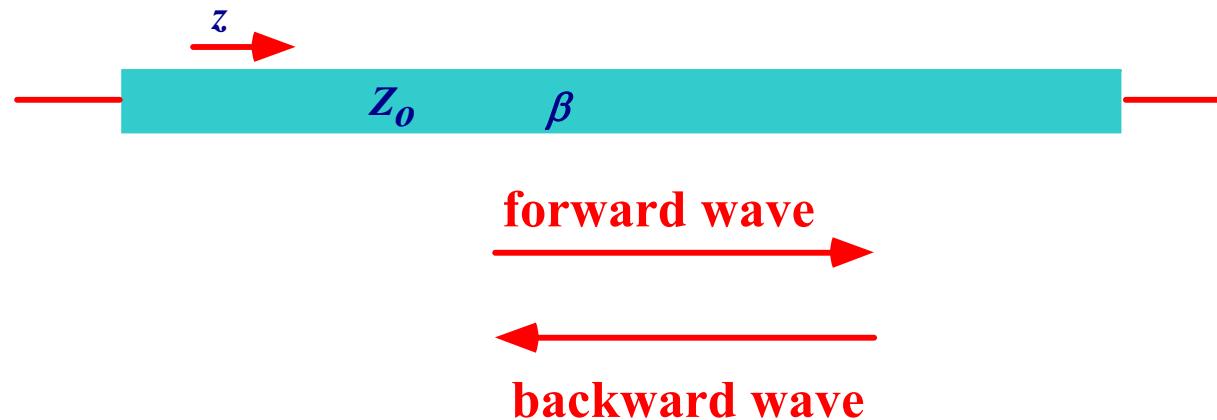

$$Z_o = \sqrt{\frac{L}{C}}$$

$$V(z) = \underbrace{V_+ e^{-j\beta z}}_{\substack{\text{Forward Wave}}} + \underbrace{V_- e^{+j\beta z}}_{\substack{\text{Backward Wave}}}$$
$$I(z) = \underbrace{\frac{V_+}{Z_o} e^{-j\beta z}}_{\substack{\text{Forward Wave}}} - \underbrace{\frac{V_-}{Z_o} e^{+j\beta z}}_{\substack{\text{Backward Wave}}}$$

# TL Solutions


**Propagation constant**  $\beta = \omega\sqrt{LC}$    **Propagation velocity**  $v = \frac{1}{\sqrt{LC}}$

**Characteristic impedance**  $Z_o = \sqrt{\frac{L}{C}}$    **Wavelength**  $\lambda = \frac{v}{f}$

$$V(z,t) = \overbrace{V_+ \cos(\omega t - \beta z)}^{\text{Forward Wave}} + \overbrace{V_- \cos(\omega t + \beta z)}^{\text{Backward Wave}}$$

$$I(z,t) = \underbrace{\frac{V_+}{Z_o} \cos(\omega t - \beta z)}_{\text{Forward Wave}} - \underbrace{\frac{V_-}{Z_o} \cos(\omega t + \beta z)}_{\text{Backward Wave}}$$

# Reflection Coefficient

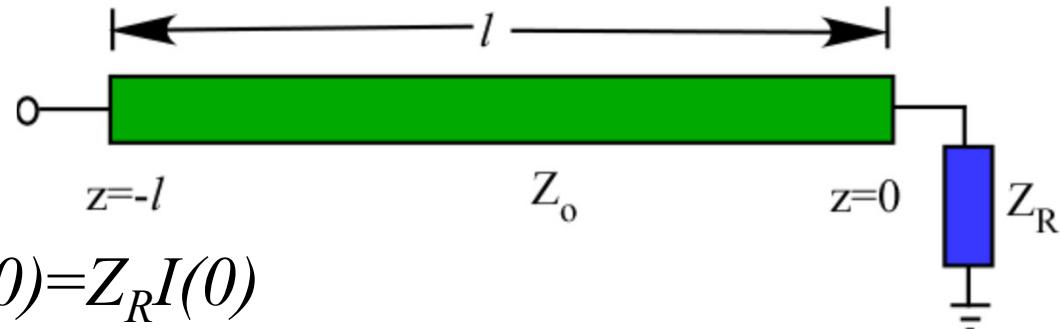

At  $z=0$ , we have  $V(0)=Z_R I(0)$

But from the TL equations:

$$V(0) = V_+ + V_-$$

$$I(0) = \frac{V_+}{Z_o} - \frac{V_-}{Z_o}$$

$$\frac{Z_R}{Z_o}(V_+ - V_-) = V_+ + V_-$$

Which gives  $V_- = \Gamma_R V_+$

where  $\Gamma_R = \frac{Z_R - Z_o}{Z_R + Z_o}$  is the load reflection coefficient

# Reflection Coefficient

- If  $Z_R = Z_o, \Gamma_R = 0$ , no reflection, the line is matched
- If  $Z_R = 0$ , short circuit at the load,  $\Gamma_R = -1$
- If  $Z_R \rightarrow \infty$ , open circuit at the load,  $\Gamma_R = +1$

$V$  and  $I$  can be written in terms of  $\Gamma_R$


$$V(z) = V_+ \left[ e^{-j\beta z} + \Gamma_R e^{+j\beta z} \right]$$

$$V(z) = V_+ e^{-j\beta z} \left[ 1 + \Gamma_R e^{+2j\beta z} \right]$$

$$I(z) = \frac{V_+}{Z_o} \left[ e^{-j\beta z} - \Gamma_R e^{+j\beta z} \right]$$

$$I(z) = \frac{V_+ e^{-j\beta z}}{Z_o} \left[ 1 - \Gamma_R e^{+2j\beta z} \right]$$

# Generalized Impedance

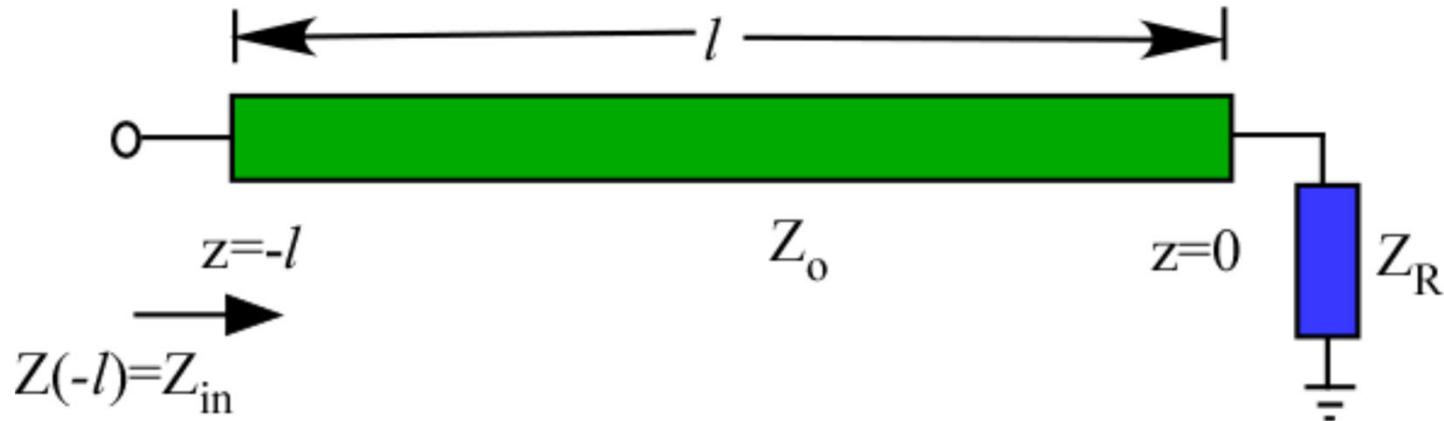


$$Z(z) = \frac{V(z)}{I(z)} = Z_o \left[ \frac{e^{-j\beta z} + \Gamma_R e^{+j\beta z}}{e^{-j\beta z} - \Gamma_R e^{+j\beta z}} \right]$$

$$Z(-l) = Z_o \left[ \frac{Z_R + jZ_o \tan \beta l}{Z_o + jZ_R \tan \beta l} \right]$$

Impedance  
transformation  
equation

# Generalized Impedance

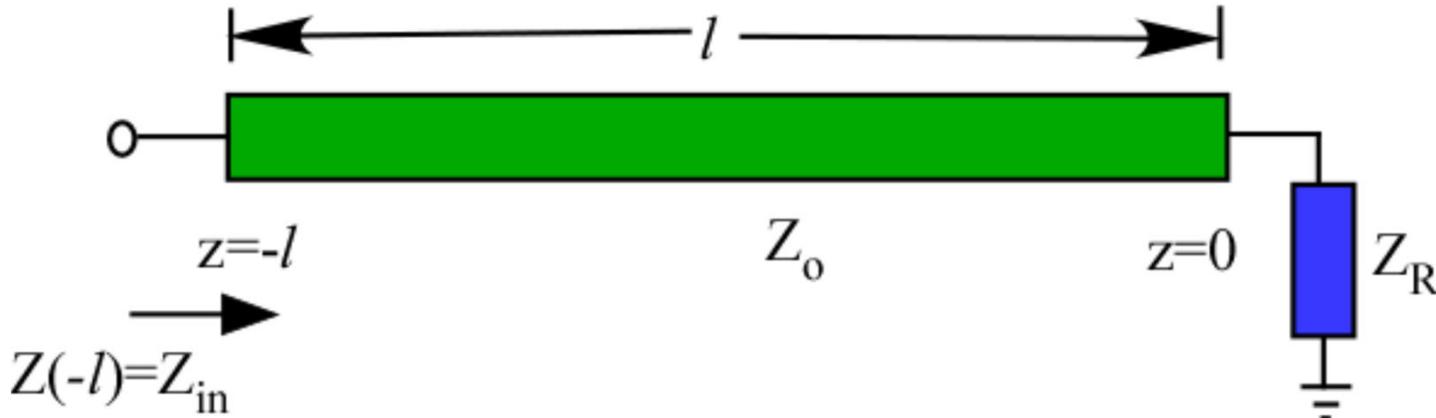

- Short circuit  $Z_R = 0$ , line appears inductive for  $0 < l < \lambda/2$

$$Z(-l) = jZ_o \tan \beta l$$

- Open circuit  $Z_R \rightarrow \infty$ , line appears capacitive for  $0 < l < \lambda/2$

$$Z(-l) = \frac{Z_o}{j \tan \beta l}$$

- If  $l = \lambda/4$ , the line is a quarter-wave transformer

$$Z(-l) = \frac{Z_o^2}{Z_R}$$

# Generalized Reflection Coefficient

$$\Gamma(z) = \frac{\text{Backward traveling wave at } z}{\text{Forward traveling wave at } z} = \frac{V_b(z)}{V_f(z)}$$

$$\Gamma(z) = \frac{V_- e^{+j\beta z}}{V_+ e^{-j\beta z}} = \frac{V_-}{V_+} e^{+2j\beta z} = \Gamma_R e^{+2j\beta z}$$

Reflection coefficient  
transformation equation



$$\Gamma(-l) = \Gamma_R e^{-2j\beta l}$$

$$Z(z) = Z_o \frac{1 + \Gamma(z)}{1 - \Gamma(z)}$$


$$\Gamma(z) = \frac{Z(z) - Z_o}{Z(z) + Z_o}$$

# Voltage Standing Wave Ratio (VSWR)

$$V(z) = V_+ e^{-j\beta z} \left[ 1 + \Gamma_R e^{+2j\beta z} \right]$$

We follow the magnitude of the voltage along the TL

$$|V(z)| = |V_+ e^{-j\beta z}| \left| 1 + \Gamma_R e^{+2j\beta z} \right| = |V_+| \left| 1 + \Gamma_R e^{+2j\beta z} \right|$$

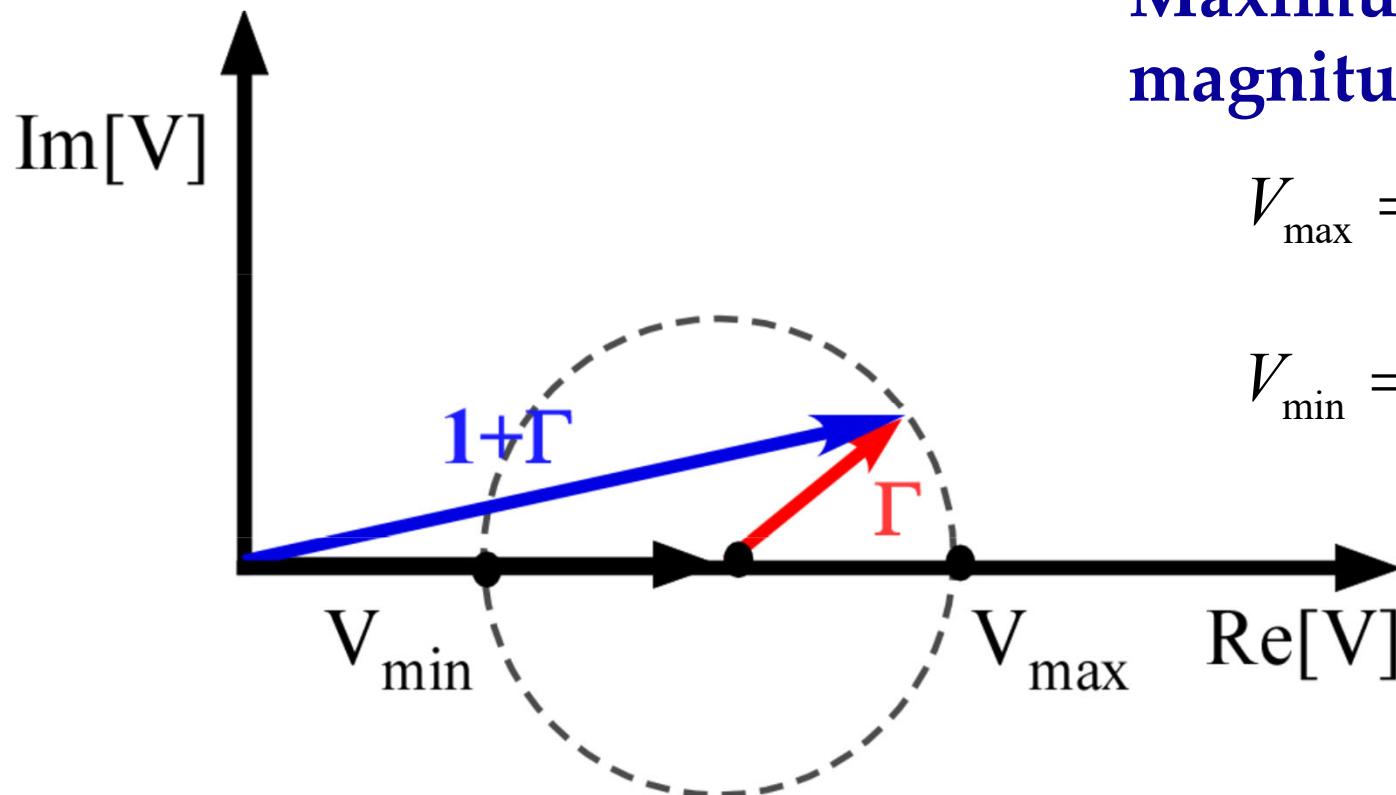

Maximum and minimum magnitudes given by


$$V_{\max} = \left[ 1 + |\Gamma_R| \right]$$

$$V_{\min} = \left[ 1 - |\Gamma_R| \right]$$

# Voltage Standing Wave Ratio (VSWR)


Define Voltage Standing Wave Ratio as:

$$VSWR = \frac{V_{\max}}{V_{\min}} = \frac{1 + |\Gamma_R|}{1 - |\Gamma_R|}$$

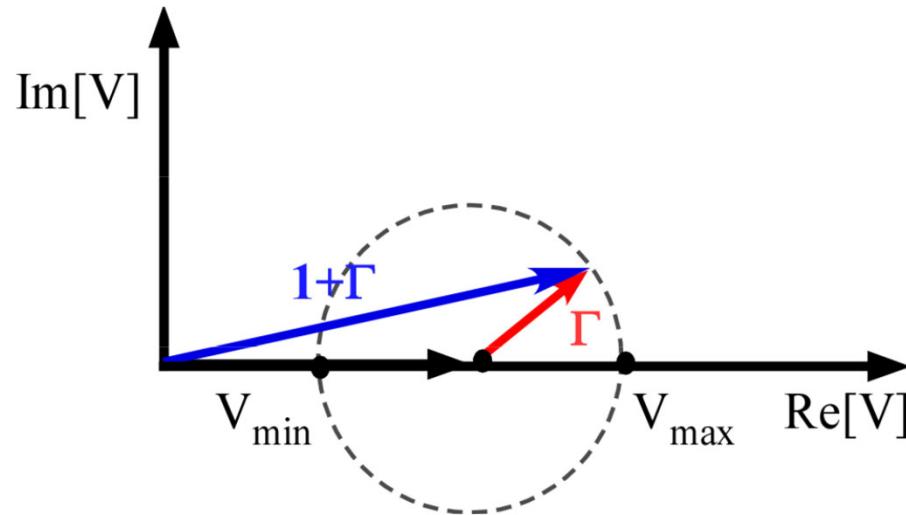


It is a measure of the interaction between forward and backward waves

# VSWR – Arbitrary Load

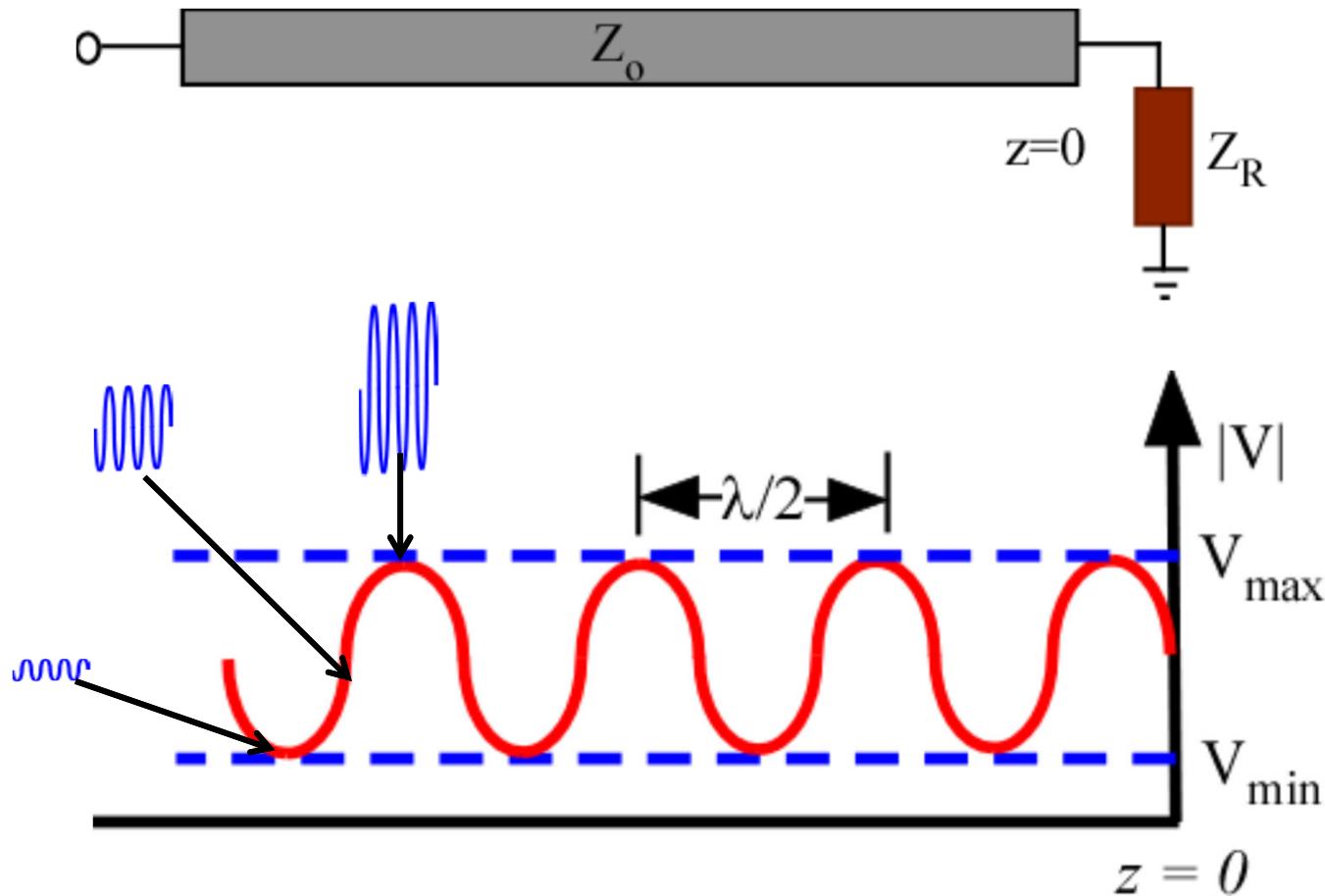


Shows variation of amplitude along line

# VSWR – For Short Circuit Load

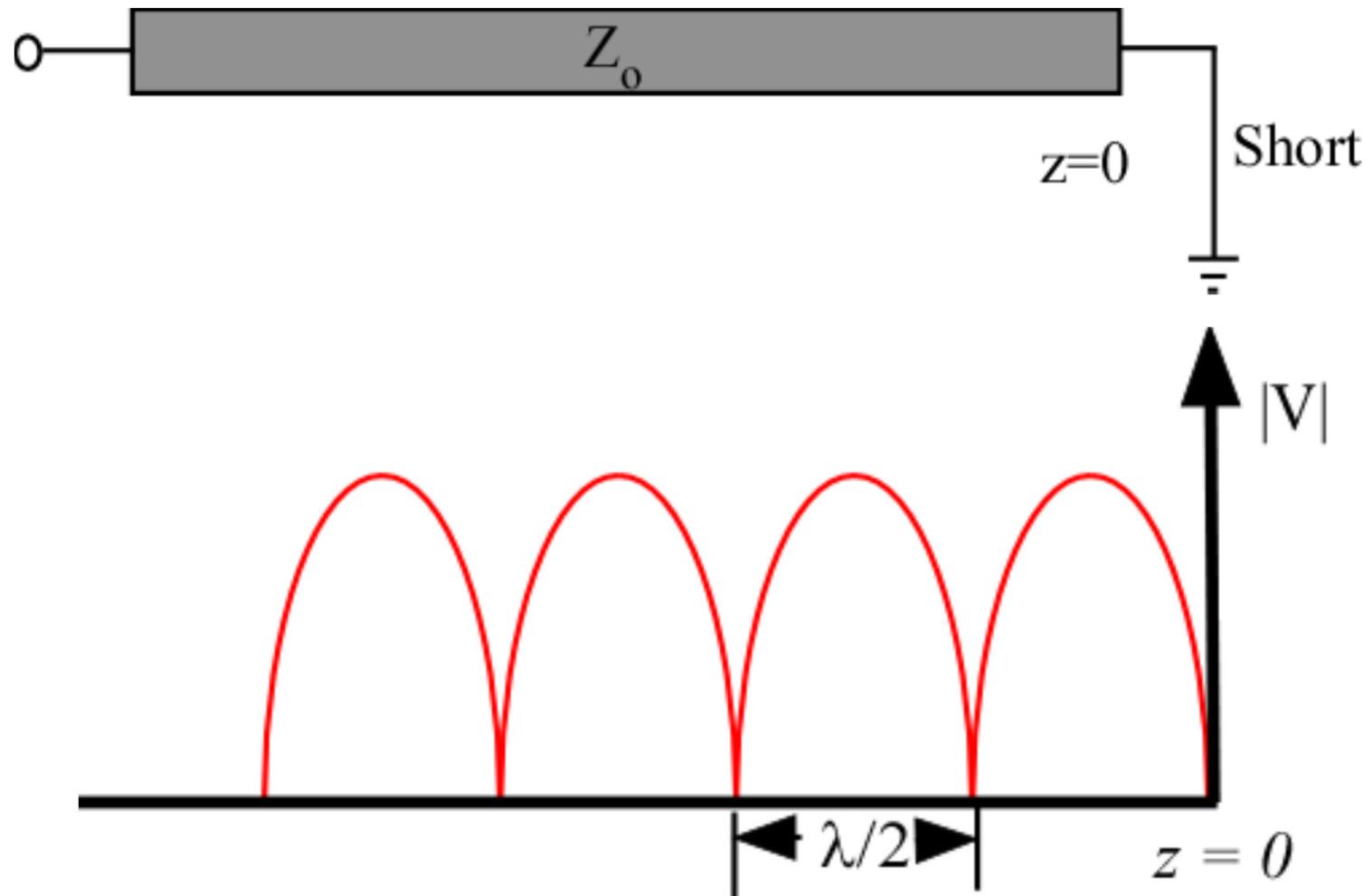


Voltage minimum is reached at load

# VSWR – For Open Circuit Load

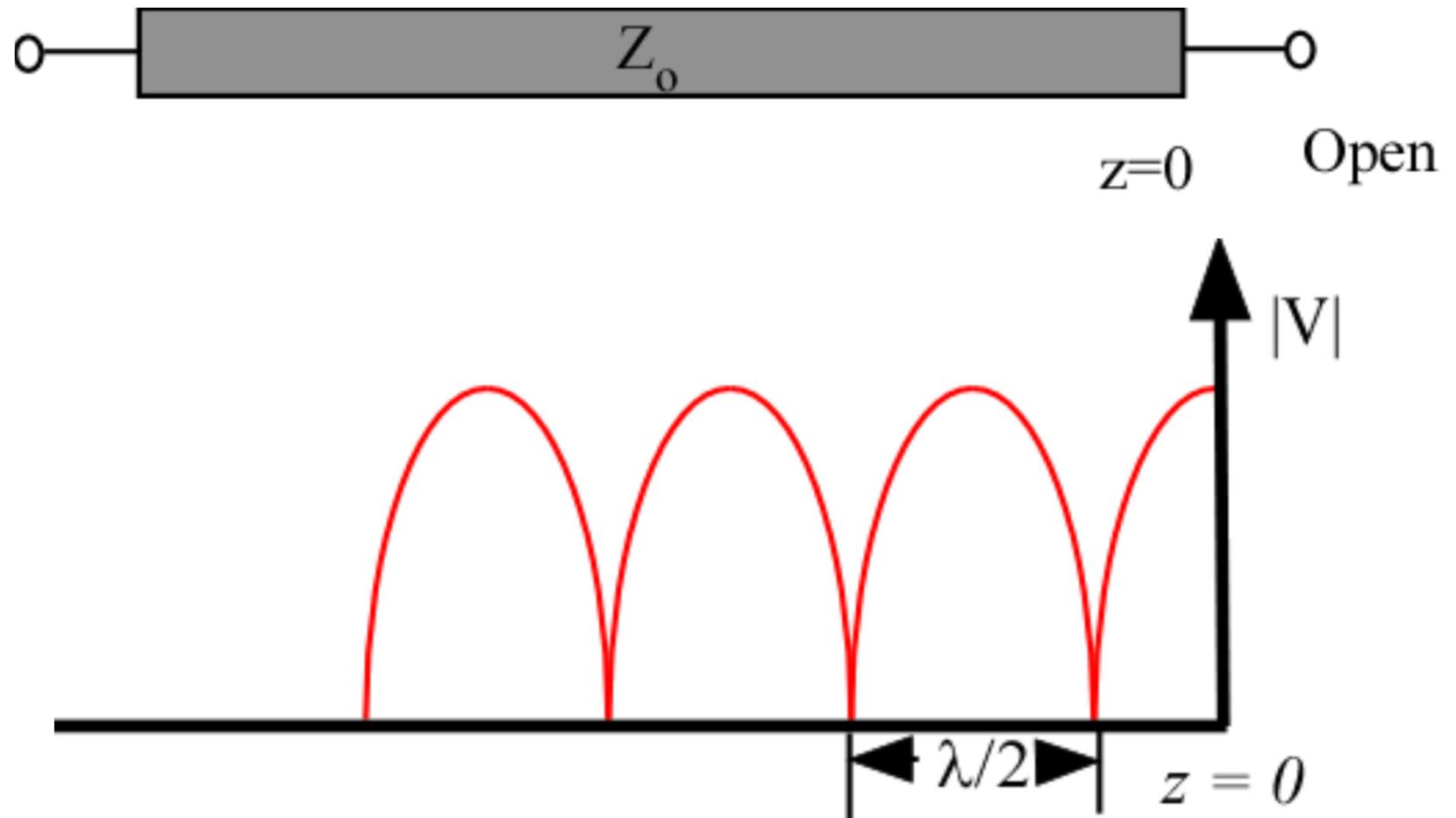


**Voltage maximum is reached at load**

# VSWR – For Open Matched Load

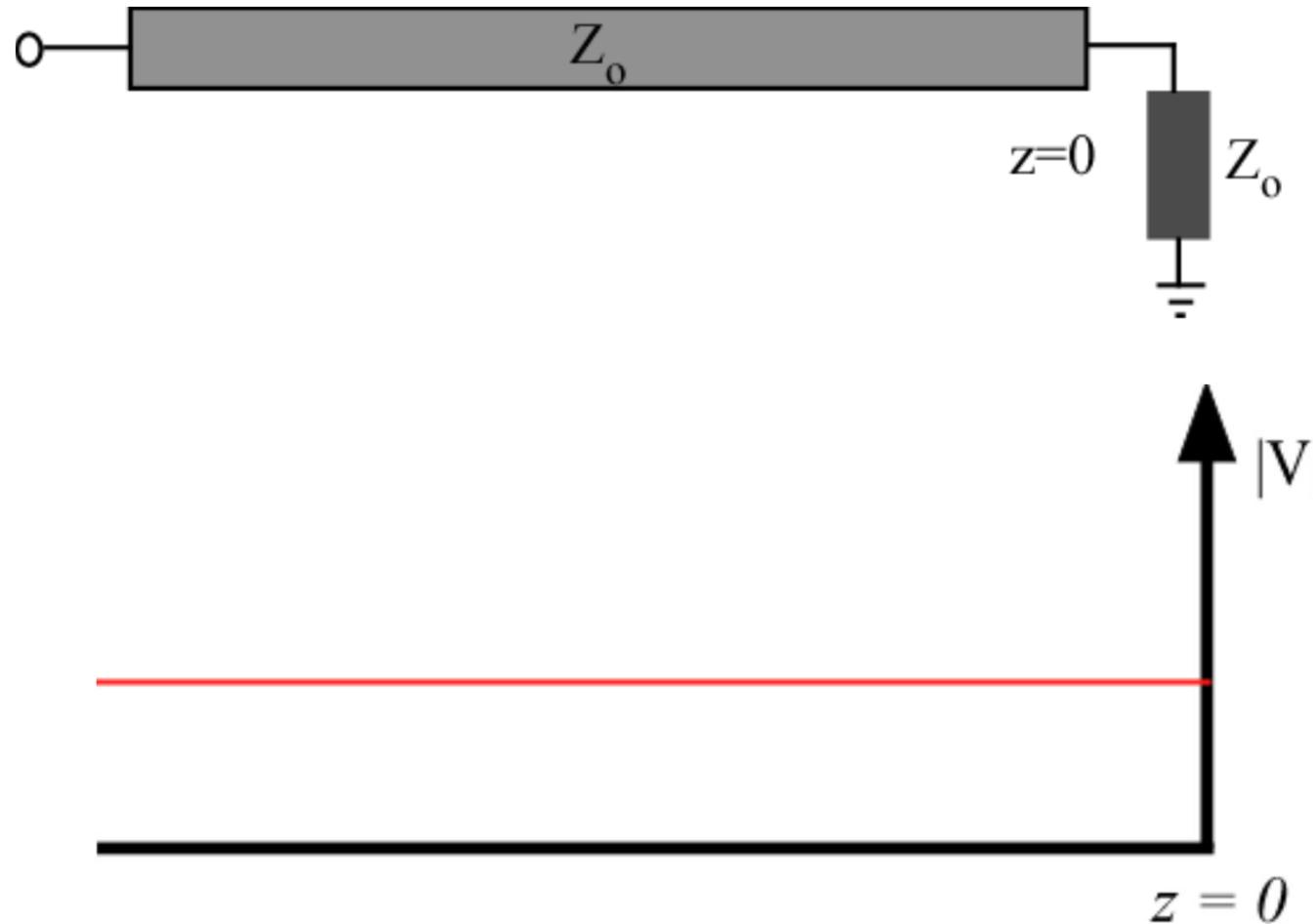


No variation in amplitude along line

# Application: Slotted-Line Measurement

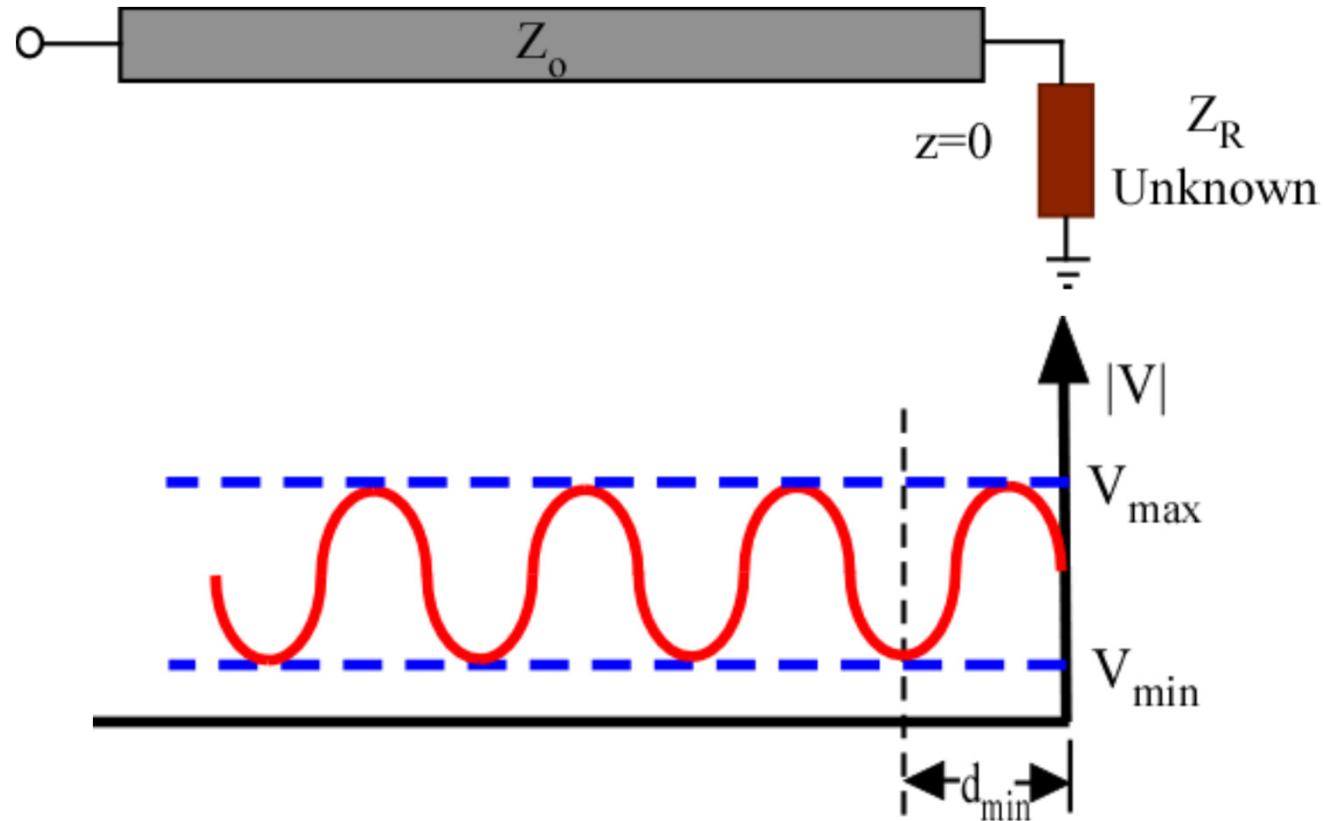

- Measure VSWR =  $V_{max}/V_{min}$
- Measure location of first minimum

# Application: Slotted-Line Measurement

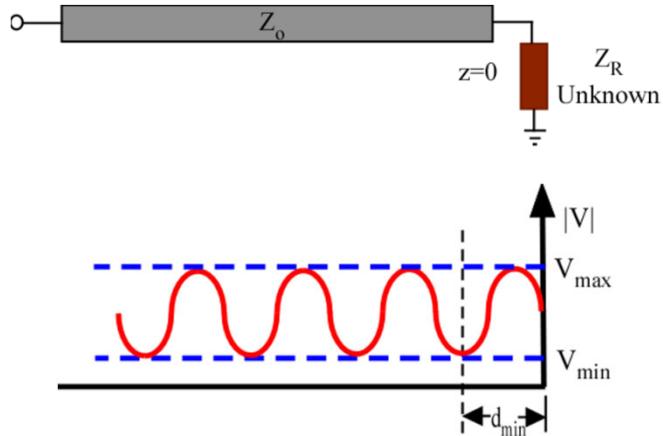

**At minimum,**  $\Gamma(z) = \text{pure real} = -|\Gamma_R|$

**Therefore,**  $\Gamma(-d_{\min}) = \Gamma_R e^{-2j\beta d_{\min}} = -|\Gamma_R|$

$$\text{So, } \Gamma_R = -|\Gamma_R| e^{+2j\beta d_{\min}}$$

$$\text{Since } |\Gamma_R| = \frac{VSWR - 1}{VSWR + 1} \quad \text{then} \quad \Gamma_R = -\left(\frac{VSWR - 1}{VSWR + 1}\right) e^{+2j\beta d_{\min}}$$

$$\text{and } Z_R = Z_0 \left( \frac{1 + \Gamma_R}{1 - \Gamma_R} \right)$$

# Summary of TL Equations

Voltage

$$V(z) = V_+ e^{-j\beta z} \left[ 1 + \Gamma_R e^{+2j\beta z} \right]$$

Current

$$I(z) = \frac{V_+}{Z_o} e^{-j\beta z} \left[ 1 - \Gamma_R e^{+2j\beta z} \right]$$

Impedance Transformation  $\rightarrow$

$$Z(-l) = Z_o \left[ \frac{Z_R + jZ_o \tan \beta l}{Z_o + jZ_R \tan \beta l} \right]$$

Reflection Coefficient Transformation  $\rightarrow$

$$\Gamma(-l) = \Gamma_R e^{-2j\beta l}$$


Reflection Coefficient – to Impedance  $\rightarrow$

$$Z(z) = Z_o \frac{1 + \Gamma(z)}{1 - \Gamma(z)}$$

Impedance to Reflection Coefficient  $\rightarrow$

$$\Gamma(z) = \frac{Z(z) - Z_o}{Z(z) + Z_o}$$

# Determining $V_+$

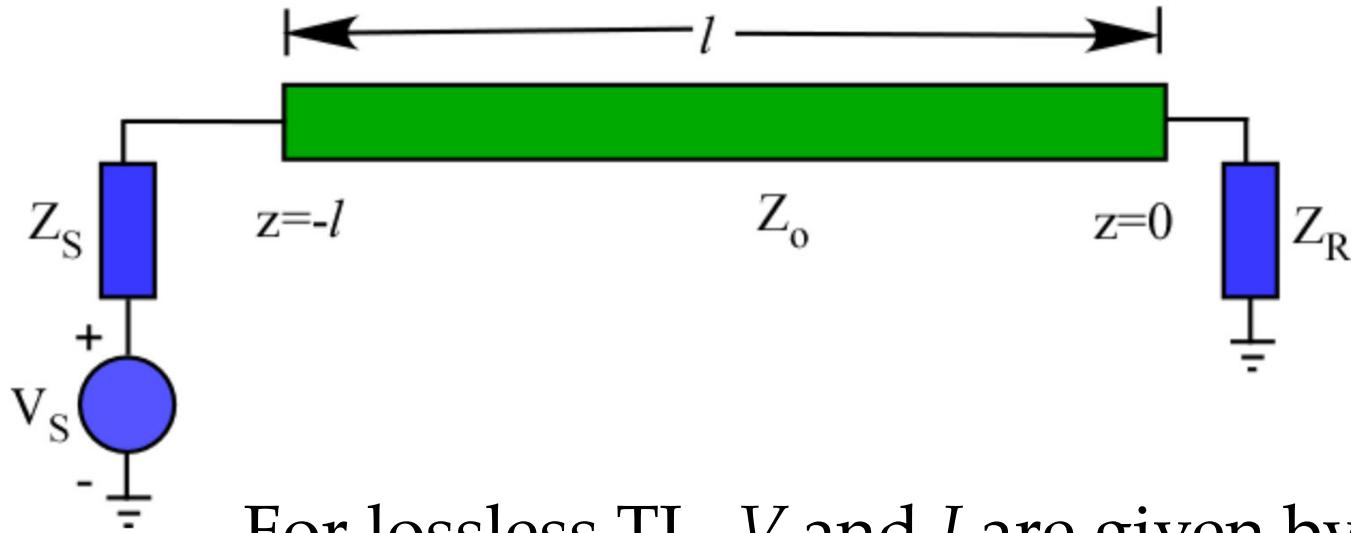

For lossless TL,  $V$  and  $I$  are given by

$$V(z) = V_+ e^{-j\beta z} \left[ 1 + \Gamma_R e^{+2j\beta z} \right]$$


reflection coefficient  
at the load

$$\Gamma_R = \frac{Z_R - Z_0}{Z_R + Z_0}$$

$$I(z) = \frac{V_+ e^{-j\beta z}}{Z_0} \left[ 1 - \Gamma_R e^{+2j\beta z} \right]$$

$$At z = -l, \quad V_S = Z_S I(-l) + V(-l)$$

# Determining $V_+$

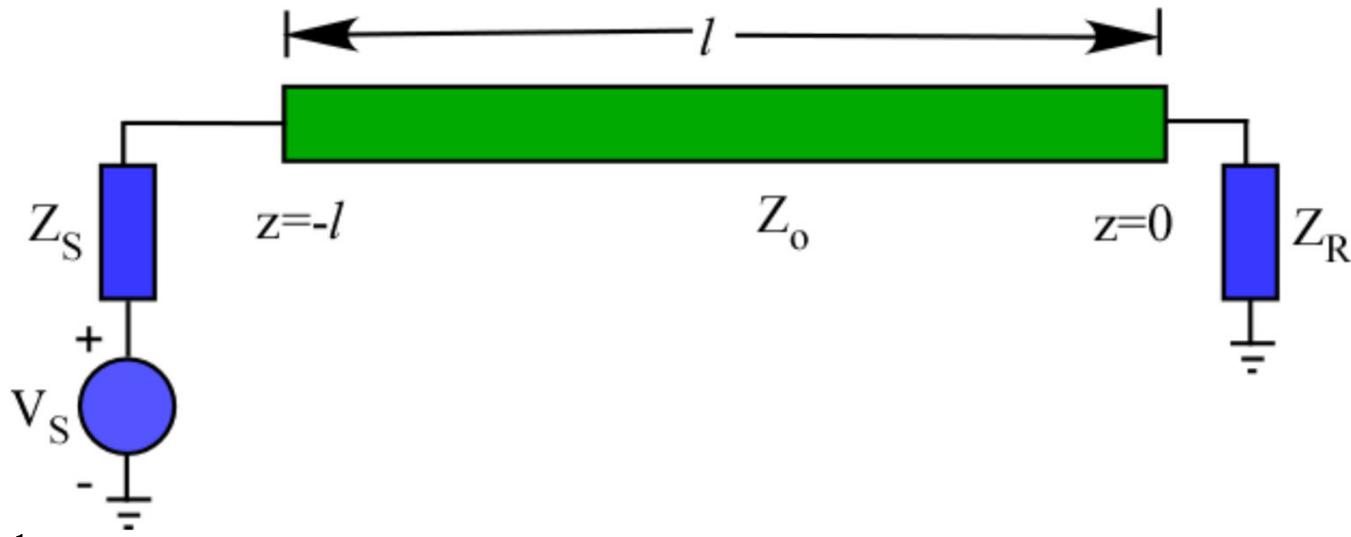

this leads to

$$V_S = V_+ e^{+j\beta l} \left( 1 + \Gamma_R e^{-2j\beta l} \right) + \frac{Z_S}{Z_o} V_+ e^{+j\beta l} \left( 1 - \Gamma_R e^{-2j\beta l} \right)$$

or


$$V_S = V_+ \left( e^{+j\beta l} + \Gamma_R e^{-j\beta l} + \frac{Z_S}{Z_o} e^{+j\beta l} - \Gamma_R \frac{Z_S}{Z_o} e^{-j\beta l} \right)$$

$$V_S = V_+ \left( e^{+j\beta l} \left( 1 + \frac{Z_S}{Z_o} \right) + \Gamma_R e^{-j\beta l} \left( 1 - \frac{Z_S}{Z_o} \right) \right)$$
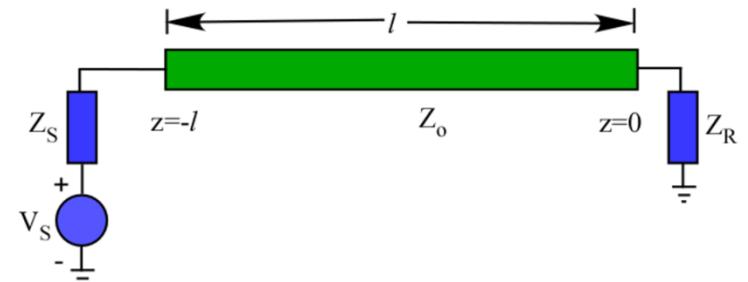
# Determining $V_+$

Divide through by  $\left(1 + \frac{Z_S}{Z_o}\right) = \frac{1}{T_S}$

$$V_+ \left( e^{+j\beta l} - \Gamma_S \Gamma_R e^{-j\beta l} \right) = T_S V_S$$




$$\text{with } T_S = \left(1 + \frac{Z_S}{Z_o}\right)^{-1} = \frac{Z_o}{Z_S + Z_o} \quad \text{and} \quad \Gamma_S = \frac{Z_S - Z_o}{Z_S + Z_o}$$

From which

$$V_+ = \frac{T_S V_S e^{-j\beta l}}{1 - \Gamma_S \Gamma_R e^{-2j\beta l}}$$


# TL Example

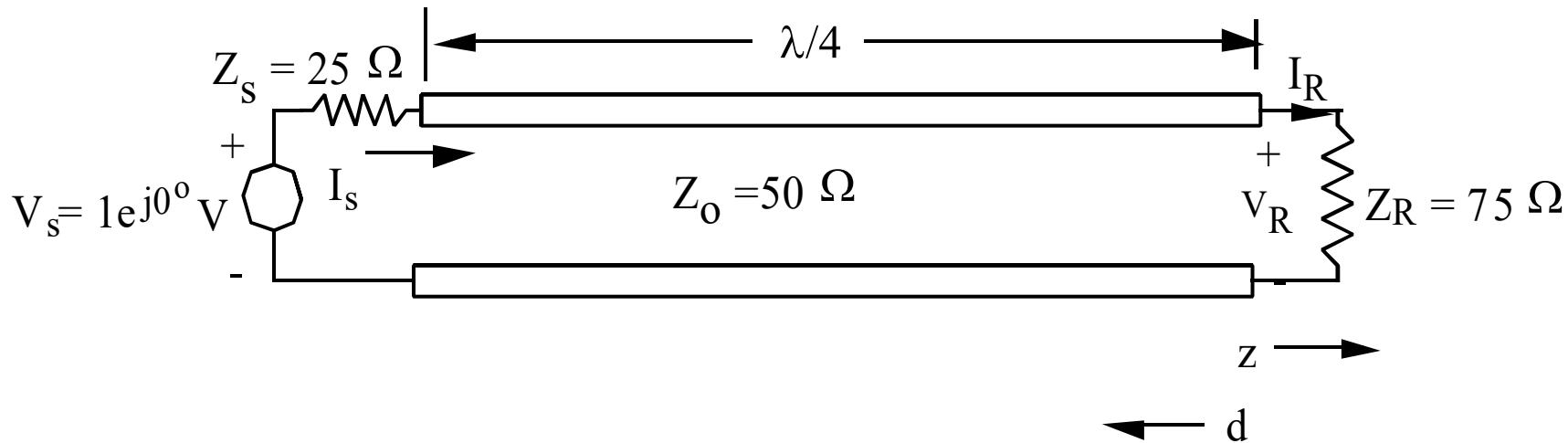

A signal generator having an internal resistance  $Z_s = 25 \Omega$  and an open circuit phasor voltage  $V_s = 1e^{j0^\circ}$  volt is connected to a  $50\text{-}\Omega$  lossless transmission line as shown in the above picture. The load impedance is  $Z_R = 75 \Omega$  and the line length is  $\lambda/4$ .

Find the magnitude and phase of the load current  $I_R$ .

# TL Example – Cont'

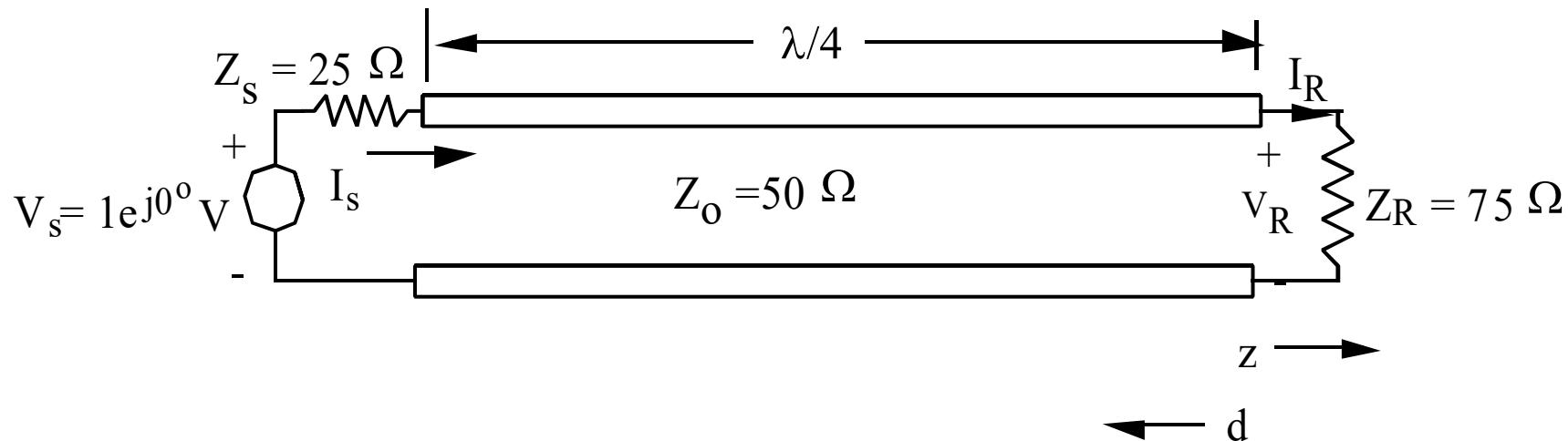

$$V_+ = \frac{T_s V_s e^{-j\beta l}}{1 - \Gamma_R \Gamma_s e^{-2j\beta l}} \quad T_s = \frac{Z_o}{Z_s + Z_o} = \frac{50}{50 + 25} = 2/3$$

$$\Gamma_s = \frac{Z_s - Z_o}{Z_s + Z_o} = \frac{25 - 50}{25 + 50} = -1/3 \quad \Gamma_R = \frac{Z_R - Z_o}{Z_R + Z_o} = \frac{75 - 50}{75 + 50} = 1/5$$

# TL Example – Cont'

$$\beta l = \frac{2\pi}{\lambda} \frac{\lambda}{4} = \frac{\pi}{2} \Rightarrow e^{-j\beta l} = -j$$

$$V_+ = \frac{(2/3)(1)(-j)}{1 - (-1/3)(1/5)(-1)} = \frac{-j2/3}{1 - 1/15} = -j5/7$$

$$V_+ = -j0.714285 \text{ V}$$

$$I_R = \frac{V_+}{Z_o} [1 - \Gamma_R] = -j \frac{0.714285}{50} [1 - 0.2] = -j \frac{0.714285 \times 0.8}{50}$$

$$I_R = -j0.014285 \text{ A}$$

# Frequency-Domain TL Solution

$$V(z) = V_+ e^{-j\beta z} \left[ 1 + \Gamma_R e^{+2j\beta z} \right]$$

$$I(z) = \frac{V_+ e^{-j\beta z}}{Z_o} \left[ 1 - \Gamma_R e^{+2j\beta z} \right]$$

$$V_+ = \frac{T_S V_S e^{-j\beta l}}{1 - \Gamma_S \Gamma_R e^{-2j\beta l}}$$

Magnitude of reflection coefficients at source and load is less than 1.

# Geometric Series Expansion

Since  $|\Gamma_S \Gamma_R e^{-2j\beta l}| \leq 1$

$V_+$  can be expanded in a geometric series form

$$V_+ = \frac{T_S V_S e^{-j\beta l}}{1 - \Gamma_S \Gamma_R e^{-2j\beta l}}$$

$$V_+ = T_S \sum_{k=0}^{\infty} V_S \Gamma_S^k \Gamma_R^k e^{-2j\beta kl} e^{-j\beta l}$$

$$V(z) = T_S \sum_{k=0}^{\infty} V_S \Gamma_S^k \Gamma_R^k e^{-j\beta l(2k+1)} e^{-j\beta z} + T_S \sum_{k=0}^{\infty} V_S \Gamma_S^k \Gamma_R^{k+1} e^{-j\beta l(2k+1)} e^{+j\beta z}$$

$$\beta = \frac{\omega}{v}$$

$$V(z) = T_S \sum_{k=0}^{\infty} V_S \Gamma_S^k \Gamma_R^k e^{-j\frac{\omega}{v}[z+(2k+1)l]} + T_S \sum_{k=0}^{\infty} V_S \Gamma_S^k \Gamma_R^{k+1} e^{-j\frac{\omega}{v}[z+(2k+1)l]}$$

# TL Time-Domain Solution

$$v(z, t) = T_S \sum_{k=0}^{\infty} \Gamma_S^k \Gamma_R^k v_s \left( t - \frac{(2k+1)l + z}{v_o} \right)$$

$$+ T_S \sum_{k=0}^{\infty} \Gamma_S^k \Gamma_R^{k+1} v_s \left( t - \frac{(2k+1)l - z}{v_o} \right)$$

at  $z=0$

$$v(0, t) = T_S \sum_{k=0}^{\infty} \Gamma_S^k \Gamma_R^k v_s \left( t - \frac{(2k+1)l}{v_o} \right)$$

$$+ T_S \sum_{k=0}^{\infty} \Gamma_S^k \Gamma_R^{k+1} v_s \left( t - \frac{(2k+1)l}{v_o} \right)$$

# TL Time-Domain Solution

At  $z=-l$

$$v(-l, t) = T_S \sum_{k=0}^{\infty} \Gamma_S^k \Gamma_R^k v_s \left( t - \frac{(2k+1)l + l}{v_o} \right)$$

$$+ T_S \sum_{k=0}^{\infty} \Gamma_S^k \Gamma_R^{k+1} v_s \left( t - \frac{(2k+1)l + l}{v_o} \right)$$


$$v(-l, t) = T_S \sum_{k=0}^{\infty} \Gamma_S^k \Gamma_R^k v_s \left( t - \frac{2kl}{v_o} \right)$$

$$+ T_S \sum_{k=0}^{\infty} \Gamma_S^k \Gamma_R^{k+1} v_s \left( t - \frac{2(k+1)l}{v_o} \right)$$

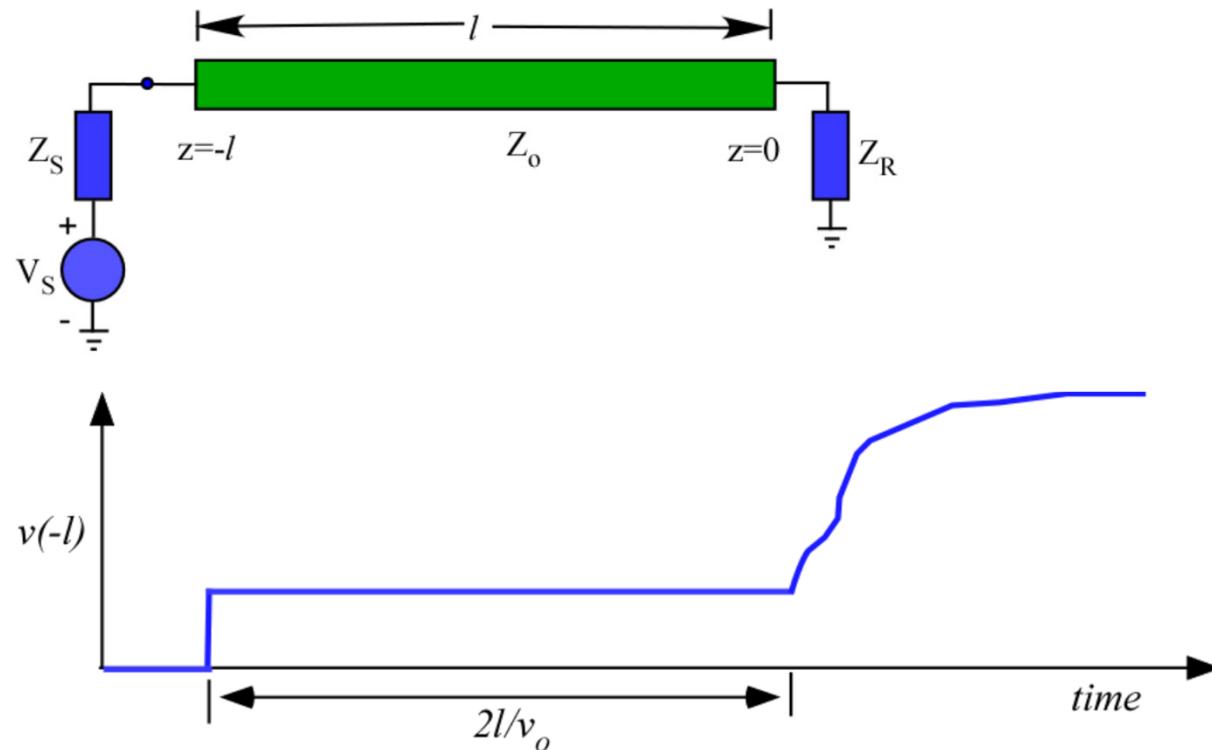
# TL - Time-Domain Reflectometer

For TDR,  $Z_S = Z_o \rightarrow \Gamma_S = 0$ , and retain only  $k=1$

$$v(-l, t) = T_S v_s(t) + T_S \Gamma_R v_s\left(t - \frac{2l}{v_o}\right)$$




# Wave Shifting Method

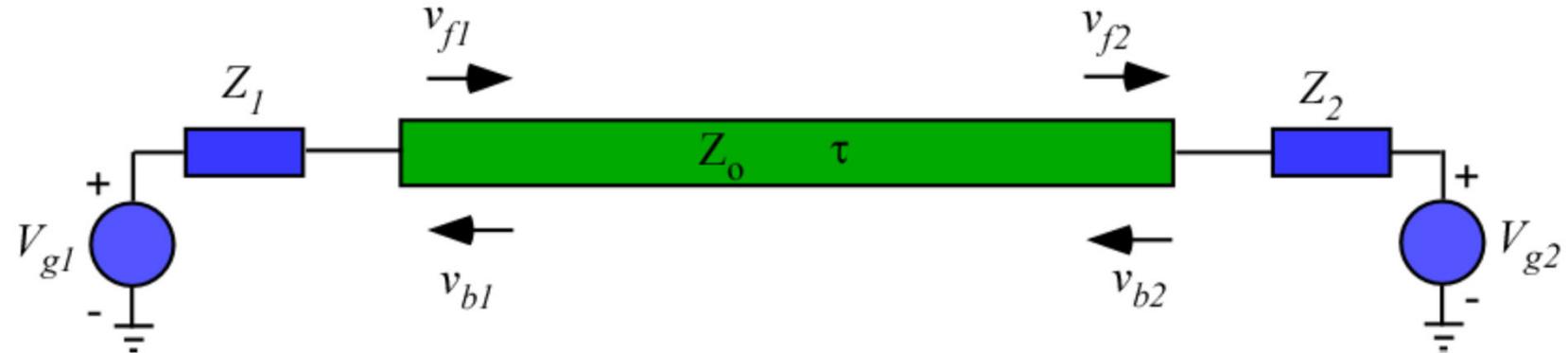

- $v_{f1}(t)$  Forward traveling wave at port 1 (measured at near end of line)
- $v_{f2}(t)$  Forward traveling wave at port 2 (measured at far end of line)
- $v_{b1}(t)$  Backward traveling wave at port 1 (measured at near end of line)
- $v_{b2}(t)$  Backward traveling wave at port 2 (measured at far end of line)

# Wave Shifting Solution\*

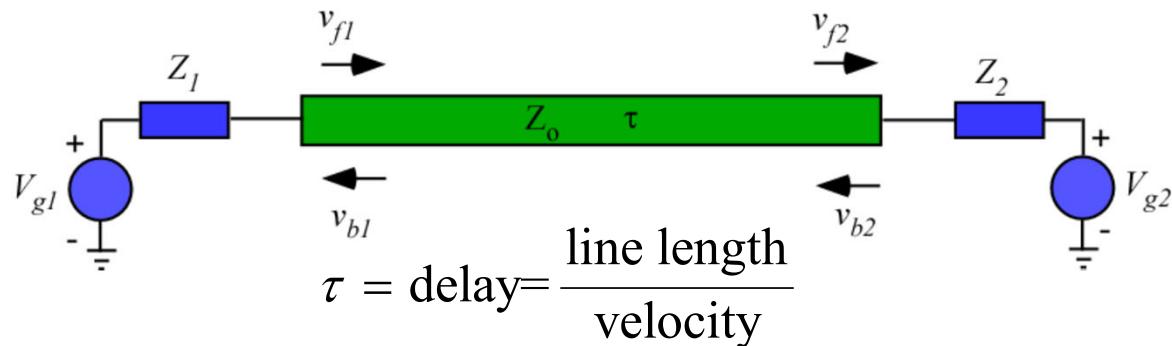

$$v_{f1}(t) = \Gamma_1 v_{b2}(t - \tau) + T_1 V_{g1}(t)$$

$$v_{b2}(t) = \Gamma_2 v_{f1}(t - \tau) + T_2 V_{g2}(t)$$

$$v_{f2}(t) = v_{f1}(t - \tau)$$

$$v_{b1}(t) = v_{b2}(t - \tau)$$

$$v_1(t) = v_{f1}(t) + v_{b1}(t)$$

$$v_2(t) = v_{f2}(t) + v_{b2}(t)$$

$$\Gamma_1 = \frac{Z_1 - Z_o}{Z_1 + Z_o}$$

$$T_1 = \frac{Z_o}{Z_1 + Z_o}$$

$$\Gamma_2 = \frac{Z_2 - Z_o}{Z_2 + Z_o}$$

$$T_2 = \frac{Z_o}{Z_2 + Z_o}$$

\*Schutt-Aine & Mittra, *Trans. Microwave Theory Tech.*, pp. 529-536, vol. 36 March 1988.

# Frequency Dependence of Lumped Circuit Models

- At higher frequencies, a lumped circuit model is no longer accurate for interconnects and one must use a distributed model
- Transition frequency depends on the dimensions and relative magnitude of the interconnect parameters.

$$f \approx \frac{0.3 \times 10^9}{10d\sqrt{\epsilon_r}}$$

$$t_r \approx \frac{0.35}{f}$$

# Lumped Circuit or Transmission Line?

- **Determine frequency or bandwidth of signal**
  - RF/Microwave:  $f = \text{operating frequency}$
  - Digital:  $f = 0.35/t_r$
- **Determine the propagation velocity and wavelength**
  - Material medium  $v = c/(\epsilon_r)^{1/2}$
  - Obtain wavelength  $\lambda = v/f$
- **Compare wavelength with feature size**
  - If  $\lambda \gg d$ , use lumped circuit:  $L_{\text{tot}} = L^* \text{ length}$ ,  $C_{\text{tot}} = C^* \text{ length}$
  - If  $\lambda \approx 10d$  or  $\lambda < 10d$ , use transmission-line model

# Frequency Dependence of Lumped Circuit Models

<u>Level</u>	<u>Dimension</u>	<u>Frequency</u>	<u>Edge rate</u>
PCB line	10 in	> 55 MHz	< 7ns
Package	1 in	> 400 MHz	< 0.9 ns
VLSI int*	100 um	> 8 GHz	< 50 ps

\* Using RC criterion for distributed effect