

# **ECE 546**

## **Lecture 10**

# **MOS Transistors**

Spring 2024


Jose E. Schutt-Aine  
Electrical & Computer Engineering  
University of Illinois  
[jesa@illinois.edu](mailto:jesa@illinois.edu)

# MOS Technologies

Parameter	0.8 $\mu\text{m}$ NMOS	0.8 $\mu\text{m}$ PMOS	0.5 $\mu\text{m}$ NMOS	0.5 $\mu\text{m}$ PMOS	0.25 $\mu\text{m}$ NMOS	0.25 $\mu\text{m}$ PMOS	0.18 $\mu\text{m}$ NMOS	0.18 $\mu\text{m}$ PMOS	0.13 $\mu\text{m}$ NMOS	0.13 $\mu\text{m}$ PMOS	65 nm NMOS	65 nm PMOS	28 nm NMOS	28 nm PMOS
$t_{\text{ox}}$ (nm)	15	15	9	9	6	6	4	4	2.7	2.7	1.4	1.4	1.4	1.4
$C_{\text{ox}}$ (fF/ $\mu\text{m}^2$ )	2.3	2.3	3.8	3.8	5.8	5.8	8.6	8.6	12.8	12.8	25	25	34	34
$\mu$ (cm <sup>2</sup> /V.s)	550	250	500	180	460	160	450	100	400	100	216	40	220	200
$\mu C_{\text{ox}}$ ( $\mu\text{A}/\text{V}^2$ )	127	58	190	68	267	93	387	86	511	128	540	100	750	680
$V_{\text{to}}$ (V)	0.7	-0.7	0.7	-0.8	0.5	-0.6	0.5	-0.5	0.4	-0.4	0.35	-0.35	0.3	-0.3
$V_{\text{DD}}$ (V)	5	5	3.3	3.3	2.5	2.5	1.8	1.8	1.3	1.3	1	1	0.9	0.9
$ V_{\text{A}} $ (V/ $\mu\text{m}$ )	25	20	20	10	5	6	5	6	5	6	3	3	1.5	1.5
$C_{\text{ov}}$ (fF/ $\mu\text{m}$ )	0.2	0.2	0.4	0.4	0.3	0.3	0.37	0.33	0.36	0.33	0.33	0.31	0.4	0.4

22nm BSIM4  
 32nm BSIM4  
 45nm BSIM4  
 65nm BSIM4  
 90nm BSIM4  
 130nm BSIM4  
 90nm BSIM3  
 130nm BSIM3  
 180nm BSIM3

# NMOS Transistor

 


- **NMOS Transistor**


- N-Channel MOSFET
- Built on p-type substrate
- MOS devices are smaller than BJTs
- MOS devices consume less power than BJTs

# NMOS Transistor - Layout


Top View

 

Cross Section

 

# MOS Regions of Operation

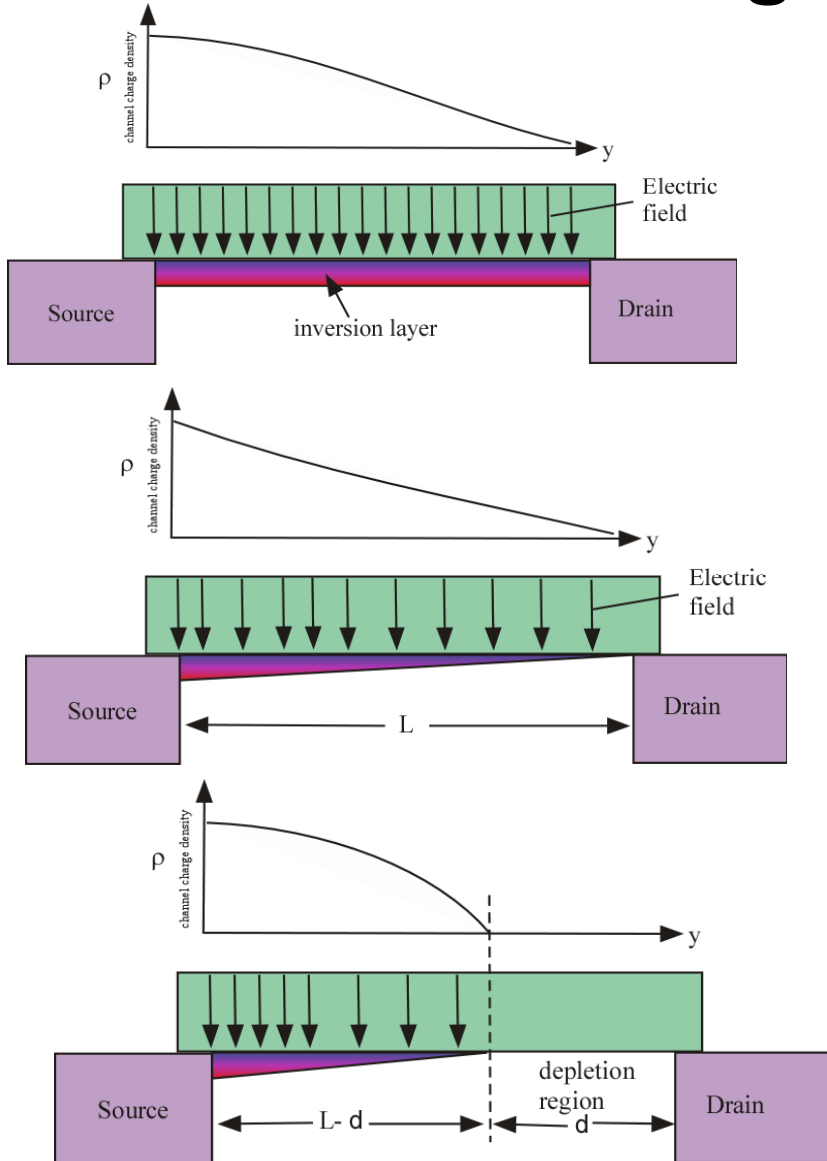

Triode

**Resistive**

$$V_{GS} > V_T$$

$$V_{DS} \text{ small}$$

**Nonlinear**

$$V_{GS} > V_T$$

$$V_{DS} < (V_{GS} - V_T)$$

Active

**Saturation**


$$V_{GS} > V_T$$

$$V_{DS} \geq V_{GS} - V_T$$

# MOS Transistor Operation

- **As  $V_G$  increases from zero**
  - Holes in the p substrate are repelled from the gate area leaving negative ions behind
  - A depletion region is created
  - No current flows since no carriers are available
- **As  $V_G$  increases**
  - The width of the depletion region and the potential at the oxide-silicon interface also increase
  - When the interface potential reaches a sufficiently positive value, electrons flow in the “*channel*”. The transistor is turned on
- **As  $V_G$  rises further**
  - The charge in the depletion region remains relatively constant
  - The channel current continues to increase

# MOS – Triode Region - 1

 

$$I_D = \mu \frac{W}{L} C_{ox} [(V_{GS} - V_T) V_{DS}]$$

$$V_{DS} \ll (V_{GS} - V_T)$$

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = \frac{3.9\epsilon_o}{t_{ox}}$$

$C_{ox}$ : gate oxide capacitance


$\mu$ : electron mobility

$L$ : channel length

$W$ : channel width

$V_T$ : threshold voltage

# MOS – Triode Region

 


FET is like a linear resistor with

$$r_{ds} = \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)}$$



# MOS – Triode Region - 2

 

$$V_{GS} > V_T$$

$$V_{DS} < (V_{GS} - V_T)$$


$$I_D = \mu_n C_{ox} \frac{W}{L} \left[ (V_{GS} - V_T) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$

- Charge distribution is nonuniform across channel
- Less charge induced in proximity of drain

# MOS – Active Region

Saturation occurs at pinch off when

$$V_{DS} = (V_{GS} - V_T) = V_{DSP}$$

 

$$V_{GS} > V_T$$

$$V_{DS} > (V_{GS} - V_T)$$

(saturation)


$$I_D = \mu_n C_{ox} \frac{W}{2L} (V_{GS} - V_T)^2$$

# MOS Threshold Voltage

The value of  $V_G$  for which the channel is “*inverted*” is called the threshold voltage  $V_T$  (or  $V_t$ ).

- **Characteristics of the threshold voltage**
  - Depends on equilibrium potential
  - Controlled by inversion in channel
  - Adjusted by implantation of dopants into the channel
  - Can be positive or negative
  - Influenced by the body effect

# MOS – Active Region

 

- **Saturation**
  - Channel is pinched off
  - Increase in  $V_{DS}$  has little effect on  $i_D$
  - Square-law behavior wrt  $(V_{GS} - V_T)$
  - Acts like a current source

# Body Effect

- **The body effect**
  - $V_T$  varies with bias between source and body
  - Leads to modulation of  $V_T$


## Potential on substrate affects threshold voltage

$$V_T(V_{SB}) = V_{T0} + \gamma \left[ \left( 2|\phi_F| + V_{SB} \right)^{1/2} - \left( 2|\phi_F| \right)^{1/2} \right]$$

$$|\phi_F| = \left( \frac{kT}{q} \right) \ln \left( \frac{N_a}{n_i} \right) \quad \text{Fermi potential of material}$$

$$\gamma = \frac{\left( 2qN_a\epsilon_s \right)^{1/2}}{C_{ox}} \quad \text{Body bias coefficient}$$

# Channel-Length Modulation

 


With depletion layer widening, the channel length is in effect reduced from  $L$  to  $L - \Delta L$  → Channel-length modulation

This leads to the following I-V relationship

$$i_D = \frac{1}{2} k'_n \frac{W}{L} (v_{GS} - V_T)^2 (1 + \lambda v_{DS})$$


Where  $\lambda$  is a process technology parameter

# Channel-Length Modulation

 


Channel-length modulation causes  $i_D$  to increase with  $v_{DS}$  in saturation region


# Gate Capacitance

 

$$V_{GT} < 0$$

 

$$V_{GT} > 0, V_{DS} \text{ small}$$

 

$$V_{GT} > 0, V_{DS} \text{ large}$$

- **Capacitance**

- Depends on bias
- Fringing fields are present
- Account for overlap C



# Capacitance

- **Gate Capacitance**


- $C_G$  determines the amount of charge to switch gate
- Several distributed components
- Large discontinuity as device turns on
- At saturation capacitance is entirely between gate and source

$$C_{gs} = C_{gso} + \frac{2}{3}WLC_{ox} \left[ 1 - \left( \frac{1-X}{2-X} \right)^2 \right]$$

Define  $X = \frac{V_{DS}}{V_{GS} - V_T}$



$$C_{gd} = C_{gdo} + \frac{2}{3}WLC_{ox} \left[ 1 - \left( \frac{1}{2-X} \right)^2 \right]$$

# MOS Capacitances

 


- **Expect capacitance between every two of the four terminals.**

# PMOS Transistor

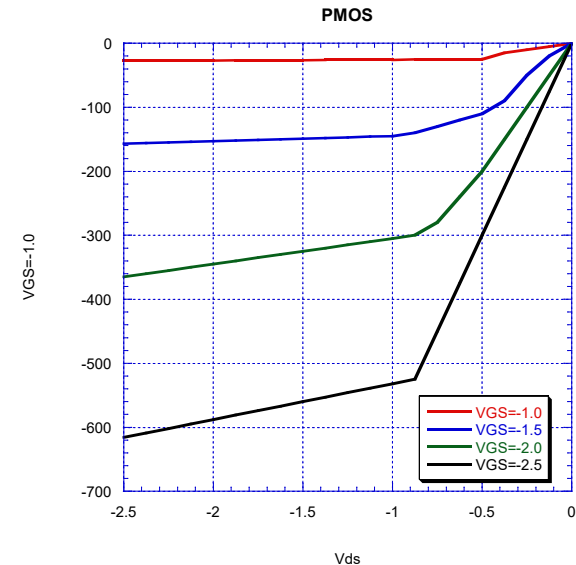 

- All polarities are reversed from nMOS
- $V_{GS}$ ,  $V_{DS}$  and  $V_t$  are negative
- Current  $i_D$  enters source and leaves through drain
- Hole mobility is lower  $\Rightarrow$  low transconductance
- nMOS favored over pMOS

# Complementary MOS

 

- **CMOS Characteristics**

- Combine nMOS and pMOS transistors
- pMOS size is larger for electrical symmetry

# CMOS

- **Advantages**

- Virtually, no DC power consumed
- No DC path between power and ground
- Excellent noise margins ( $V_{OL}=0$ ,  $V_{OH}=V_{DD}$ )
- Inverter has sharp transfer curve

- **Drawbacks**

- Requires more transistors
- Process is more complicated
- pMOS size larger to achieve electrical symmetry
- Latch up

# Voltage Transfer Characteristics (VTC)


The static operation of a logic circuit is determined by its VTC

- In low state: noise margin is  $NM_L$

$$NM_L = V_{IL} - V_{OL}$$

- In high state: noise margin is  $NM_H$


$$NM_H = V_{OH} - V_{IH}$$

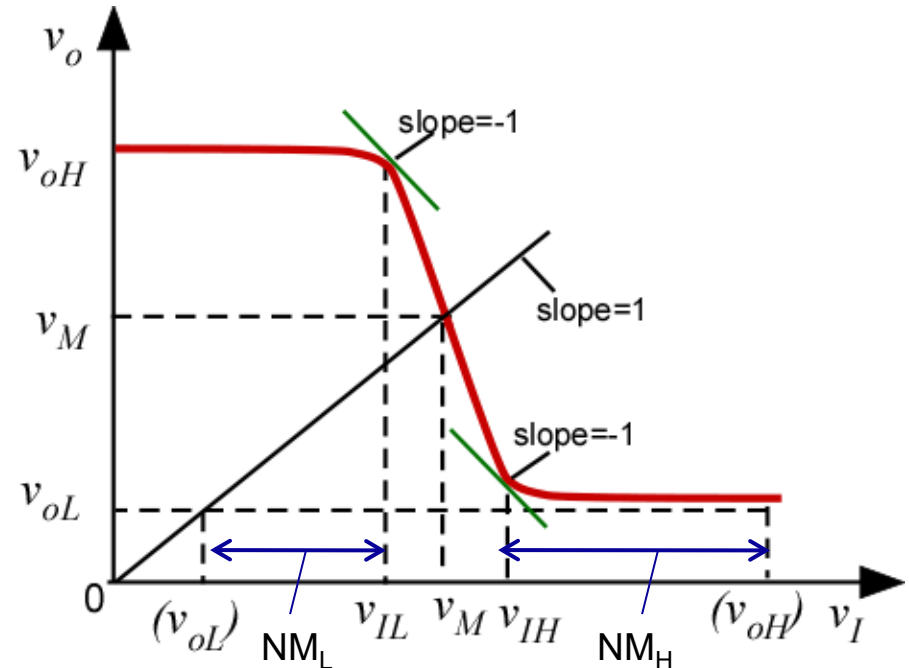

$V_{IL}$  and  $V_{IH}$  are the points where the slope of the VTC=-1

Optimum:  $NM_L = NM_H = V_{DD} / 2$

# Switching Time & Propagation Delay

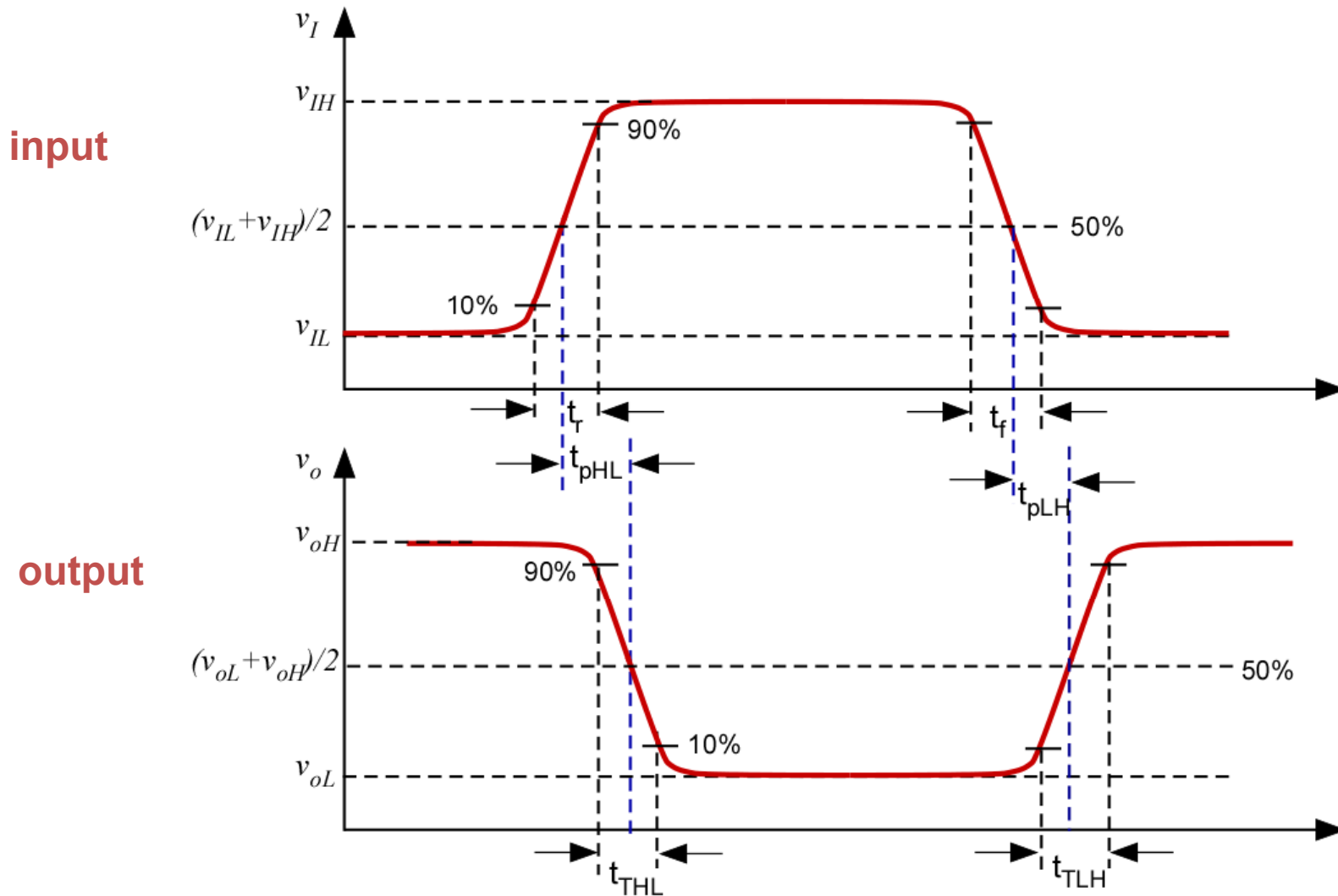

# Switching Time & Propagation Delay

$t_r$ =rise time (from 10% to 90%)

$t_f$ =fall time (from 90% to 10%)


$t_{pLH}$ =low-to-high propagation delay

$t_{pHL}$ =high-to-low propagation delay


Inverter propagation delay: 
$$t_p = \frac{1}{2} (t_{pLH} + t_{pHL})$$



# NMOS Switch

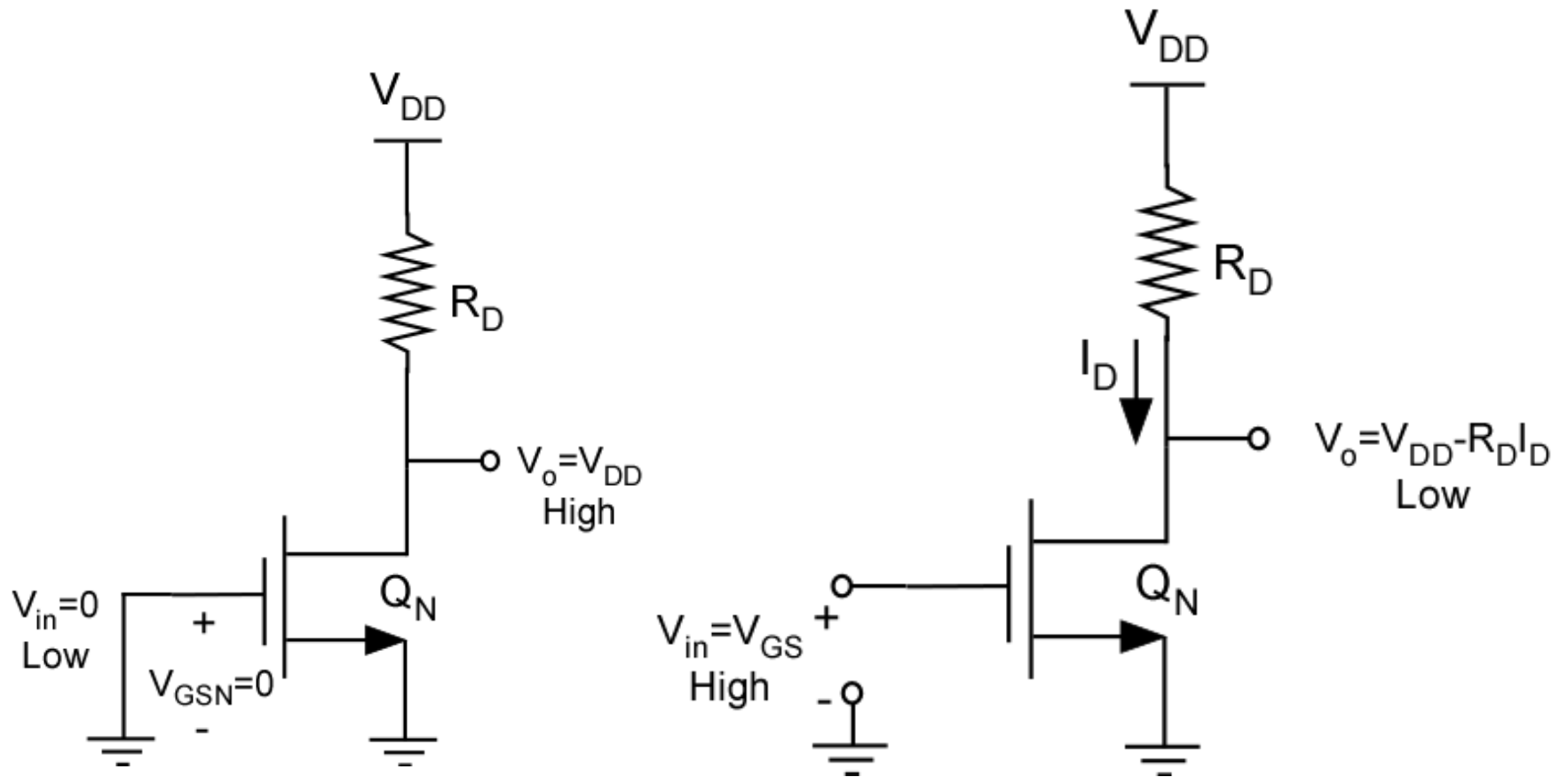

# CMOS Switch

 

CMOS switch is called an inverter

The body of each device is connected to its source → NO BODY EFFECT

# CMOS Switch – Input Low

NMOS


$$V_{GSN} < V_{TN} \Rightarrow \text{OFF}$$

$r_{dsn}$  high

PMOS

$$r_{dsp} = \frac{1}{k'_p \left(\frac{W}{L}\right)_p (V_{DD} - |V_{TP}|)}$$

$r_{dsp}$  is low

 


# CMOS Switch – Input High

NMOS

$$r_{dsn} = \frac{1}{k'_n \left(\frac{W}{L}\right)_n (V_{DD} - V_{TN})}$$

$r_{dsn}$  is low

 


PMOS

$$V_{GSP} > V_{TP} \Rightarrow OFF$$



$r_{dsp}$  high

# CMOS Inverter

 

$$r_{dsn} = \frac{1}{k'_N \left(\frac{W}{L}\right)_n (V_{DD} - V_T)}$$
  
$$r_{dsp} = \frac{1}{k'_P \left(\frac{W}{L}\right)_p (V_{DD} - V_T)}$$



**Short switching  
transient current  
→ low power**

# CMOS Inverter


## Advantages of CMOS inverter

- Output voltage levels are 0 and  $V_{DD}$  → signal swing is maximum possible
- Static power dissipation is zero
- Low resistance paths to  $V_{DD}$  and ground when needed
- High output driving capability → increased speed
- Input resistance is infinite → high fan-out

**Load driving capability of CMOS is high. Transistors can sink or source large load currents that can be used to charge and discharge load capacitances.**
 
# Matched CMOS Inverter VTC


CMOS inverter can be made to switch at specific threshold voltage by appropriately sizing the transistors



$$\left(\frac{W}{L}\right)_p = \frac{\mu_n}{\mu_p} \left(\frac{W}{L}\right)_n$$

**Symmetrical transfer characteristics is obtained via matching  $\rightarrow$  equal current driving capabilities in both directions (pull-up and pull-down)**

# CMOS Dynamic Operation

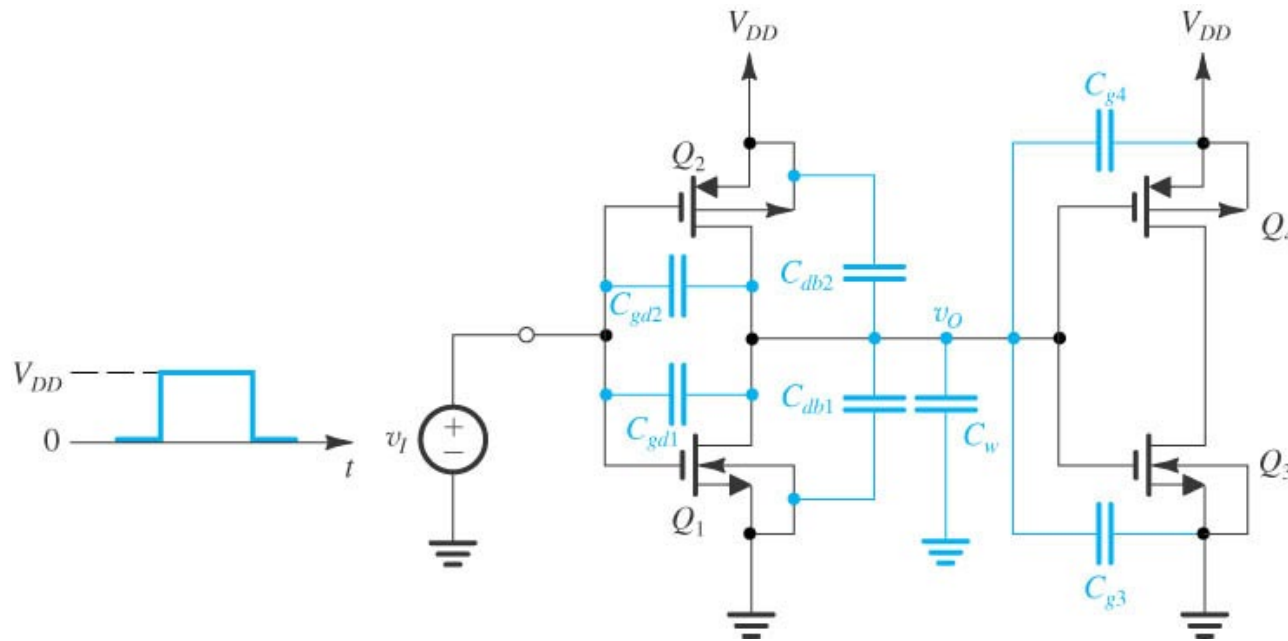

- Exact analysis is too tedious
- Replace all the capacitances in the circuit by a single equivalent capacitance  $C$  connected between the output node of the inverter and ground
- Analyze capacitively loaded inverter to determine propagation delay




# CMOS Dynamic Operation

$$t_P = \frac{1}{2} (t_{PHL} + t_{PLH})$$


- Components can be equalized by matching transistors
- $t_p$  is proportional to  $C \rightarrow$  reduce capacitance
- Larger  $V_{DD}$  means lower  $t_p$
- Conflicting requirements exist

# CMOS – Dynamic Power Dissipation

 
 
## In every cycle

- $Q_N$  dissipate  $\frac{1}{2} CV_{DD}^2$  of energy
- $Q_P$  dissipate  $\frac{1}{2} CV_{DD}^2$  of energy
- Total energy dissipation is  $CV_{DD}^2$



If inverter is switched at  $f$  cycles per second, dynamic power dissipation is:  $P_D = fCV_{DD}^2$

# Digital Logic - Generalization

De Morgan's Law

$$\overline{A + B + C + \dots} = \bar{A} \cdot \bar{B} \cdot \bar{C} \cdot \dots$$

$$\overline{A \cdot B \cdot C \cdot \dots} = \bar{A} + \bar{B} + \bar{C} + \dots$$


Distributive Law

$$AB + AC + BC + BD = A(B + C) + B(C + D)$$

- **General Procedure**
  1. Design PDN to satisfy logic function
  2. Construct PUN to be complementary of PDN in every way
  3. Optimize using distributive rule

# Pull-Down and Pull-Up

**PDN-parallel NMOS**

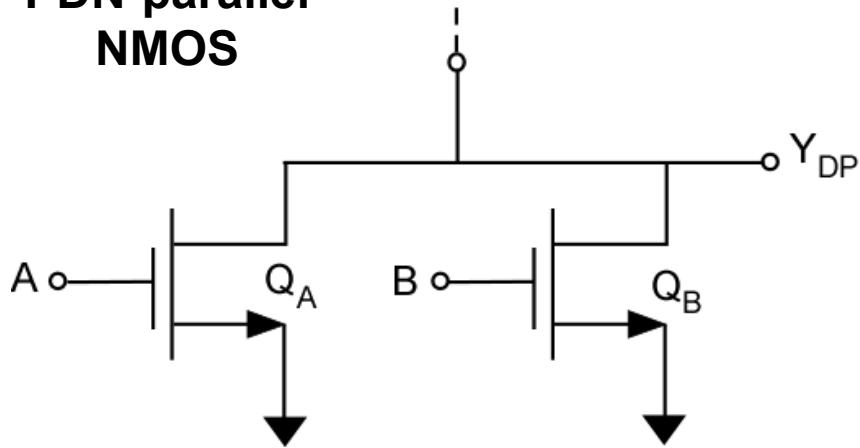


$$Y_{DP} = \overline{A + B}$$

	A	B	$Y_{DP}$
	0	0	1
	0	1	0
	1	0	0
	1	1	0

**Truth Tables**


**PUN-series PMOS**

 

$$Y_{US} = \overline{A} \overline{B}$$



	A	B	$Y_{US}$
	0	0	1
	0	1	0
	1	0	0
	1	1	0

# Two-Input NOR Gate

 

$$Y = \overline{A + B} = \overline{A} \overline{B}$$

# Pull-Down and Pull-Up

 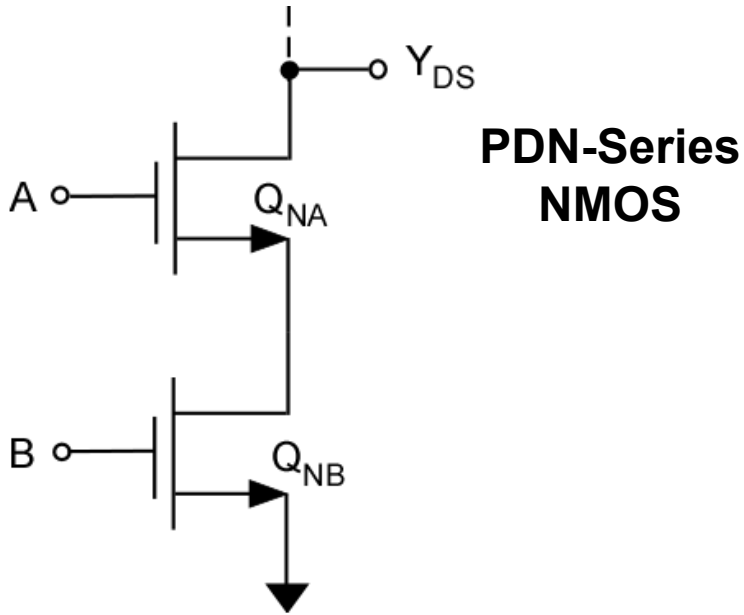

$$Y_{DS} = \overline{A} \overline{B}$$


	A	B	$Y_{DS}$
	0	0	1
	0	1	1
	1	0	1
	1	1	0

**Truth Tables**

$$Y_{UP} = \overline{A} + \overline{B}$$

	A	B	$Y_{UP}$
	0	0	1
	0	1	1
	1	0	1
	1	1	0

# Two-Input NAND Gate

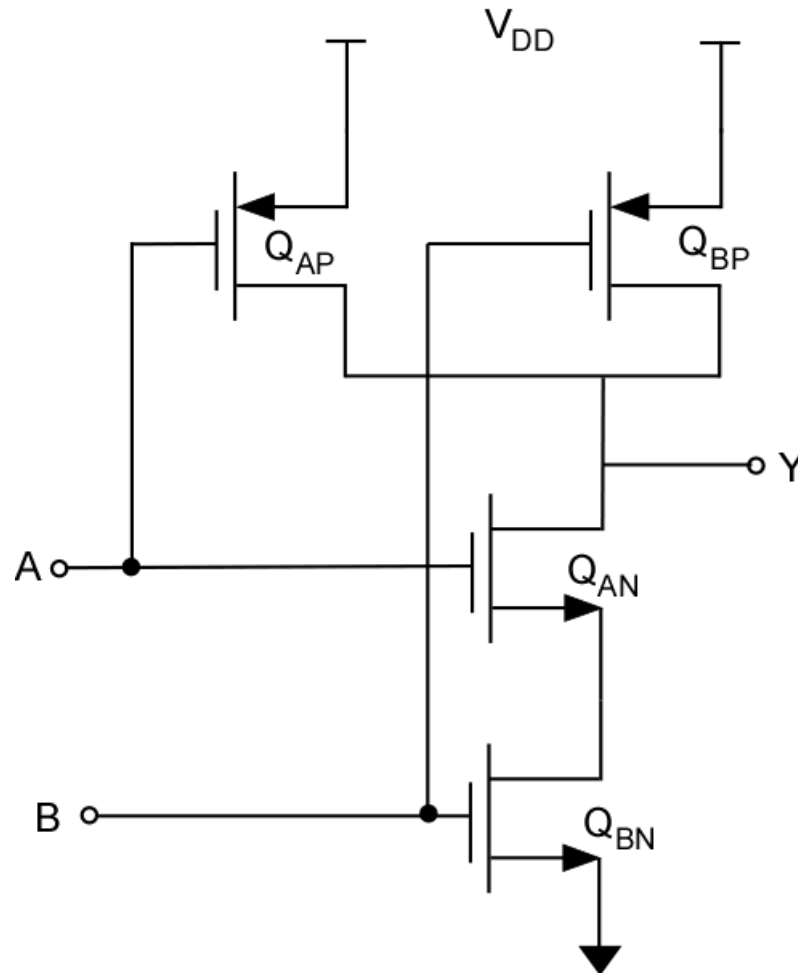


$$Y = \overline{AB} = \overline{A} + \overline{B}$$
 
# CMOS Logic Gate Circuits

- **Two Networks**

- Pull-down network (PDN) with NMOS
- Pull-up network (PUN) with PMOS



**PUN conducts when inputs are low and consists of PMOS transistors**

**PDN consists of NMOS transistors and is active when inputs are high**

- **PDN and PUN utilize devices**

- In parallel to form OR functions
- In series to form AND functions



# Basic Logic Function




Basic  
Function

**INVERTER**

**NOR**

**NAND**

Symbol

   

# Devices  
PUN

**1**  
**PMOS**

**2**  
**PMOS-Series**

**2**  
**PMOS-Parallel**

# Devices  
PDN

**1**  
**NMOS**

**2**  
**NMOS-Parallel**

**2**  
**NMOS-Series**

Truth  
Table

	A	Y
0	1	
1	0	


	A	B	Y
0	0	1	
0	1	0	
1	0	0	
1	1	0	

	A	B	Y
0	0	1	
0	1	1	
1	0	1	
1	1	0	

# Example

Implement the function


$$\bar{Y} = A\bar{B} + C$$

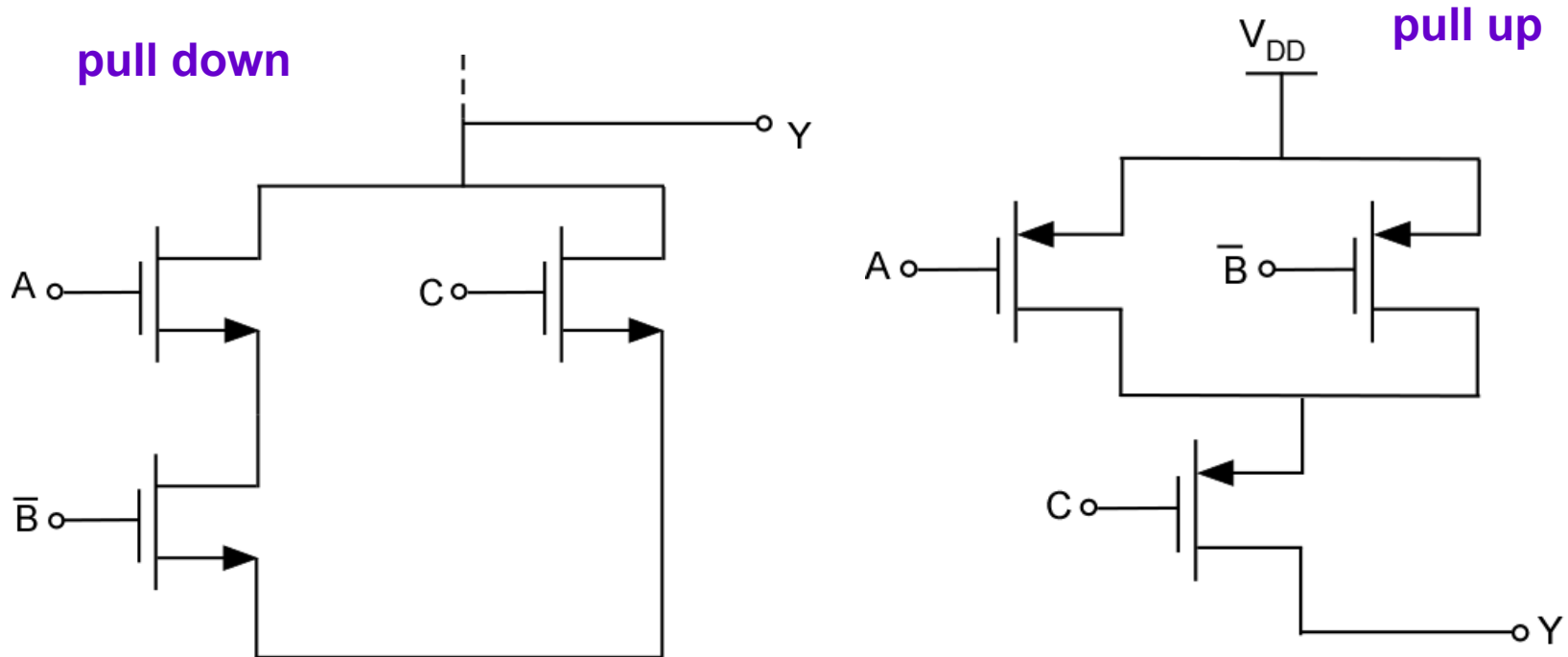

$$Y = \overline{A\bar{B} + C} = \overline{A\bar{B}} \cdot \bar{C} = (\bar{A} + B) \cdot \bar{C}$$
 
# Exclusive-OR (XOR) Function


$$Y = A\bar{B} + \bar{A}B \quad \bar{Y} = (\bar{A} + B)(A + \bar{B})$$



pull down

XOR

	A	B	Y
	0	0	0
	0	1	1
	1	0	1
	1	1	0

 

pull up