

# ECE 546

## Lecture 12

# Integrated Circuits

Spring 2024

Jose E. Schutt-Aine  
Electrical & Computer Engineering  
University of Illinois  
[jesa@illinois.edu](mailto:jesa@illinois.edu)

# Integrated Circuits


- **IC Requirements**

- Biasing of ICs is based on the use of constant current sources
- Use current mirrors
- Source circuits are used as loads


# Integrated Circuits

- **Analog Design Requirements**
  - Analog ICs may need resistors and capacitors for the design of amplifiers
  - Resistors and capacitors occupy the space of tens or hundreds of MOS devices
  - It is important to minimize their use



# Transistor Biasing

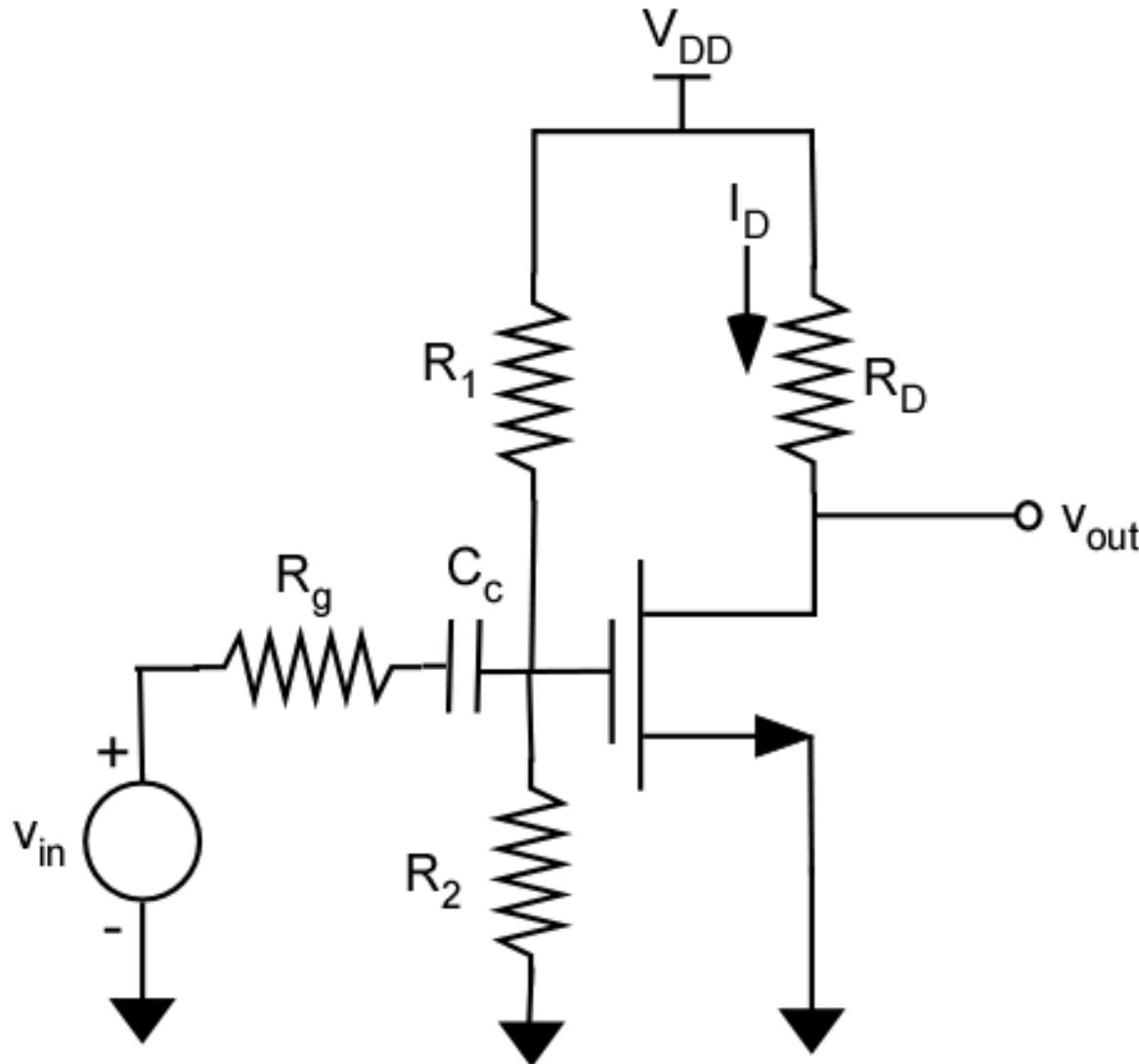

# Transistor Biasing

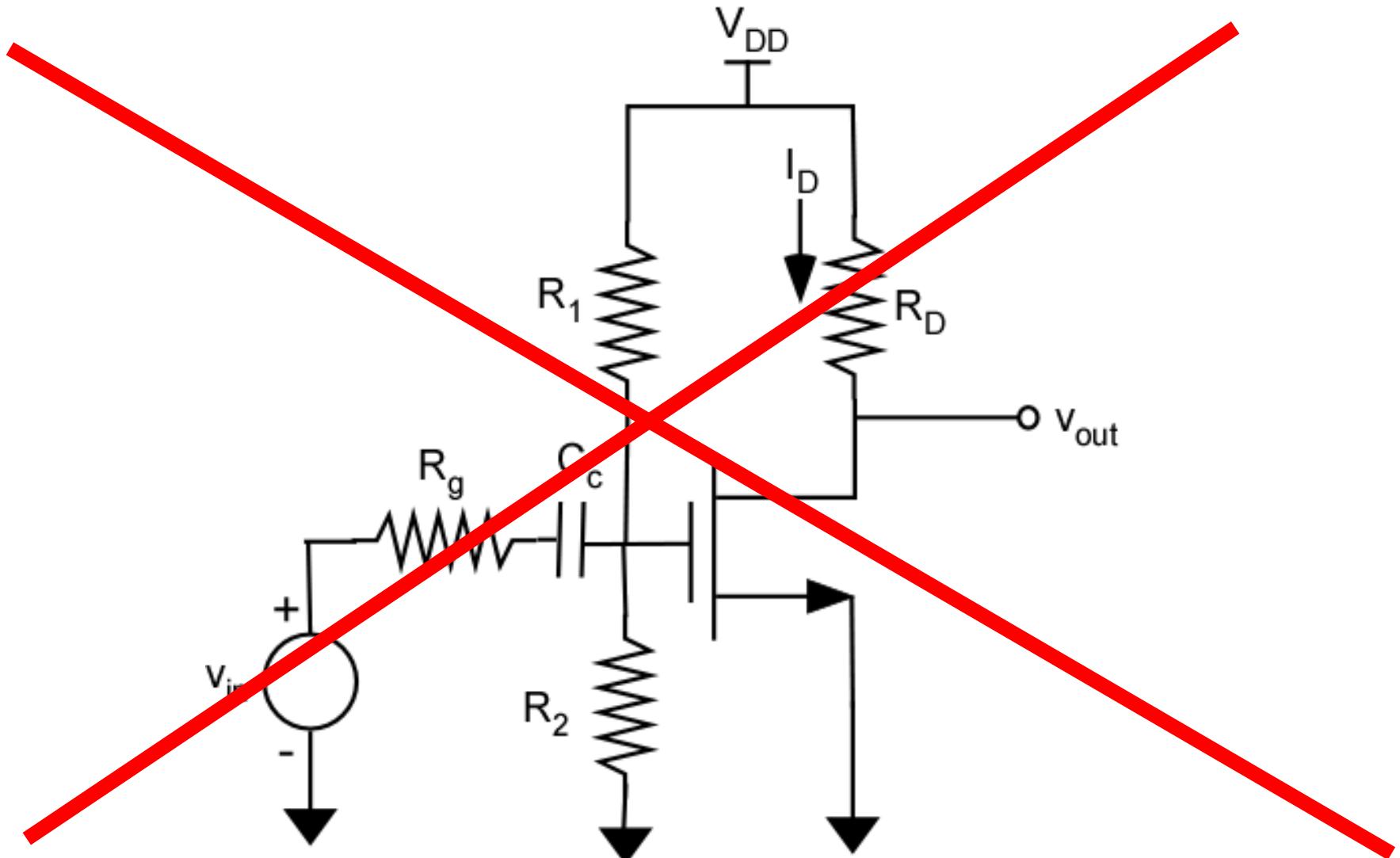


# Current Mirrors

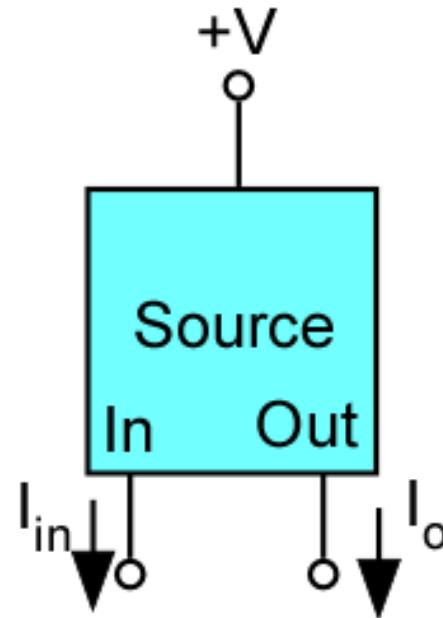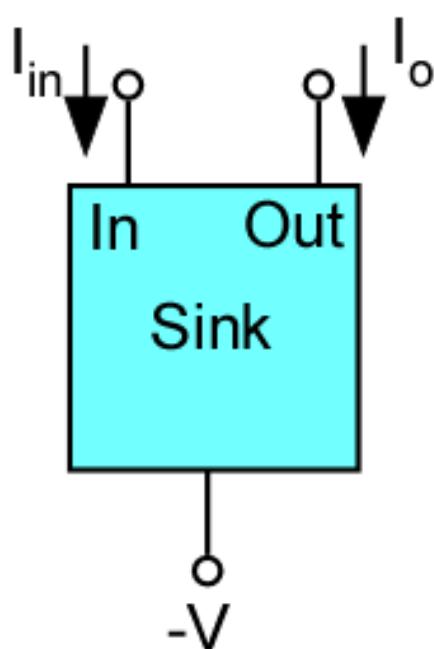

A current mirror will reproduce a reference current to the output while allowing the output voltage to assume any value within a specified range.  $I_o = K I_{in}$  where  $K$  is a factor that can be less than or equal or greater than 1

# MOS Current Mirror

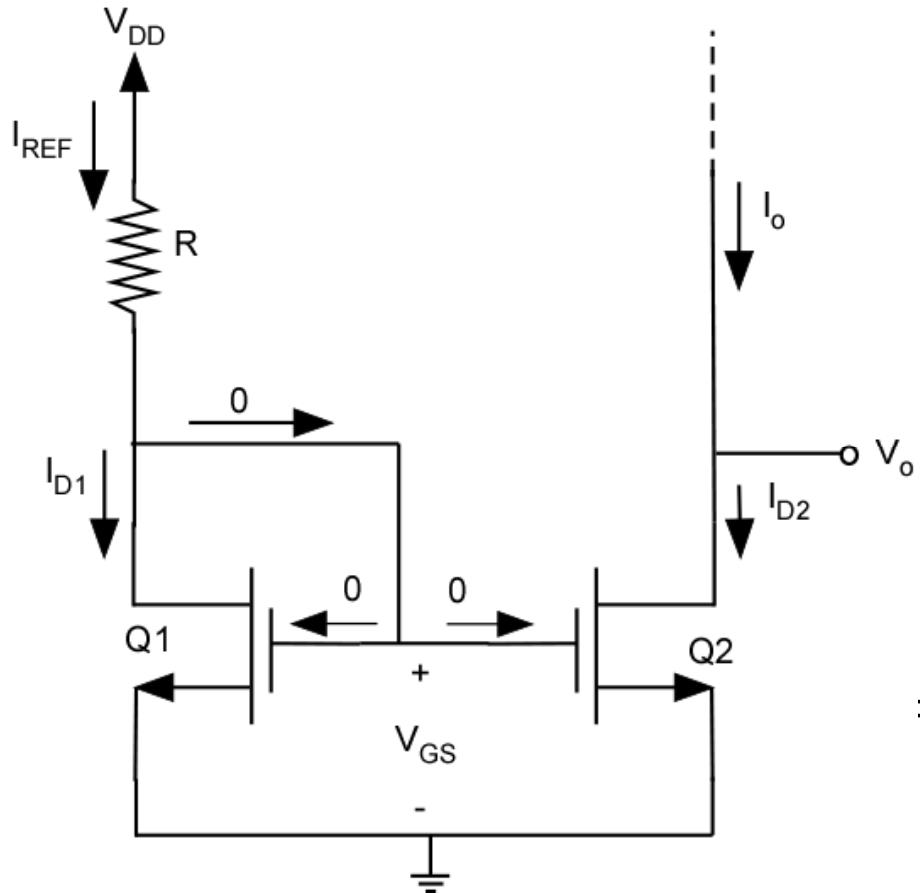

$$I_{D1} = \frac{1}{2} k_n \left( \frac{W}{L} \right)_1 (V_{GS} - V_{Tn})^2$$

$$I_{D1} = I_{REF} = \frac{V_{DD} - V_{GS}}{R}$$

$$= I_{D2} = \frac{1}{2} k_n \left( \frac{W}{L} \right)_2 (V_{GS} - V_{Tn})^2$$

R is usually external to IC

# MOS Current Mirror

**Assuming that the transistors are using the same process**

$$\frac{I_o}{I_{REF}} = \frac{(W/L)_2}{(W/L)_1} = \frac{W_2 L_1}{W_1 L_2}$$

- **Can be limited by**
  - Channel length modulation ( $\lambda$ )
  - Threshold voltage mismatch
  - Imperfect geometrical matching

# MOS Current Mirror

$$\frac{I_o}{I_{REF}} = \frac{W_2 L_1}{W_1 L_2} \left[ \frac{1 + \lambda(V_{DS2} - V_{DSP2})}{1 + \lambda(V_{DS1} - V_{DSP1})} \right]$$

- **Some Properties**

1. MOS current mirrors draw zero control current → better than BJT's
2. Matching of threshold voltages harder than in BJT's

# Example

A matched pair of MOSFETs are used in a current mirror with  $\lambda = 0.032 \text{ V}^{-1}$ ,  $\mu C_{ox} = 70 \text{ } \mu\text{A/V}^2$ ,  $W/2L = 10$ , and  $V_T = 0.9 \text{ V}$ . Find the value of  $R$  to create an input current of 100  $\mu\text{A}$ . Calculate the output current when  $V_o = 3 \text{ V}$ .

Use drain current equation in active region to calculate


$$I_{D1} = \frac{\mu C_{ox} W}{2L} [V_{GS} - V_T]^2 (1 + \lambda V_{DS1})$$

$$I_{D1} = 100 = 700 [V_{GS} - 0.9]^2 (1 + 0.032 * V_{GS})$$

We can now solve for the value of  $V_{GS}$

# Example

## MOS Current Mirror

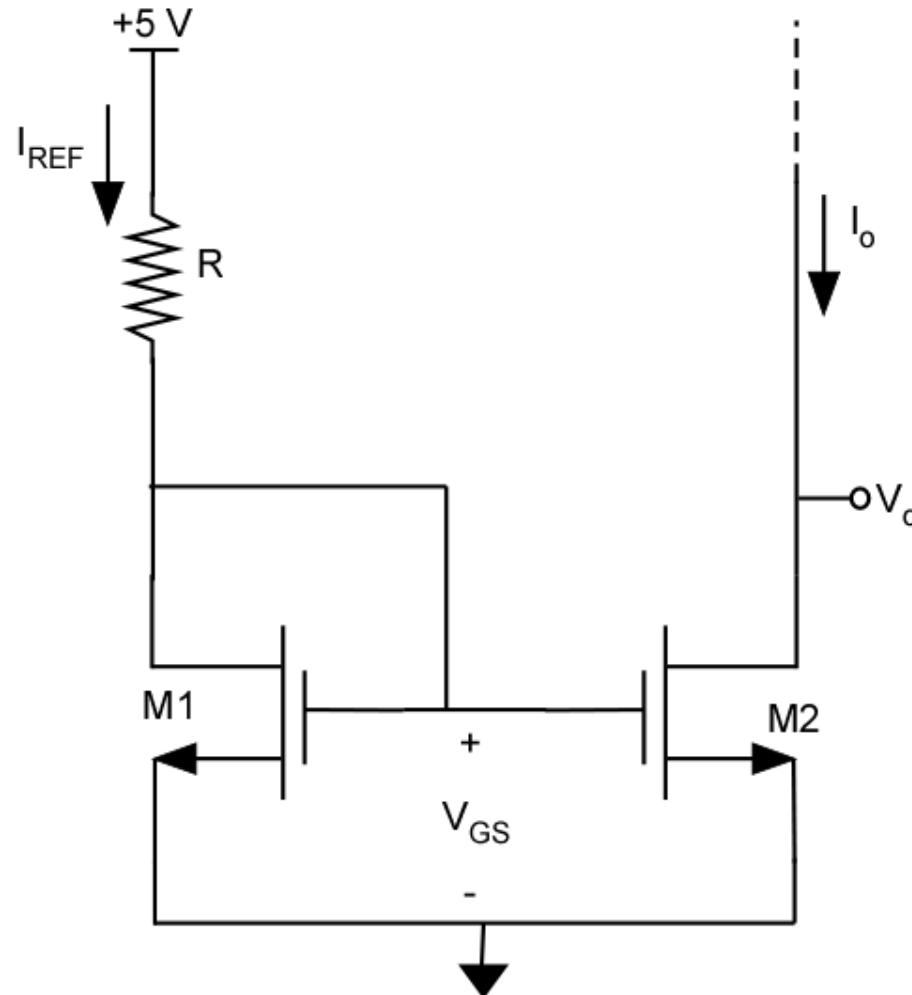

# Example

$$V_{GS} = 1.272 \text{ V}$$

The resistance needed is:

$$R = \frac{5 - V_{DS1}}{I_{D1}} = \frac{5 - 1.272}{0.1} = 37.2 \text{ k}\Omega$$


The output current is calculated from:

$$I_{D2} = \frac{\mu C_{ox} W}{2L} [V_{GS} - V_T]^2 (1 + \lambda V_{DS1})$$

$$I_{D2} = 700 [1.272 - 0.9]^2 (1 + 0.032 \times 3) = 106 \text{ } \mu\text{A}$$

$$I_{D2} = 106 \text{ } \mu\text{A}$$


# Ideal MOS Common Source CKT

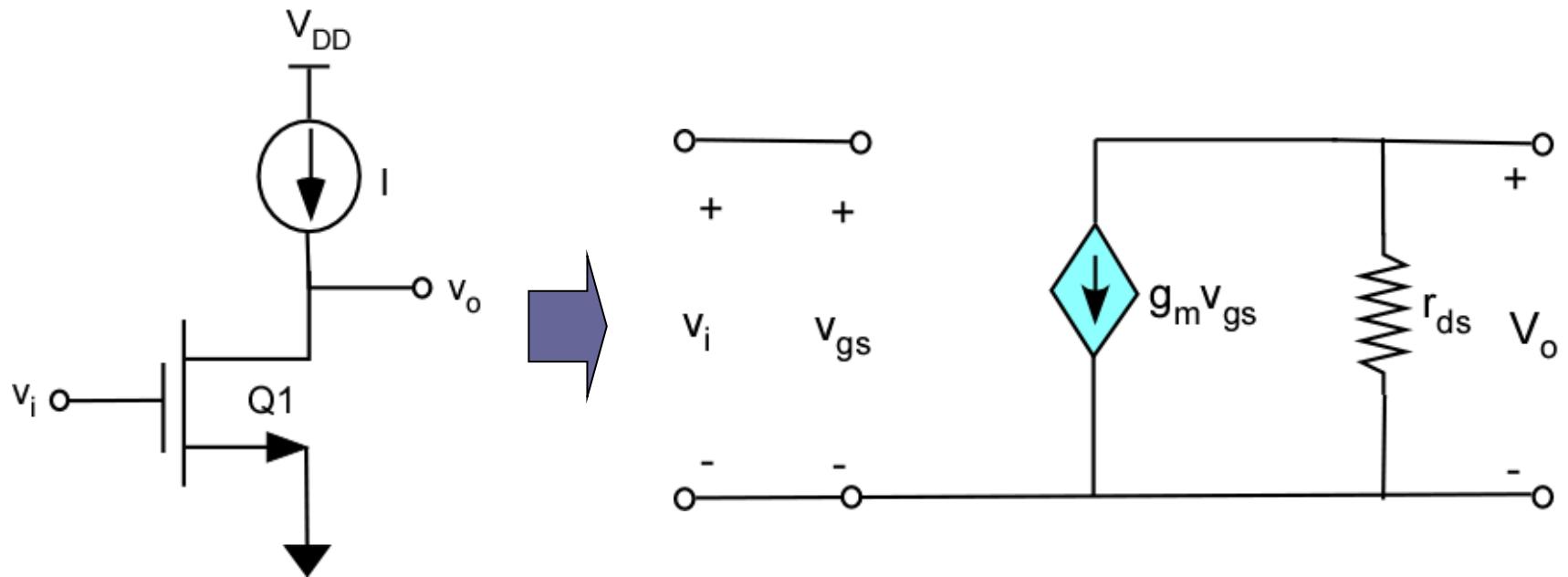

$$R_i = \infty, \quad A_{vo} = -g_m r_{ds}, \quad R_o = r_{ds}$$

*Intrinsic gain is  $g_m r_{ds}$*

# PMOS Implementation of Active Load

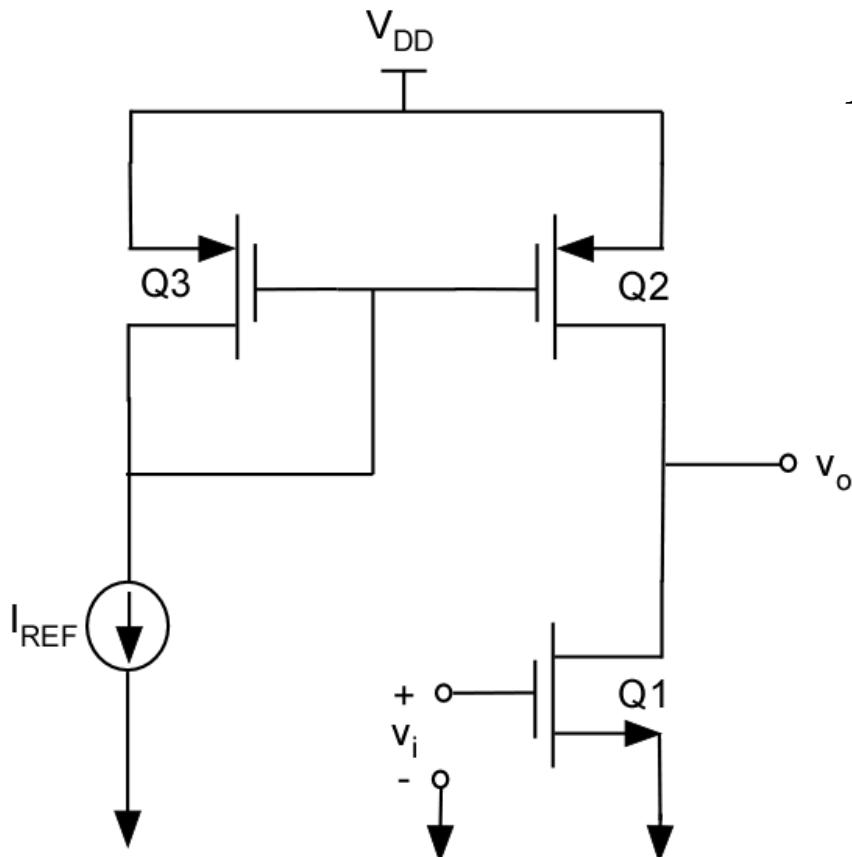

Let  $r_{ds1} = r_{o1}$  for  $Q_1$

$r_{ds2} = r_{o2}$  for  $Q_2$

then,  $R_{out} = r_{o1} \parallel r_{o2}$

$$A_{MB} = -g_{m1}R_{out}$$

$$\text{Let } g_{o1} = \frac{1}{r_{o1}} = g_{ds1}$$

$$g_{o2} = \frac{1}{r_{o2}} = g_{ds2}$$

# PMOS Implementation of Active Load

Can show that the 3dB point is given:

$$f_{2o} = \frac{(g_{01} + g_{02})}{2\pi(C_{db1} + C_{db2} + C_{gd1} + C_{gd2})}$$

**Large incremental load leads to high gain while maintaining acceptable DC current (resistor would not work)**