

ECE 546


Lecture -13

Scattering Parameters

Spring 2024


Jose E. Schutt-Aine
Electrical & Computer Engineering
University of Illinois
jesa@illinois.edu

Transfer Function Representation

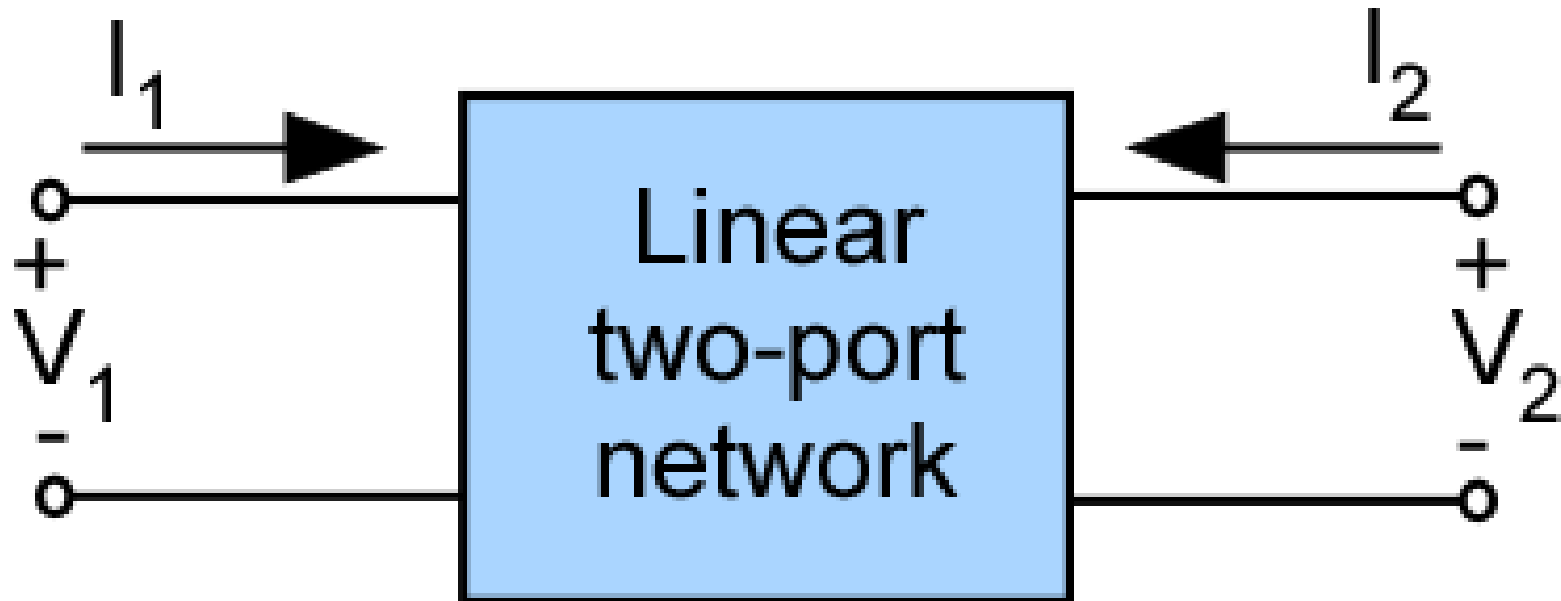

Use a two-terminal representation of system for input and output


Y-parameter Representation

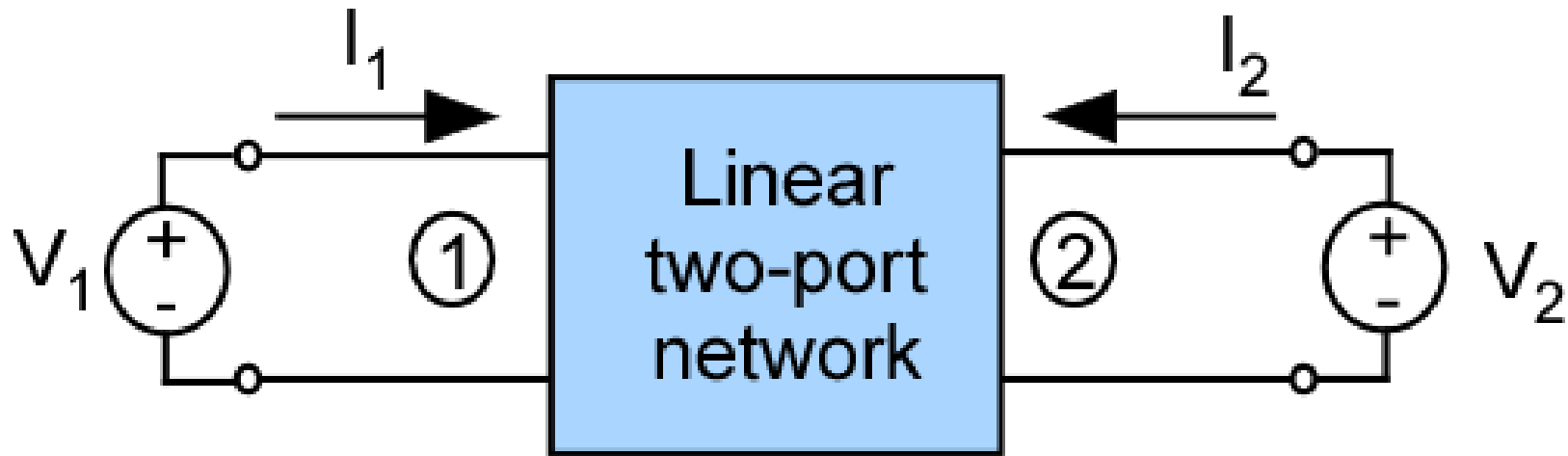

$$I_1 = y_{11}V_1 + y_{12}V_2$$

$$I_2 = y_{21}V_1 + y_{22}V_2$$


Y Parameter Calculations

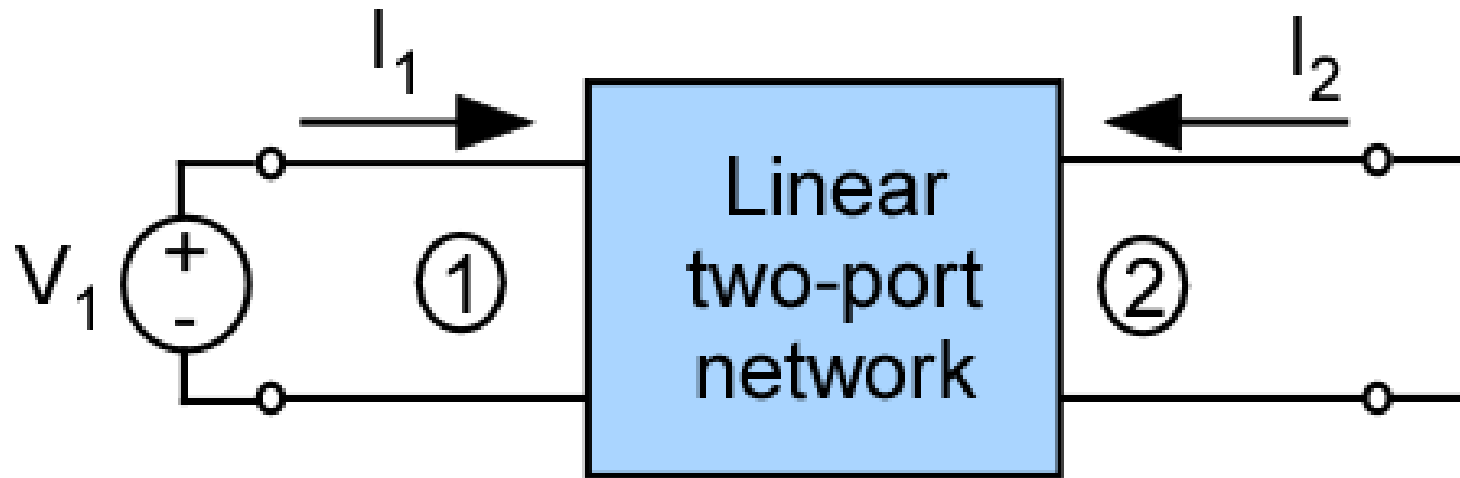

$$y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} \quad y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0}$$

To make $V_2=0$, place a short at port 2


Z Parameters

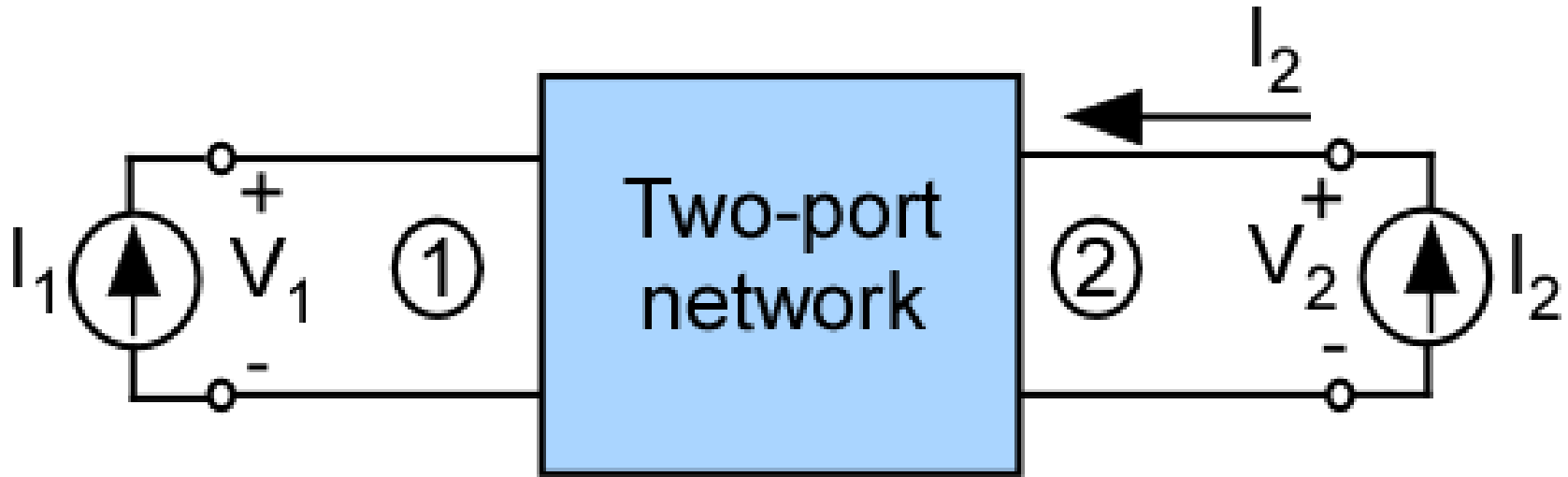

$$V_1 = z_{11}I_1 + z_{12}I_2$$

$$V_2 = z_{21}I_1 + z_{22}I_2$$


Z-parameter Calculations

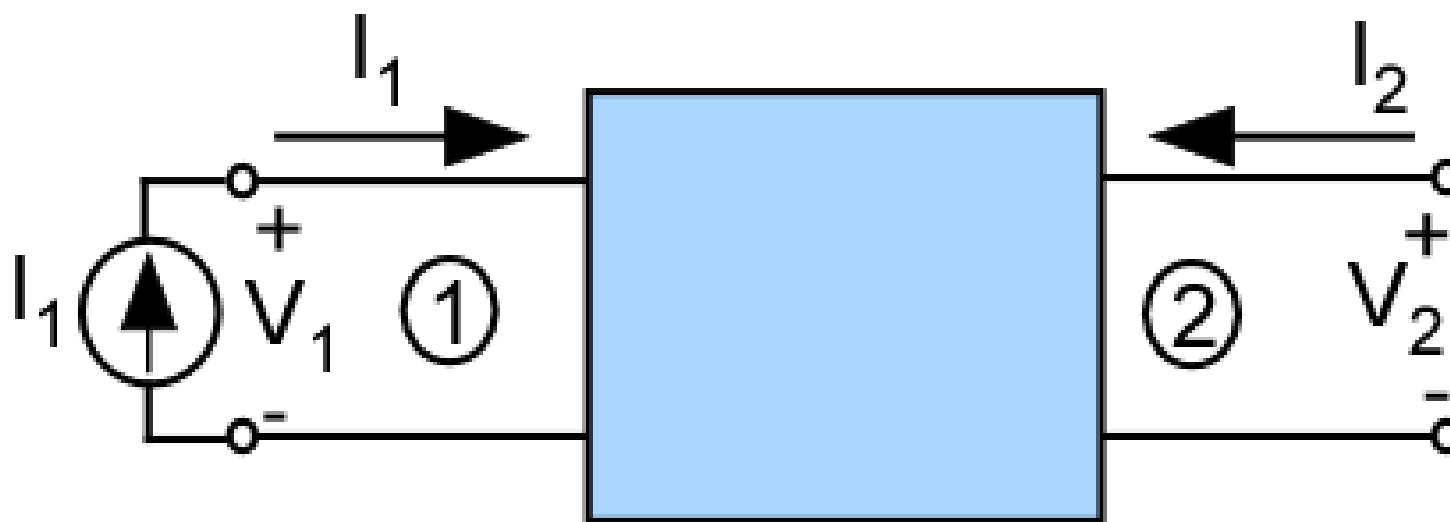

$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} \quad z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$

To make $I_2=0$, place an open at port 2


H Parameters

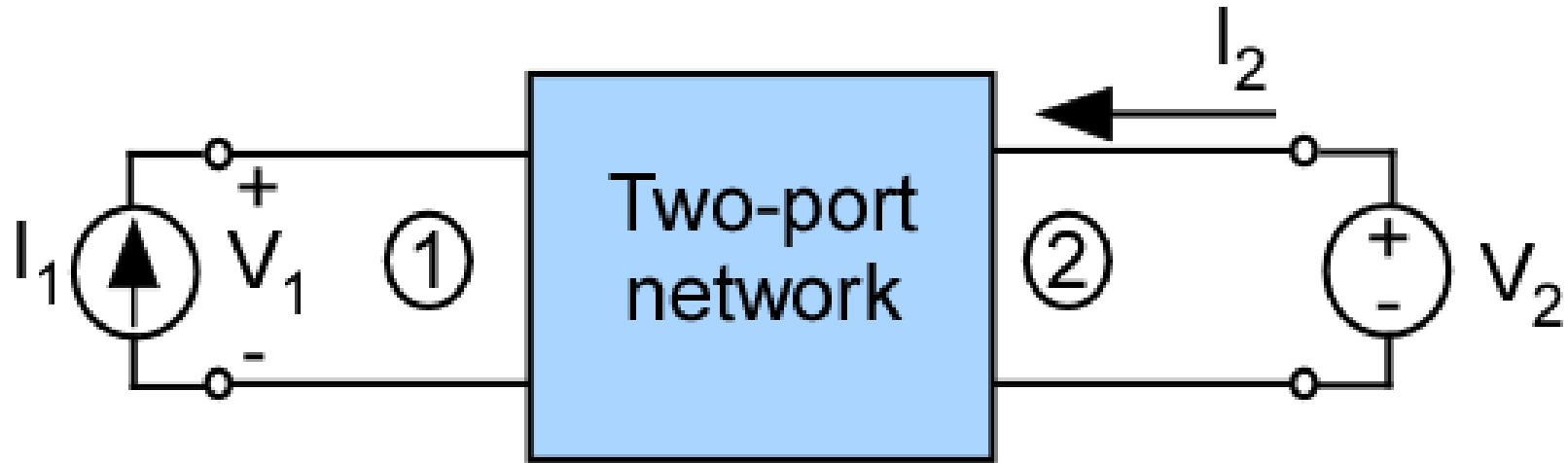

$$V_1 = h_{11}I_1 + h_{12}V_2$$

$$I_2 = h_{21}I_1 + h_{22}V_2$$


H Parameter Calculations

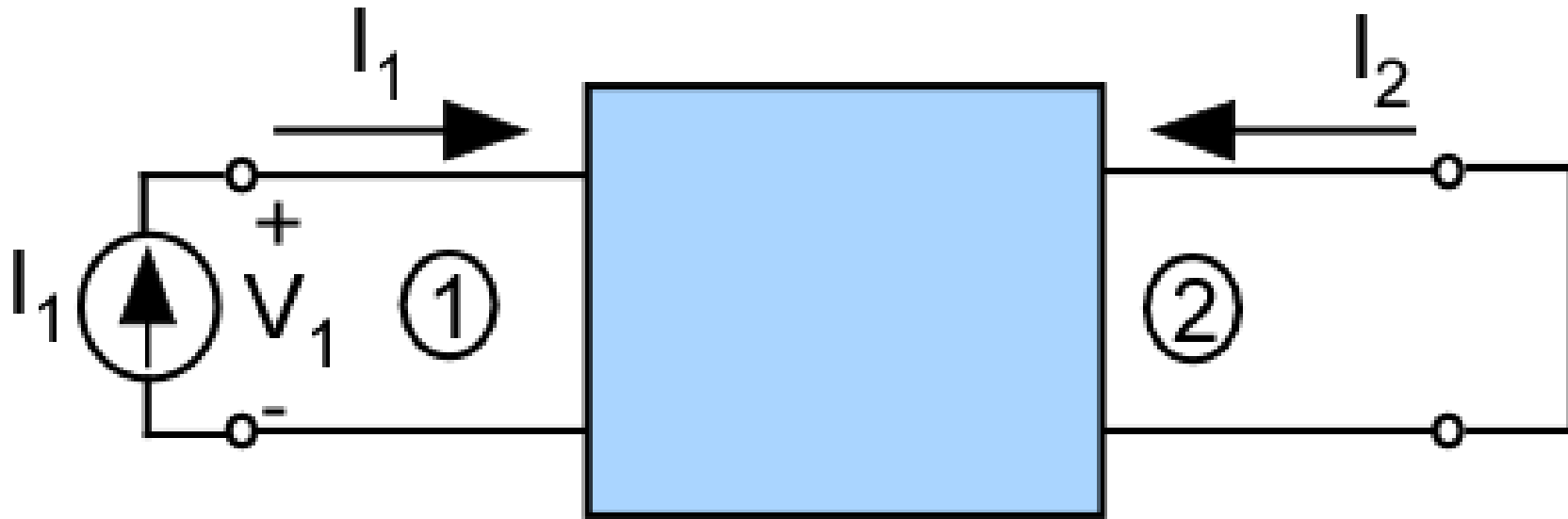

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} \quad h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0}$$

To make $V_2=0$, place a short at port 2


G Parameters

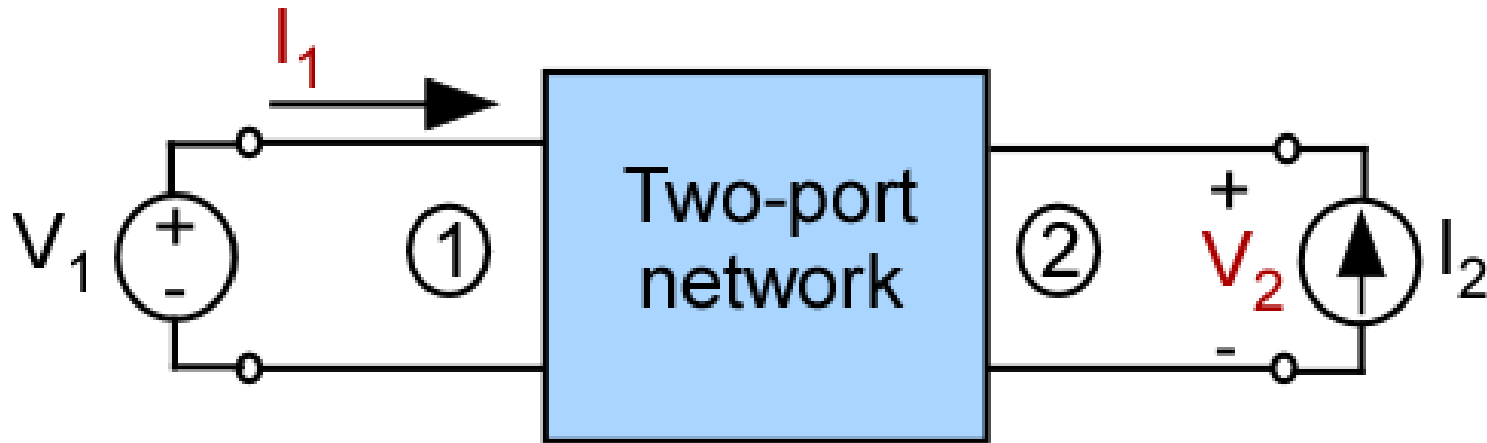

$$I_1 = g_{11}V_1 + g_{12}I_2$$

$$V_2 = g_{21}V_1 + g_{22}I_2$$

G-Parameter Calculations

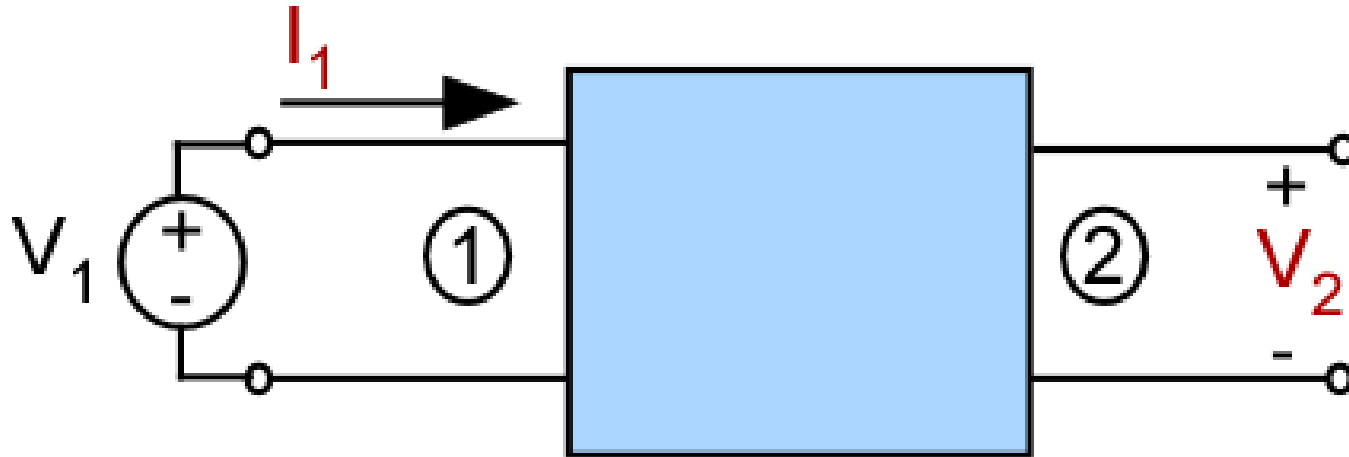

$$g_{11} = \left. \frac{I_1}{V_1} \right|_{I_2=0} \quad g_{21} = \left. \frac{V_2}{V_1} \right|_{I_2=0}$$

To make $I_2=0$, place an open at port 2

TWO-PORT NETWORK REPRESENTATION



Z Parameters

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$


Y Parameters

$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

- At microwave frequencies, it is more difficult to measure total voltages and currents.
- Short and open circuits are difficult to achieve at high frequencies.
- Most active devices are not short- or open-circuit stable.

Wave Approach

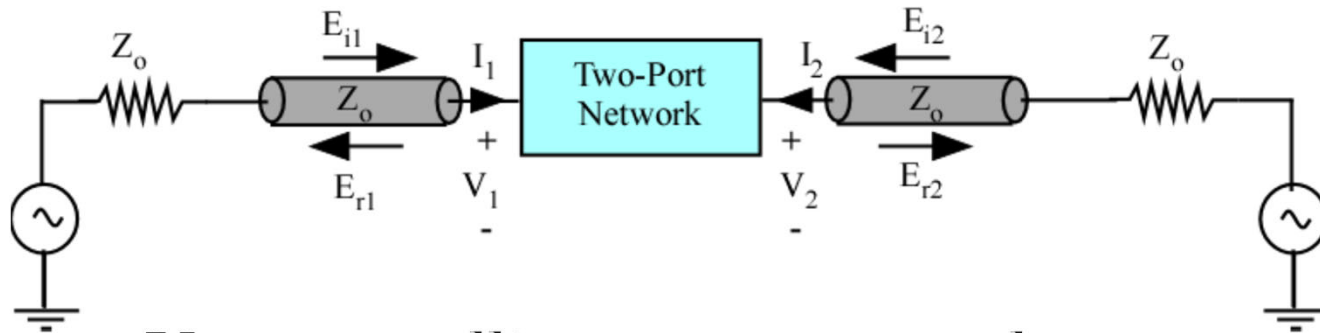


Use a travelling wave approach

$$V_1 = E_{i1} + E_{r1} \quad V_2 = E_{i2} + E_{r2}$$

$$I_1 = \frac{E_{i1} - E_{r1}}{Z_o} \quad I_2 = \frac{E_{i2} - E_{r2}}{Z_o}$$

- Total voltage and current are made up of sums of forward and backward traveling waves.
- Traveling waves can be determined from standing-wave ratio.

Wave Approach

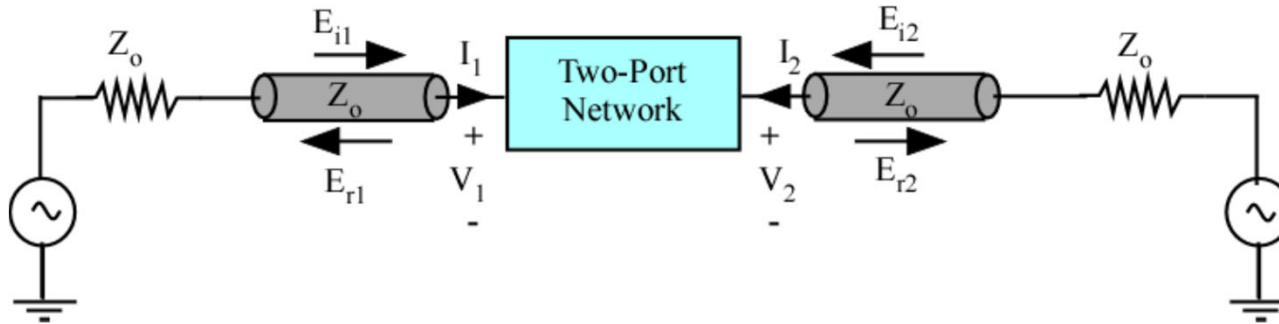

$$a_1 = \frac{E_{i1}}{\sqrt{Z_o}}$$

$$a_2 = \frac{E_{i2}}{\sqrt{Z_o}}$$

$$b_1 = \frac{E_{r1}}{\sqrt{Z_o}}$$


$$b_2 = \frac{E_{r2}}{\sqrt{Z_o}}$$

Z_o is the reference impedance of the system

$$b_1 = S_{11} a_1 + S_{12} a_2$$

$$b_2 = S_{21} a_1 + S_{22} a_2$$

Wave Approach

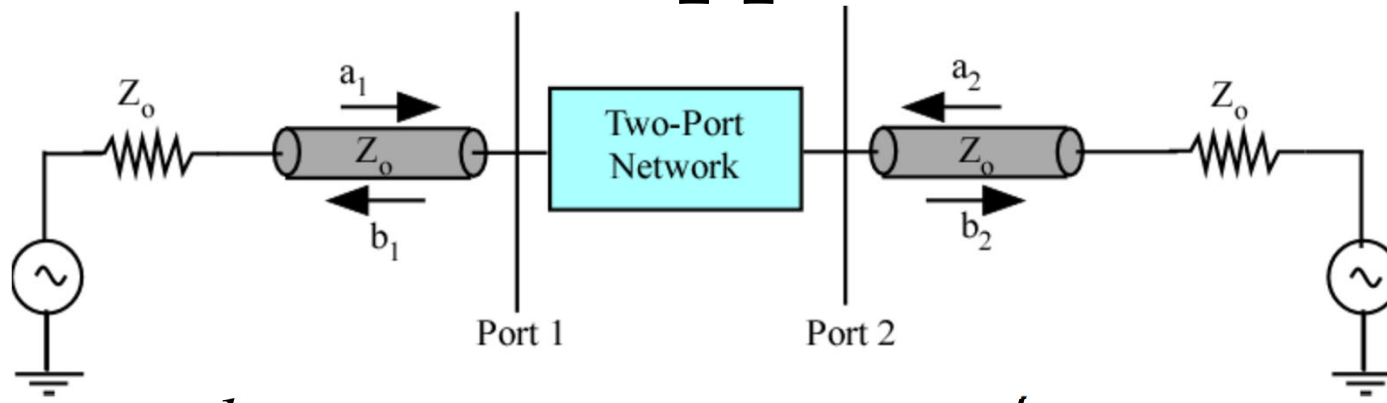

$$S_{11} = \frac{b_1}{a_1} \Big|_{a_2=0}$$

$$S_{21} = \frac{b_2}{a_1} \Big|_{a_2=0}$$

$$S_{12} = \frac{b_1}{a_2} \Big|_{a_1=0}$$


$$S_{22} = \frac{b_2}{a_2} \Big|_{a_1=0}$$

To make $a_i = 0$

- 1) Provide no excitation at port i
- 2) Match port i to the characteristic impedance of the reference lines.

CAUTION : a_i and b_i are the traveling waves in the reference lines.


S-Parameters of Resistor

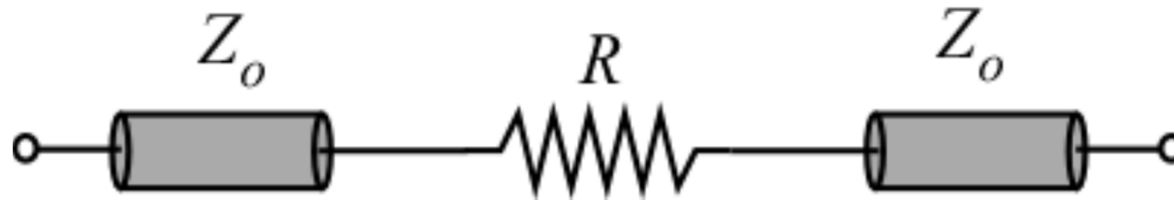

Determine S-Parameter of 2-port resistance

- Insert R between two reference TL
- Provide excitation at port 1 for S_{11} and S_{21}
- Provide excitation at port 2 for S_{12} and S_{23}
- Can use symmetry and reciprocity


S-Parameters of Resistor

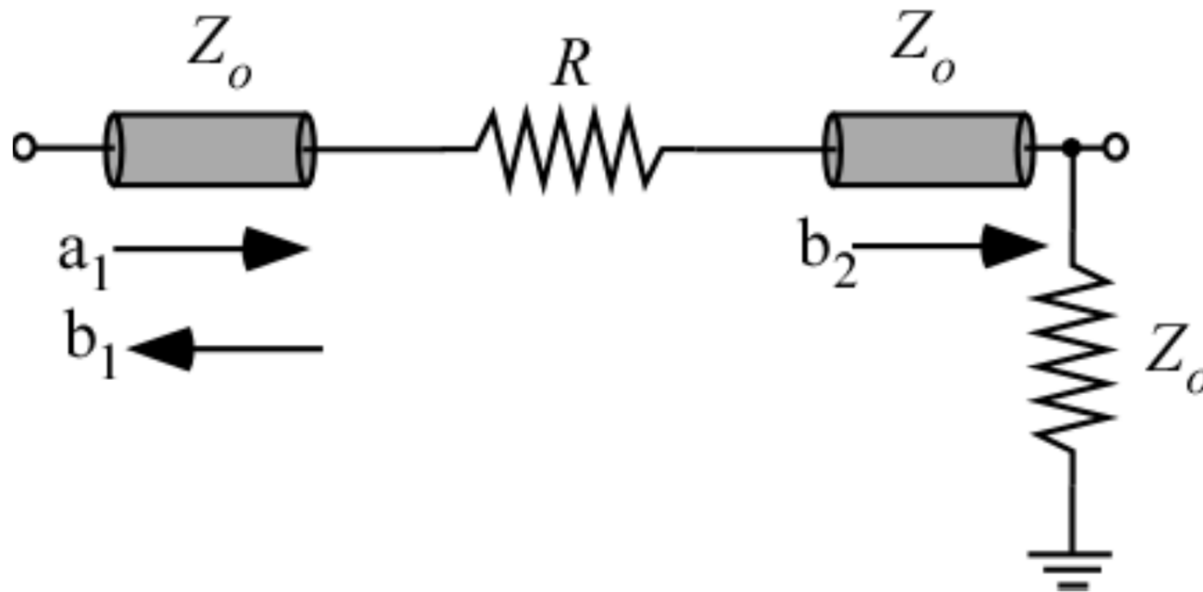

$$S_{11} = \frac{b_1}{a_1} = \Gamma = \frac{(R + Z_o) - Z_o}{(R + Z_o) + Z_o} = \frac{R}{R + 2Z_o}$$

$$S_{11} = \frac{R}{R + 2Z_o} \quad \text{and by symmetry,} \quad S_{22} = \frac{R}{R + 2Z_o}$$

Calculating S_{21} of Resistor

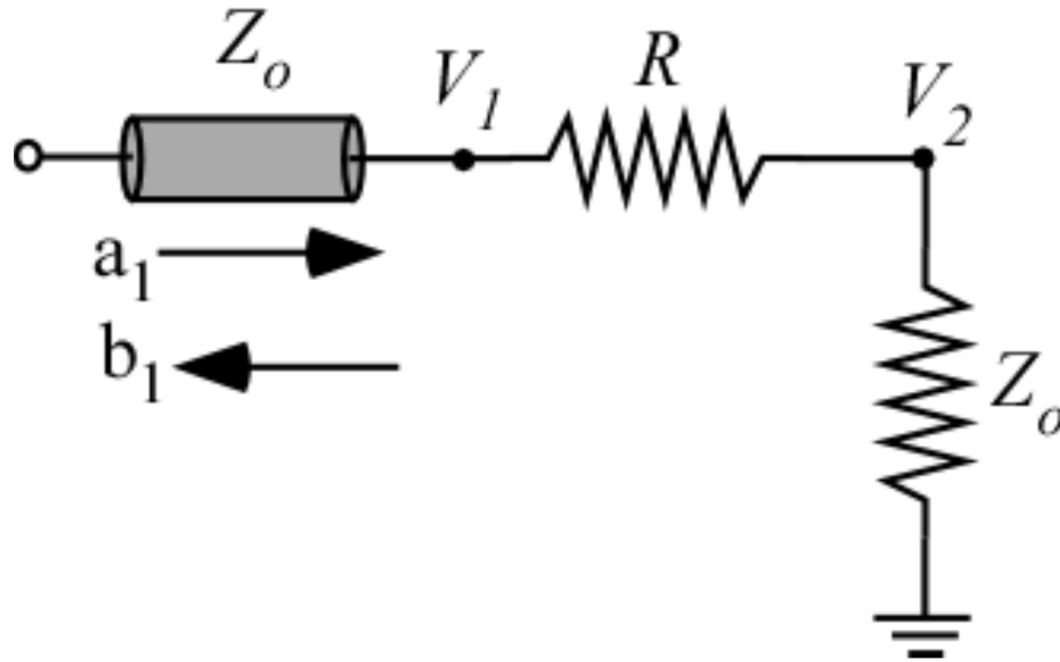

Since $a_2=0$, the total voltage in port 2 is: $V_2 = b_2\sqrt{Z_o}$


$$V_2 = \frac{V_1 Z_o}{R + Z_o} = \frac{\sqrt{Z_o} (a_1 + b_1) Z_o}{R + Z_o} = \frac{\sqrt{Z_o} (a_1 + S_{11} a_1) Z_o}{R + Z_o}$$

S-Parameters of Resistor

$$V_2 = \frac{Z_o \sqrt{Z_o} (1 + S_{11}) a_1}{R + Z_o} = \frac{2Z_o a_1 \sqrt{Z_o}}{R + 2Z_o}$$

$$S_{21} = \frac{b_2}{a_1} = \frac{V_2}{\sqrt{Z_o}} \frac{1}{a_1} = \frac{2Z_o}{R + 2Z_o}$$

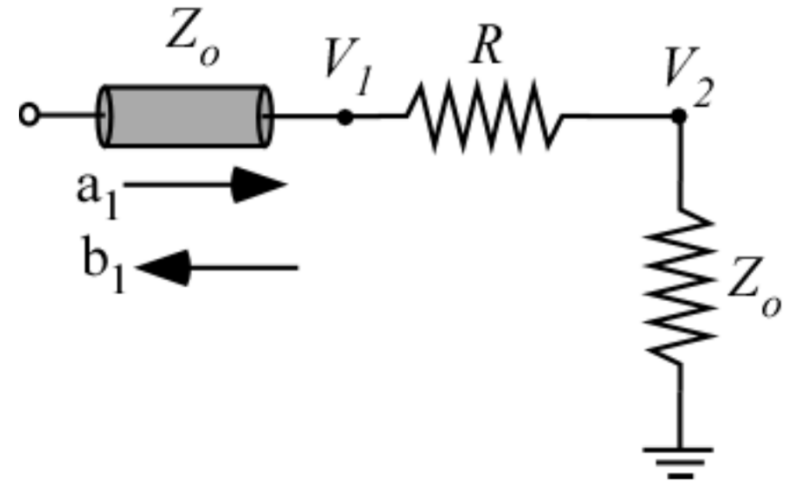
$$S_{21} = \frac{2Z_o}{R + 2Z_o} \quad \text{and by reciprocity,} \quad S_{12} = \frac{2Z_o}{R + 2Z_o}$$



S parameters of resistor R

$$S = \begin{bmatrix} \frac{R}{R + 2Z_o} & \frac{2Z_o}{R + 2Z_o} \\ \frac{2Z_o}{R + 2Z_o} & \frac{R}{R + 2Z_o} \end{bmatrix}$$

Y-Parameters of TL

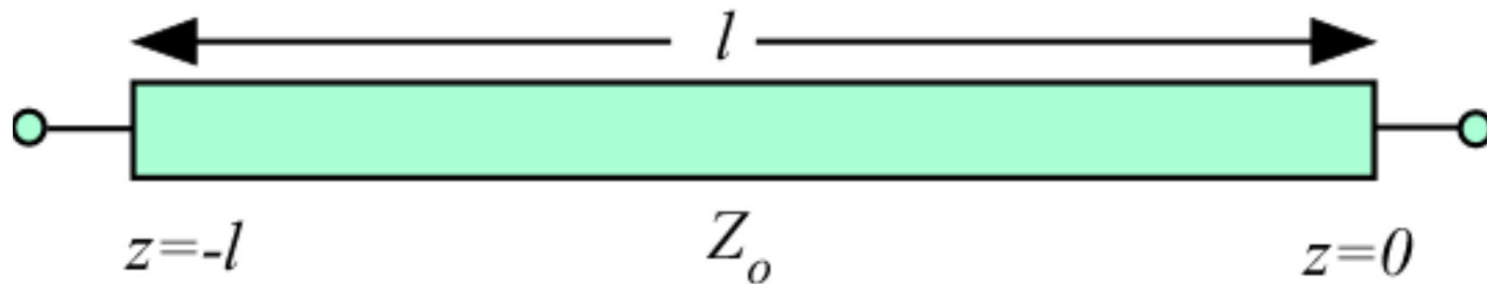

at port 1

$$V_1 = V_+ e^{+j\beta l} + V_- e^{-j\beta l}$$

$$I_1 = Y_o (V_+ e^{+j\beta l} - V_- e^{-j\beta l})$$


at port 2 ($z = 0$)

$$V_2 = V_+ + V_-$$

$$I_2 = -Y_o (V_+ - V_-)$$

$$V_+ = \frac{V_2 - Z_o I_2}{2} \quad \text{and} \quad V_- = \frac{V_2 + Z_o I_2}{2}$$

Y-Parameters of TL

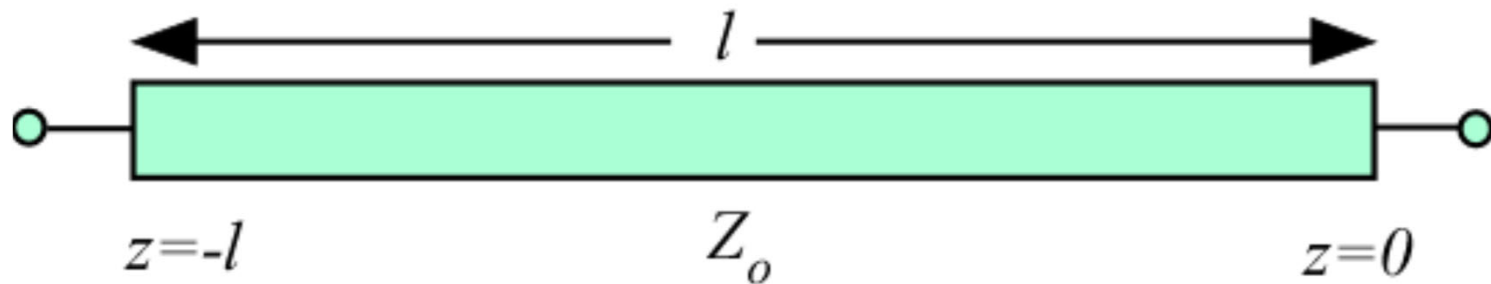

So that

$$V_1 = \left(\frac{V_2 - Z_o I_2}{2} \right) e^{+j\beta l} + \left(\frac{V_2 + Z_o I_2}{2} \right) e^{-j\beta l}$$


$$I_1 = Y_o \left(\frac{V_2 - Z_o I_2}{2} \right) e^{+j\beta l} - Y_o \left(\frac{V_2 + Z_o I_2}{2} \right) e^{-j\beta l}$$

and

$$V_1 = V_2 \cos \beta l - Z_o I_2 j \sin \beta l$$

$$I_1 = +Y_o V_2 j \sin \beta l - I_2 \cos \beta l$$

Y-Parameters of TL

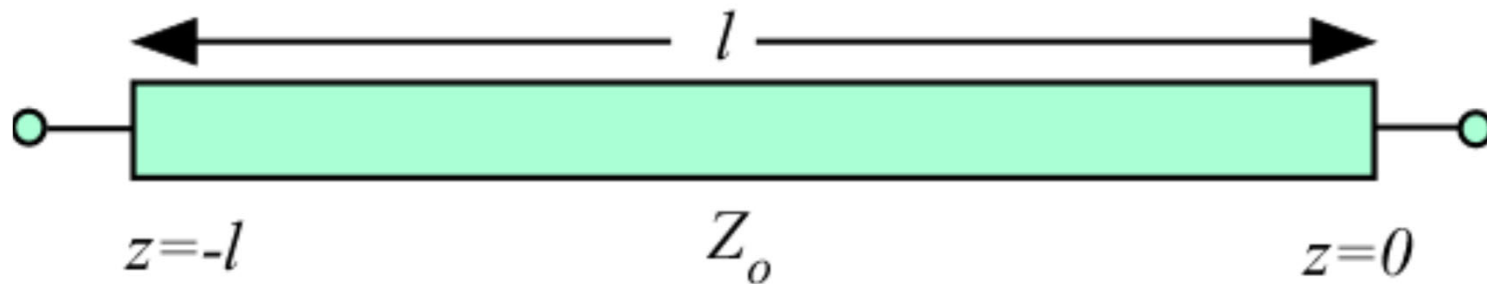

Using definitions for Y_{11}

$$Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} = \frac{-I_2 \cos \beta l}{-jZ_o I_2 \sin \beta l} = \frac{-jY_o \cos \beta l}{\sin \beta l}$$


and

$$Y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0} = \frac{-I_2}{-jZ_o I_2 \sin \beta l} = \frac{+jY_o}{\sin \beta l}$$

$$Y_{22} = Y_{11} \text{ by symmetry}$$

$$Y_{12} = Y_{21} \text{ by reciprocity}$$

S-Parameters of TL

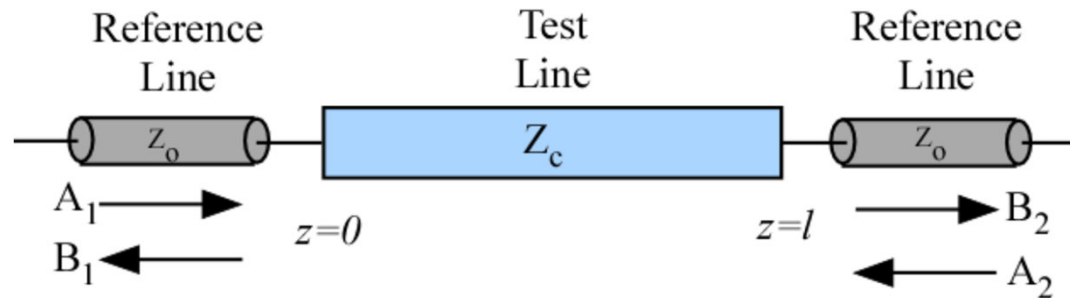

$$S_{11} = S_{22} = \frac{(1 - X^2)\Gamma}{1 - X^2\Gamma^2}$$

$$S_{12} = S_{21} = \frac{(1 - \Gamma^2)X}{1 - X^2\Gamma^2}$$


$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$\Gamma = \frac{Z_c - Z_{ref}}{Z_c + Z_{ref}}$$

$$Z_c = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

$$X = e^{-\gamma l}$$

S-Parameters of Lossless TL

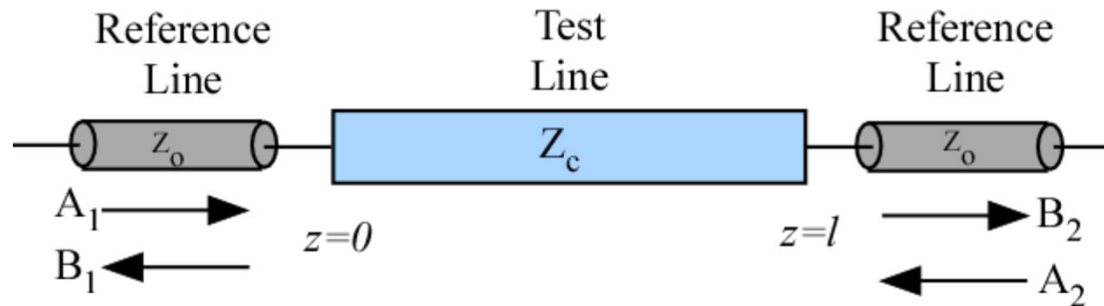

$$\beta = \omega\sqrt{LC}$$

$$S_{11} = S_{22} = \frac{(1 - X^2)\Gamma}{1 - X^2\Gamma^2}$$

$$\Gamma = \frac{Z_c - Z_{ref}}{Z_c + Z_{ref}}$$

$$Z_c = \sqrt{\frac{L}{C}}$$

$$S_{12} = S_{21} = \frac{(1 - \Gamma^2)X}{1 - X^2\Gamma^2}$$


$$X = e^{-j\beta l}$$

If $Z_c = Z_{ref}$

$$S_{11} = S_{22} = 0$$

$$S_{12} = S_{21} = e^{-j\beta l}$$


Two-Ports in Parallel*

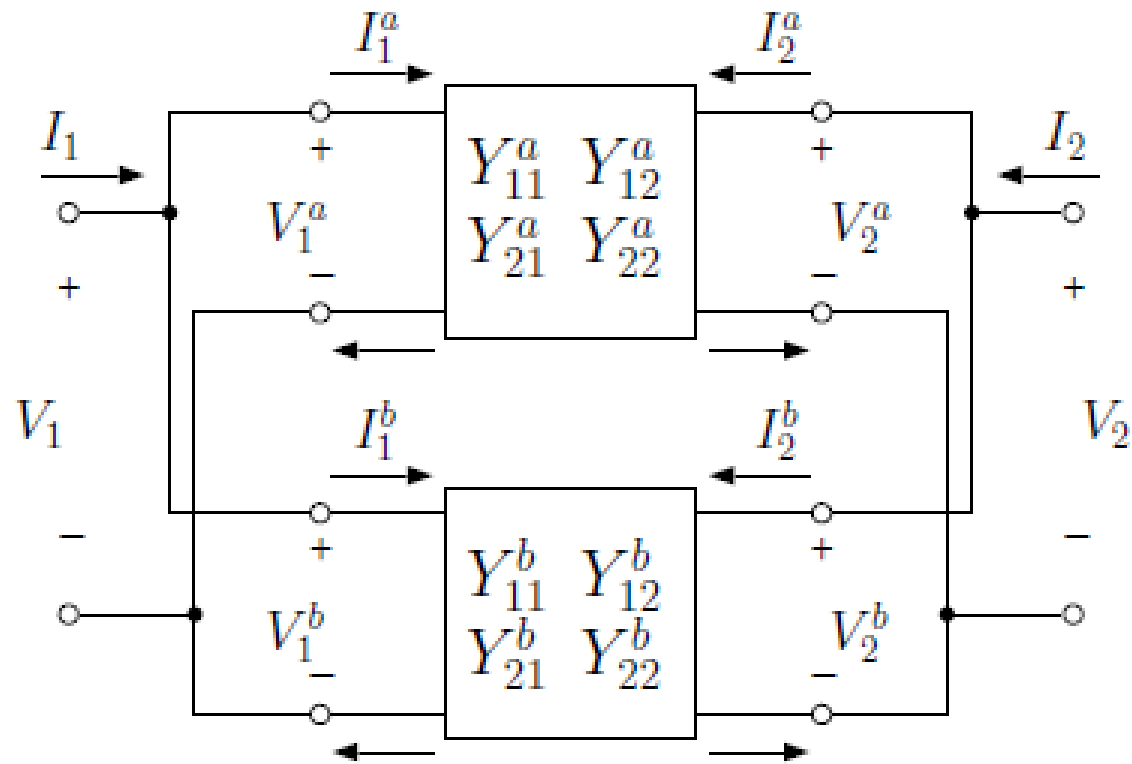

$$\mathbf{Y} = \mathbf{Y}^a + \mathbf{Y}^b$$

* S. Franke, ECE 453 - *Wireless Communication Systems*, Spring 2019.


Two-Ports in Series*

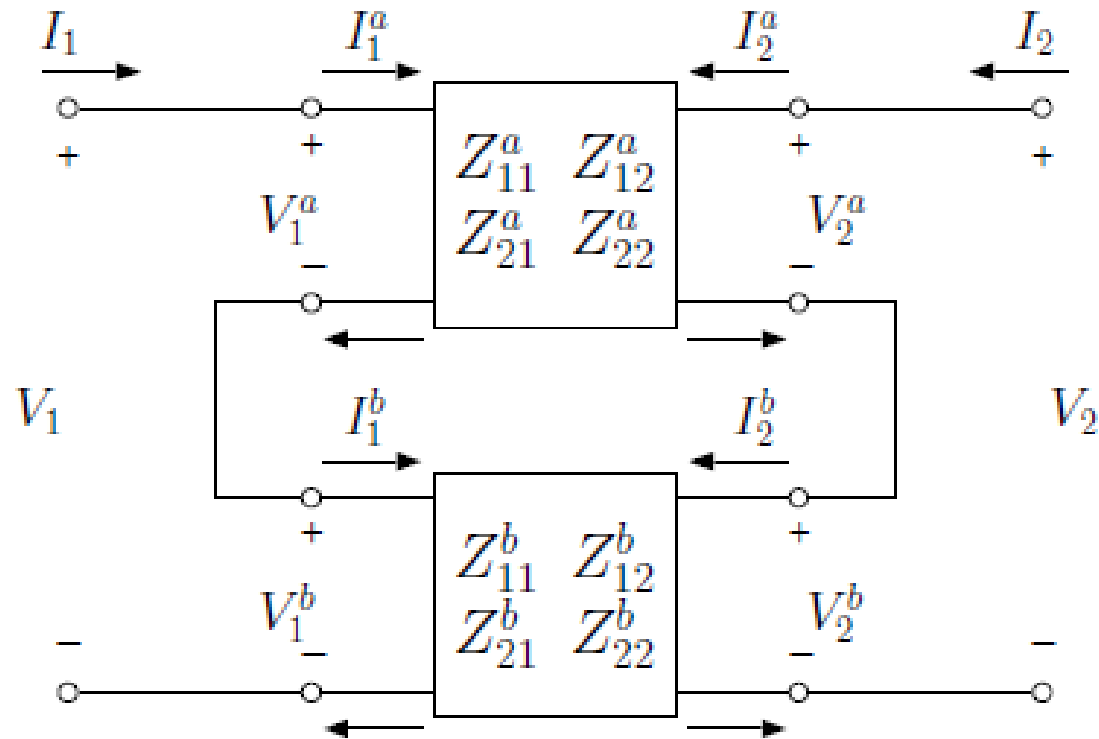

$$\mathbf{Z} = \mathbf{Z}^a + \mathbf{Z}^b$$

* S. Franke, ECE 453 - *Wireless Communication Systems*, Spring 2019.

ABCD -Parameters

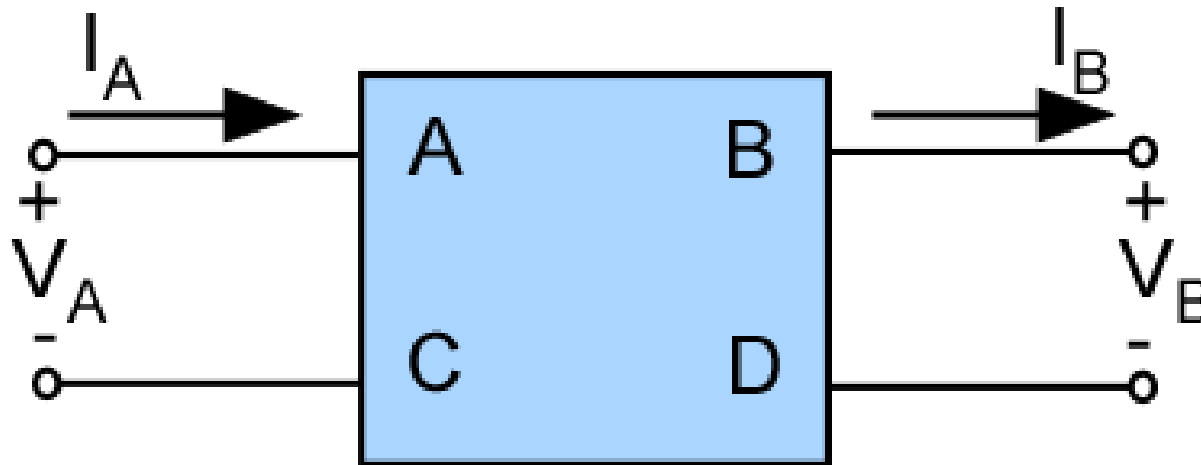

$$V_A = AV_B + BI_B$$

$$I_A = CV_B + DI_B$$


ABCD -Parameters

$$V_A = V_1$$

$$V_B = V_2$$



$$I_A = I_1$$

$$I_B = -I_2$$

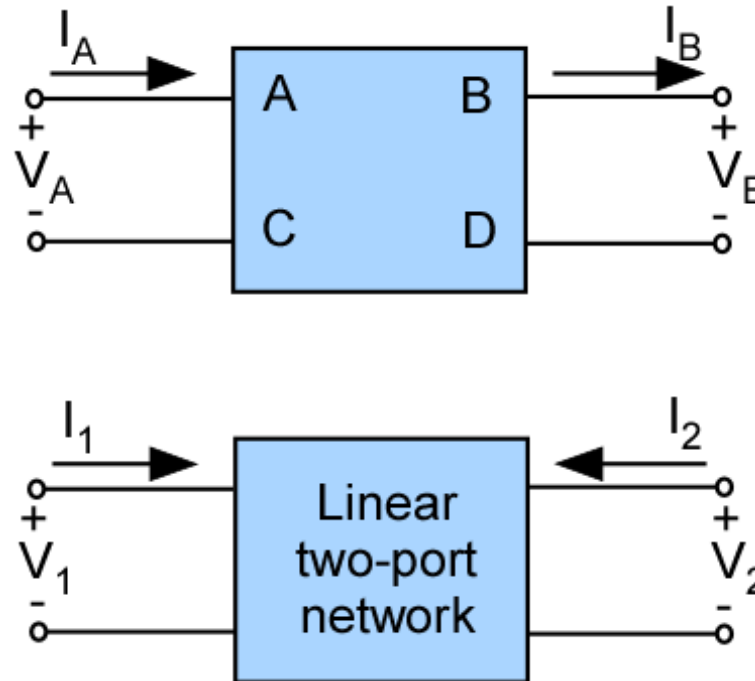

Relationship with Z parameters is obtained by first expressing ABCD parameters in terms of Z parameters

ABCD -Parameters

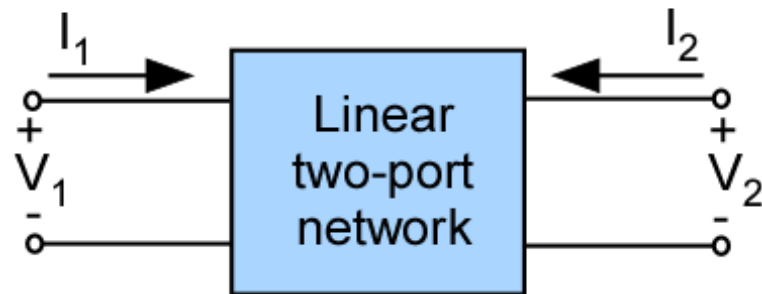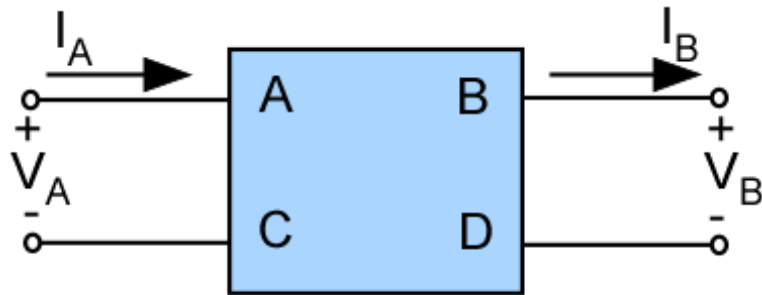

From

$$V_A = Z_{11}I_A - Z_{12}I_B$$

$$V_B = Z_{21}I_A - Z_{22}I_B$$

We get

$$A = \frac{Z_{11}}{Z_{21}}$$


$$B = \frac{\Delta}{Z_{21}}$$

$$C = \frac{1}{Z_{21}}$$

$$D = \frac{Z_{22}}{Z_{21}}$$


$$\Delta = Z_{11}Z_{22} - Z_{12}Z_{21}$$

ABCD -Parameters

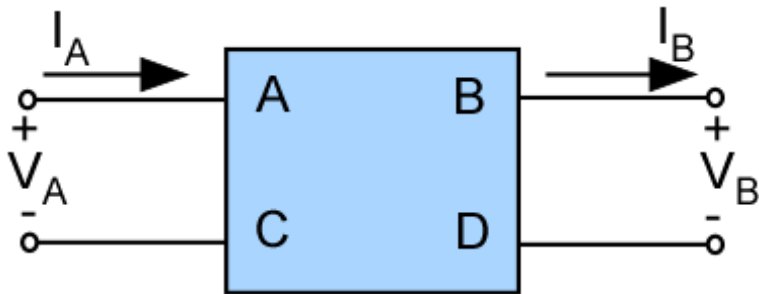

$$Z_{11} = \frac{A}{C}$$

$$Z_{12} = \frac{(AD - BC)}{C}$$

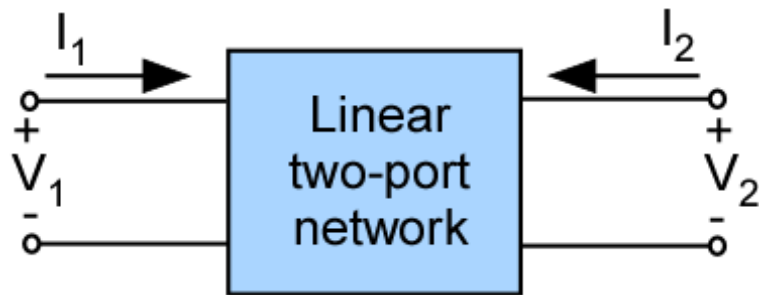

$$Z_{21} = \frac{1}{C}$$


$$Z_{22} = \frac{D}{C}$$

For a reciprocal network, $Z_{21} = Z_{12}$, therefore

$$AD - BC = 1$$

← Reciprocity condition
for ABCD parameters

ABCD -Parameters

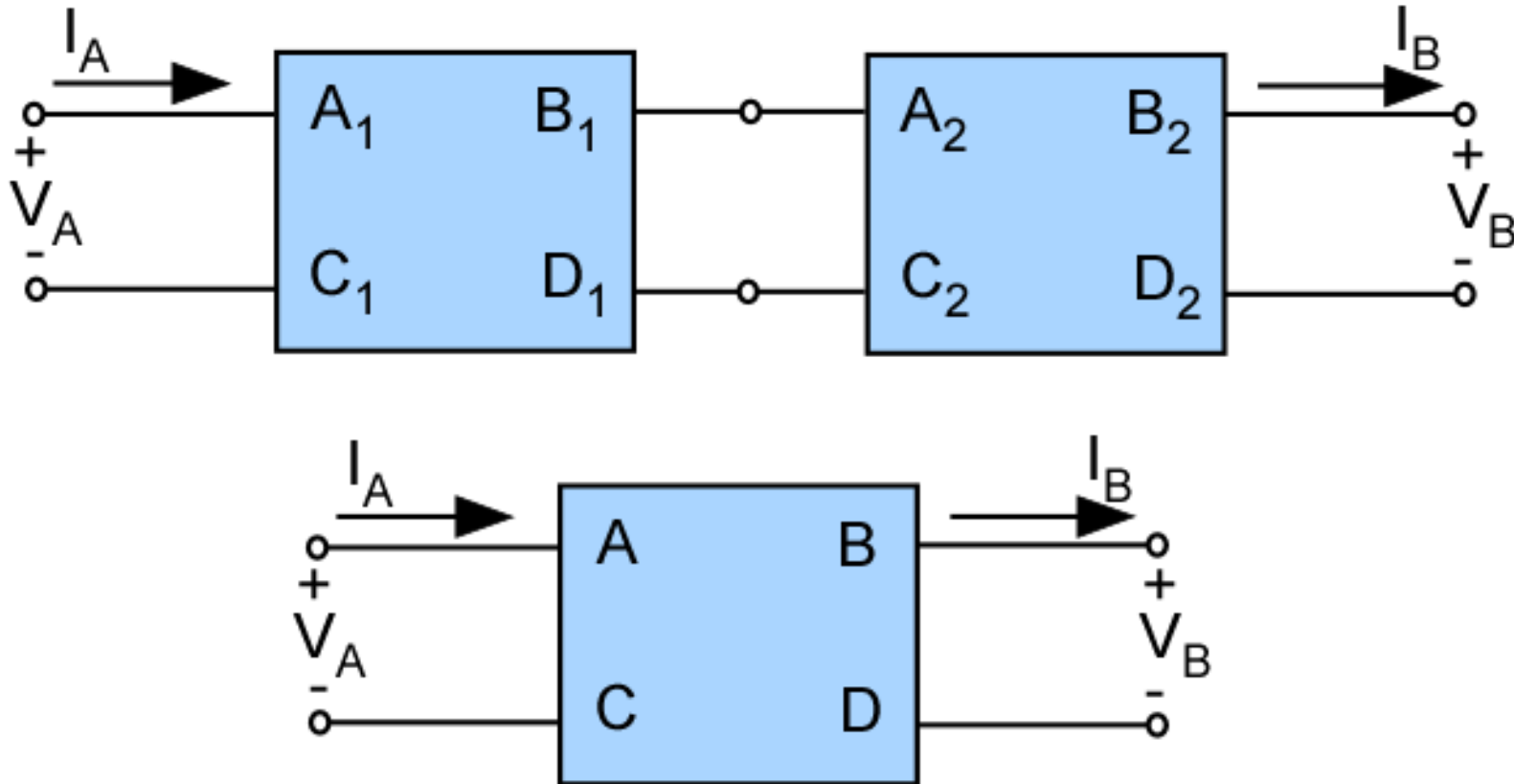

When cascading two-ports, it is best to use ABCD parameters. Put voltage and currents in cascadable form with the input variables in terms of the output variables

$$\mathbf{ABCD} = (\mathbf{ABCD})_1 \cdot (\mathbf{ABCD})_2$$

Scattering Transfer Parameters

In T-Parameters, traveling waves at the input are related to those at the output

$$\begin{aligned} b_1 &= S_{11}a_1 + S_{12}a_2 & b_1 &= T_{11}a_2 + T_{12}b_2 \\ b_2 &= S_{21}a_1 + S_{22}a_2 & a_1 &= T_{21}a_2 + T_{22}b_2 \end{aligned}$$

$$\begin{pmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{pmatrix} = \begin{pmatrix} T_{12}T_{22}^{-1} & T_{11} - T_{12}T_{21}T_{22}^{-1} \\ T_{22}^{-1} & -T_{21}T_{22}^{-1} \end{pmatrix}$$

$$\begin{pmatrix} T_{11} & T_{12} \\ T_{21} & T_{22} \end{pmatrix} = \begin{pmatrix} S_{12} - S_{11}S_{22}S_{21}^{-1} & S_{11}S_{21}^{-1} \\ -S_{22}S_{21}^{-1} & S_{21}^{-1} \end{pmatrix}$$

T parameters can be cascaded $\mathbf{T} = \mathbf{T}_A \cdot \mathbf{T}_B$

Parameter Conversion*

7.7.1 Converting to Y-parameters

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} \frac{Z_{22}}{D_Z} & -\frac{Z_{12}}{D_Z} \\ -\frac{Z_{21}}{D_Z} & \frac{Z_{11}}{D_Z} \end{bmatrix} = \begin{bmatrix} \frac{1}{h_{11}} & -\frac{h_{12}}{h_{11}} \\ \frac{h_{21}}{h_{11}} & \frac{D_h}{h_{11}} \end{bmatrix} = \begin{bmatrix} \frac{D}{B} & -\frac{D_{ABCD}}{B} \\ -\frac{1}{B} & \frac{A}{B} \end{bmatrix}$$

7.7.2 Converting to Z-parameters

$$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} \frac{Y_{22}}{D_Y} & -\frac{Y_{12}}{D_Y} \\ -\frac{Y_{21}}{D_Y} & \frac{Y_{11}}{D_Y} \end{bmatrix} = \begin{bmatrix} \frac{D_h}{h_{22}} & \frac{h_{12}}{h_{22}} \\ -\frac{h_{21}}{h_{22}} & \frac{1}{h_{22}} \end{bmatrix} = \begin{bmatrix} \frac{A}{C} & \frac{D_{ABCD}}{C} \\ \frac{1}{C} & \frac{D}{C} \end{bmatrix}$$

7.7.3 Converting to h-parameters

$$\begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} = \begin{bmatrix} \frac{D_Z}{Z_{22}} & \frac{Z_{12}}{Z_{22}} \\ -\frac{Z_{21}}{Z_{22}} & \frac{1}{Z_{22}} \end{bmatrix} = \begin{bmatrix} \frac{1}{Y_{11}} & -\frac{Y_{12}}{Y_{11}} \\ \frac{Y_{21}}{Y_{11}} & \frac{D_Y}{Y_{11}} \end{bmatrix} = \begin{bmatrix} \frac{B}{D} & \frac{D_{ABCD}}{D} \\ -\frac{1}{D} & \frac{C}{D} \end{bmatrix}$$

7.7.4 Converting to ABCD-parameters

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \frac{Z_{11}}{Z_{21}} & \frac{D_Z}{Z_{21}} \\ \frac{1}{Z_{21}} & \frac{Z_{22}}{Z_{21}} \end{bmatrix} = \begin{bmatrix} -\frac{Y_{22}}{Y_{21}} & -\frac{1}{Y_{21}} \\ -\frac{D_Y}{Y_{21}} & -\frac{Y_{11}}{Y_{21}} \end{bmatrix} = \begin{bmatrix} -\frac{D_h}{h_{21}} & -\frac{h_{11}}{h_{21}} \\ -\frac{h_{22}}{h_{21}} & -\frac{1}{h_{21}} \end{bmatrix}$$

* M. Steer, *Microwave and RF Design*, Scitech Publishing, 2nd Edition 2013.

N-Port S Parameters

$$\begin{bmatrix} b_1 \\ b_2 \\ \cdot \\ b_n \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} & \cdot & \cdot \\ S_{21} & S_{22} & \cdot & \cdot \\ \cdot & \cdot & \cdot & \cdot \\ \cdot & \cdot & \cdot & S_{nn} \end{bmatrix} \begin{bmatrix} a_1 \\ a_2 \\ \cdot \\ a_n \end{bmatrix}$$

$$\mathbf{b} = \mathbf{S}\mathbf{a}$$

If $b_i = 0$, then no reflected wave on port $i \rightarrow$ port is matched

$$a_i = \frac{V_i^+}{\sqrt{Z_{oi}}}$$

V_i^+ : incident voltage wave in port i

V_i^- : reflected voltage wave in port i

$$b_i = \frac{V_i^-}{\sqrt{Z_{oi}}}$$

Z_{oi} : impedance in port i

N-Port S Parameters

$$\mathbf{v} = \sqrt{Z_o} (\mathbf{a} + \mathbf{b}) \quad (1) \quad \mathbf{i} = \frac{1}{\sqrt{Z_o}} (\mathbf{a} - \mathbf{b}) \quad (2) \quad \mathbf{v} = \mathbf{Z}\mathbf{i} \quad (3)$$

Substitute (1) and (2) into (3)

$$\sqrt{Z_o} (\mathbf{a} + \mathbf{b}) = \mathbf{Z} \frac{1}{\sqrt{Z_o}} (\mathbf{a} - \mathbf{b})$$

Defining \mathbf{S} such that $\mathbf{b} = \mathbf{S}\mathbf{a}$ and substituting for \mathbf{b}

$$Z_o (\mathbf{U} + \mathbf{S})\mathbf{a} = \mathbf{Z}(\mathbf{U} - \mathbf{S})\mathbf{a}$$

\mathbf{U} : unit matrix

$\mathbf{S} \rightarrow \mathbf{Z}$

$$\mathbf{Z} = Z_o (\mathbf{U} + \mathbf{S})(\mathbf{U} - \mathbf{S})^{-1}$$

$\mathbf{Z} \rightarrow \mathbf{S}$

$$\mathbf{S} = (\mathbf{Z} + Z_o \mathbf{U})^{-1} (\mathbf{Z} - Z_o \mathbf{U})$$

N-Port S Parameters

If the port reference impedances are different, we define \mathbf{k} as

$$\mathbf{k} = \begin{bmatrix} \sqrt{Z_{o1}} & & & \\ & \sqrt{Z_{o2}} & & \\ & & \ddots & \\ & & & \sqrt{Z_{on}} \end{bmatrix}$$

$$\mathbf{v} = \mathbf{k}(\mathbf{a} + \mathbf{b}) \quad \text{and} \quad \mathbf{i} = \mathbf{k}^{-1}(\mathbf{a} - \mathbf{b}) \quad \text{and} \quad \mathbf{k}(\mathbf{a} + \mathbf{b}) = \mathbf{Z}\mathbf{k}^{-1}(\mathbf{a} - \mathbf{b})$$

$\mathbf{Z} \rightarrow \mathbf{S}$

$$\mathbf{S} = (\mathbf{Z}\mathbf{k}^{-1} + \mathbf{k})(\mathbf{Z}\mathbf{k}^{-1} - \mathbf{k})^{-1}$$

$\mathbf{S} \rightarrow \mathbf{Z}$

$$\mathbf{Z} = \mathbf{k}(\mathbf{U} + \mathbf{S})(\mathbf{U} - \mathbf{S})^{-1} \mathbf{k}$$

Normalization

Assume original S parameters as S_1 with system k_1 . Then the representation S_2 on system k_2 is given by

Transformation Equation

$$S_2 = \left[k_1(U + S_1)(U - S_1)^{-1}k_1k_2 + k_2 \right]^{-1} \left[k_1(U + S_1)(U - S_1)^{-1}k_1k_2 - k_2 \right]$$

If Z is symmetric, S is also symmetric

Dissipated Power

$$P_d = \frac{1}{2} \mathbf{a}^T (\mathbf{U} - \mathbf{S}^T \mathbf{S}^*) \mathbf{a}^*$$

The dissipation matrix \mathbf{D} is given by:

$$\mathbf{D} = \mathbf{U} - \mathbf{S}^T \mathbf{S}^*$$

Passivity insures that the system will always be stable provided that it is connected to another passive network

For passivity

- (1) the determinant of \mathbf{D} must be ≥ 0
- (2) the determinant of the principal minors must be ≥ 0

≥ 0

Dissipated Power

When the dissipation matrix is 0, we have a lossless network →

$$\mathbf{S}^T \mathbf{S}^* = \mathbf{U}$$

The \mathbf{S} matrix is unitary.

For a lossless two-port:

$$|S_{11}|^2 + |S_{21}|^2 = 1$$



$$|S_{22}|^2 + |S_{12}|^2 = 1$$

If in addition the network is reciprocal, then


$$S_{12} = S_{21} \quad \text{and} \quad |S_{11}| = |S_{22}| = \sqrt{1 - |S_{12}|^2}$$

Flow Graph Definitions

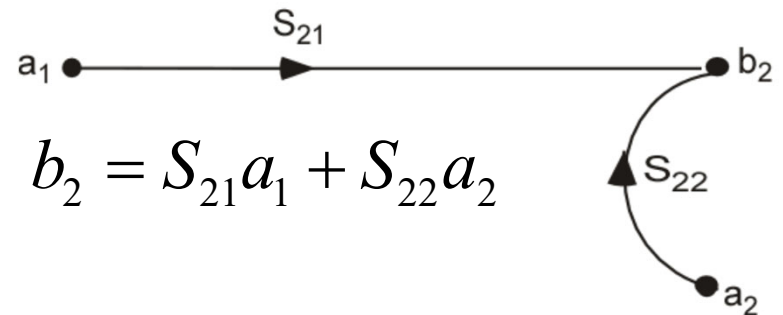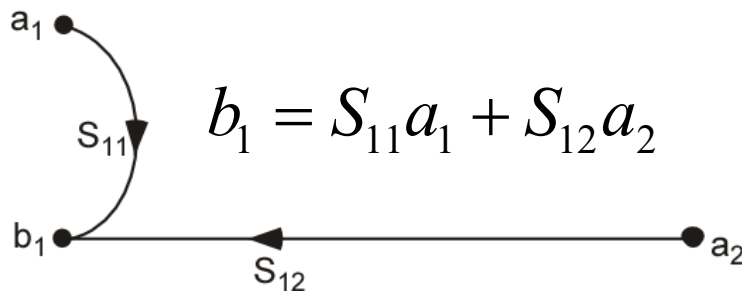
- Voltage waves designated as nodes.
- S parameters designated as branches
- Branches enter dependent nodes and emanate from independent nodes




Two-Port Flow Graph

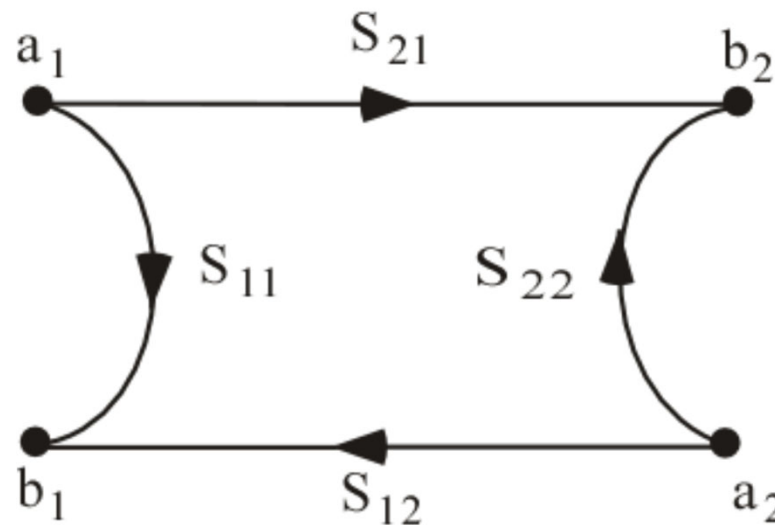

Flow Graph for Source

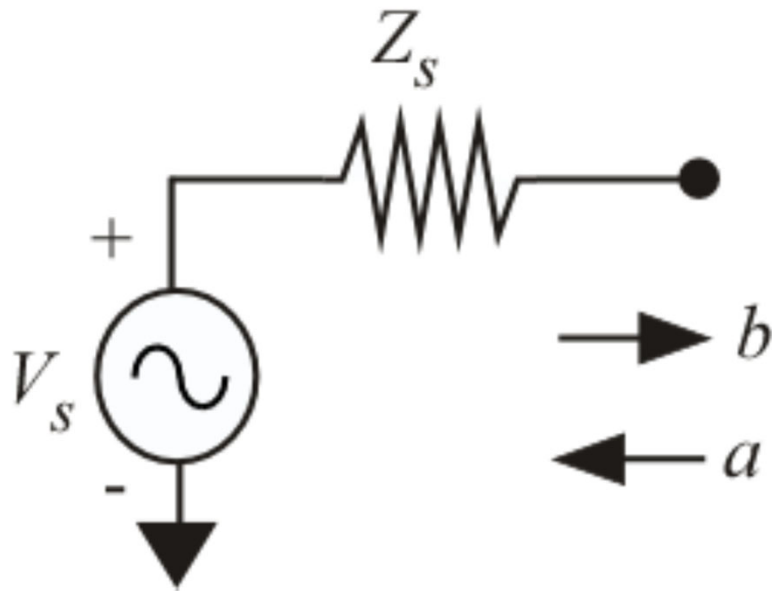


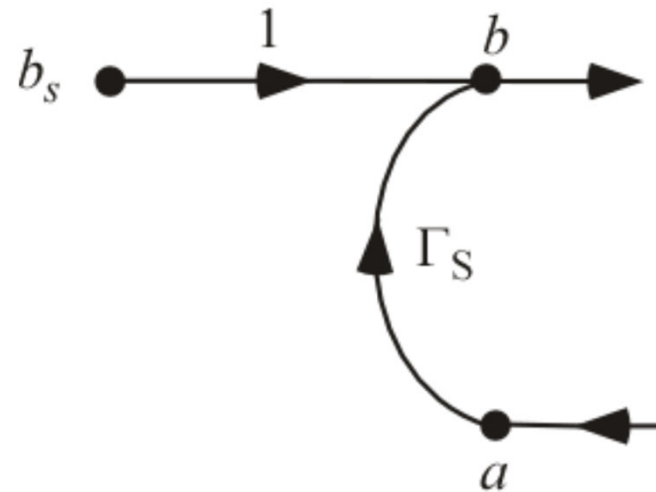
$$b_s = \frac{V_s \sqrt{Z_o}}{Z_s + Z_o}$$



$$\Gamma_s = \frac{Z_s - Z_o}{Z_s + Z_o}$$


b_s is power wave associated with power dissipated in a load of value Z_o connected to the source.

Flow Graph for Load

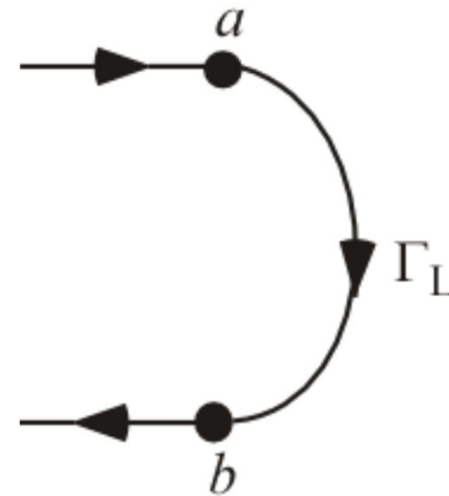
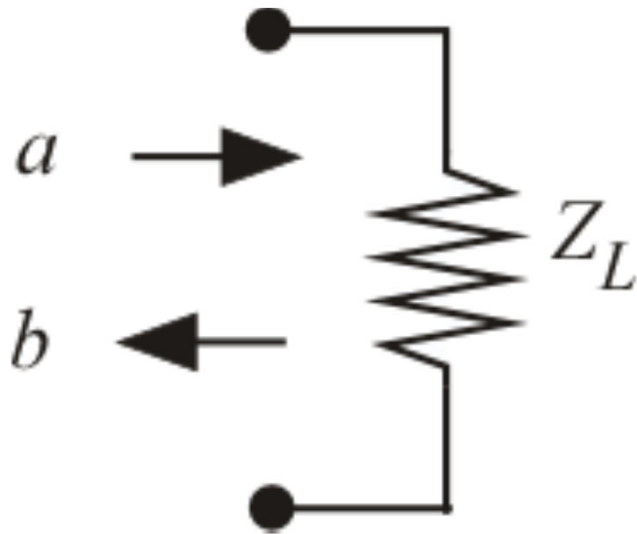


$$\Gamma_L = \frac{Z_L - Z_o}{Z_L + Z_o}$$

Flow Graph for Composite Circuit

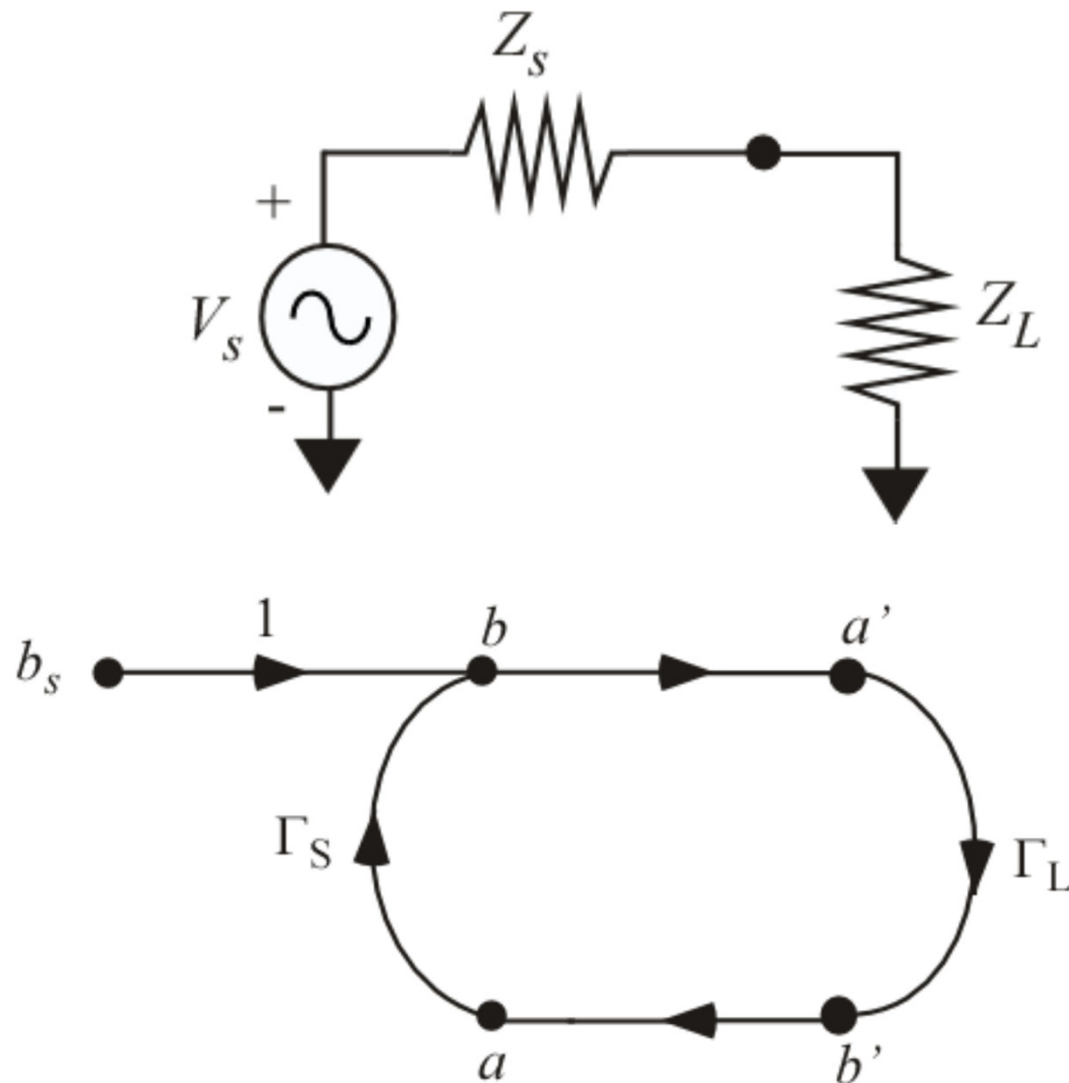

Flow Graph of Complete Two-Port

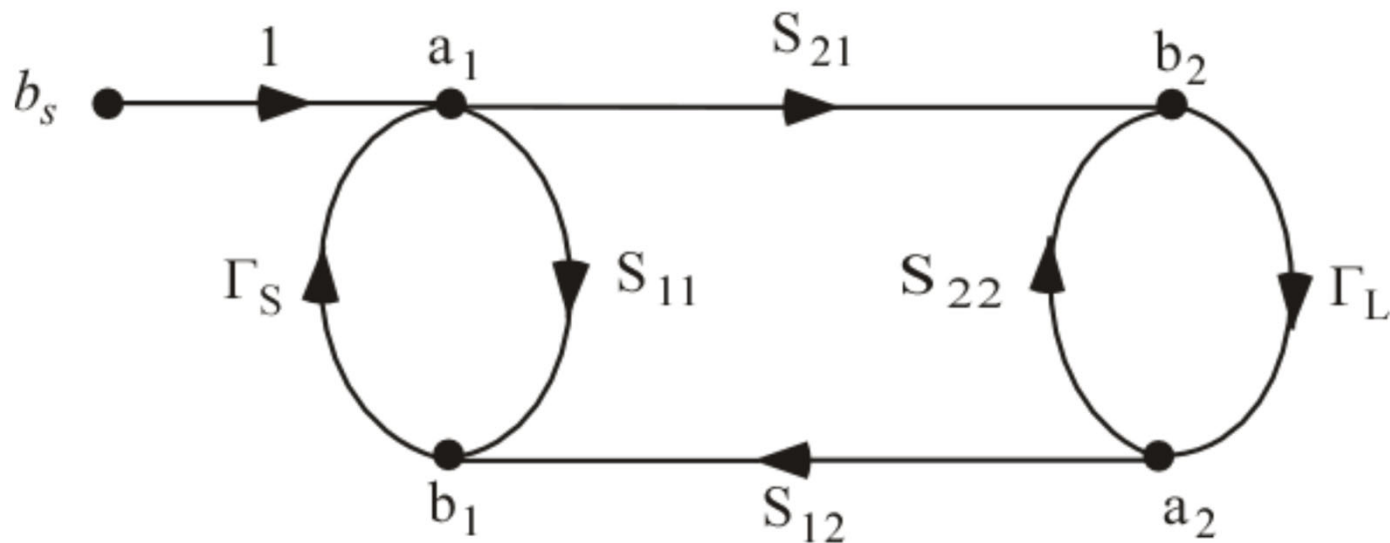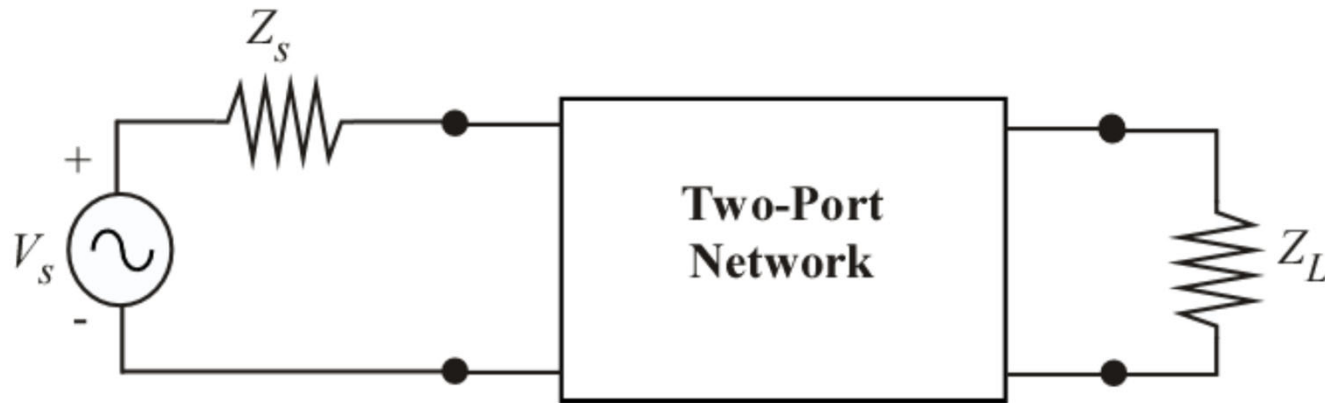

Loop Definitions

- A first order loop is defined as the product of the branches encountered in a journey starting from anode and moving in the direction of the arrows back to that original node
- A second order loop is defined as the product of any two **non-touching** first order loops.
- A third order loop is defined as the product of any three **non-touching** first order loops.

Mason's Non-Touching Loop Rule


$$T = \frac{P_1 \left[1 - \sum L(1)^{(1)} + \sum L(2)^{(1)} - \dots \right] + P_2 \left[1 - \sum L(1)^{(2)} + \dots \right] + \dots}{1 - \sum L(1) + \sum L(2) - \sum L(3) + \dots}$$

T : ratio of dependent variable over independent variable

P_k 's: are the various paths connecting the two variables of interest

$L(j)^{(k)}$ is a loop of order j that does not touch path k

Example: Find b_2/b_s

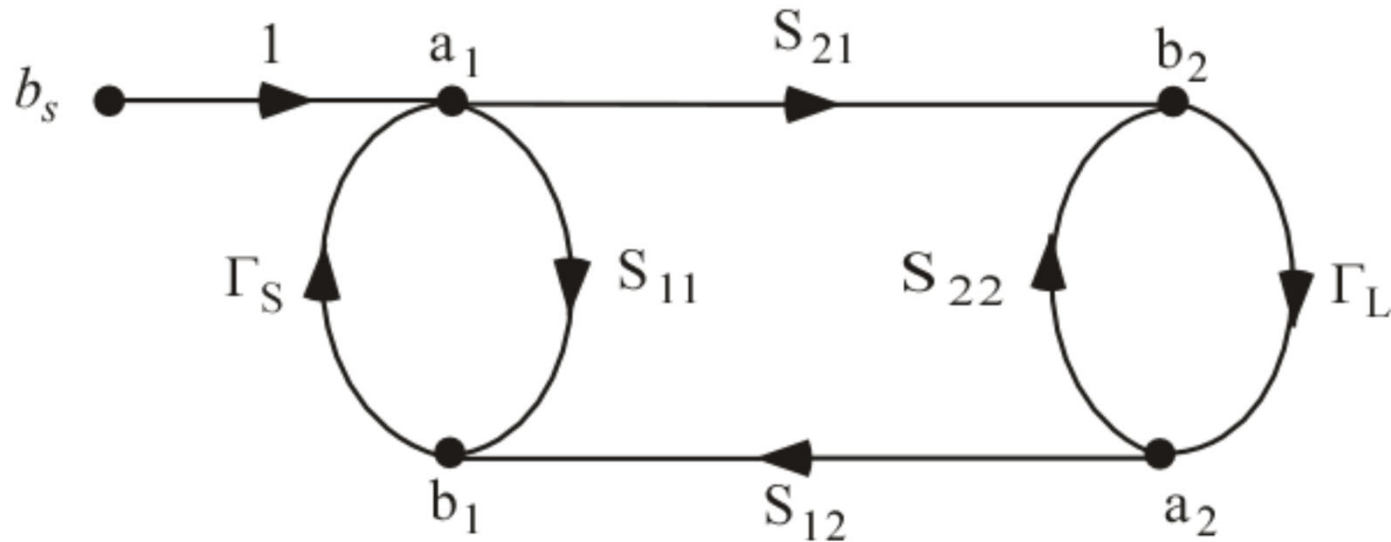


First Order Loops: $S_{11}\Gamma_S$, $S_{22}\Gamma_L$, $S_{21}S_{12}\Gamma_L\Gamma_S$

Second Order Loops: $S_{11}\Gamma_S S_{22}\Gamma_L$

Paths: S_{21}

$$\frac{b_2}{b_s} = \frac{S_{21}}{1 - S_{11}\Gamma_S - S_{22}\Gamma_L - S_{21}S_{12}\Gamma_L\Gamma_S + S_{11}\Gamma_S S_{22}\Gamma_L}$$

Lossy and Dispersive Line

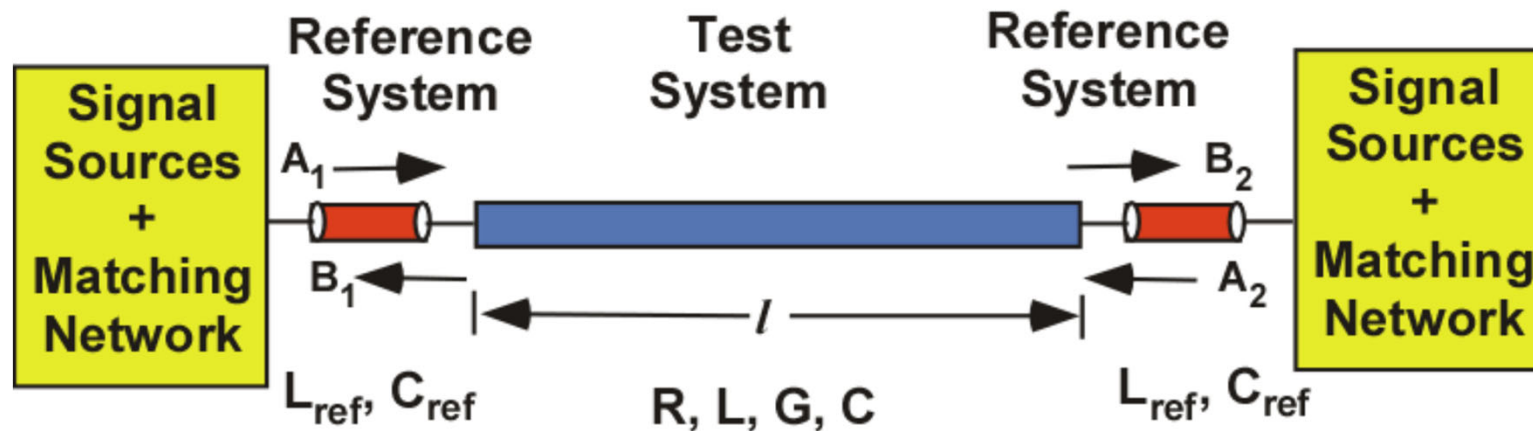


$$S_{11} = S_{22} = \frac{(1 - \alpha^2) \rho}{1 - \rho^2 \alpha^2}$$

$$S_{21} = S_{12} = \frac{(1 - \rho^2) \alpha}{1 - \rho^2 \alpha^2}$$

$$\alpha = e^{-\gamma l}$$


$$\rho = \frac{Z_c(\omega) - Z_o}{Z_c(\omega) + Z_o}$$

Frequency-Domain Formulation*

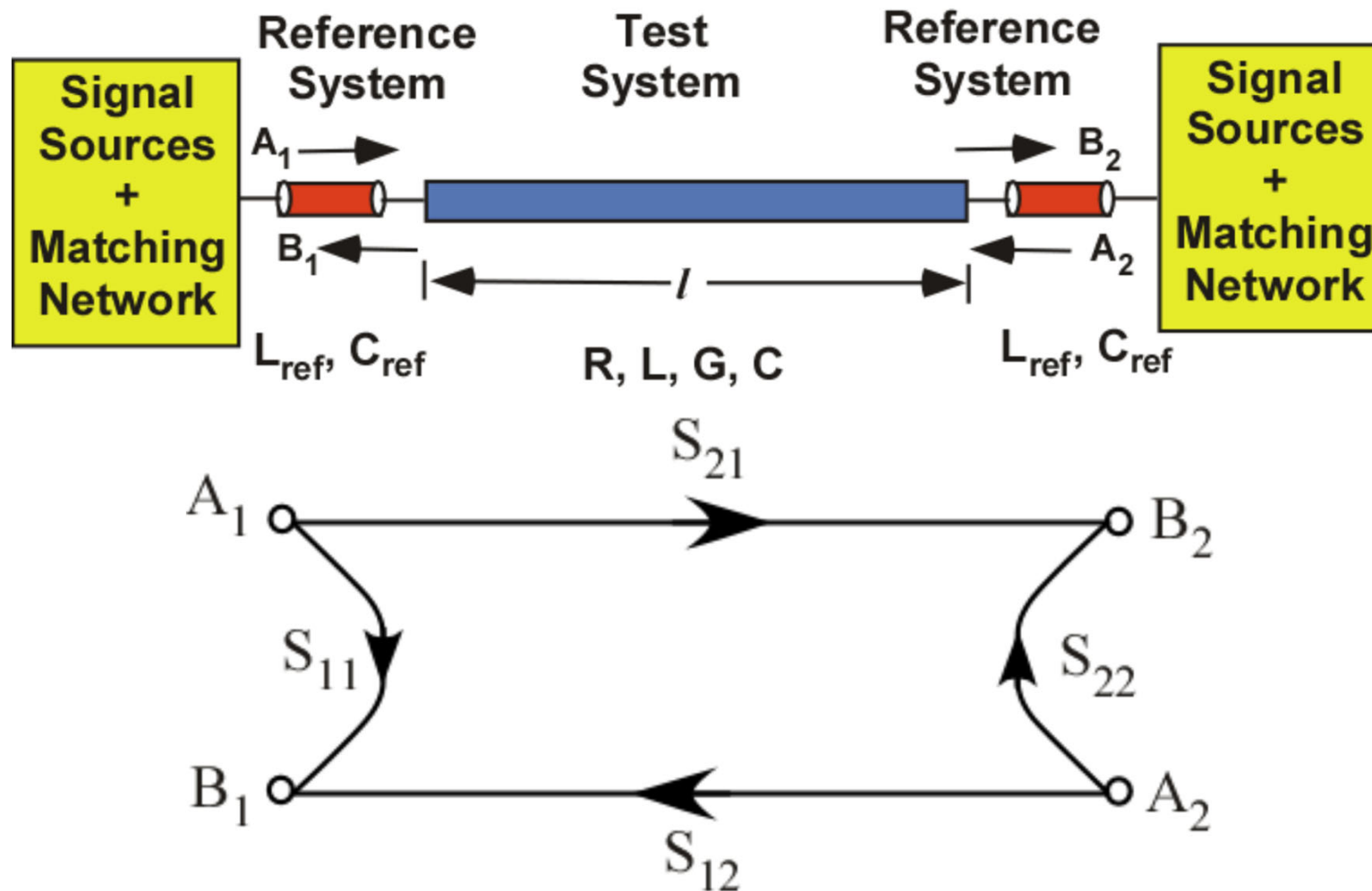

* J. E. Schutt-Aine and R. Mittra, "Scattering Parameter Transient analysis of transmission lines loaded with nonlinear terminations," IEEE Trans. Microwave Theory Tech., vol. MTT-36, pp. 529-536, March 1988.



Frequency-Domain

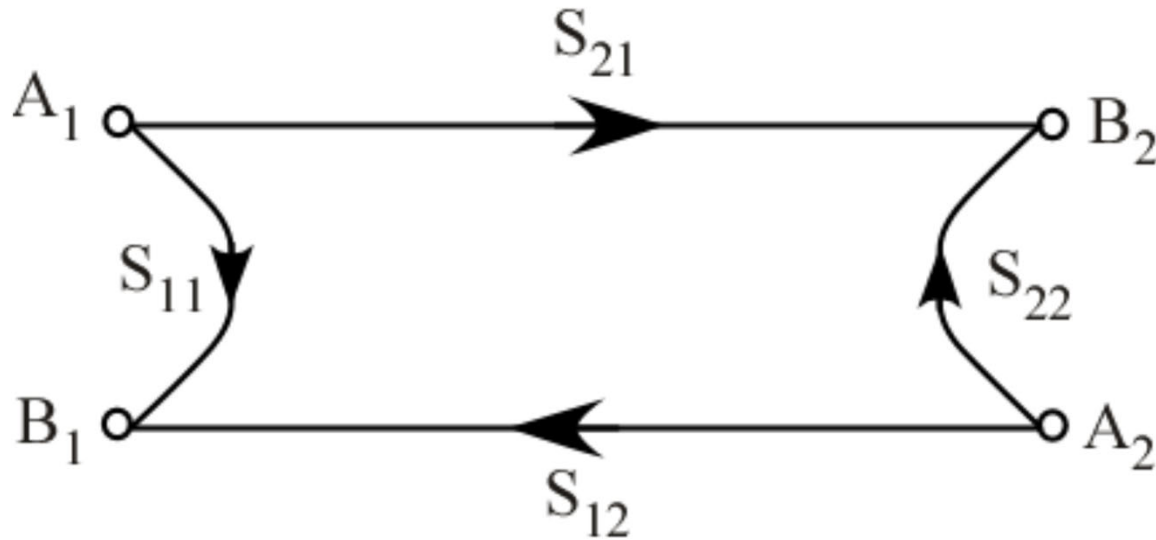


$$B_1(\omega) = S_{11}(\omega) A_1(\omega) + S_{12}(\omega) A_2(\omega)$$

$$B_2(\omega) = S_{21}(\omega) A_1(\omega) + S_{22}(\omega) A_2(\omega)$$

Time-Domain Formulation

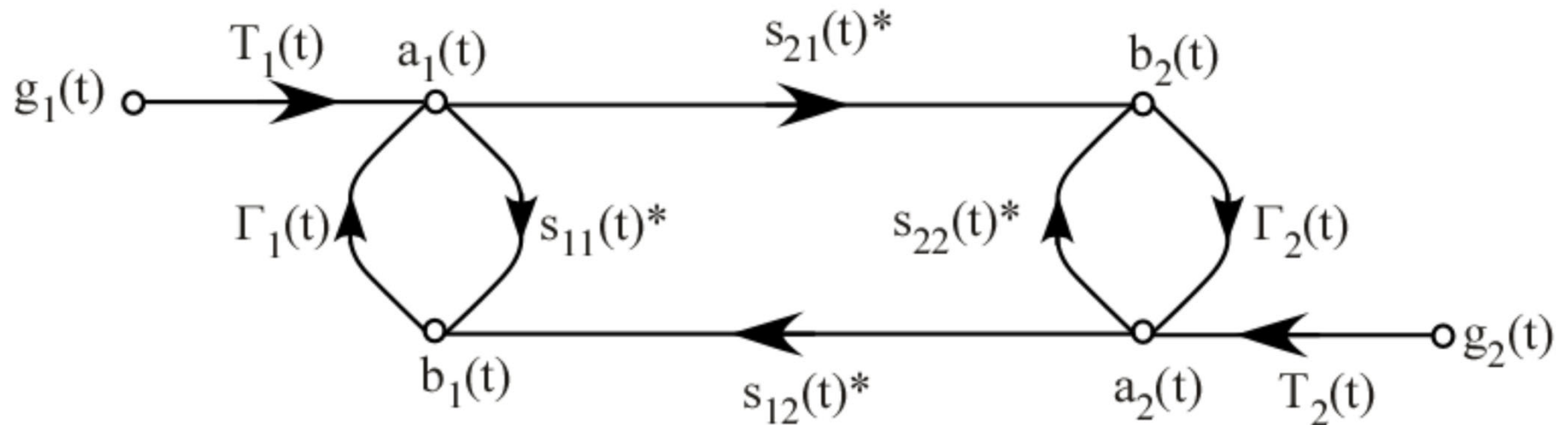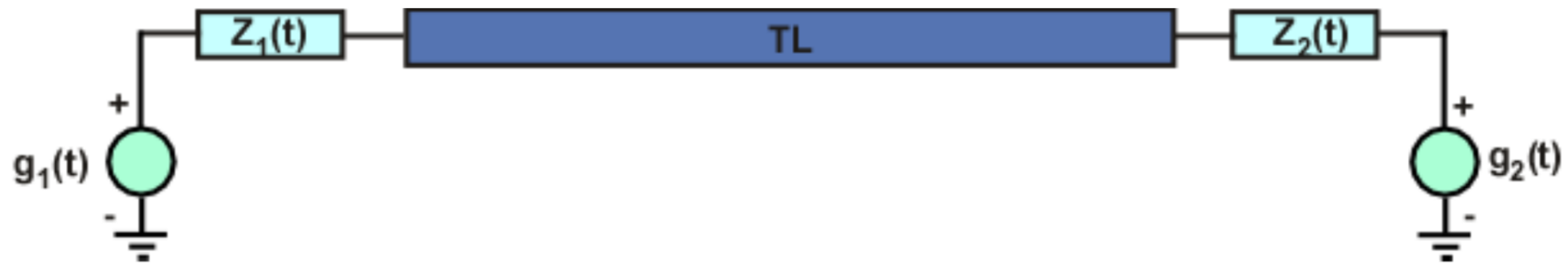

Time-Domain Formulation

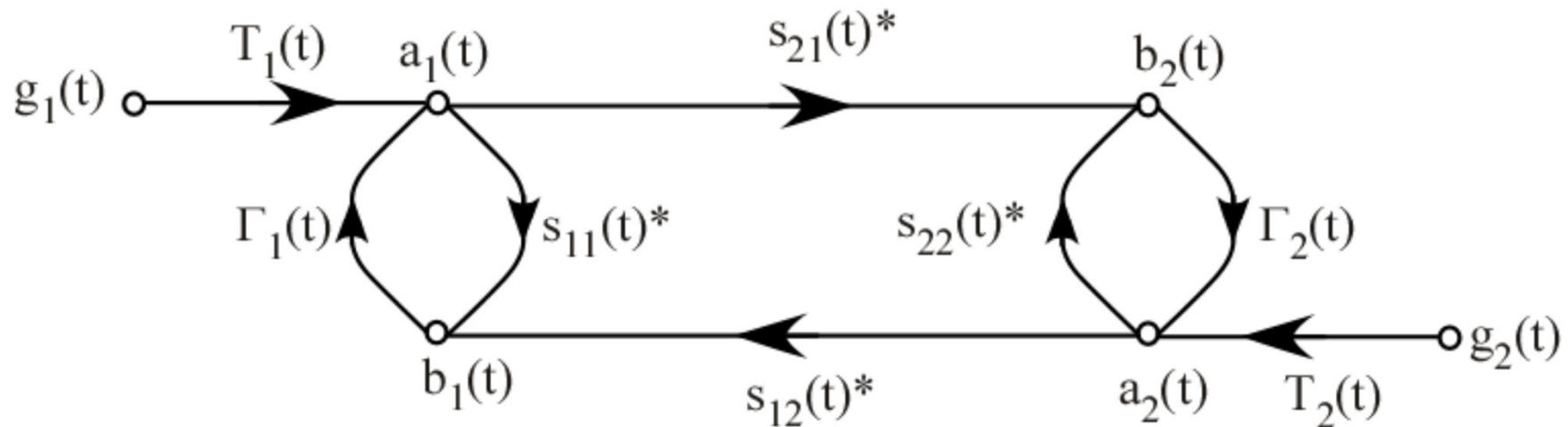

$$b_1(t) = s_{11}(t)^* a_1(t) + s_{12}(t)^* a_2(t)$$

$$b_2(t) = s_{21}(t)^* a_1(t) + s_{22}(t)^* a_2(t)$$

$$a_1(t) = \Gamma_1(t) b_1(t) + T_1(t) g_1(t)$$

$$a_2(t) = \Gamma_2(t) b_2(t) + T_2(t) g_2(t)$$

$$T_i(t) = \frac{Z_o}{Z_i(t) + Z_o}$$

$$\Gamma_i(t) = \frac{Z_i(t) - Z_o}{Z_i(t) + Z_o}$$

Time-Domain Solutions

$$a_1(t) = \frac{\left[1 - \Gamma_2(t)s'_{22}(0)\right] \left[T_1(t)g_1(t) + \Gamma_1(t)M_1(t)\right]}{\Delta(t)} + \frac{\left[\Gamma_1(t)s'_{12}(0)\right] \left[T_2(t)g_2(t) + \Gamma_2(t)M_2(t)\right]}{\Delta(t)}$$
$$a_2(t) = \frac{\left[1 - \Gamma_1(t)s'_{11}(0)\right] \left[T_2(t)g_2(t) + \Gamma_2(t)M_2(t)\right]}{\Delta(t)} + \frac{\left[\Gamma_2(t)s'_{21}(0)\right] \left[T_1(t)g_1(t) + \Gamma_1(t)M_1(t)\right]}{\Delta(t)}$$

Time-Domain Solutions

$$b_1(t) = s'_{11}(0)a_1(t) + s'_{12}(0)a_2(t) + M_1(t)$$

$$b_2(t) = s'_{21}(0)a_1(t) + s'_{22}(0)a_2(t) + M_2(t)$$

$$\Delta(t) = \left[1 - \Gamma_1(t)s'_{11}(0)\right] \left[1 - \Gamma_2(t)s'_{22}(0)\right] - \Gamma_1(t)s'_{12}(0)\Gamma_2(t)s'_{21}(0)$$

$$M_1(t) = H_{11}(t) + H_{12}(t)$$

$$M_2(t) = H_{21}(t) + H_{22}(t)$$

$$s'_{ij}(0) = s_{ij}(0)\Delta\tau$$

$$H_{ij}(t) = \sum_{\tau=1}^{t-1} s_{ij}(t-\tau)a_j(\tau)\Delta\tau$$

Special Case – Lossless Line

$$s_{11}(t) = s_{22}(t) = 0 \qquad s_{12}(t) = s_{21}(t) = \delta\left(t - \frac{l}{v}\right)$$

$$M_1(t) = a_2\left(t - \frac{l}{v}\right) \qquad M_2(t) = a_1\left(t - \frac{l}{v}\right)$$

$$a_1(t) = T_1(t)g_1(t) + \Gamma_1(t)a_2\left(t - \frac{l}{v}\right)$$

$$a_2(t) = T_2(t)g_2(t) + \Gamma_2(t)a_1\left(t - \frac{l}{v}\right)$$

$$b_1(t) = a_2\left(t - \frac{l}{v}\right)$$

$$b_2(t) = a_1\left(t - \frac{l}{v}\right)$$

Wave Shifting Solution

Time-Domain Solutions

$$v_1(t) = a_1(t) + b_1(t)$$

$$v_2(t) = a_2(t) + b_2(t)$$

$$i_1(t) = \frac{a_1(t)}{Z_o} - \frac{b_1(t)}{Z_o}$$


$$i_2(t) = \frac{a_2(t)}{Z_o} - \frac{b_2(t)}{Z_o}$$

Simulations





Line length = 1.27m

$Z_0 = 73 \Omega$


$v = 0.142 \text{ m/ns}$

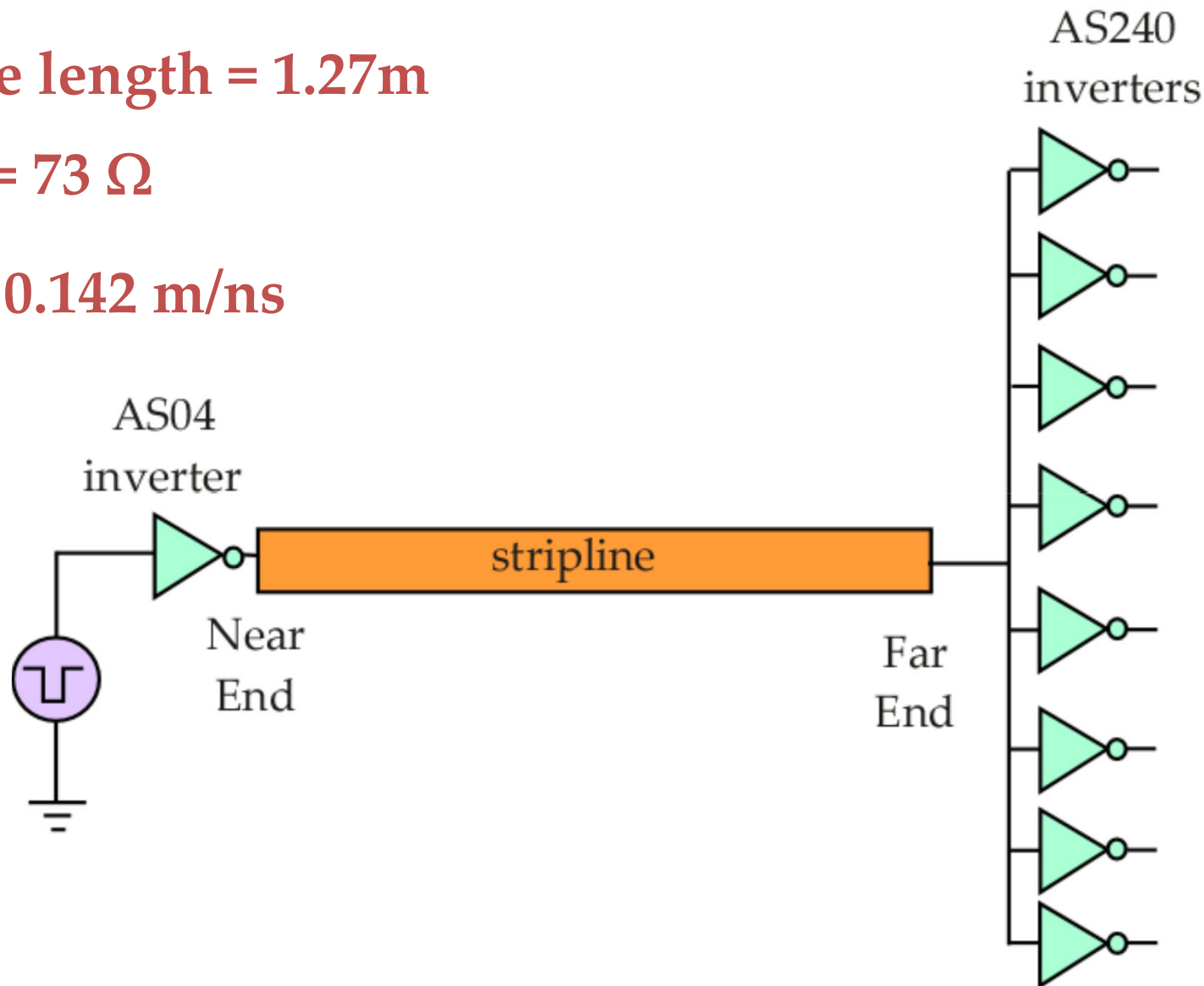



Simulations

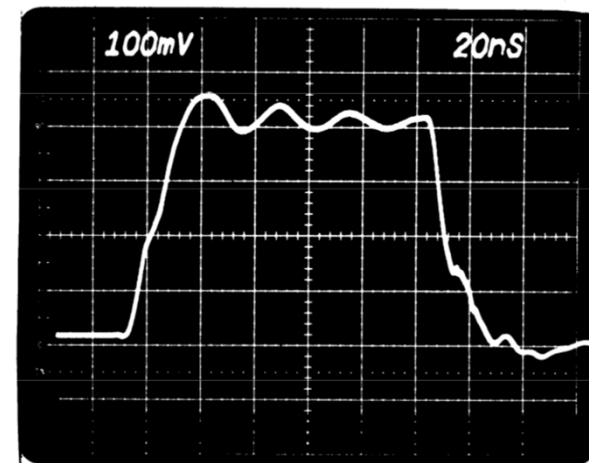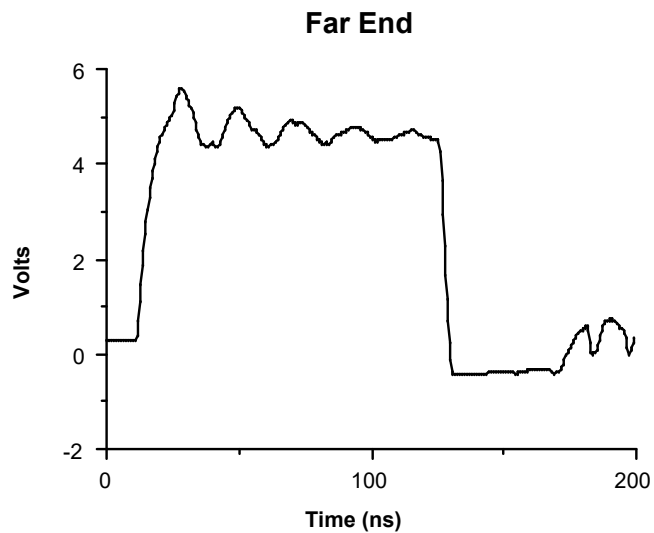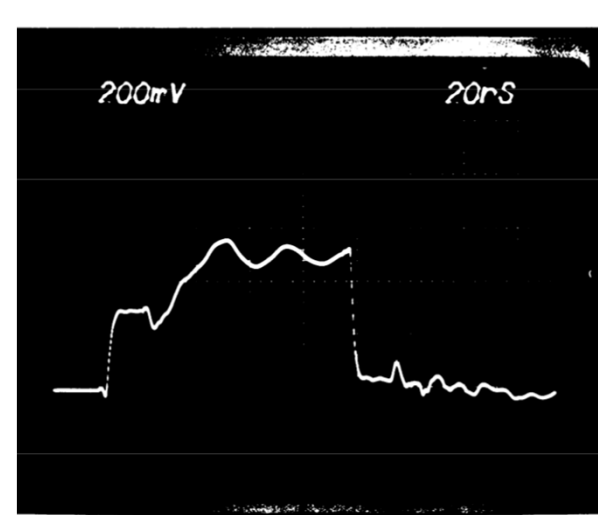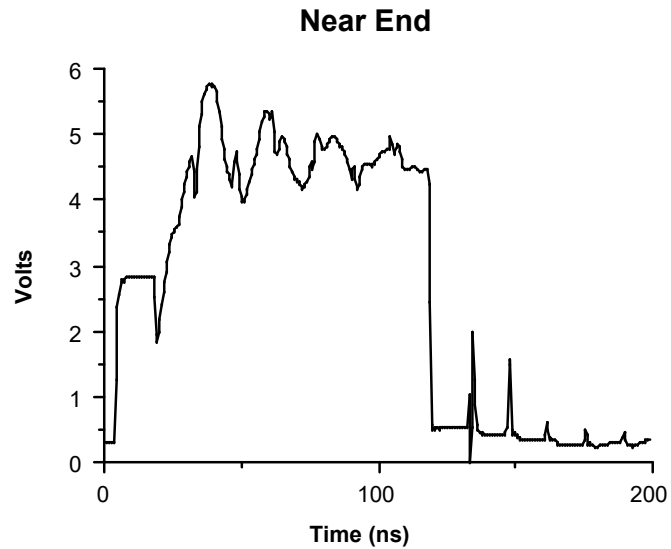


Simulations

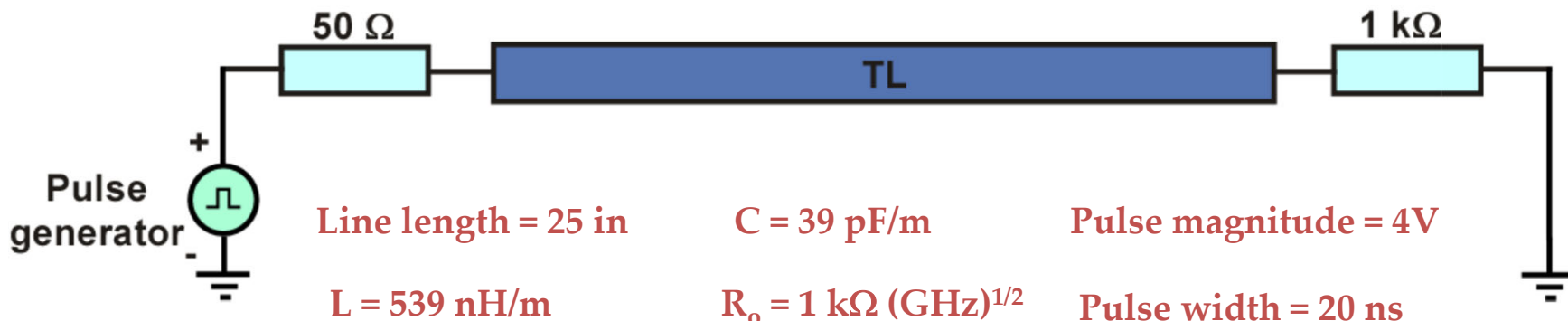

Rise and fall times = 1ns

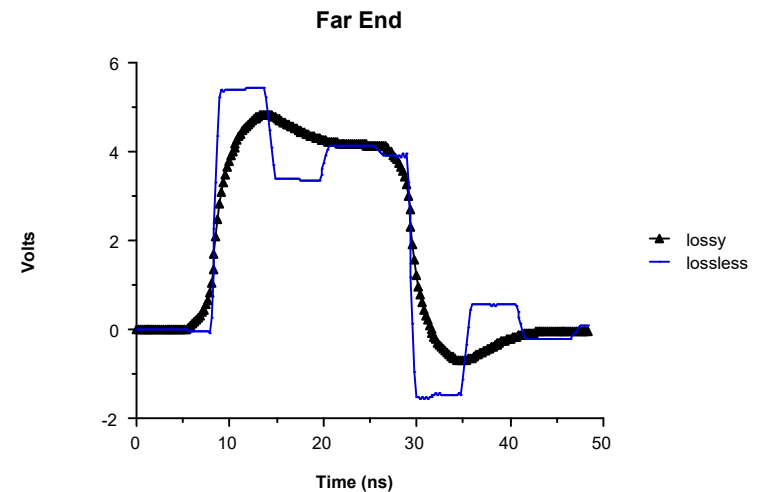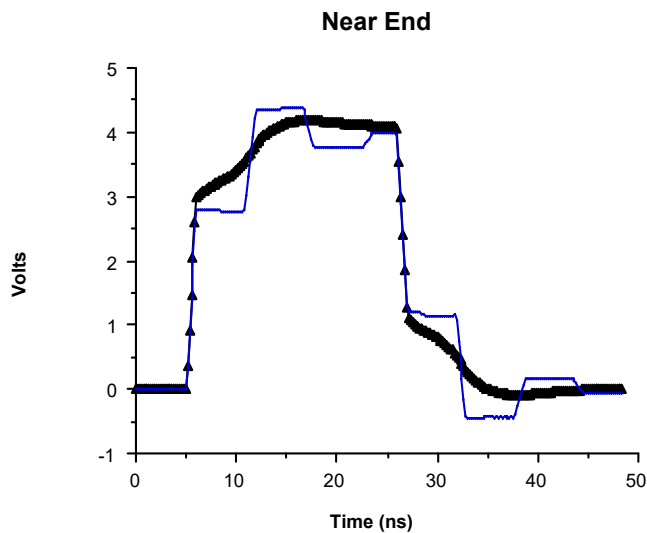

N-Line S-Parameters*

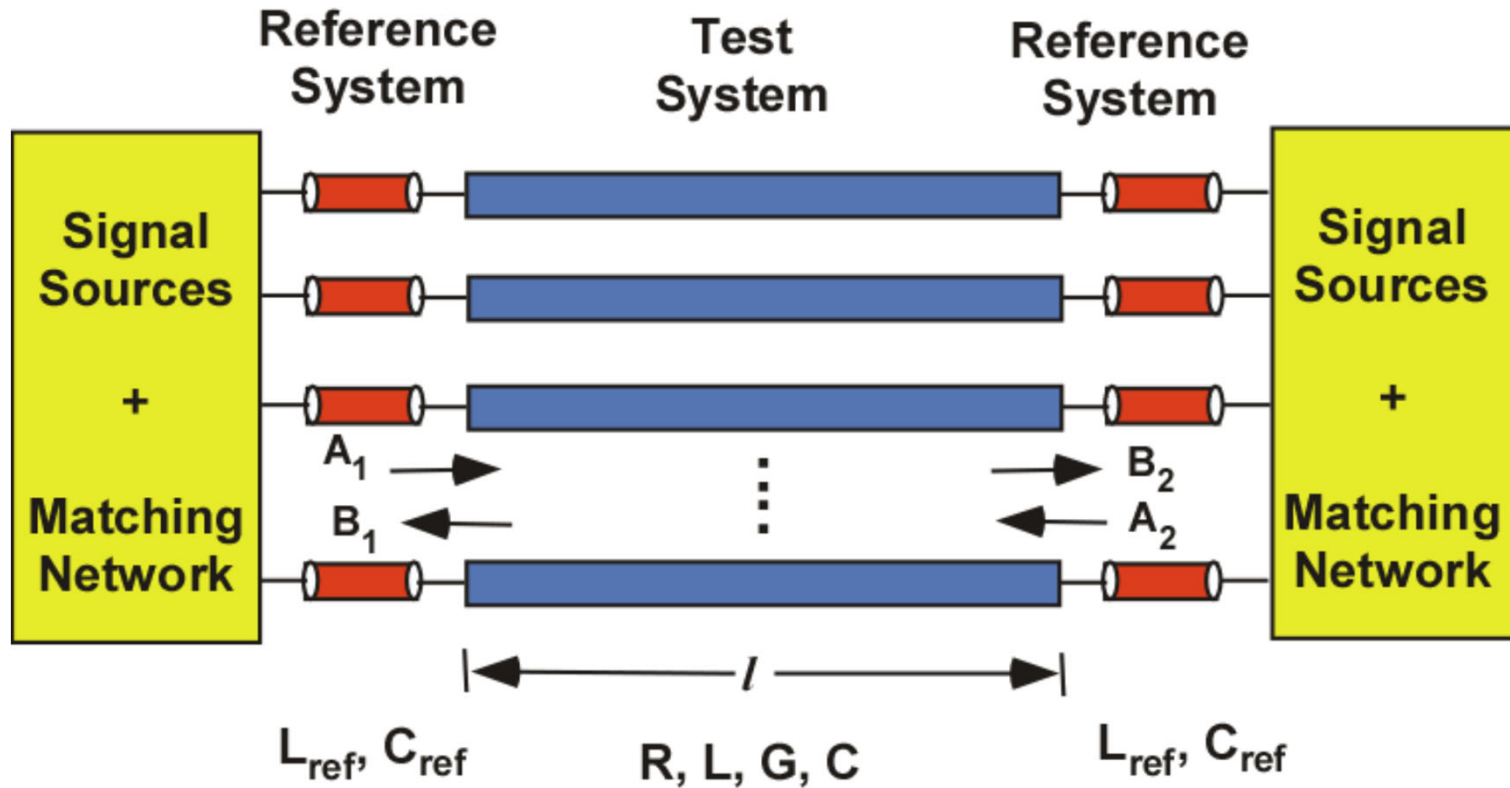


$$B_1 = S_{11} A_1 + S_{12} A_2$$

$$B_2 = S_{21} A_1 + S_{22} A_2$$

* J. E. Schutt-Aine and R. Mittra, "Transient analysis of coupled lossy transmission lines with nonlinear terminations," IEEE Trans. Circuit Syst., vol. CAS-36, pp. 959-967, July 1989.

Scattering Parameters for N-Line

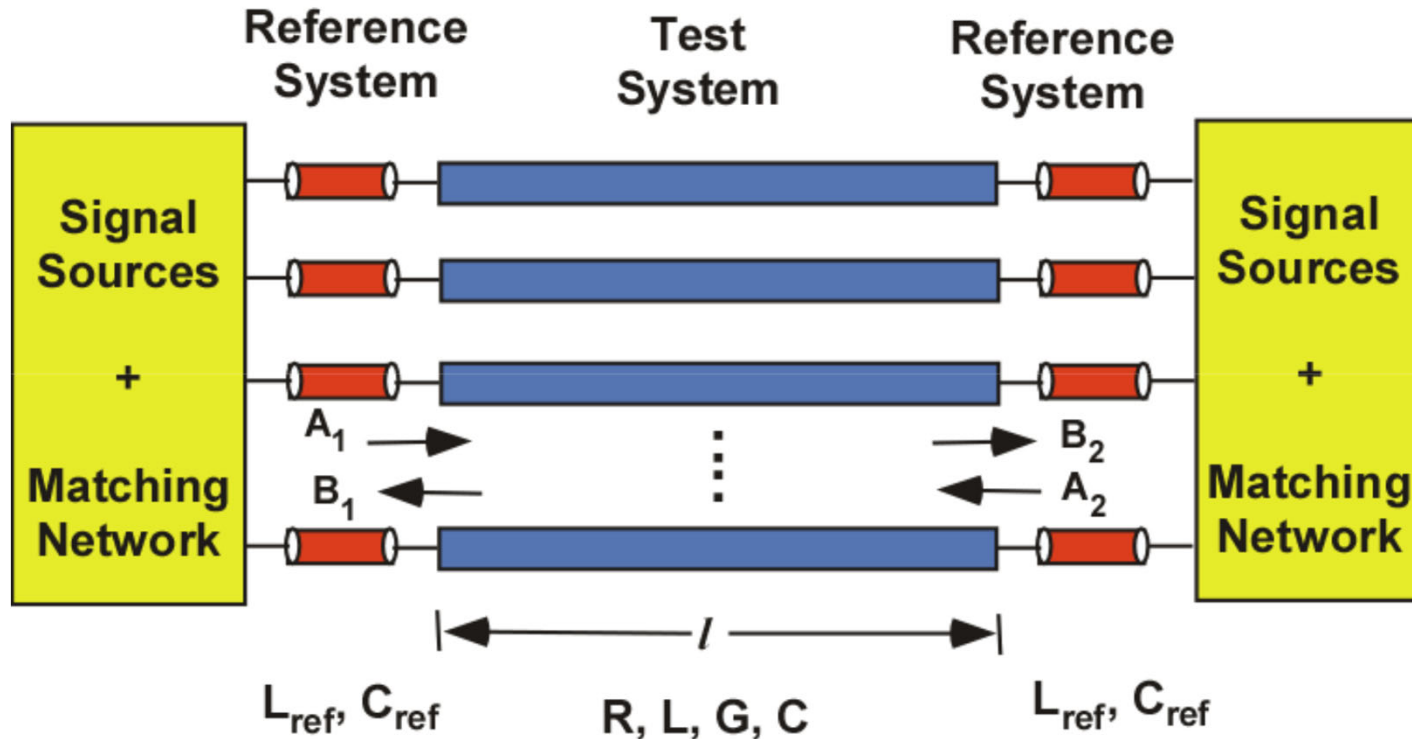

$$S_{21} = S_{12} = 2\mathbf{E}_0\mathbf{E}^{-1} [1 - \Gamma] \Psi [1 - \Gamma\Psi\Gamma\Psi]^{-1} \mathbf{T}$$

$$S_{11} = S_{22} = \mathbf{T}^{-1} [\Gamma - \Psi\Gamma\Psi] [1 - \Gamma\Psi\Gamma\Psi]^{-1} \mathbf{T}$$

$$\Gamma = \left[1 + \mathbf{E}\mathbf{E}_0^{-1}\mathbf{Z}_0\mathbf{H}_0\mathbf{H}^{-1}\mathbf{Z}_m^{-1} \right]^{-1} \left[1 - \mathbf{E}\mathbf{E}_0^{-1}\mathbf{Z}_0\mathbf{H}_0\mathbf{H}^{-1}\mathbf{Z}_m^{-1} \right]$$

$$\mathbf{T} = \left[1 + \mathbf{E}\mathbf{E}_0^{-1}\mathbf{Z}_0\mathbf{H}_0\mathbf{H}^{-1}\mathbf{Z}_m^{-1} \right]^{-1} \mathbf{E}\mathbf{E}_0^{-1} \quad \Psi = \mathbf{W}(-l)$$

Scattering Parameter Matrices

E_0 : Reference system voltage eigenvector matrix

E : Test system voltage eigenvector matrix

H_0 : Reference system current eigenvector matrix

H : Test system current eigenvector matrix

Z_0 : Reference system modal impedance matrix

Z_m : Test system modal impedance matrix

Solution

$$\mathbf{V}_m = \mathbf{E}\mathbf{V}$$

$$\mathbf{I}_m = \mathbf{H}\mathbf{I}$$

$$\mathbf{V}_m(x) = [\mathbf{W}(-x)\mathbf{A} + \mathbf{W}(x)\mathbf{B}]$$

$$\mathbf{I}_m(x) = \mathbf{Z}_m^{-1} [\mathbf{W}(-x)\mathbf{A} + \mathbf{W}(x)\mathbf{B}]$$

$$\mathbf{Z}_m = \Lambda_m^{-1} \mathbf{E} \mathbf{Z} \mathbf{H}^{-1}$$

$$\mathbf{Z}_c = \mathbf{E}^{-1} \mathbf{Z}_m \mathbf{H} = \mathbf{E}^{-1} \Lambda_m^{-1} \mathbf{E} \mathbf{Z}$$

Solutions

$$\begin{aligned} a_1(t) = & \Delta_1^{-1} [1 - \Gamma_1(t)s'_{11}(0)]^{-1} [T_1(t)g_1(t) + \Gamma_1(t)M_1(t)] \\ & - \Delta_1^{-1} [1 - \Gamma_1(t)s'_{11}(0)]^{-1} [1 - \Gamma_2(t)s'_{22}(0)]^{-1} \times \\ & [\Gamma_1(t)s'_{21}(0)] [T_2(t)g_2(t) + \Gamma_2(t)M_2(t)] \end{aligned}$$

$$\begin{aligned} a_2(t) = & \Delta_2^{-1} [1 - \Gamma_2(t)s'_{22}(0)]^{-1} [T_2(t)g_2(t) + \Gamma_2(t)M_2(t)] \\ & - \Delta_2^{-1} [1 - \Gamma_2(t)s'_{22}(0)]^{-1} [1 - \Gamma_1(t)s'_{11}(0)]^{-1} \times \\ & [\Gamma_1(t)s'_{12}(0)] [T_1(t)g_1(t) + \Gamma_1(t)M_1(t)] \end{aligned}$$

Solutions

$$\Delta_1(t) = 1 - \left[1 - \Gamma_1(t)s'_{11}(0)\right]^{-1} \left[1 - \Gamma_2(t)s'_{22}(0)\right]^{-1} \Gamma_1(t)s'_{21}(0)\Gamma_2(t)s'_{12}(0)$$

$$\Delta_2(t) = 1 - \left[1 - \Gamma_2(t)s'_{22}(0)\right]^{-1} \left[1 - \Gamma_1(t)s'_{11}(0)\right]^{-1} \Gamma_2(t)s'_{12}(0)\Gamma_1(t)s'_{21}(0)$$



$$b_1(t) = s'_{11}(0)a_1(t) + s'_{12}(0)a_2(t) + M_1(t)$$

$$b_2(t) = s'_{21}(0)a_1(t) + s'_{22}(0)a_2(t) + M_2(t)$$

Solutions

$$v_{m1}(t) = a_1(t) + b_1(t) \Rightarrow v_1(t) = E_o^{-1} [a_1(t) + b_1(t)]$$
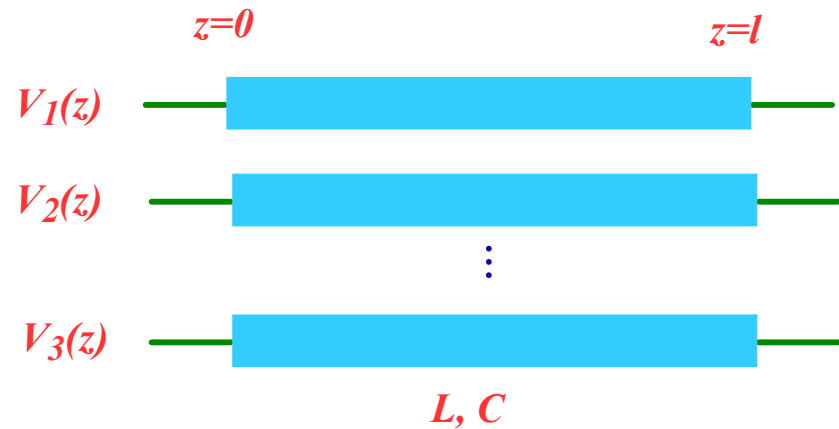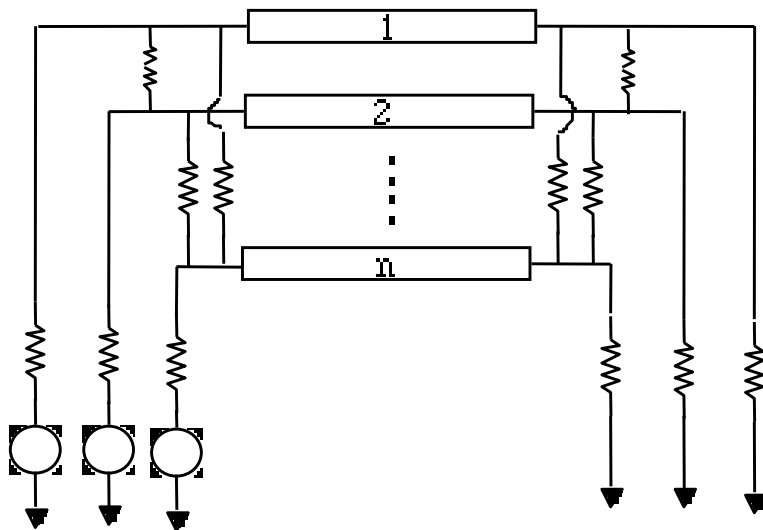
$$v_{m2}(t) = a_2(t) + b_2(t) \Rightarrow v_2(t) = E_o^{-1} [a_2(t) + b_2(t)]$$



Lossless Case – Wave Shifting

$$s_{21}(t) = s_{12}(t) = \delta(t - \tau_m)$$

$$M_1(t) = a_2(t - \tau_m)$$

$$M_2(t) = a_1(t - \tau_m)$$

$$a_1(t) = T_1(t)g_1(t) + \Gamma_1(t)a_2(t - \tau_m)$$

$$a_2(t) = T_2(t)g_3(t) + \Gamma_3(t)a_1(t - \tau_m)$$

$$b_1(t) = a_2(t - \tau_m)$$


$$b_2(t) = a_1(t - \tau_m)$$

Solution for Lossless Lines

$$\delta(\mathbf{t} - \tau_{\mathbf{m}}) = \begin{pmatrix} \delta(t - \tau_{m1}) & & & \\ & \delta(t - \tau_{m2}) & & \\ & & \bullet & \\ & & & \delta(t - \tau_{mn}) \end{pmatrix}$$

$$\mathbf{a}_i(\mathbf{t} - \tau_{\mathbf{m}}) = \begin{bmatrix} a_1(t - \tau_{m1}) \\ a_2(t - \tau_{m2}) \\ \bullet \\ a_n(t - \tau_{mn}) \end{bmatrix}$$

N-Line Network

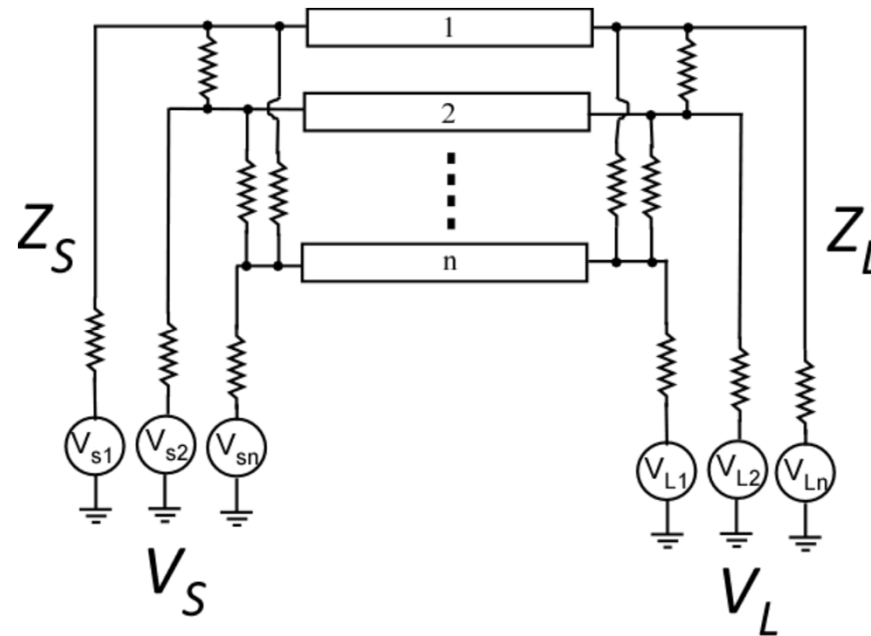

Z_S : Source impedance matrix

Z_L : Load impedance matrix

V_S : Source vector

N-Line Simulation

- Get L and C matrices and calculate LC product
- Get square root of eigenvalues and eigenvectors of LC matrix Λ_m
- Arrange eigenvectors into the voltage eigenvector matrix E
- Get square root of eigenvalues and eigenvectors of CL matrix Λ_m
- Arrange eigenvectors into the current eigenvector matrix H
- Invert matrices E, H, Λ_m .
- Calculate the line impedance matrix $Z_C \rightarrow Z_C = E^{-1} \Lambda_m^{-1} E L$
- Construct source and load impedance matrices $Z_S(t)$ and $Z_L(t)$
- Construct source and load reflection coefficient matrices $\Gamma_1(t)$ and $\Gamma_2(t)$. Indices 1 and 2 refer to near and far ends respectively.

$$\Gamma_1(t) = - \left[\mathbf{1} + E Z_S Z_C^{-1} E^{-1} \right]^{-1} \left[\mathbf{1} - E Z_S Z_C^{-1} E^{-1} \right]$$


$$\Gamma_2(t) = - \left[\mathbf{1} + E Z_L Z_C^{-1} E^{-1} \right]^{-1} \left[\mathbf{1} - E Z_L Z_C^{-1} E^{-1} \right]$$

Procedure for Coupled Lines

- Construct source and load transmission coefficient matrices $T_1(t)$ and $T_2(t)$

$$T_1(t) = \left[\mathbf{1} + \mathbf{E}Z_S\mathbf{Z}_C^{-1}\mathbf{E}^{-1} \right]^{-1}$$
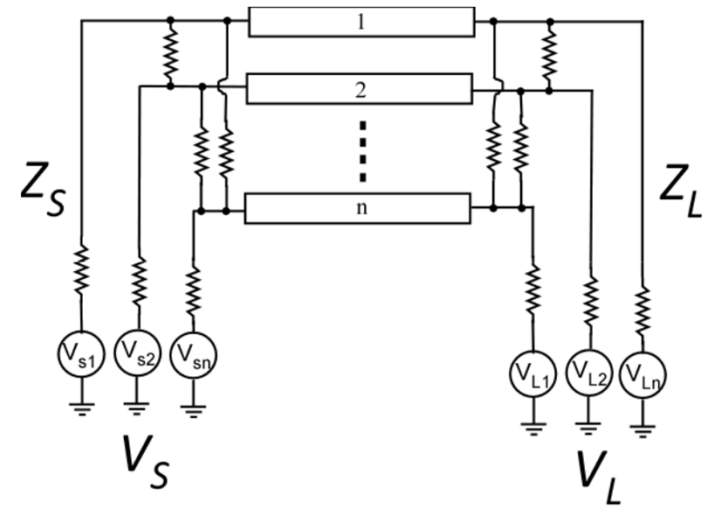
$$T_2(t) = \left[\mathbf{1} + \mathbf{E}Z_L\mathbf{Z}_C^{-1}\mathbf{E}^{-1} \right]^{-1}$$



- Calculate modal voltage source vectors:

$$\mathbf{g}_1(t) = \mathbf{E}\mathbf{V}_S(t)$$

$$\mathbf{g}_2(t) = \mathbf{E}\mathbf{V}_L(t)$$

$$\mathbf{V}_S = \begin{bmatrix} V_{s1} \\ V_{s2} \\ \cdot \\ V_{sn} \end{bmatrix} \quad \mathbf{V}_L = \begin{bmatrix} V_{L1} \\ V_{L2} \\ \cdot \\ V_{Ln} \end{bmatrix}$$

Procedure for Coupled Lines

- Calculate modal voltage wave vectors:

$$\mathbf{a}_1(t) = \mathbf{T}_1(t)\mathbf{g}_1(t) + \mathbf{\Gamma}_1(t)\mathbf{a}_2(t - \tau_m)$$

$$\mathbf{a}_2(t) = \mathbf{T}_2(t)\mathbf{g}_2(t) + \mathbf{\Gamma}_2(t)\mathbf{a}_1(t - \tau_m)$$

$$\mathbf{b}_1(t) = \mathbf{a}_2(t - \tau_m)$$

$$\mathbf{b}_2(t) = \mathbf{a}_1(t - \tau_m)$$

$$\text{where } \mathbf{a}_2(t - \tau_m) = \begin{bmatrix} \mathbf{a}_{i\text{-mode-1}}(t - \tau_{m1}) \\ \mathbf{a}_{i\text{-mode-2}}(t - \tau_{m2}) \\ \cdot \\ \mathbf{a}_{i\text{-mode-n}}(t - \tau_{mn}) \end{bmatrix}$$

τ_{mi} is the delay associated with mode i . $\tau_{mi} = \text{length}/\text{velocity}$ of mode i . The modal voltage wave vectors $\mathbf{a}_1(t)$ and $\mathbf{a}_2(t)$ need to be stored since they contain the history of the system.

Procedure for Coupled Lines

- Calculate total modal voltage wave vectors:

$$\mathbf{V}_{m1}(t) = \mathbf{a}_1(t) + \mathbf{b}_1(t)$$

$$\mathbf{V}_{m2}(t) = \mathbf{a}_2(t) + \mathbf{b}_2(t)$$

- Calculate line voltage wave vectors

$$\mathbf{V}_1(t) = \mathbf{E}^{-1}\mathbf{V}_{m1}(t) \quad \mathbf{V}_2(t) = \mathbf{E}^{-1}\mathbf{V}_{m2}(t) \quad \mathbf{V}_1(t) = \begin{bmatrix} V_{near-line-1} \\ V_{near-line-2} \\ \vdots \\ V_{near-line-n} \end{bmatrix} \quad \mathbf{V}_2(t) = \begin{bmatrix} V_{far-line-1} \\ V_{far-line-2} \\ \vdots \\ V_{far-line-n} \end{bmatrix}$$

Note: subscripts 1 and 2 refer to near and far ends respectively

N-Line - Additional Notes

Eigenvalue matrix


$$\Lambda_m = \begin{bmatrix} \frac{1}{v_{m1}} & & & \\ & \frac{1}{v_{m2}} & & \\ & & \bullet & \\ & & & \frac{1}{v_{mn}} \end{bmatrix}$$

For two-line case, two modes: even and odd. In addition, \mathbf{E} and \mathbf{H} are equal and are independent of the entries of \mathbf{L} and \mathbf{C}

$$\mathbf{E} = \begin{bmatrix} 1 & 1 \\ 1 & -1 \end{bmatrix}$$

$$\mathbf{H} = \begin{bmatrix} 1 & 1 \\ 1 & -1 \end{bmatrix}$$

Source and Load Terminations

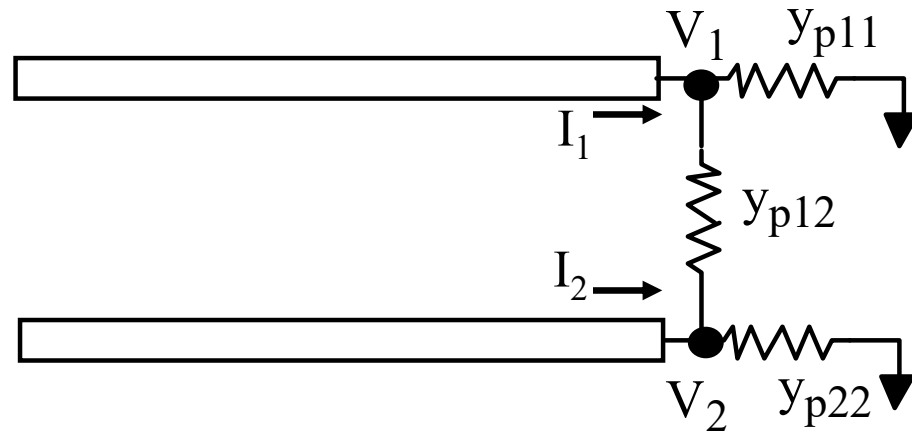

$$I_1 = y_{p11}V_1 + y_{p12}(V_1 - V_2)$$

$$I_1 = y_{11}V_1 + y_{12}V_2$$

$$y_{11} = y_{p11} + y_{p12}$$

$$I_2 = y_{p22}V_2 + y_{p12}(V_2 - V_1)$$

$$I_2 = y_{21}V_1 + y_{22}V_2$$

$$y_{22} = y_{p22} + y_{p12}$$

$$y_{12} = y_{21} = -y_{p12}$$

In general for a multiline system

$$\mathbf{I} = \mathbf{YV} \Rightarrow \mathbf{V} = \mathbf{ZY} \quad \mathbf{Z} = \mathbf{Y}^{-1}$$

Note: $y_{ii} \neq y_{pii}$

$$y_{ij} = -y_{pij} \quad \text{for } i \neq j$$

$$z_{ij} \neq \frac{1}{y_{pij}}$$

Termination Network Construction


To get impedance matrix Z

- Get physical impedance values y_{pij}
- Calculate y_{ij} 's from y_{pij} 's
- Construct Y matrix
- Invert Y matrix to obtain Z matrix

Remark: If $y_{pij} = 0$ for all $i \neq j$, then $Y = Z^{-1}$ and $z_{ii} = 1/y_{ii}$

Why Use S Parameters?

Y-Parameter

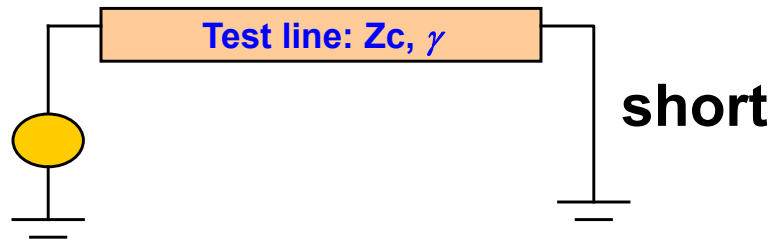

$$Y_{11} = \frac{1 + e^{-2\gamma l}}{Z_c (1 - e^{-2\gamma l})}$$


Z_c : microstrip characteristic impedance

γ : complex propagation constant

l : length of microstrip

Y_{11} can be unstable

S-Parameter

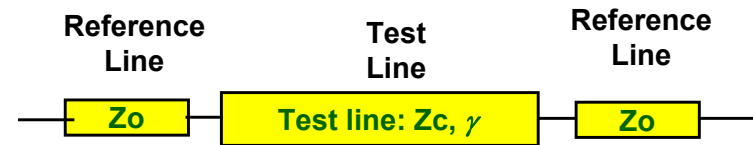

$$S_{11} = \frac{(1 - e^{-2\gamma l})\Gamma}{1 - \Gamma^2 e^{-2\gamma l}}$$

$$\Gamma = \frac{Z_c - Z_o}{Z_c + Z_o}$$

S_{11} is always stable

Choice of Reference

$$\Gamma = \frac{Z_c - Z_{ref}}{Z_c + Z_{ref}}$$

$$Z_c = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

Z_{ref} is arbitrary

What is the best choice for Z_{ref} ?

At high frequencies $Z_c \rightarrow \sqrt{\frac{L}{C}}$

Thus, if we choose $Z_{ref} = \sqrt{\frac{L}{C}}$

$$S_{12} \rightarrow e^{-j\omega\sqrt{LC}d} = X_o \qquad S_{11} \rightarrow 0$$

Choice of Reference

S-Parameter measurements (or simulations) are made using a 50-ohm system. For a 4-port, the reference impedance is given by:

$$Z_o = \begin{bmatrix} 50.0 & 0.0 & 0.0 & 0.0 \\ 0.0 & 50.0 & 0.0 & 0.0 \\ 0.0 & 0.0 & 50.0 & 0.0 \\ 0.0 & 0.0 & 0.0 & 50.0 \end{bmatrix}$$

Z: Impedance matrix (of blackbox)
S: S-parameter matrix
Z_o: Reference impedance
I: Unit matrix

$$S = \left[ZZ_o^{-1} + I \right]^{-1} \left[ZZ_o^{-1} - I \right]$$

$$Z = \left[I + S \right] \left[I - S \right]^{-1} Z_o$$

Reference Transformation

Method: Change reference impedance from uncoupled to coupled system to get new S-parameter representation

$$Z_o = \begin{matrix} 50.0 & 0.0 & 0.0 & 0.0 \\ 0.0 & 50.0 & 0.0 & 0.0 \\ 0.0 & 0.0 & 50.0 & 0.0 \\ 0.0 & 0.0 & 0.0 & 50.0 \end{matrix} \quad \text{Uncoupled system}$$

$$Z_o = \begin{matrix} 328.0 & 69.6 & 328.9 & 69.6 \\ 69.6 & 328.8 & 69.6 & 328.9 \\ 328.9 & 69.6 & 328.8 & 69.6 \\ 69.6 & 328.9 & 69.6 & 328.8 \end{matrix} \quad \text{Coupled system}$$

as an example...

Choice of Reference

using


$$Z_0 = \begin{bmatrix} 50.0 & 0.0 & 0.0 & 0.0 \\ 0.0 & 50.0 & 0.0 & 0.0 \\ 0.0 & 0.0 & 50.0 & 0.0 \\ 0.0 & 0.0 & 0.0 & 50.0 \end{bmatrix}$$

as reference...

using

$$Z_0 = \begin{bmatrix} 328.0 & 69.6 & 328.9 & 69.6 \\ 69.6 & 328.8 & 69.6 & 328.9 \\ 328.9 & 69.6 & 328.8 & 69.6 \\ 69.6 & 328.9 & 69.6 & 328.8 \end{bmatrix}$$

as reference...

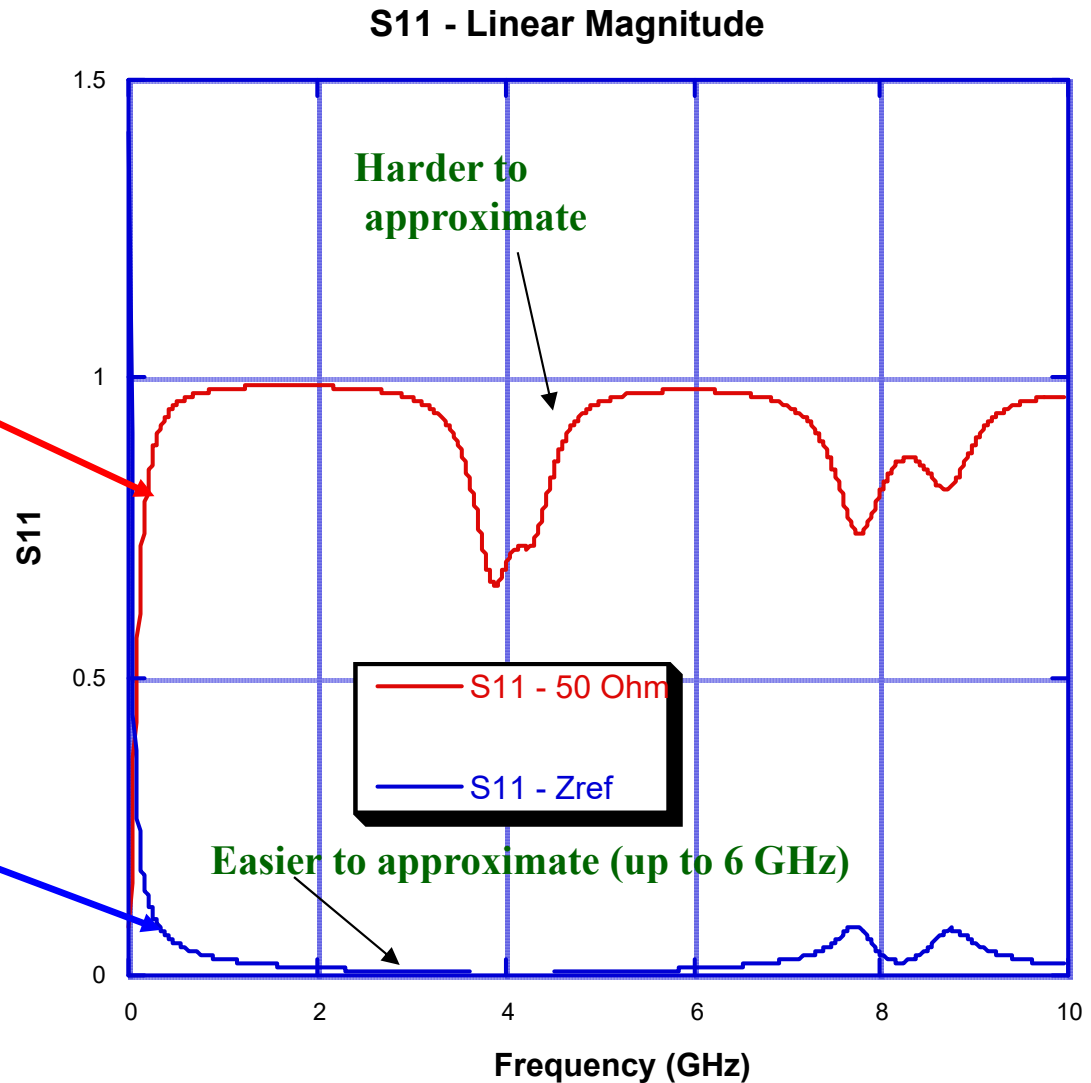

Choice of Reference

using

$$Z_0 = \begin{bmatrix} 50.0 & 0.0 & 0.0 & 0.0 \\ 0.0 & 50.0 & 0.0 & 0.0 \\ 0.0 & 0.0 & 50.0 & 0.0 \\ 0.0 & 0.0 & 0.0 & 50.0 \end{bmatrix}$$


as reference...

using

$$Z_0 = \begin{bmatrix} 328.0 & 69.6 & 328.9 & 69.6 \\ 69.6 & 328.8 & 69.6 & 328.9 \\ 328.9 & 69.6 & 328.8 & 69.6 \\ 69.6 & 328.9 & 69.6 & 328.8 \end{bmatrix}$$

as reference...

S11 - Linear Magnitude

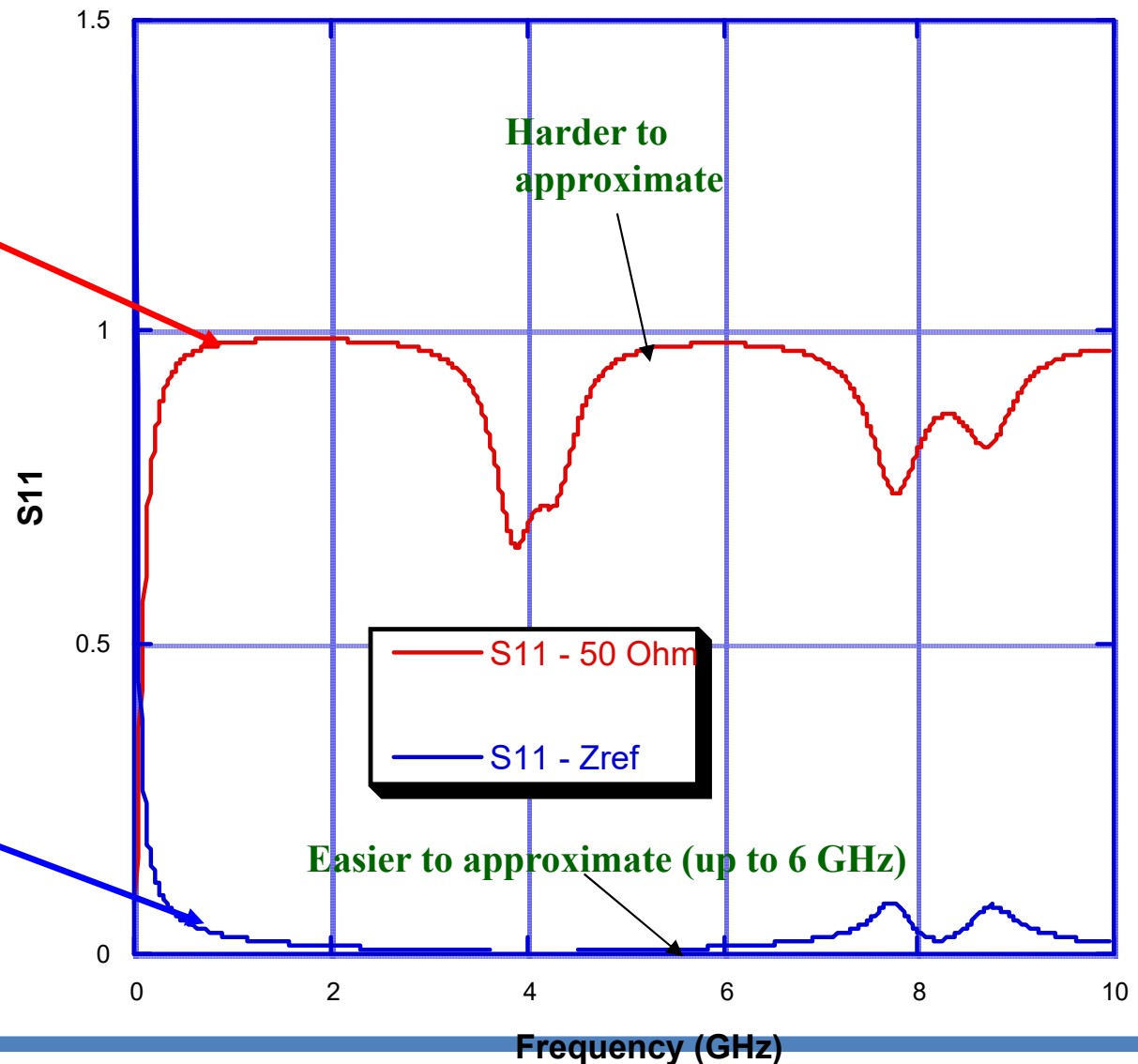

Choice of Reference

using

$$Z_0 = \begin{bmatrix} 50.0 & 0.0 & 0.0 & 0.0 \\ 0.0 & 50.0 & 0.0 & 0.0 \\ 0.0 & 0.0 & 50.0 & 0.0 \\ 0.0 & 0.0 & 0.0 & 50.0 \end{bmatrix}$$


as reference...

using

$$Z_0 = \begin{bmatrix} 328.0 & 69.6 & 328.9 & 69.6 \\ 69.6 & 328.8 & 69.6 & 328.9 \\ 328.9 & 69.6 & 328.8 & 69.6 \\ 69.6 & 328.9 & 69.6 & 328.8 \end{bmatrix}$$

as reference...

S12 - Linear Magnitude

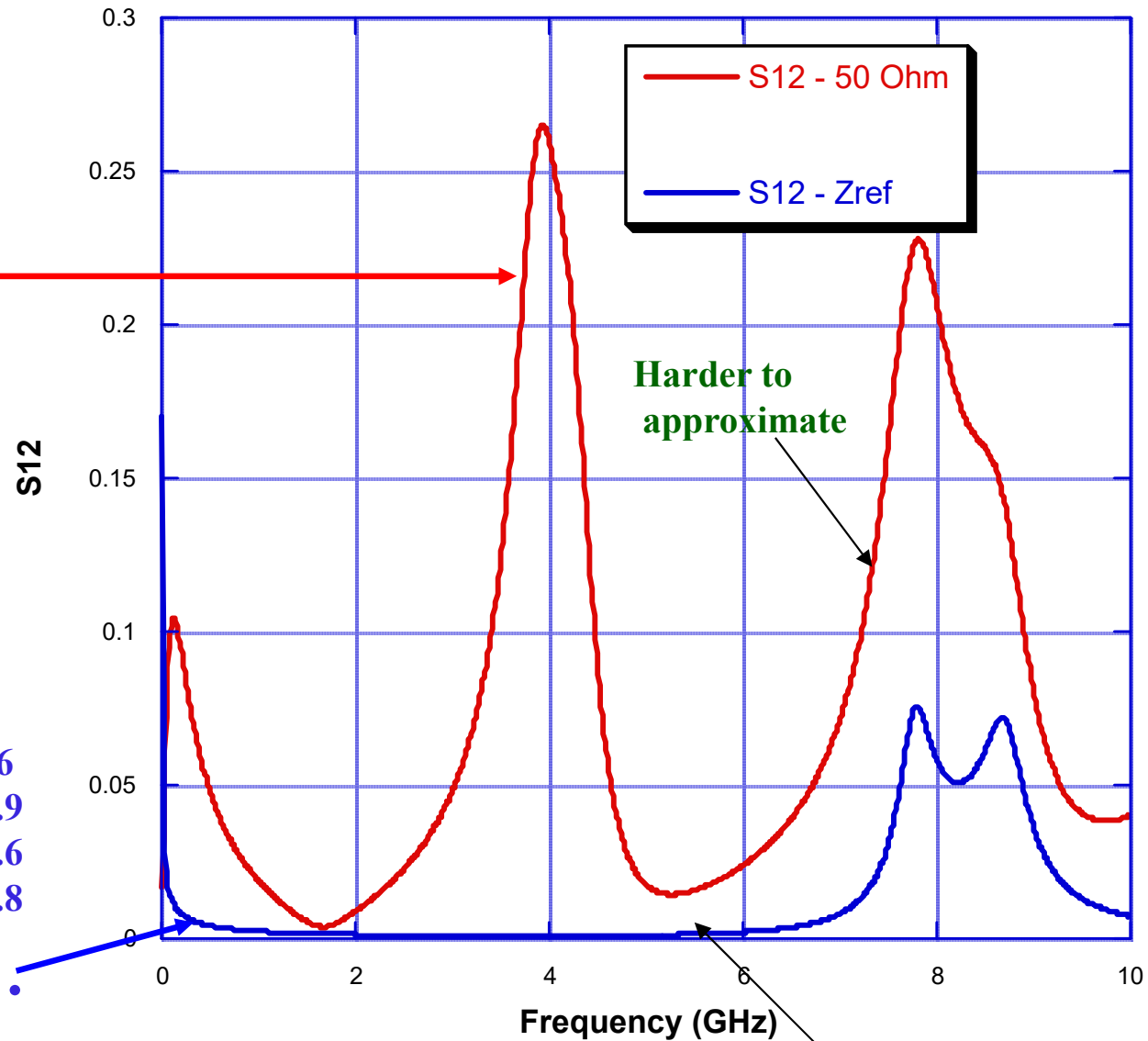

Easier to approximate (up to 6 GHz)

Choice of Reference

S31 - Linear Magnitude

using


$$Z_0 = \begin{bmatrix} 328.0 & 69.6 & 328.9 & 69.6 \\ 69.6 & 328.8 & 69.6 & 328.9 \\ 328.9 & 69.6 & 328.8 & 69.6 \\ 69.6 & 328.9 & 69.6 & 328.8 \end{bmatrix}$$

as reference...


using

$$Z_0 = \begin{bmatrix} 50.0 & 0.0 & 0.0 & 0.0 \\ 0.0 & 50.0 & 0.0 & 0.0 \\ 0.0 & 0.0 & 50.0 & 0.0 \\ 0.0 & 0.0 & 0.0 & 50.0 \end{bmatrix}$$


as reference...

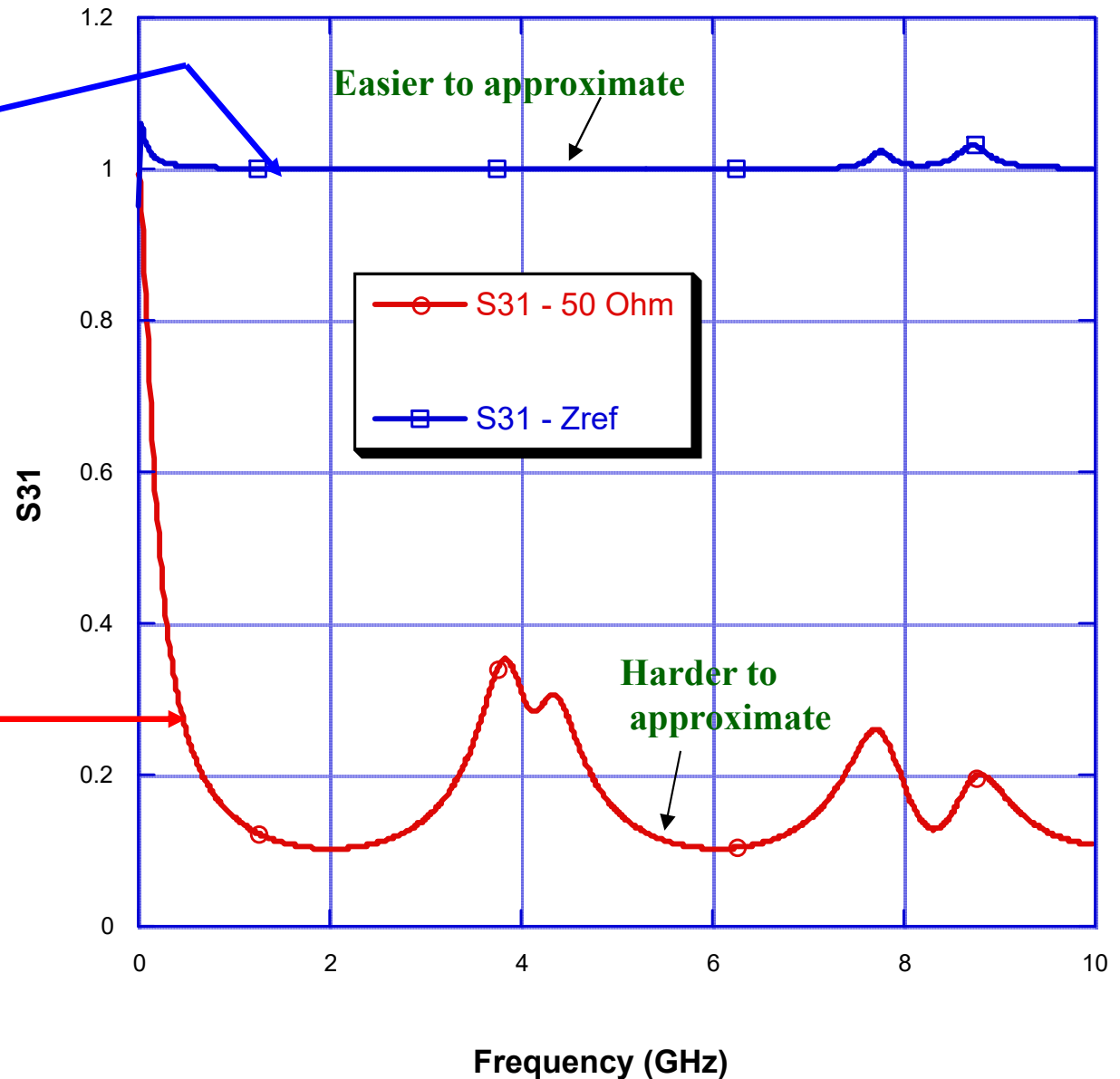

Choice of Reference

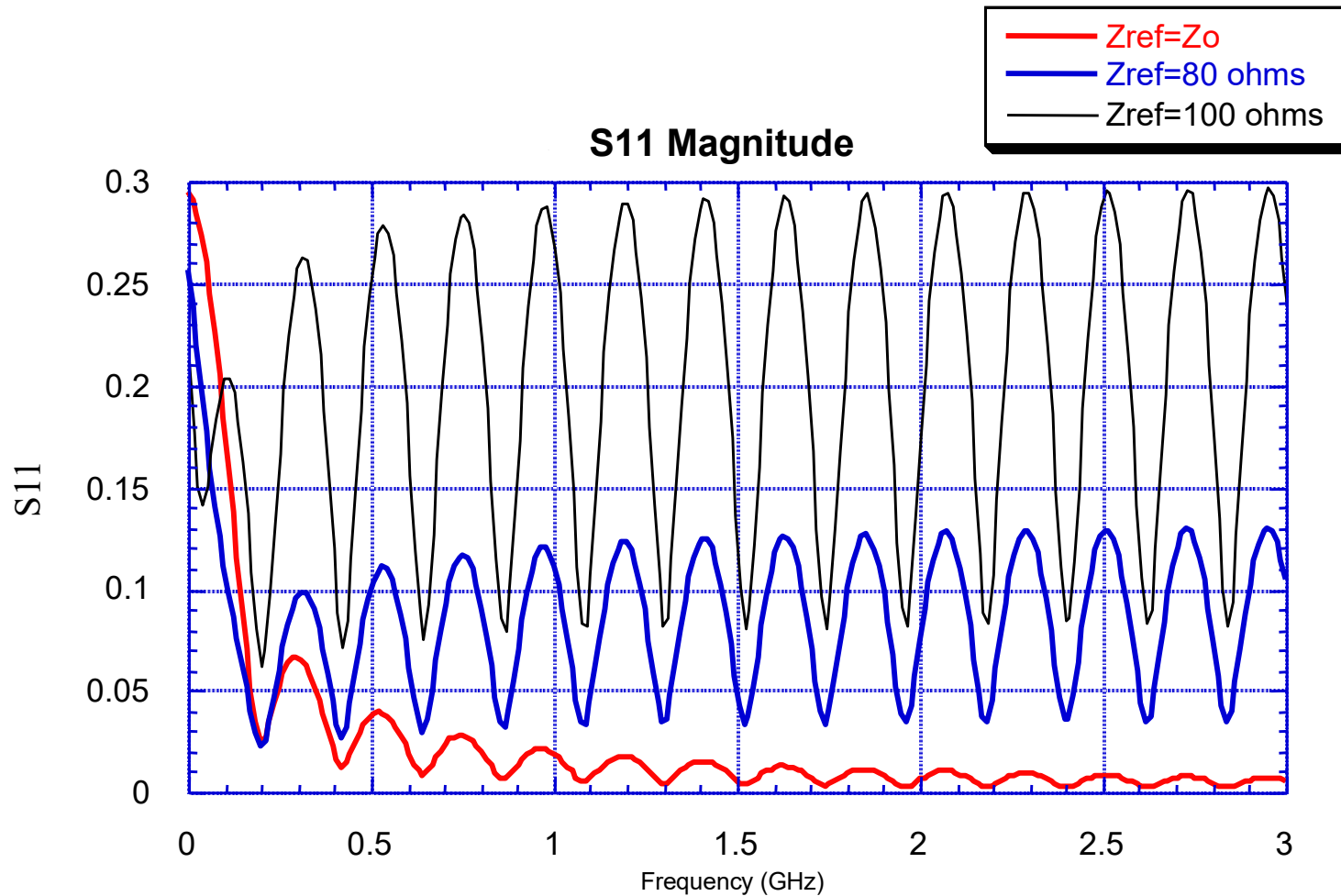

Choice of Reference

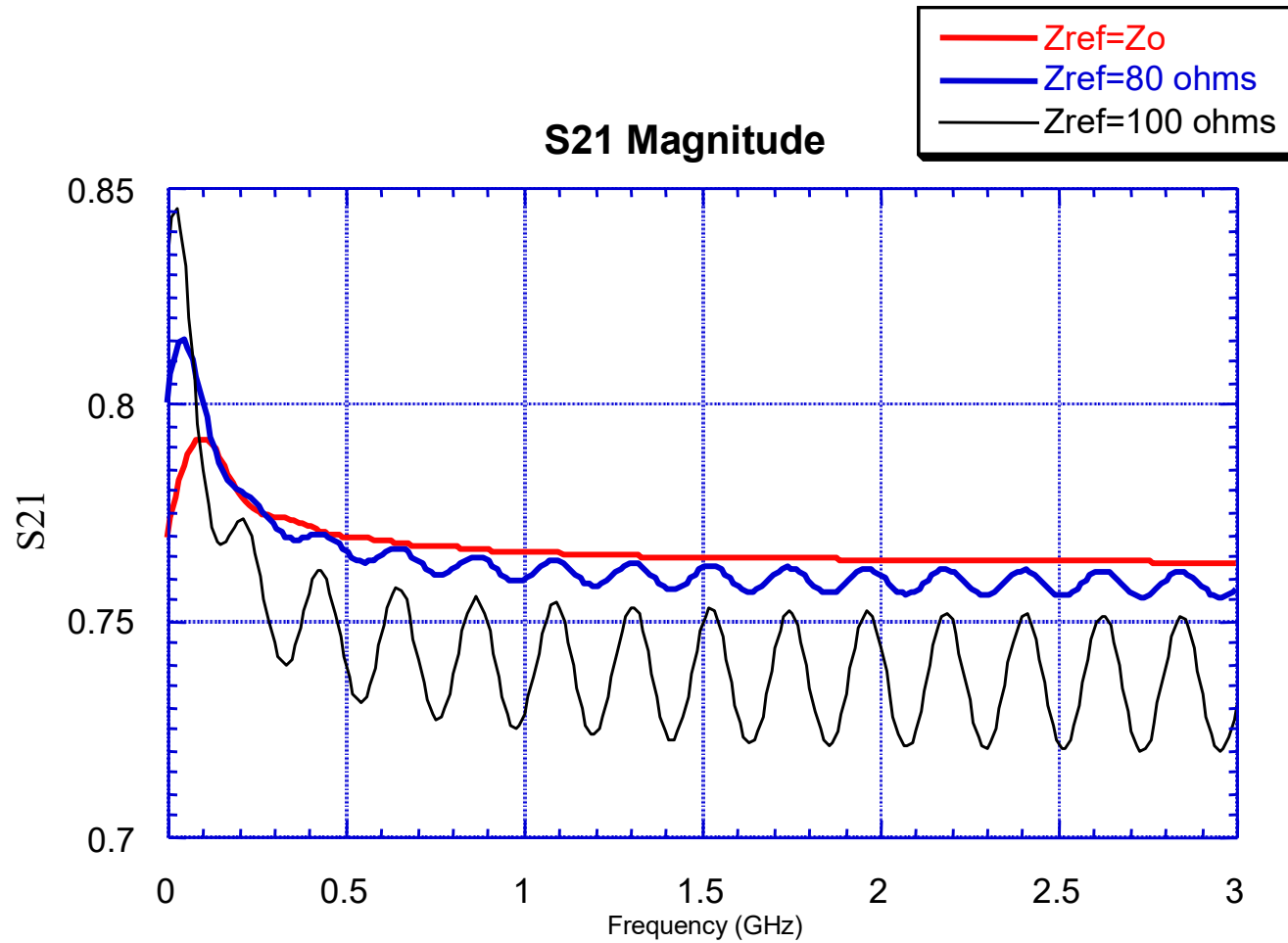

Differential Scattering Parameters



$$S_{AA} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix}$$

$$S_{AB} = \begin{bmatrix} S_{13} & S_{14} \\ S_{23} & S_{24} \end{bmatrix}$$

$$S_{BA} = \begin{bmatrix} S_{31} & S_{32} \\ S_{41} & S_{42} \end{bmatrix}$$

$$S_{BB} = \begin{bmatrix} S_{33} & S_{34} \\ S_{43} & S_{44} \end{bmatrix}$$

Differential Scattering Parameters



$$S_{Modal} = E_o S_{Line} E_o^{-1}$$

Where E_o is the eigenvector matrix associated with the reference line.

$$E_o = \begin{bmatrix} 1 & 1 \\ 1 & -1 \end{bmatrix}$$

$$E_o^{-1} = \begin{bmatrix} 1/2 & 1/2 \\ 1/2 & -1/2 \end{bmatrix}$$

Differential Scattering Parameters



$$S_{AA-Modal} = E_o S_{AA} E_o^{-1} = \begin{bmatrix} 1 & 1 \\ 1 & -1 \end{bmatrix} \begin{bmatrix} s_{11} & s_{12} \\ s_{21} & s_{22} \end{bmatrix} \begin{bmatrix} 1/2 & 1/2 \\ 1/2 & -1/2 \end{bmatrix}$$

$$S_{AA-Modal} = \begin{bmatrix} \overbrace{\left(s_{11} + s_{12} \right) + \left(s_{21} + s_{22} \right)}^{\text{common-to-common}} & \overbrace{\left(s_{11} - s_{12} \right) + \left(s_{21} - s_{22} \right)}^{\text{common-to-differential}} \\ \underbrace{\left(s_{11} + s_{12} \right) - \left(s_{21} + s_{22} \right)}_{\text{differential-to-common}} & \underbrace{\left(s_{11} - s_{12} \right) - \left(s_{21} - s_{22} \right)}_{\text{differential-to-differential}} \end{bmatrix}$$

Differential Scattering Parameters



$$S_{BA-Modal} = E_o S_{BA} E_o^{-1} = \begin{bmatrix} 1 & 1 \\ 1 & -1 \end{bmatrix} \begin{bmatrix} s_{31} & s_{32} \\ s_{41} & s_{42} \end{bmatrix} \begin{bmatrix} 1/2 & 1/2 \\ 1/2 & -1/2 \end{bmatrix}$$

$$S_{BA-Modal} = \begin{bmatrix} \overbrace{\left(s_{31} + s_{32} \right) + \left(s_{41} + s_{42} \right)}^{\text{common-to-common}} & \overbrace{\left(s_{31} - s_{32} \right) + \left(s_{41} - s_{42} \right)}^{\text{common-to-differential}} \\ \overbrace{\left(s_{31} + s_{32} \right) - \left(s_{41} + s_{42} \right)}^{\text{differential-to-common}} & \overbrace{\left(s_{31} - s_{32} \right) - \left(s_{41} - s_{42} \right)}^{\text{differential-to-differential}} \end{bmatrix}$$